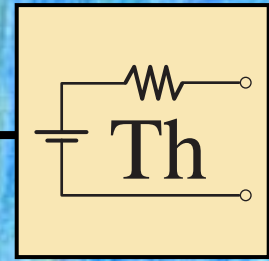


# 9



## Network Theorems

### 9.1 INTRODUCTION

This chapter will introduce the important fundamental theorems of network analysis. Included are the **superposition, Thévenin's, Norton's, maximum power transfer, substitution, Millman's, and reciprocity theorems**. We will consider a number of areas of application for each. A thorough understanding of each theorem is important because a number of the theorems will be applied repeatedly in the material to follow.

### 9.2 SUPERPOSITION THEOREM

The **superposition theorem**, like the methods of the last chapter, can be used to find the solution to networks with two or more sources that are not in series or parallel. The most obvious advantage of this method is that it does not require the use of a mathematical technique such as determinants to find the required voltages or currents. Instead, each source is treated independently, and the algebraic sum is found to determine a particular unknown quantity of the network.


The superposition theorem states the following:

*The current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produced independently by each source.*

When one is applying the theorem, it is possible to consider the effects of two sources at the same time and reduce the number of networks that have to be analyzed, but, in general,

$$\boxed{\begin{array}{l} \text{Number of networks} \\ \text{to be analyzed} \end{array}} = \boxed{\begin{array}{l} \text{Number of} \\ \text{independent sources} \end{array}} \quad (9.1)$$


To consider the effects of each source independently requires that sources be removed and replaced without affecting the final result. To

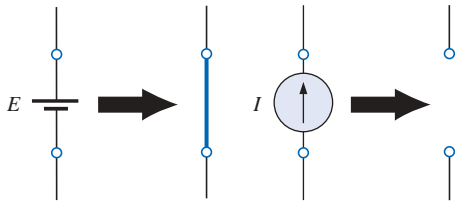

**FIG. 9.1**  
Removing the effects of ideal sources.

remove a voltage source when applying this theorem, the difference in potential between the terminals of the voltage source must be set to zero (short circuit); removing a current source requires that its terminals be opened (open circuit). Any internal resistance or conductance associated with the displaced sources is not eliminated but must still be considered.


Figure 9.1 reviews the various substitutions required when removing an ideal source, and Figure 9.2 reviews the substitutions with practical sources that have an internal resistance.

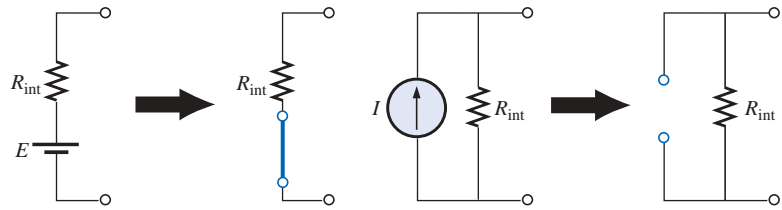

**FIG. 9.2**  
Removing the effects of practical sources.

The total current through any portion of the network is equal to the algebraic sum of the currents produced independently by each source. That is, for a two-source network, if the current produced by one source is in one direction, while that produced by the other is in the opposite direction through the same resistor, *the resulting current is the difference of the two and has the direction of the larger*. If the individual currents are in the same direction, *the resulting current is the sum of two in the direction of either current*. This rule holds true for the voltage across a portion of a network as determined by polarities, and it can be extended to networks with any number of sources.

The superposition principle is not applicable to power effects since the power loss in a resistor varies as the square (nonlinear) of the current or voltage. For instance, the current through the resistor  $R$  of Fig. 9.3(a) is  $I_1$  due to one source of a two-source network. The current through the same resistor due to the other source is  $I_2$  as shown in Fig. 9.3(b). Applying the superposition theorem, the total current through the resistor due to both sources is  $I_T$ , as shown in Fig. 9.3(c) with

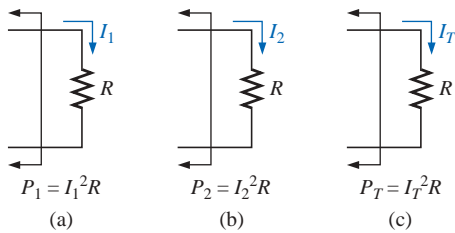

**FIG. 9.3**  
Demonstration of the fact that superposition is not applicable to power effects.

$$I_T = I_1 + I_2$$

The power delivered to the resistor in Fig. 9.3(a) is

$$P_1 = I_1^2 R$$

while the power delivered to the same resistor in Fig. 9.3(b) is

$$P_2 = I_2^2 R$$

If we assume that the total power delivered in Fig. 9.3(c) can be obtained by simply adding the power delivered due to each source, we find that

$$P_T = P_1 + P_2 = I_1^2 R + I_2^2 R = I_T^2 R$$

or

$$I_T^2 = I_1^2 + I_2^2$$



This final relationship between current levels is incorrect, however, as can be demonstrated by taking the total current determined by the superposition theorem and squaring it as follows:

$$I_T^2 = (I_1 + I_2)^2 = I_1^2 + I_2^2 + 2I_1I_2$$


which is certainly different from the expression obtained from the addition of power levels.

In general, therefore,

***the total power delivered to a resistive element must be determined using the total current through or the total voltage across the element and cannot be determined by a simple sum of the power levels established by each source.***

**EXAMPLE 9.1** Determine  $I_1$  for the network of Fig. 9.4.

**Solution:** Setting  $E = 0$  V for the network of Fig. 9.4 results in the network of Fig. 9.5(a), where a short-circuit equivalent has replaced the 30-V source.

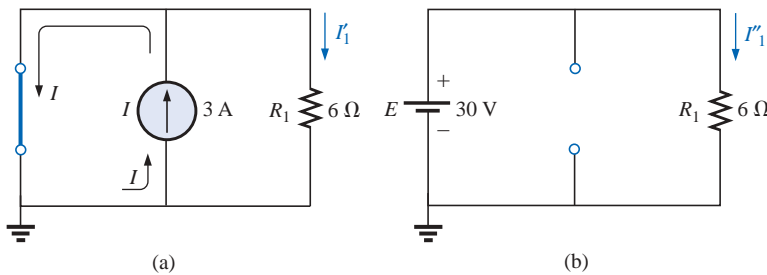

**FIG. 9.5**

(a) The contribution of  $I$  to  $I_1$ ; (b) the contribution of  $E$  to  $I_1$ .

As shown in Fig. 9.5(a), the source current will choose the short-circuit path, and  $I'_1 = 0$  A. If we applied the current divider rule,

$$I'_1 = \frac{R_{sc}I}{R_{sc} + R_1} = \frac{(0 \Omega)I}{0 \Omega + 6 \Omega} = 0 \text{ A}$$


Setting  $I$  to zero amperes will result in the network of Fig. 9.5(b), with the current source replaced by an open circuit. Applying Ohm's law,

$$I''_1 = \frac{E}{R_1} = \frac{30 \text{ V}}{6 \Omega} = 5 \text{ A}$$

Since  $I'_1$  and  $I''_1$  have the same defined direction in Fig. 9.5(a) and (b), the current  $I_1$  is the sum of the two, and


$$I_1 = I'_1 + I''_1 = 0 \text{ A} + 5 \text{ A} = \mathbf{5 \text{ A}}$$

Note in this case that the current source has no effect on the current through the 6-Ω resistor. The voltage across the resistor must be fixed at 30 V because they are parallel elements.

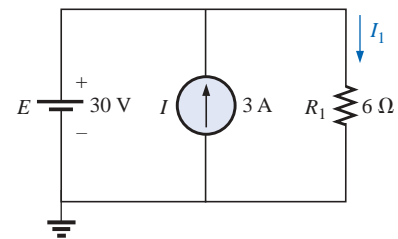

**FIG. 9.4**  
Example 9.1.

**EXAMPLE 9.2** Using superposition, determine the current through the 4- $\Omega$  resistor of Fig. 9.6. Note that this is a two-source network of the type considered in Chapter 8.

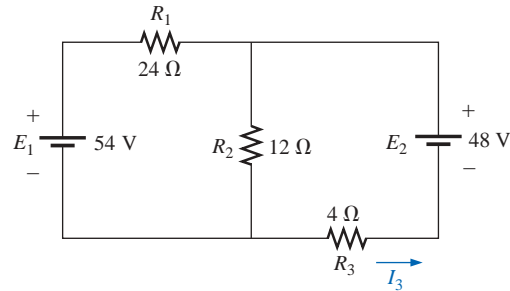


**FIG. 9.6**

Example 9.2.

**Solution:** Considering the effects of a 54-V source (Fig. 9.7):

$$R_T = R_1 + R_2 \parallel R_3 = 24 \Omega + 12 \Omega \parallel 4 \Omega = 24 \Omega + 3 \Omega = 27 \Omega$$

$$I = \frac{E_1}{R_T} = \frac{54 \text{ V}}{27 \Omega} = 2 \text{ A}$$

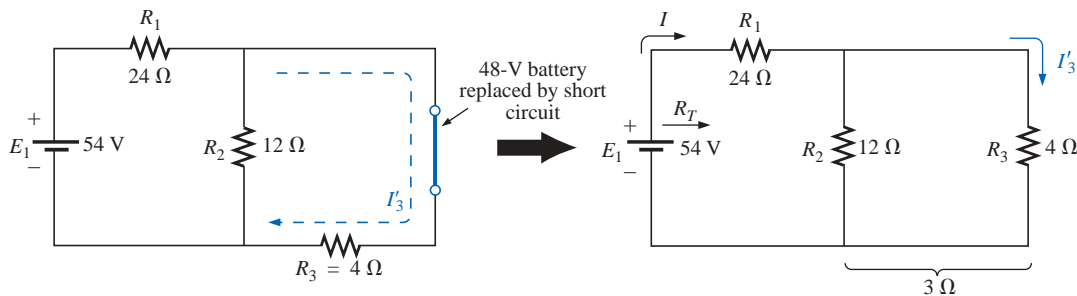

**FIG. 9.7**

The effect of  $E_1$  on the current  $I_3$ .


Using the current divider rule,

$$I'_3 = \frac{R_2 I}{R_2 + R_3} = \frac{(12 \Omega)(2 \text{ A})}{12 \Omega + 4 \Omega} = \frac{24 \text{ A}}{16} = 1.5 \text{ A}$$

Considering the effects of the 48-V source (Fig. 9.8):

$$R_T = R_3 + R_1 \parallel R_2 = 4 \Omega + 24 \Omega \parallel 12 \Omega = 4 \Omega + 8 \Omega = 12 \Omega$$

$$I''_3 = \frac{E_2}{R_T} = \frac{48 \text{ V}}{12 \Omega} = 4 \text{ A}$$

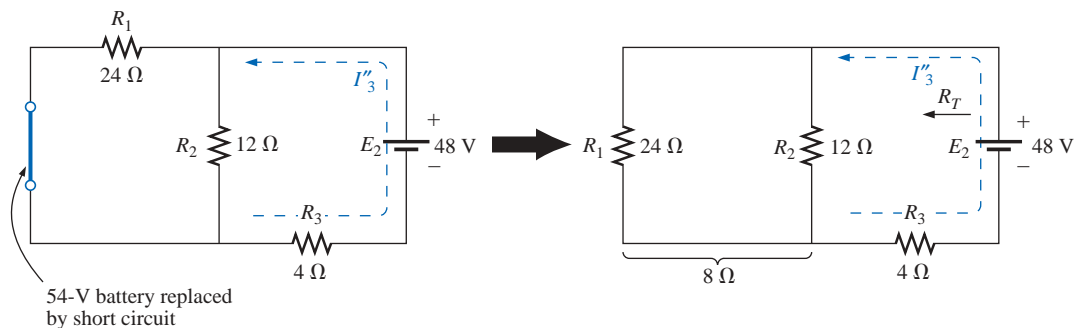

**FIG. 9.8**

The effect of  $E_2$  on the current  $I_3$ .




The total current through the 4-Ω resistor (Fig. 9.9) is

$$I_3 = I''_3 - I'_3 = 4 \text{ A} - 1.5 \text{ A} = \mathbf{2.5 \text{ A}} \quad (\text{direction of } I''_3)$$

**EXAMPLE 9.3**

- a. Using superposition, find the current through the 6-Ω resistor of the network of Fig. 9.10.

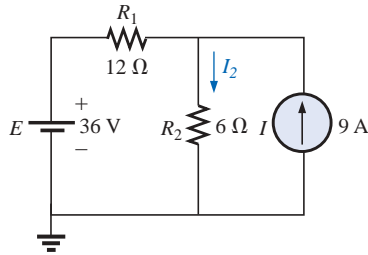

**FIG. 9.10**  
Example 9.3.

- b. Demonstrate that superposition is not applicable to power levels.

**Solutions:**

- a. Considering the effect of the 36-V source (Fig. 9.11):

$$I'_2 = \frac{E}{R_T} = \frac{E}{R_1 + R_2} = \frac{36 \text{ V}}{12 \Omega + 6 \Omega} = 2 \text{ A}$$


Considering the effect of the 9-A source (Fig. 9.12):

Applying the current divider rule,

$$I''_2 = \frac{R_1 I}{R_1 + R_2} = \frac{(12 \Omega)(9 \text{ A})}{12 \Omega + 6 \Omega} = \frac{108 \text{ A}}{18} = 6 \text{ A}$$

The total current through the 6-Ω resistor (Fig. 9.13) is

$$I_2 = I'_2 + I''_2 = 2 \text{ A} + 6 \text{ A} = \mathbf{8 \text{ A}}$$

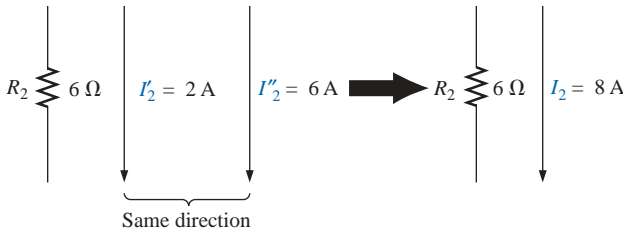

**FIG. 9.13**  
The resultant current for  $I_2$ .

- b. The power to the 6-Ω resistor is


$$\text{Power} = I^2 R = (8 \text{ A})^2 (6 \Omega) = \mathbf{384 \text{ W}}$$

The calculated power to the 6-Ω resistor due to each source, *misusing* the principle of superposition, is


$$P_1 = (I'_2)^2 R = (2 \text{ A})^2 (6 \Omega) = 24 \text{ W}$$

$$P_2 = (I''_2)^2 R = (6 \text{ A})^2 (6 \Omega) = 216 \text{ W}$$


$$P_1 + P_2 = 240 \text{ W} \neq 384 \text{ W}$$

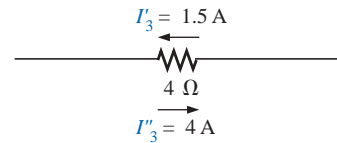

**FIG. 9.9**  
The resultant current for  $I_3$ .

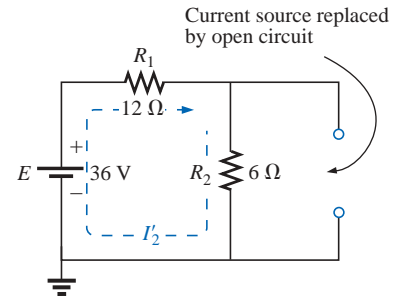

**FIG. 9.11**  
The contribution of  $E$  to  $I_2$ .

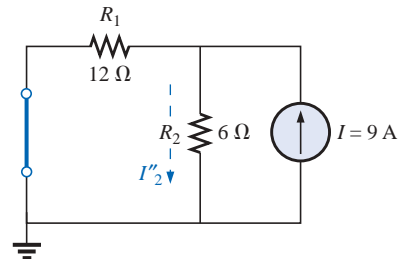

**FIG. 9.12**  
The contribution of  $I$  to  $I_2$ .



This results because  $2\text{ A} + 6\text{ A} = 8\text{ A}$ , but

$$(2\text{ A})^2 + (6\text{ A})^2 \neq (8\text{ A})^2$$

As mentioned previously, the superposition principle is not applicable to power effects since power is proportional to the square of the current or voltage ( $I^2R$  or  $V^2/R$ ).

Figure 9.14 is a plot of the power delivered to the  $6\text{-}\Omega$  resistor versus current.

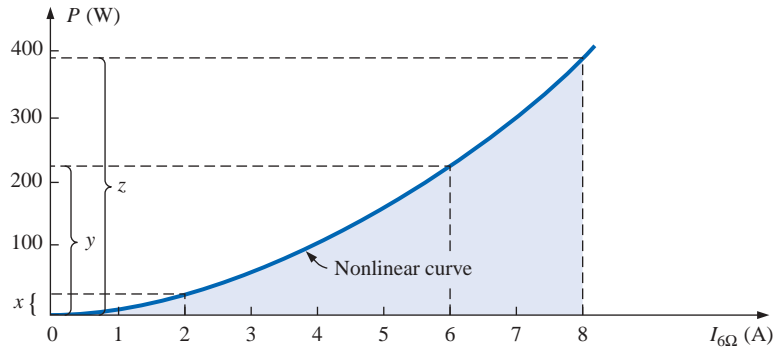


FIG. 9.14

Plotting the power delivered to the  $6\text{-}\Omega$  resistor versus current through the resistor.

Obviously,  $x + y \neq z$ , or  $24\text{ W} + 216\text{ W} \neq 384\text{ W}$ , and superposition does not hold. However, for a linear relationship, such as that between the voltage and current of the fixed-type  $6\text{-}\Omega$  resistor, superposition can be applied, as demonstrated by the graph of Fig. 9.15, where  $a + b = c$ , or  $2\text{ A} + 6\text{ A} = 8\text{ A}$ .

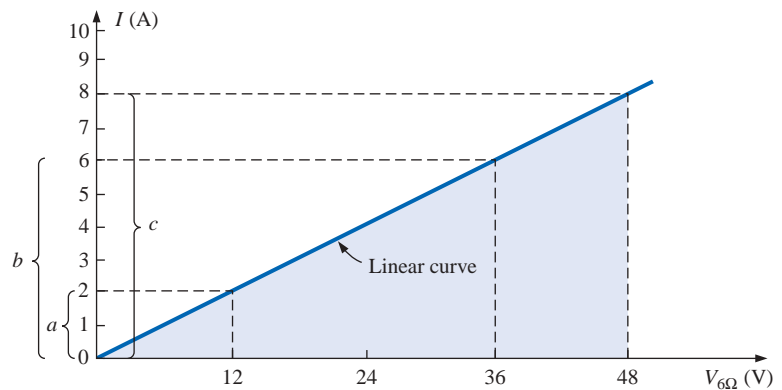


FIG. 9.15

Plotting  $I$  versus  $V$  for the  $6\text{-}\Omega$  resistor.


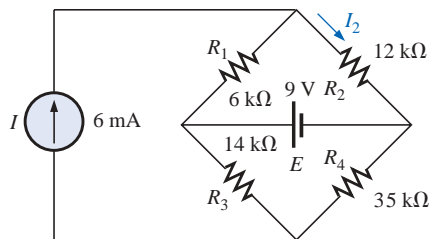


FIG. 9.16  
Example 9.4.

**EXAMPLE 9.4** Using the principle of superposition, find the current  $I_2$  through the  $12\text{-k}\Omega$  resistor of Fig. 9.16.

**Solution:** Considering the effect of the  $6\text{-mA}$  current source (Fig. 9.17):

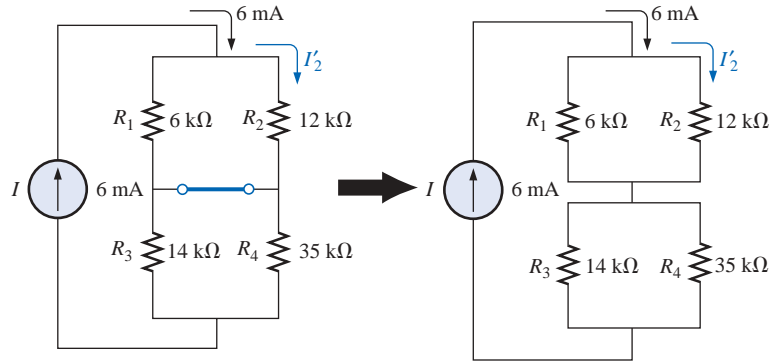

**FIG. 9.17**


The effect of the current source  $I$  on the current  $I_2$ .

Current divider rule:

$$I'_2 = \frac{R_1 I}{R_1 + R_2} = \frac{(6 \text{ k}\Omega)(6 \text{ mA})}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = 2 \text{ mA}$$

Considering the effect of the 9-V voltage source (Fig. 9.18):

$$I''_2 = \frac{E}{R_1 + R_2} = \frac{9 \text{ V}}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = 0.5 \text{ mA}$$

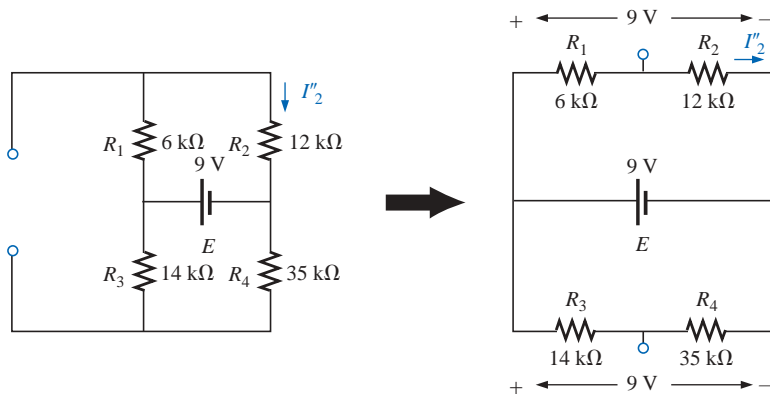


**FIG. 9.18**

The effect of the voltage source  $E$  on the current  $I_2$ .

Since  $I'_2$  and  $I''_2$  have the same direction through  $R_2$ , the desired current is the sum of the two:


$$\begin{aligned} I_2 &= I'_2 + I''_2 \\ &= 2 \text{ mA} + 0.5 \text{ mA} \\ &= \mathbf{2.5 \text{ mA}} \end{aligned}$$

**EXAMPLE 9.5** Find the current through the 2-Ω resistor of the network of Fig. 9.19. The presence of three sources will result in three different networks to be analyzed.

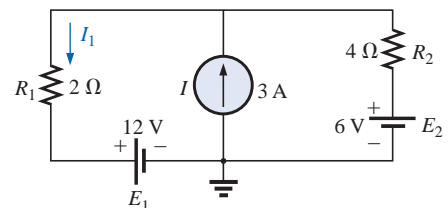

**FIG. 9.19**

Example 9.5.

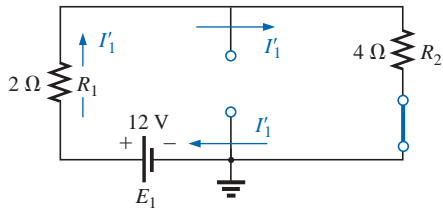


**FIG. 9.20**  
The effect of  $E_1$  on the current  $I_1$ .

**Solution:** Considering the effect of the 12-V source (Fig. 9.20):

$$I'_1 = \frac{E_1}{R_1 + R_2} = \frac{12 \text{ V}}{2 \Omega + 4 \Omega} = \frac{12 \text{ V}}{6 \Omega} = 2 \text{ A}$$

Considering the effect of the 6-V source (Fig. 9.21):

$$I''_1 = \frac{E_2}{R_1 + R_2} = \frac{6 \text{ V}}{2 \Omega + 4 \Omega} = \frac{6 \text{ V}}{6 \Omega} = 1 \text{ A}$$

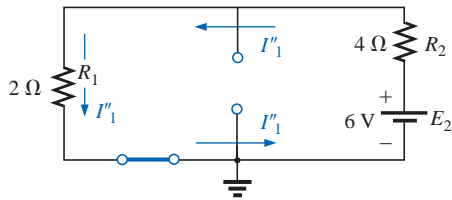


**FIG. 9.21**  
The effect of  $E_2$  on the current  $I_1$ .

Considering the effect of the 3-A source (Fig. 9.22):

Applying the current divider rule,

$$I'''_1 = \frac{R_2 I}{R_1 + R_2} = \frac{(4 \Omega)(3 \text{ A})}{2 \Omega + 4 \Omega} = \frac{12 \text{ A}}{6} = 2 \text{ A}$$


The total current through the 2-Ω resistor appears in Fig. 9.23, and

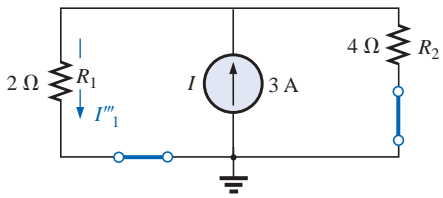

**FIG. 9.22**  
The effect of  $I$  on the current  $I_1$ .

$$I_1 = \overbrace{I''_1 + I'''_1}^{\text{Same direction as } I_1 \text{ in Fig. 9.19}} - \overbrace{I'_1}^{\text{Opposite direction to } I_1 \text{ in Fig. 9.19}}$$

$$= 1 \text{ A} + 2 \text{ A} - 2 \text{ A} = 1 \text{ A}$$

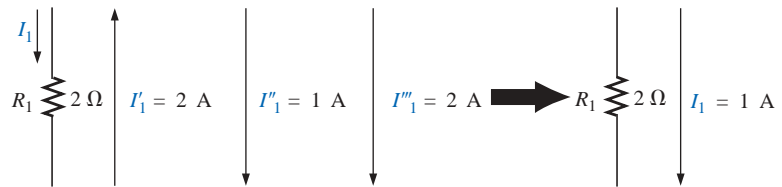


**FIG. 9.23**  
The resultant current  $I_1$ .
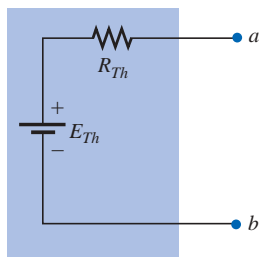
### 9.3 THÉVENIN'S THEOREM

Thévenin's theorem states the following:

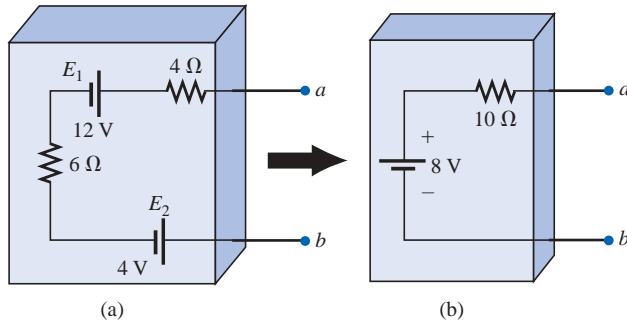
*Any two-terminal, linear bilateral dc network can be replaced by an equivalent circuit consisting of a voltage source and a series resistor, as shown in Fig. 9.24.*



**FIG. 9.24**  
Thévenin equivalent circuit.

In Fig. 9.25(a), for example, the network within the container has only two terminals available to the outside world, labeled  $a$  and  $b$ . It is possible using Thévenin's theorem to replace everything in the container with one source and one resistor, as shown in Fig. 9.25(b), and maintain the same terminal characteristics at terminals  $a$  and  $b$ . That is, any load connected to terminals  $a$  and  $b$  will not know whether it is hooked up to the network of Fig. 9.25(a) or Fig. 9.25(b). The load will receive the same current, voltage, and power from either configuration of Fig. 9.25. Throughout the discussion to follow, however, always keep in mind that

*the Thévenin equivalent circuit provides an equivalence at the terminals only—the internal construction and characteristics of the original network and the Thévenin equivalent are usually quite different.*

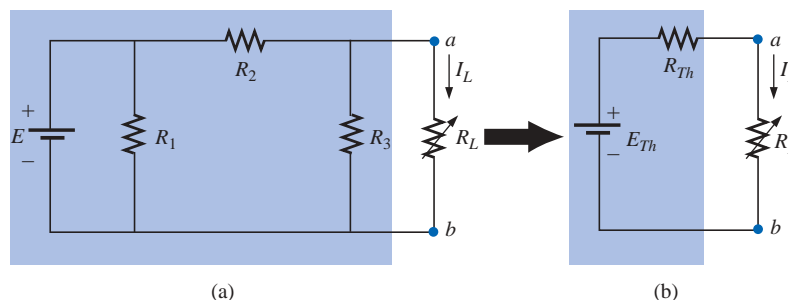

**FIG. 9.25**

The effect of applying Thévenin's theorem.

For the network of Fig. 9.25(a), the Thévenin equivalent circuit can be found quite directly by simply combining the series batteries and resistors. Note the exact similarity of the network of Fig. 9.25(b) to the Thévenin configuration of Fig. 9.24. The method described below will allow us to extend the procedure just applied to more complex configurations and still end up with the relatively simple network of Fig. 9.24.

In most cases, other elements will be connected to the right of terminals  $a$  and  $b$  in Fig. 9.25. To apply the theorem, however, the network to be reduced to the Thévenin equivalent form must be isolated as shown in Fig. 9.25, and the two “holding” terminals identified. Once the proper Thévenin equivalent circuit has been determined, the voltage, current, or resistance readings between the two “holding” terminals will be the same whether the original or the Thévenin equivalent circuit is connected to the left of terminals  $a$  and  $b$  in Fig. 9.25. Any load connected to the right of terminals  $a$  and  $b$  of Fig. 9.25 will receive the same voltage or current with either network.

This theorem achieves two important objectives. First, as was true for all the methods previously described, it allows us to find any particular voltage or current in a linear network with one, two, or any other number of sources. Second, we can concentrate on a specific portion of a network by replacing the remaining network with an equivalent circuit. In Fig. 9.26, for example, by finding the Thévenin equivalent circuit for the network in the shaded area, we can quickly calculate the change in current through or voltage across the variable resistor  $R_L$  for the various values that it may assume. This is demonstrated in Example 9.6.


**FIG. 9.26**

Substituting the Thévenin equivalent circuit for a complex network.

French (Meaux,  
Paris)  
(1857–1927)  
Telegraph Engineer,  
Commandant and  
Educator  
École Polytech-  
nique and École  
Supérieure de  
Télégraphie



Courtesy of the Bibliothèque  
École Polytechnique, Paris, France

Although active in the study and design of telegraphic systems (including underground transmission), cylindrical condensers (capacitors), and electromagnetism, he is best known for a theorem first presented in the French *Journal of Physics—Theory and Applications* in 1883. It appeared under the heading of “Sur un nouveau théorème d’électricité dynamique” (“On a new theorem of dynamic electricity”) and was originally referred to as the *equivalent generator theorem*. There is some evidence that a similar theorem was introduced by Hermann von Helmholtz in 1853. However, Professor Helmholtz applied the theorem to animal physiology and not to communication or generator systems, and therefore he has not received the credit in this field that he might deserve. In the early 1920s AT&T did some pioneering work using the equivalent circuit and may have initiated the reference to the theorem as simply Thévenin’s theorem. In fact, Edward L. Norton, an engineer at AT&T at the time, introduced a current source equivalent of the Thévenin equivalent currently referred to as the Norton equivalent circuit. As an aside, Commandant Thévenin was an avid skier and in fact was commissioner of an international ski competition in Chamonix, France, in 1912.

### LEON-CHARLES THÉVENIN



Before we examine the steps involved in applying this theorem, it is important that an additional word be included here to ensure that the implications of the Thévenin equivalent circuit are clear. In Fig. 9.26, the entire network, except  $R_L$ , is to be replaced by a single series resistor and battery as shown in Fig. 9.24. The values of these two elements of the Thévenin equivalent circuit must be chosen to ensure that the resistor  $R_L$  will react to the network of Fig. 9.26(a) in the same manner as to the network of Fig. 9.26(b). In other words, the current through or voltage across  $R_L$  must be the same for either network for any value of  $R_L$ .

The following sequence of steps will lead to the proper value of  $R_{Th}$  and  $E_{Th}$ .

**Preliminary:**

1. Remove that portion of the network across which the Thévenin equivalent circuit is to be found. In Fig. 9.26(a), this requires that the load resistor  $R_L$  be temporarily removed from the network.
2. Mark the terminals of the remaining two-terminal network. (The importance of this step will become obvious as we progress through some complex networks.)

$R_{Th}$ :

3. Calculate  $R_{Th}$  by first setting all sources to zero (voltage sources are replaced by short circuits, and current sources by open circuits) and then finding the resultant resistance between the two marked terminals. (If the internal resistance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.)

$E_{Th}$ :

4. Calculate  $E_{Th}$  by first returning all sources to their original position and finding the open-circuit voltage between the marked terminals. (This step is invariably the one that will lead to the most confusion and errors. In all cases, keep in mind that it is the open-circuit potential between the two terminals marked in step 2.)

**Conclusion:**

5. Draw the Thévenin equivalent circuit with the portion of the circuit previously removed placed between the terminals of the equivalent circuit. This step is indicated by the placement of the resistor  $R_L$  between the terminals of the Thévenin equivalent circuit as shown in Fig. 9.26(b).

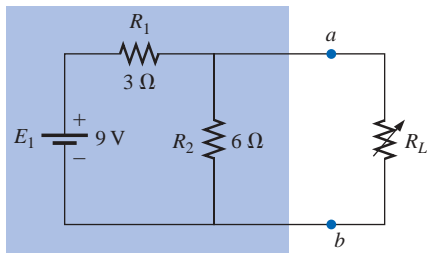


FIG. 9.27  
Example 9.6.

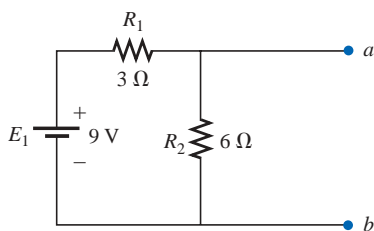


FIG. 9.28  
Identifying the terminals of particular importance when applying Thévenin's theorem.


**EXAMPLE 9.6** Find the Thévenin equivalent circuit for the network in the shaded area of the network of Fig. 9.27. Then find the current through  $R_L$  for values of  $2\ \Omega$ ,  $10\ \Omega$ , and  $100\ \Omega$ .

**Solution:**

Steps 1 and 2 produce the network of Fig. 9.28. Note that the load resistor  $R_L$  has been removed and the two “holding” terminals have been defined as  $a$  and  $b$ .

Step 3: Replacing the voltage source  $E_1$  with a short-circuit equivalent yields the network of Fig. 9.29(a), where

$$R_{Th} = R_1 \parallel R_2 = \frac{(3\ \Omega)(6\ \Omega)}{3\ \Omega + 6\ \Omega} = 2\ \Omega$$

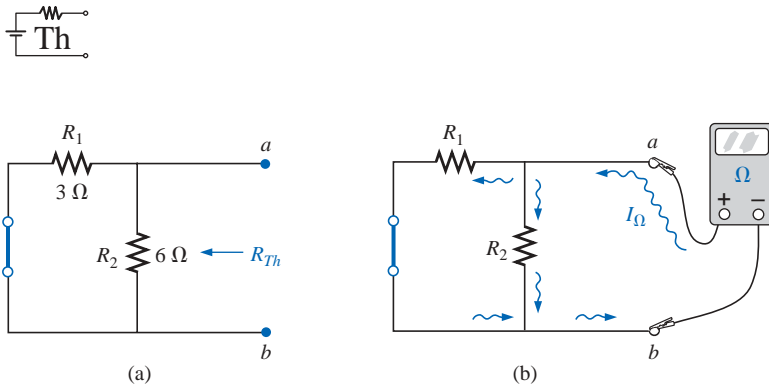
**FIG. 9.29**

Determining  $R_{Th}$  for the network of Fig. 9.28.

The importance of the two marked terminals now begins to surface. They are the two terminals across which the Thévenin resistance is measured. It is no longer the total resistance as seen by the source, as determined in the majority of problems of Chapter 7. If some difficulty develops when determining  $R_{Th}$  with regard to whether the resistive elements are in series or parallel, consider recalling that the ohmmeter sends out a trickle current into a resistive combination and senses the level of the resulting voltage to establish the measured resistance level. In Fig. 9.29(b), the trickle current of the ohmmeter approaches the network through terminal  $a$ , and when it reaches the junction of  $R_1$  and  $R_2$ , it splits as shown. The fact that the trickle current splits and then recombines at the lower node reveals that the resistors are in parallel as far as the ohmmeter reading is concerned. In essence, the path of the sensing current of the ohmmeter has revealed how the resistors are connected to the two terminals of interest and how the Thévenin resistance should be determined. Keep the above in mind as you work through the various examples of this section.

*Step 4:* Replace the voltage source (Fig. 9.30). For this case, the open-circuit voltage  $E_{Th}$  is the same as the voltage drop across the  $6\text{-}\Omega$  resistor. Applying the voltage divider rule,

$$E_{Th} = \frac{R_2 E_1}{R_2 + R_1} = \frac{(6\ \Omega)(9\ \text{V})}{6\ \Omega + 3\ \Omega} = \frac{54\ \text{V}}{9} = 6\ \text{V}$$

It is particularly important to recognize that  $E_{Th}$  is the open-circuit potential between points  $a$  and  $b$ . Remember that an open circuit can have any voltage across it, but the current must be zero. In fact, the current through any element in series with the open circuit must be zero also. The use of a voltmeter to measure  $E_{Th}$  appears in Fig. 9.31. Note that it is placed directly across the resistor  $R_2$  since  $E_{Th}$  and  $V_{R_2}$  are in parallel.


*Step 5* (Fig. 9.32):

$$I_L = \frac{E_{Th}}{R_{Th} + R_L}$$


$$R_L = 2\ \Omega: \quad I_L = \frac{6\ \text{V}}{2\ \Omega + 2\ \Omega} = 1.5\ \text{A}$$

$$R_L = 10\ \Omega: \quad I_L = \frac{6\ \text{V}}{2\ \Omega + 10\ \Omega} = 0.5\ \text{A}$$


$$R_L = 100\ \Omega: \quad I_L = \frac{6\ \text{V}}{2\ \Omega + 100\ \Omega} = 0.059\ \text{A}$$

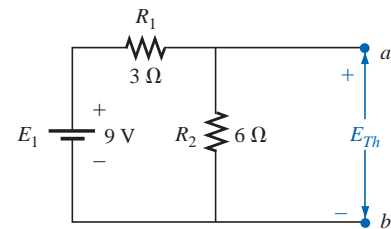
**FIG. 9.30**


Determining  $E_{Th}$  for the network of Fig. 9.28.

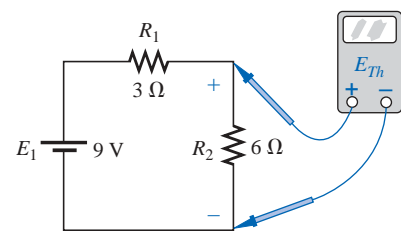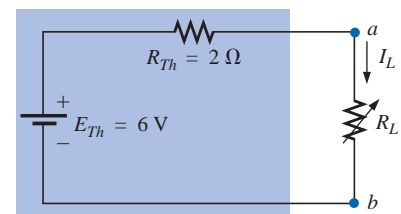
**FIG. 9.31**


Measuring  $E_{Th}$  for the network of Fig. 9.28.


**FIG. 9.32**


Substituting the Thévenin equivalent circuit for the network external to  $R_L$  in Fig. 9.27.

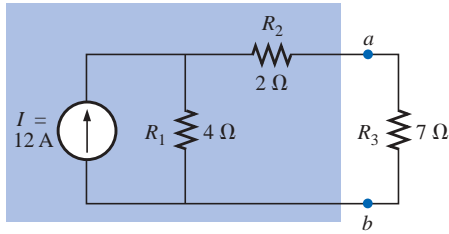

**FIG. 9.33**  
Example 9.7.

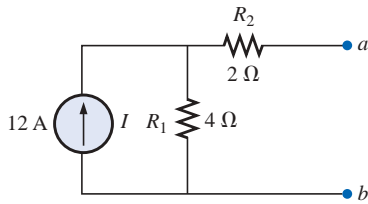

**FIG. 9.34**  
Establishing the terminals of particular interest for the network of Fig. 9.33.

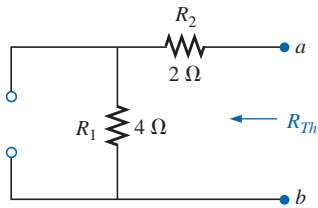

**FIG. 9.35**  
Determining  $R_{Th}$  for the network of Fig. 9.34.

If Thévenin's theorem were unavailable, each change in  $R_L$  would require that the entire network of Fig. 9.27 be reexamined to find the new value of  $R_L$ .

**EXAMPLE 9.7** Find the Thévenin equivalent circuit for the network in the shaded area of the network of Fig. 9.33.

**Solution:**

Steps 1 and 2 are shown in Fig. 9.34.

Step 3 is shown in Fig. 9.35. The current source has been replaced with an open-circuit equivalent, and the resistance determined between terminals  $a$  and  $b$ .


In this case an ohmmeter connected between terminals  $a$  and  $b$  would send out a sensing current that would flow directly through  $R_1$  and  $R_2$  (at the same level). The result is that  $R_1$  and  $R_2$  are in series and the Thévenin resistance is the sum of the two.

$$R_{Th} = R_1 + R_2 = 4 \Omega + 2 \Omega = 6 \Omega$$

Step 4 (Fig. 9.36): In this case, since an open circuit exists between the two marked terminals, the current is zero between these terminals and through the 2- $\Omega$  resistor. The voltage drop across  $R_2$  is, therefore,


$$V_2 = I_2 R_2 = (0)R_2 = 0 \text{ V}$$

and 
$$E_{Th} = V_1 = I_1 R_1 = IR_1 = (12 \text{ A})(4 \Omega) = 48 \text{ V}$$

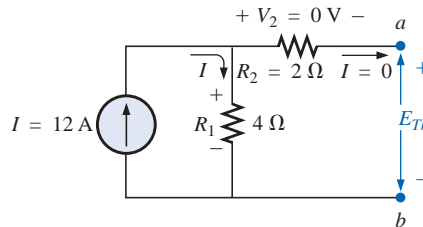


**FIG. 9.36**  
Determining  $E_{Th}$  for the network of Fig. 9.34.

Step 5 is shown in Fig. 9.37.

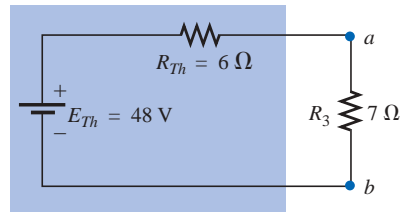

**FIG. 9.37**  
Substituting the Thévenin equivalent circuit in the network external to the resistor  $R_3$  of Fig. 9.33.


**EXAMPLE 9.8** Find the Thévenin equivalent circuit for the network in the shaded area of the network of Fig. 9.38. Note in this example that

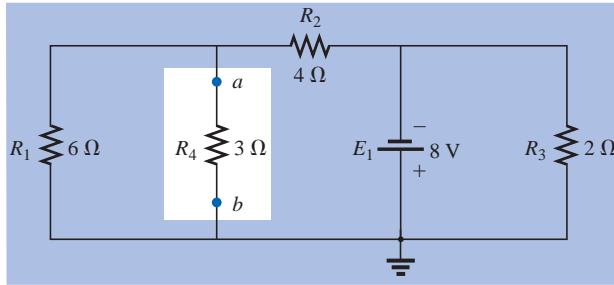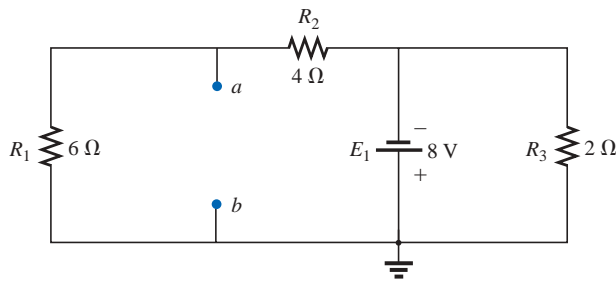
**FIG. 9.38**
*Example 9.8.*

there is no need for the section of the network to be preserved to be at the “end” of the configuration.

**Solution:**

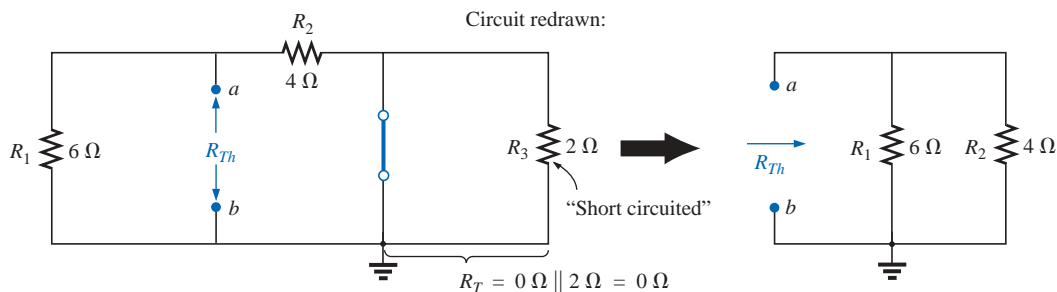
*Steps 1 and 2:* See Fig. 9.39.


**FIG. 9.39**


*Identifying the terminals of particular interest for the network of Fig. 9.38.*

*Step 3:* See Fig. 9.40. Steps 1 and 2 are relatively easy to apply, but now we must be careful to “hold” onto the terminals *a* and *b* as the Thévenin resistance and voltage are determined. In Fig. 9.40, all the remaining elements turn out to be in parallel, and the network can be redrawn as shown.

$$R_{Th} = R_1 \parallel R_2 = \frac{(6 \Omega)(4 \Omega)}{6 \Omega + 4 \Omega} = \frac{24 \Omega}{10} = 2.4 \Omega$$



**FIG. 9.40**

*Determining  $R_{Th}$  for the network of Fig. 9.39.*

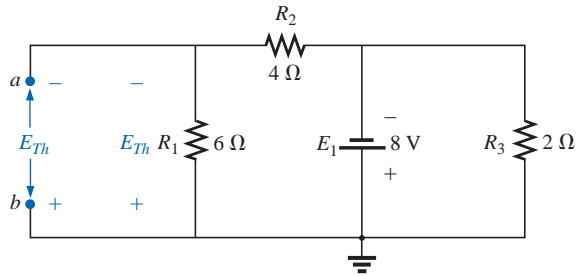

**FIG. 9.41**

Determining  $E_{Th}$  for the network of Fig. 9.39.

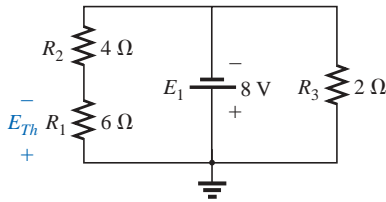


**FIG. 9.42**

Network of Fig. 9.41 redrawn.

*Step 4:* See Fig. 9.41. In this case, the network can be redrawn as shown in Fig. 9.42, and since the voltage is the same across parallel elements, the voltage across the series resistors  $R_1$  and  $R_2$  is  $E_1$ , or 8 V. Applying the voltage divider rule,

$$E_{Th} = \frac{R_1 E_1}{R_1 + R_2} = \frac{(6 \Omega)(8 \text{ V})}{6 \Omega + 4 \Omega} = \frac{48 \text{ V}}{10} = 4.8 \text{ V}$$

*Step 5:* See Fig. 9.43.

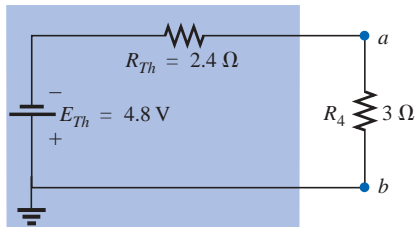


**FIG. 9.43**

Substituting the Thévenin equivalent circuit for the network external to the resistor  $R_4$  of Fig. 9.38.


The importance of marking the terminals should be obvious from Example 9.8. Note that there is no requirement that the Thévenin voltage have the same polarity as the equivalent circuit originally introduced.

**EXAMPLE 9.9** Find the Thévenin equivalent circuit for the network in the shaded area of the bridge network of Fig. 9.44.

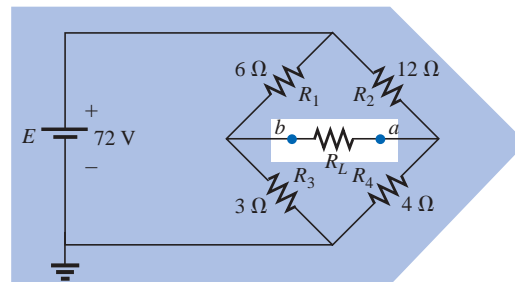

**FIG. 9.44**

Example 9.9.

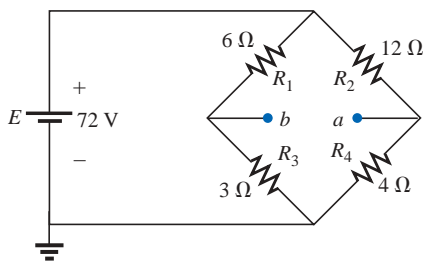

**FIG. 9.45**


Identifying the terminals of particular interest for the network of Fig. 9.44.

**Solution:**

*Steps 1 and 2* are shown in Fig. 9.45.

*Step 3:* See Fig. 9.46. In this case, the short-circuit replacement of the voltage source  $E$  provides a direct connection between  $c$  and  $c'$  of Fig. 9.46(a), permitting a “folding” of the network around the horizontal line of  $a$ - $b$  to produce the configuration of Fig. 9.46(b).

$$\begin{aligned} R_{Th} = R_{a-b} &= R_1 \parallel R_3 + R_2 \parallel R_4 \\ &= 6 \Omega \parallel 3 \Omega + 4 \Omega \parallel 12 \Omega \\ &= 2 \Omega + 3 \Omega = 5 \Omega \end{aligned}$$

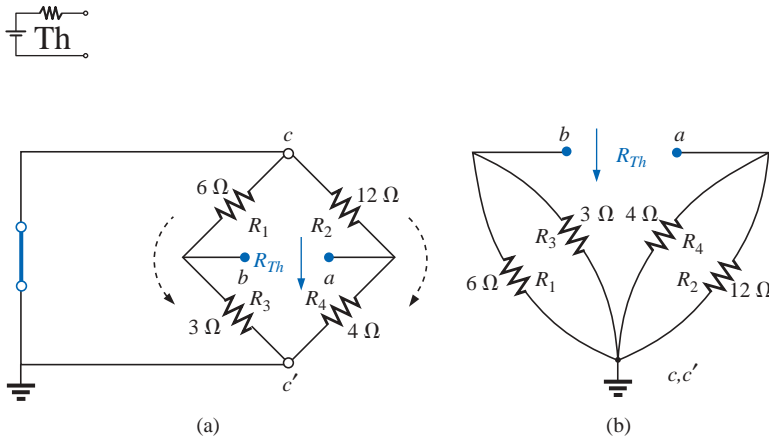


**FIG. 9.46**  
Solving for  $R_{Th}$  for the network of Fig. 9.45.

*Step 4:* The circuit is redrawn in Fig. 9.47. The absence of a direct connection between  $a$  and  $b$  results in a network with three parallel branches. The voltages  $V_1$  and  $V_2$  can therefore be determined using the voltage divider rule:

$$V_1 = \frac{R_1 E}{R_1 + R_3} = \frac{(6 \Omega)(72 \text{ V})}{6 \Omega + 3 \Omega} = \frac{432 \text{ V}}{9} = 48 \text{ V}$$

$$V_2 = \frac{R_2 E}{R_2 + R_4} = \frac{(12 \Omega)(72 \text{ V})}{12 \Omega + 4 \Omega} = \frac{864 \text{ V}}{16} = 54 \text{ V}$$

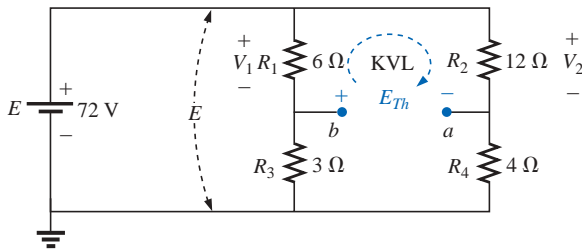

**FIG. 9.47**  
Determining  $E_{Th}$  for the network of Fig. 9.45.

Assuming the polarity shown for  $E_{Th}$  and applying Kirchhoff's voltage law to the top loop in the clockwise direction will result in


$$\sum_C V = +E_{Th} + V_1 - V_2 = 0$$

and 
$$E_{Th} = V_2 - V_1 = 54 \text{ V} - 48 \text{ V} = 6 \text{ V}$$


*Step 5* is shown in Fig. 9.48.

Thévenin's theorem is not restricted to a single passive element, as shown in the preceding examples, but can be applied across sources, whole branches, portions of networks, or any circuit configuration, as shown in the following example. It is also possible that one of the methods previously described, such as mesh analysis or superposition, may have to be used to find the Thévenin equivalent circuit.

**EXAMPLE 9.10** (Two sources) Find the Thévenin circuit for the network within the shaded area of Fig. 9.49.

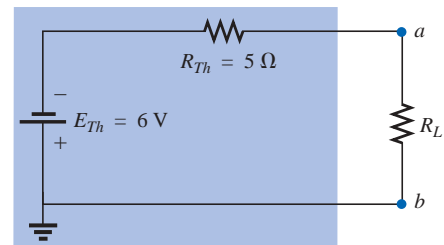

**FIG. 9.48**  
Substituting the Thévenin equivalent circuit for the network external to the resistor  $R_L$  of Fig. 9.44.

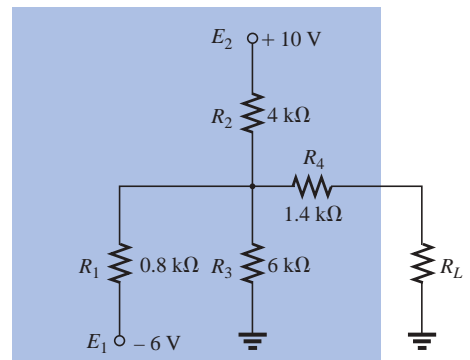

**FIG. 9.49**  
Example 9.10.

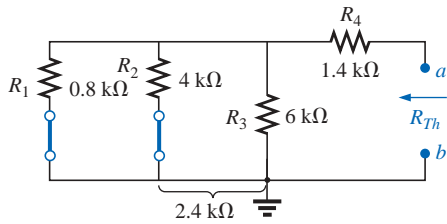


FIG. 9.51

Determining  $R_{Th}$  for the network of Fig. 9.50.

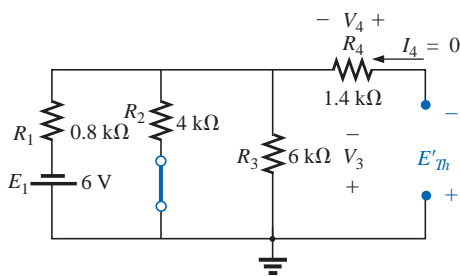


FIG. 9.52

Determining the contribution to  $E_{Th}$  from the source  $E_1$  for the network of Fig. 9.50.

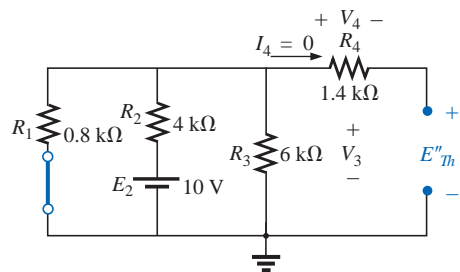


FIG. 9.53

Determining the contribution to  $E_{Th}$  from the source  $E_2$  for the network of Fig. 9.50.

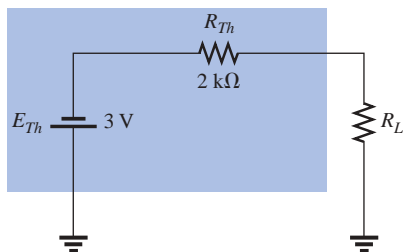


FIG. 9.54

Substituting the Thévenin equivalent circuit for the network external to the resistor  $R_L$  of Fig. 9.49.

**Solution:** The network is redrawn and steps 1 and 2 are applied as shown in Fig. 9.50.

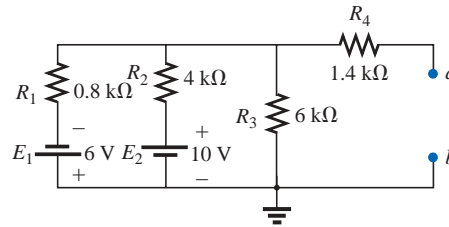


FIG. 9.50

Identifying the terminals of particular interest for the network of Fig. 9.49.

Step 3: See Fig. 9.51.

$$\begin{aligned} R_{Th} &= R_4 + R_1 \parallel R_2 \parallel R_3 \\ &= 1.4 \text{ k}\Omega + 0.8 \text{ k}\Omega \parallel 4 \text{ k}\Omega \parallel 6 \text{ k}\Omega \\ &= 1.4 \text{ k}\Omega + 0.8 \text{ k}\Omega \parallel 2.4 \text{ k}\Omega \\ &= 1.4 \text{ k}\Omega + 0.6 \text{ k}\Omega \\ &= \mathbf{2 \text{ k}\Omega} \end{aligned}$$

Step 4: Applying superposition, we will consider the effects of the voltage source  $E_1$  first. Note Fig. 9.52. The open circuit requires that  $V_4 = I_4 R_4 = (0)R_4 = 0 \text{ V}$ , and

$$E'_{Th} = V_3$$

$$R'_T = R_2 \parallel R_3 = 4 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 2.4 \text{ k}\Omega$$

Applying the voltage divider rule,

$$\begin{aligned} V_3 &= \frac{R'_T E_1}{R'_T + R_1} = \frac{(2.4 \text{ k}\Omega)(6 \text{ V})}{2.4 \text{ k}\Omega + 0.8 \text{ k}\Omega} = \frac{14.4 \text{ V}}{3.2} = 4.5 \text{ V} \\ E'_{Th} &= V_3 = 4.5 \text{ V} \end{aligned}$$

For the source  $E_2$ , the network of Fig. 9.53 will result. Again,  $V_4 = I_4 R_4 = (0)R_4 = 0 \text{ V}$ , and

$$E''_{Th} = V_3$$

$$R'_T = R_1 \parallel R_3 = 0.8 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 0.706 \text{ k}\Omega$$

$$\text{and } V_3 = \frac{R'_T E_2}{R'_T + R_2} = \frac{(0.706 \text{ k}\Omega)(10 \text{ V})}{0.706 \text{ k}\Omega + 4 \text{ k}\Omega} = \frac{7.06 \text{ V}}{4.706} = 1.5 \text{ V}$$

$$E''_{Th} = V_3 = 1.5 \text{ V}$$

Since  $E'_{Th}$  and  $E''_{Th}$  have opposite polarities,

$$\begin{aligned} E_{Th} &= E'_{Th} - E''_{Th} \\ &= 4.5 \text{ V} - 1.5 \text{ V} \\ &= \mathbf{3 \text{ V}} \quad (\text{polarity of } E'_{Th}) \end{aligned}$$


Step 5: See Fig. 9.54.

## Experimental Procedures


There are two popular experimental procedures for determining the parameters of a Thévenin equivalent network. The procedure for measuring the Thévenin voltage is the same for each, but the approach for determining the Thévenin resistance is quite different for each.



**Direct Measurement of  $E_{Th}$  and  $R_{Th}$**  For any physical network, the value of  $E_{Th}$  can be determined experimentally by measuring the open-circuit voltage across the load terminals, as shown in Fig. 9.55;  $E_{Th} = V_{oc} = V_{ab}$ . The value of  $R_{Th}$  can then be determined by completing the network with a variable  $R_L$  such as the potentiometer of Fig. 9.56(b).  $R_L$  can then be varied until the voltage appearing across the load is one-half the open-circuit value, or  $V_L = E_{Th}/2$ . For the series circuit of Fig. 9.56(a), when the load voltage is reduced to one-half the open-circuit level, the voltage across  $R_{Th}$  and  $R_L$  must be the same. If we read the value of  $R_L$  [as shown in Fig. 9.56(c)] that resulted in the preceding calculations, we will also have the value of  $R_{Th}$ , since  $R_L = R_{Th}$  if  $V_L$  equals the voltage across  $R_{Th}$ .

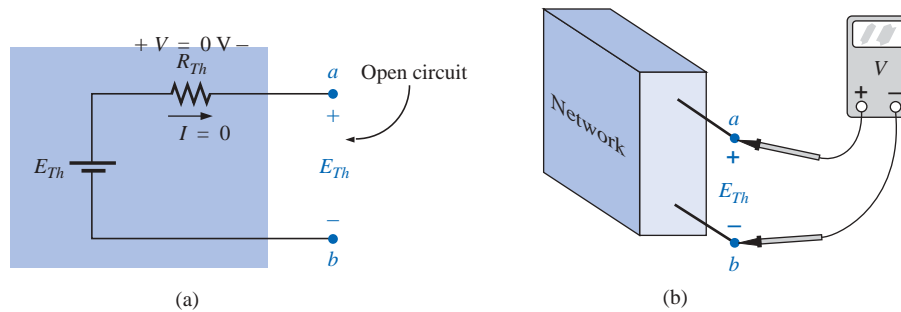

**FIG. 9.55**  
Determining  $E_{Th}$  experimentally.

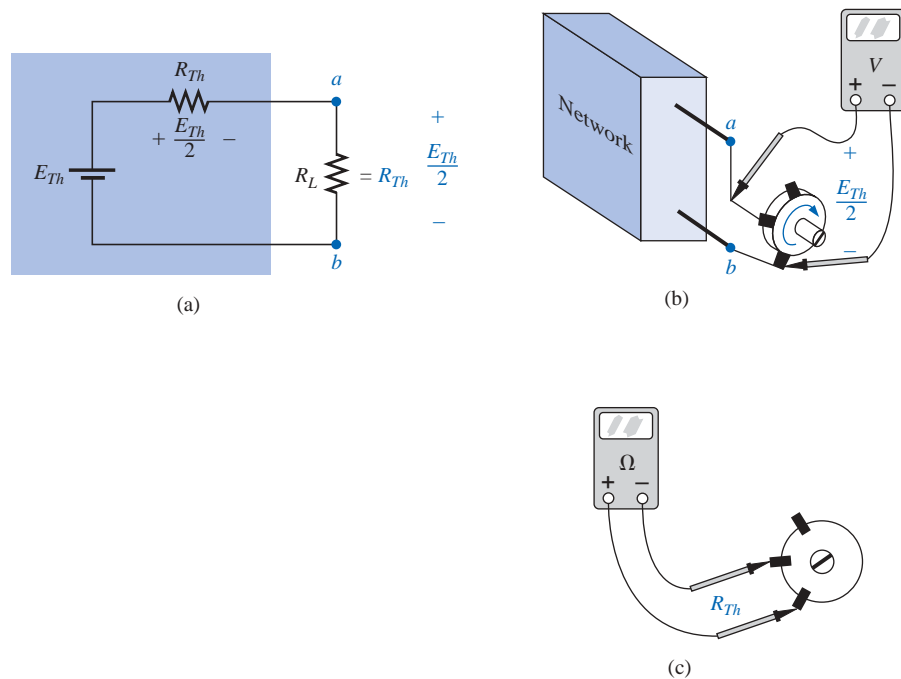

**FIG. 9.56**  
Determining  $R_{Th}$  experimentally.

**Measuring  $V_{oc}$  and  $I_{sc}$**  The Thévenin voltage is again determined by measuring the open-circuit voltage across the terminals of interest;

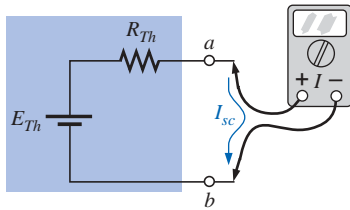


FIG. 9.57  
Measuring  $I_{sc}$ .

American (Rockland,  
Maine; Summit,  
New Jersey)  
(1898–1983)  
Electrical Engineer,  
Scientist, Inventor  
Department Head:  
Bell Laboratories  
Fellow: Acoustical  
Society and Institute  
of Radio Engineers



Courtesy of AT&T Archives

Although interested primarily in communications circuit theory and the transmission of data at high speeds over telephone lines, Edward L. Norton is best remembered for development of the dual of Thévenin's equivalent circuit, currently referred to as *Norton's equivalent circuit*. In fact, Norton and his associates at AT&T in the early 1920s are recognized as some of the first to perform pioneering work applying Thévenin's equivalent circuit and who referred to this concept simply as Thévenin's theorem. In 1926 he proposed the equivalent circuit using a current source and parallel resistor to assist in the design of recording instrumentation that was primarily current driven. He began his telephone career in 1922 with the Western Electric Company's Engineering Department, which later became Bell Laboratories. His areas of active research included network theory, acoustical systems, electromagnetic apparatus, and data transmission. A graduate of MIT and Columbia University, he held nineteen patents on his work.

#### EDWARD L. NORTON

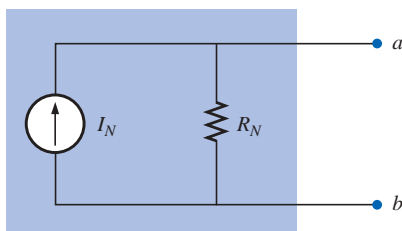


FIG. 9.58  
Norton equivalent circuit.

that is,  $E_{Th} = V_{oc}$ . To determine  $R_{Th}$ , a short-circuit condition is established across the terminals of interest, as shown in Fig. 9.57, and the current through the short circuit is measured with an ammeter. Using Ohm's law, we find that the short-circuit current is determined by

$$I_{sc} = \frac{E_{Th}}{R_{Th}}$$

and the Thévenin resistance by

$$R_{Th} = \frac{E_{Th}}{I_{sc}}$$

However,  $E_{Th} = V_{oc}$  resulting in the following equation for  $R_{Th}$ :

$$R_{Th} = \frac{V_{oc}}{I_{sc}} \quad (9.2)$$

## 9.4 NORTON'S THEOREM

It was demonstrated in Section 8.3 that every voltage source with a series internal resistance has a current source equivalent. The current source equivalent of the Thévenin network (which, you will note, satisfies the above conditions), as shown in Fig. 9.58, can be determined by **Norton's theorem**. It can also be found through the conversions of Section 8.3.

The theorem states the following:

**Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor, as shown in Fig. 9.58.**

The discussion of Thévenin's theorem with respect to the equivalent circuit can also be applied to the Norton equivalent circuit. The steps leading to the proper values of  $I_N$  and  $R_N$  are now listed.

**Preliminary:**

1. Remove that portion of the network across which the Norton equivalent circuit is found.
2. Mark the terminals of the remaining two-terminal network.

**$R_N$ :**

3. Calculate  $R_N$  by first setting all sources to zero (voltage sources are replaced with short circuits, and current sources with open circuits) and then finding the resultant resistance between the two marked terminals. (If the internal resistance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.) Since  $R_N = R_{Th}$ , the procedure and value obtained using the approach described for Thévenin's theorem will determine the proper value of  $R_N$ .

**$I_N$ :**

4. Calculate  $I_N$  by first returning all sources to their original position and then finding the short-circuit current between the marked terminals. It is the same current that would be measured by an ammeter placed between the marked terminals.



**Conclusion:**

5. Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.

The Norton and Thévenin equivalent circuits can also be found from each other by using the source transformation discussed earlier in this chapter and reproduced in Fig. 9.59.

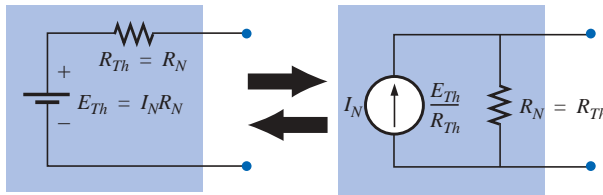


FIG. 9.59

Converting between Thévenin and Norton equivalent circuits.

**EXAMPLE 9.11** Find the Norton equivalent circuit for the network in the shaded area of Fig. 9.60.

**Solution:**

Steps 1 and 2 are shown in Fig. 9.61.

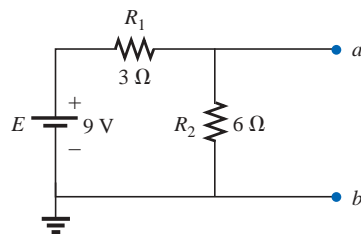


FIG. 9.61

Identifying the terminals of particular interest for the network of Fig. 9.60.

Step 3 is shown in Fig. 9.62, and

$$R_N = R_1 \parallel R_2 = 3 \Omega \parallel 6 \Omega = \frac{(3 \Omega)(6 \Omega)}{3 \Omega + 6 \Omega} = \frac{18 \Omega}{9} = 2 \Omega$$

Step 4 is shown in Fig. 9.63, clearly indicating that the short-circuit connection between terminals  $a$  and  $b$  is in parallel with  $R_2$  and eliminates its effect.  $I_N$  is therefore the same as through  $R_1$ , and the full battery voltage appears across  $R_1$  since

$$V_2 = I_2 R_2 = (0)6 \Omega = 0 \text{ V}$$

Therefore,

$$I_N = \frac{E}{R_1} = \frac{9 \text{ V}}{3 \Omega} = 3 \text{ A}$$

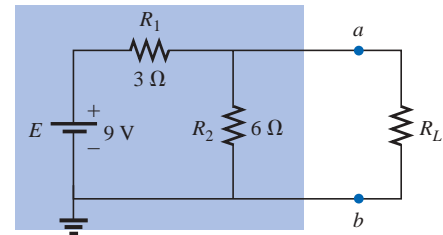


FIG. 9.60

Example 9.11.

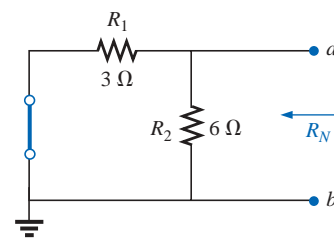


FIG. 9.62

Determining  $R_N$  for the network of Fig. 9.61.


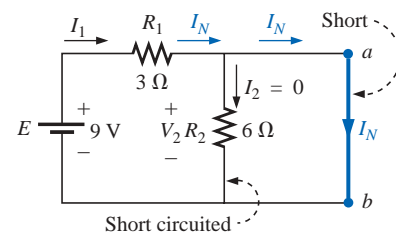



FIG. 9.63

Determining  $I_N$  for the network of Fig. 9.61.

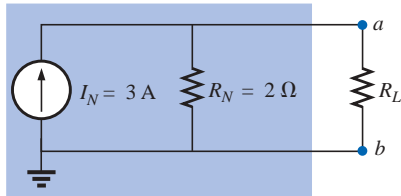


**FIG. 9.64**

Substituting the Norton equivalent circuit for the network external to the resistor  $R_L$  of Fig. 9.60.

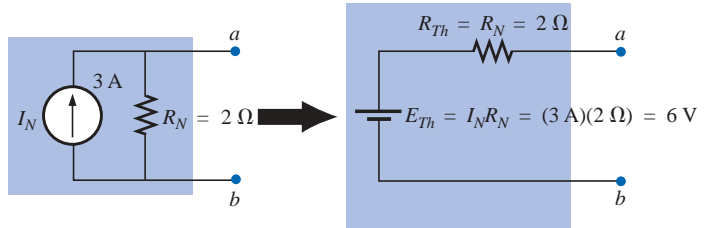

**FIG. 9.65**

Converting the Norton equivalent circuit of Fig. 9.64 to a Thévenin equivalent circuit.

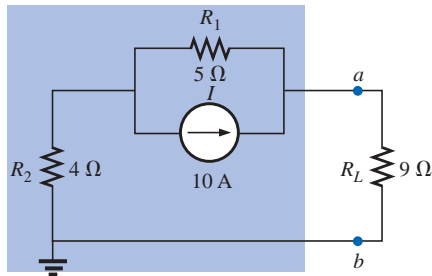


**FIG. 9.66**  
Example 9.12.

**EXAMPLE 9.12** Find the Norton equivalent circuit for the network external to the  $9\text{-}\Omega$  resistor in Fig. 9.66.


**Solution:**

*Steps 1 and 2:* See Fig. 9.67.

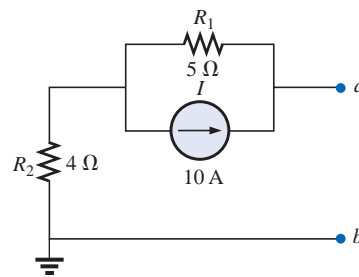

**FIG. 9.67**

Identifying the terminals of particular interest for the network of Fig. 9.66.

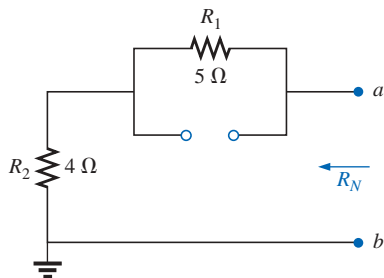

**FIG. 9.68**


Determining  $R_N$  for the network of Fig. 9.67.

*Step 3:* See Fig. 9.68, and

$$R_N = R_1 + R_2 = 5\ \Omega + 4\ \Omega = 9\ \Omega$$

*Step 4:* As shown in Fig. 9.69, the Norton current is the same as the current through the  $4\text{-}\Omega$  resistor. Applying the current divider rule,

$$I_N = \frac{R_1 I}{R_1 + R_2} = \frac{(5\ \Omega)(10\ \text{A})}{5\ \Omega + 4\ \Omega} = \frac{50\ \text{A}}{9} = 5.556\ \text{A}$$

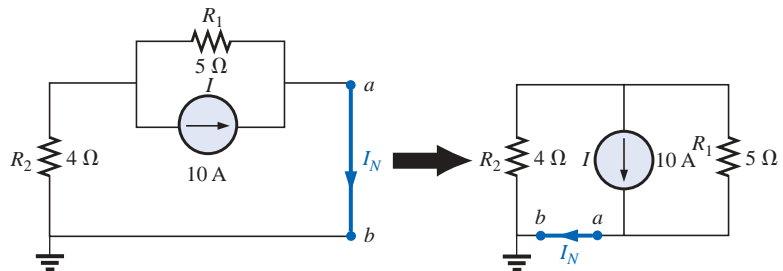


**FIG. 9.69**

Determining  $I_N$  for the network of Fig. 9.67.




Step 5: See Fig. 9.70.

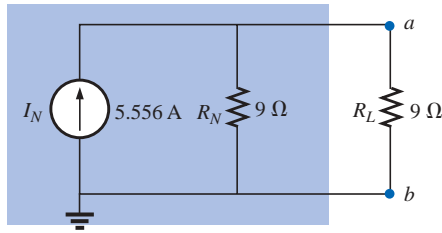

**FIG. 9.70**

Substituting the Norton equivalent circuit for the network external to the resistor  $R_L$  of Fig. 9.66.

**EXAMPLE 9.13** (Two sources) Find the Norton equivalent circuit for the portion of the network to the left of  $a-b$  in Fig. 9.71.

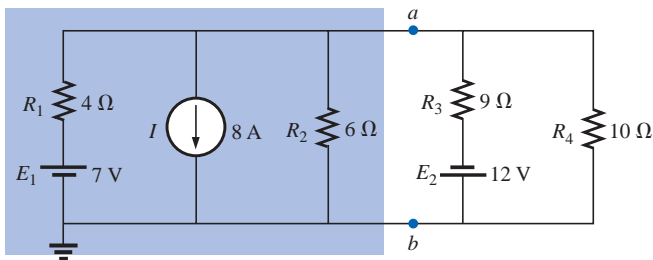


**FIG. 9.71**  
Example 9.13.

**Solution:**

Steps 1 and 2: See Fig. 9.72.

Step 3 is shown in Fig. 9.73, and


$$R_N = R_1 \parallel R_2 = 4 \Omega \parallel 6 \Omega = \frac{(4 \Omega)(6 \Omega)}{4 \Omega + 6 \Omega} = \frac{24 \Omega}{10} = 2.4 \Omega$$

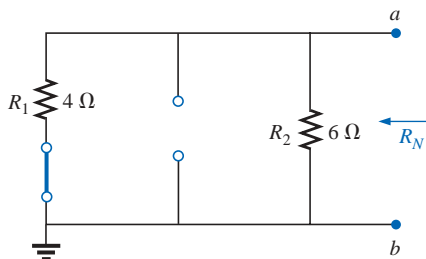

**FIG. 9.73**


Determining  $R_N$  for the network of Fig. 9.72.

Step 4: (Using superposition) For the 7-V battery (Fig. 9.74),

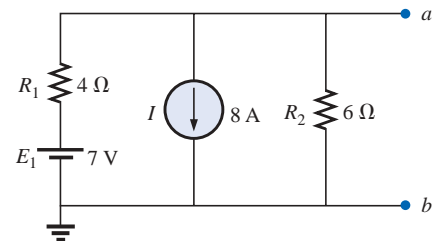

**FIG. 9.72**

Identifying the terminals of particular interest for the network of Fig. 9.71.

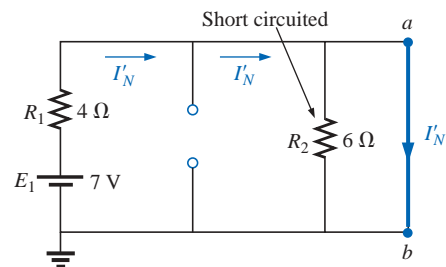

**FIG. 9.74**

Determining the contribution to  $I_N$  from the voltage source  $E_1$ .

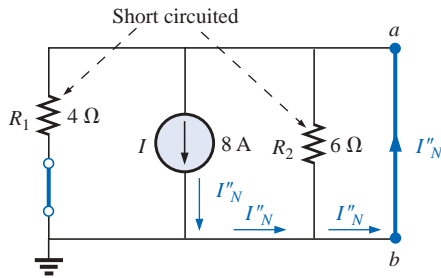


FIG. 9.75

Determining the contribution to  $I_N$  from the current source  $I$ .

$$I'_N = \frac{E_1}{R_1} = \frac{7 \text{ V}}{4 \Omega} = 1.75 \text{ A}$$

For the 8-A source (Fig. 9.75), we find that both  $R_1$  and  $R_2$  have been “short circuited” by the direct connection between  $a$  and  $b$ , and

$$I''_N = I = 8 \text{ A}$$

The result is

$$I_N = I''_N - I'_N = 8 \text{ A} - 1.75 \text{ A} = \mathbf{6.25 \text{ A}}$$

Step 5: See Fig. 9.76.

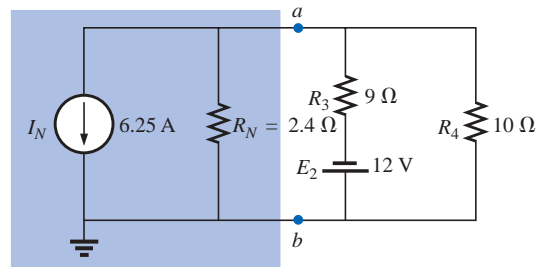


FIG. 9.76

Substituting the Norton equivalent circuit for the network to the left of terminals  $a$ - $b$  in Fig. 9.71.

### Experimental Procedure

The Norton current is measured in the same way as described for the short-circuit current for the Thévenin network. Since the Norton and Thévenin resistances are the same, the same procedures can be employed as described for the Thévenin network.

## 9.5 MAXIMUM POWER TRANSFER THEOREM

The **maximum power transfer theorem** states the following:

*A load will receive maximum power from a linear bilateral dc network when its total resistive value is exactly equal to the Thévenin resistance of the network as “seen” by the load.*

For the network of Fig. 9.77, maximum power will be delivered to the load when

$$R_L = R_{Th} \tag{9.3}$$

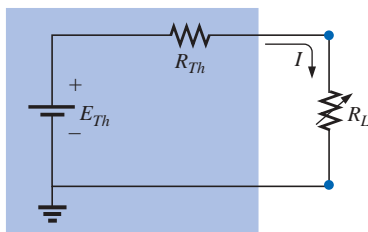
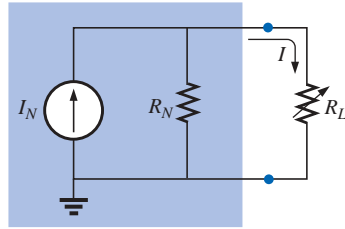


FIG. 9.77

Defining the conditions for maximum power to a load using the Thévenin equivalent circuit.

From past discussions, we realize that a Thévenin equivalent circuit can be found across any element or group of elements in a linear bilateral dc network. Therefore, if we consider the case of the Thévenin equivalent circuit with respect to the maximum power transfer theorem, we are, in essence, considering the *total* effects of any network across a resistor  $R_L$ , such as in Fig. 9.77.

For the Norton equivalent circuit of Fig. 9.78, maximum power will be delivered to the load when


**FIG. 9.78**

Defining the conditions for maximum power to a load using the Norton equivalent circuit.

$$R_L = R_N \quad (9.4)$$

This result [Eq. (9.4)] will be used to its fullest advantage in the analysis of transistor networks, where the most frequently applied transistor circuit model employs a current source rather than a voltage source.

For the network of Fig. 9.77,

$$I = \frac{E_{Th}}{R_{Th} + R_L}$$


and

$$P_L = I^2 R_L = \left( \frac{E_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

so that

$$P_L = \frac{E_{Th}^2 R_L}{(R_{Th} + R_L)^2}$$

Let us now consider an example where  $E_{Th} = 60 \text{ V}$  and  $R_{Th} = 9 \Omega$ , as shown in Fig. 9.79.

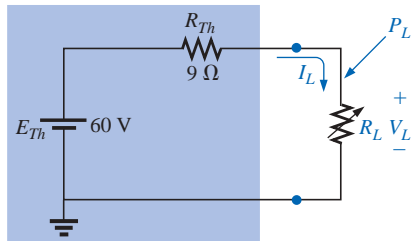
**FIG. 9.79**

Thévenin equivalent network to be used to validate the maximum power transfer theorem.

The power to the load is determined by

$$P_L = \frac{E_{Th}^2 R_L}{(R_{Th} + R_L)^2} = \frac{3600 R_L}{(9 \Omega + R_L)^2}$$

with

$$I_L = \frac{E_{Th}}{R_{Th} + R_L} = \frac{60 \text{ V}}{9 \Omega + R_L}$$

and

$$V_L = \frac{R_L(60 \text{ V})}{R_{Th} + R_L} = \frac{R_L(60 \text{ V})}{9 \Omega + R_L}$$

A tabulation of  $P_L$  for a range of values of  $R_L$  yields Table 9.1. A plot of  $P_L$  versus  $R_L$  using the data of Table 9.1 will result in the plot of Fig. 9.80 for the range  $R_L = 0.1 \Omega$  to  $30 \Omega$ .



TABLE 9.1

$R_L (\Omega)$	$P_L (W)$	$I_L (A)$	$V_L (V)$
0.1	4.35	6.59	0.66
0.2	8.51	6.52	1.30
0.5	19.94	6.32	3.16
1	36.00	6.00	6.00
2	59.50	5.46	10.91
3	75.00	5.00	15.00
4	85.21	4.62	18.46
5	91.84	4.29	21.43
6	96.00	4.00	24.00
7	98.44	3.75	26.25
8	99.65	3.53	28.23
<b>9 (<math>R_{Th}</math>)</b>	<b>100.00 (Maximum)</b>	<b>3.33 (<math>I_{max}/2</math>)</b>	<b>30.00 (<math>E_{Th}/2</math>)</b>
10	99.72	3.16	31.58
11	99.00	3.00	33.00
12	97.96	2.86	34.29
13	96.69	2.73	35.46
14	95.27	2.61	36.52
15	93.75	2.50	37.50
16	92.16	2.40	38.40
17	90.53	2.31	39.23
18	88.89	2.22	40.00
19	87.24	2.14	40.71
20	85.61	2.07	41.38
25	77.86	1.77	44.12
30	71.00	1.54	46.15
40	59.98	1.22	48.98
100	30.30	0.55	55.05
500	6.95	0.12	58.94
1000	3.54	0.06	59.47

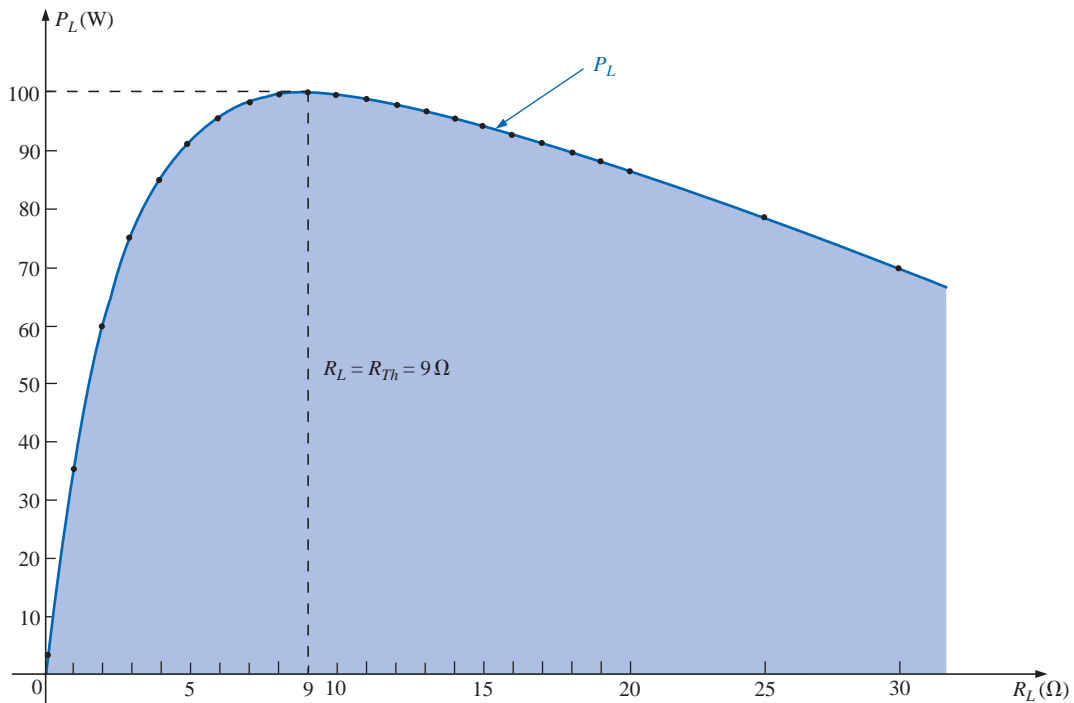



FIG. 9.80

$P_L$  versus  $R_L$  for the network of Fig. 9.79.



Note, in particular, that  $P_L$  is, in fact, a maximum when  $R_L = R_{Th} = 9 \Omega$ . The power curve increases more rapidly toward its maximum value than it decreases after the maximum point, clearly revealing that a small change in load resistance for levels of  $R_L$  below  $R_{Th}$  will have a more dramatic effect on the power delivered than similar changes in  $R_L$  above the  $R_{Th}$  level.

If we plot  $V_L$  and  $I_L$  versus the same resistance scale (Fig. 9.81), we find that both change nonlinearly, with the terminal voltage increasing with an increase in load resistance as the current decreases. Note again that the most dramatic changes in  $V_L$  and  $I_L$  occur for levels of  $R_L$  less than  $R_{Th}$ . As pointed out on the plot, when  $R_L = R_{Th}$ ,  $V_L = E_{Th}/2$  and  $I_L = I_{max}/2$ , with  $I_{max} = E_{Th}/R_{Th}$ .

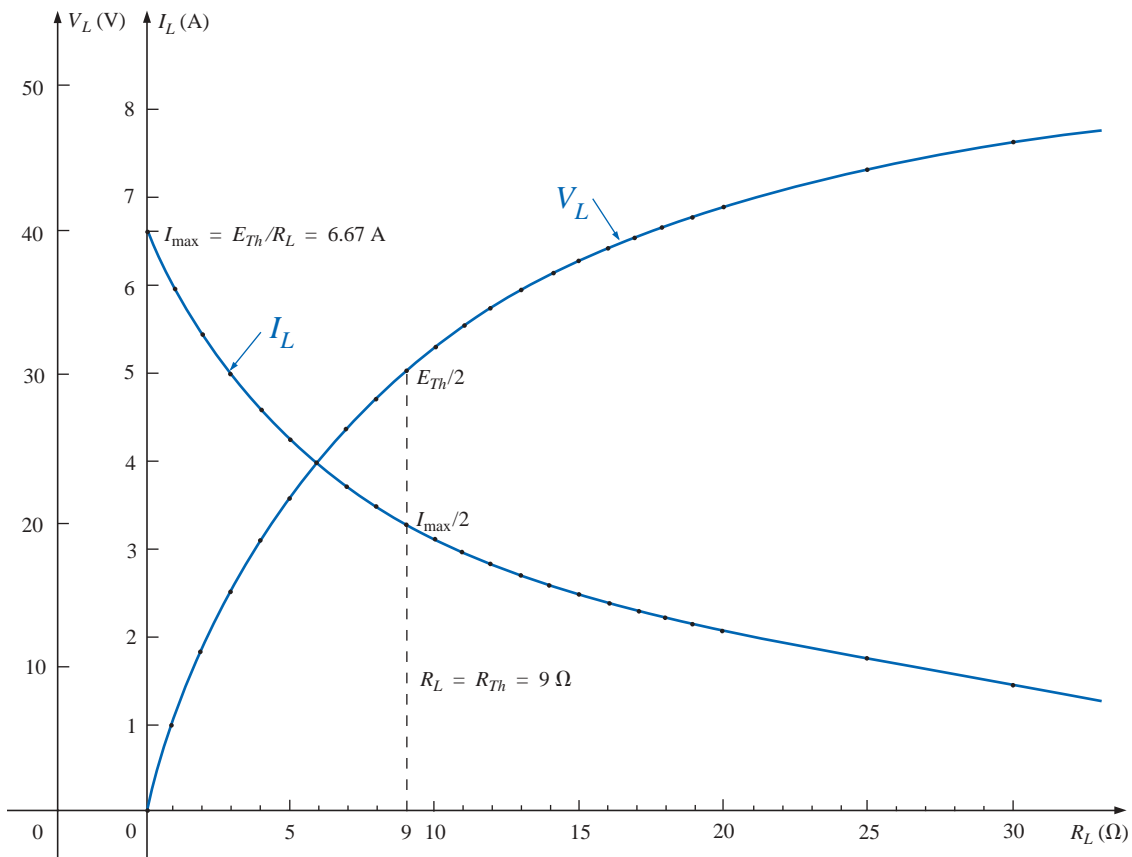

**FIG. 9.81**  
 $V_L$  and  $I_L$  versus  $R_L$  for the network of Fig. 9.79.

The dc operating efficiency of a system is defined by the ratio of the power delivered to the load to the power supplied by the source; that is,

$$\eta\% = \frac{P_L}{P_s} \times 100\% \tag{9.5}$$

For the situation defined by Fig. 9.77,

$$\eta\% = \frac{P_L}{P_s} \times 100\% = \frac{I_L^2 R_L}{I_L^2 R_T} \times 100\%$$



and 
$$\eta\% = \frac{R_L}{R_{Th} + R_L} \times 100\%$$

For  $R_L$  that is small compared to  $R_{Th}$ ,  $R_{Th} \gg R_L$  and  $R_{Th} + R_L \cong R_{Th}$ , with

$$\eta\% \cong \frac{R_L}{R_{Th}} \times 100\% = \underbrace{\left(\frac{1}{R_{Th}}\right)}_{\text{Constant}} R_L \times 100\% = kR_L \times 100\%$$


The resulting percentage efficiency, therefore, will be relatively low (since  $k$  is small) and will increase almost linearly as  $R_L$  increases.

For situations where the load resistance  $R_L$  is much larger than  $R_{Th}$ ,  $R_L \gg R_{Th}$  and  $R_{Th} + R_L \cong R_L$ .

$$\eta\% = \frac{R_L}{R_L} \times 100\% = 100\%$$

The efficiency therefore increases linearly and dramatically for small levels of  $R_L$  and then begins to level off as it approaches the 100% level for very large values of  $R_L$ , as shown in Fig. 9.82. Keep in mind, however, that the efficiency criterion is sensitive only to the ratio of  $P_L$  to  $P_s$  and not to their actual levels. At efficiency levels approaching 100%, the power delivered to the load may be so small as to have little practical value. Note the low level of power to the load in Table 9.1 when  $R_L = 1000 \Omega$ , even though the efficiency level will be

$$\eta\% = \frac{R_L}{R_{Th} + R_L} \times 100\% = \frac{1000}{1009} \times 100\% = 99.11\%$$

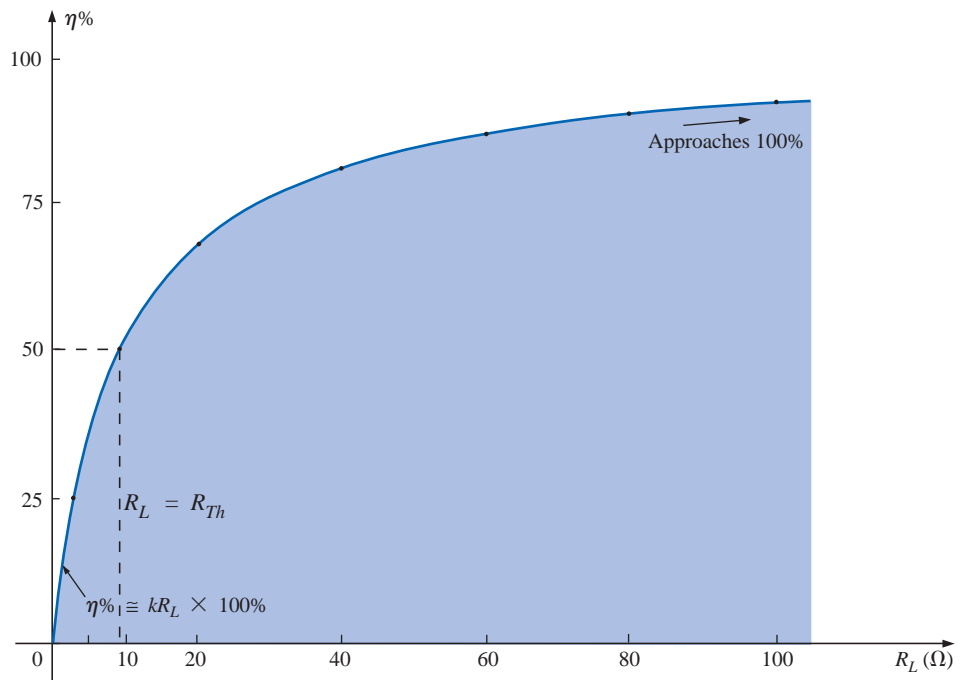

**FIG. 9.82**

*Efficiency of operation versus increasing values of  $R_L$ .*



When  $R_L = R_{Th}$ ,

$$\eta\% = \frac{R_L}{R_{Th} + R_L} \times 100\% = \frac{R_L}{2R_L} \times 100\% = \mathbf{50\%}$$

Under maximum power transfer conditions, therefore,  $P_L$  is a maximum, but the dc efficiency is only 50%; that is, only half the power delivered by the source is getting to the load.

A relatively low efficiency of 50% can be tolerated in situations where power levels are relatively low, such as in a wide variety of electronic systems. However, when large power levels are involved, such as at generating stations, efficiencies of 50% would not be acceptable. In fact, a great deal of expense and research is dedicated to raising power-generating and transmission efficiencies a few percentage points. Raising an efficiency level of a 10-mega-kW power plant from 94% to 95% (a 1% increase) can save 0.1 mega-kW, or 100 million watts, of power—an enormous saving!

Consider a change in load levels from  $9\ \Omega$  to  $20\ \Omega$ . In Fig. 9.80, the power level has dropped from 100 W to 85.61 W (a 14.4% drop), but the efficiency has increased substantially to 69% (a 38% increase), as shown in Fig. 9.82. For each application, therefore, a balance point must be identified where the efficiency is sufficiently high without reducing the power to the load to insignificant levels.

Figure 9.83 is a semilog plot of  $P_L$  and the power delivered by the source  $P_s = E_{Th}I_L$  versus  $R_L$  for  $E_{Th} = 60\ \text{V}$  and  $R_{Th} = 9\ \Omega$ . A semilog graph employs one log scale and one linear scale, as implied by the prefix *semi*, meaning *half*. Log scales are discussed in detail in Chapter 23. For the moment, note the wide range of  $R_L$  permitted using the log scale compared to Figs. 9.80 through 9.82.

It is now quite clear that the  $P_L$  curve has only one maximum (at  $R_L = R_{Th}$ ), whereas  $P_s$  decreases for every increase in  $R_L$ . In particular, note that for low levels of  $R_L$ , only a small portion of the power delivered by the source makes it to the load. In fact, even when  $R_L = R_{Th}$ , the source is generating twice the power absorbed by the load. For values of  $R_L$  greater than  $R_{Th}$ , the two curves approach each other until eventually they are essentially the same at high levels of  $R_L$ . For the range  $R_L = R_{Th} = 9\ \Omega$  to  $R_L = 100\ \Omega$ ,  $P_L$  and  $P_s$  are relatively close in magnitude, suggesting that this would be an appropriate range of operation, since a majority of the power delivered by the source is getting to the load and the power levels are still significant.

The power delivered to  $R_L$  under maximum power conditions ( $R_L = R_{Th}$ ) is

$$I = \frac{E_{Th}}{R_{Th} + R_L} = \frac{E_{Th}}{2R_{Th}}$$


$$P_L = I^2 R_L = \left( \frac{E_{Th}}{2R_{Th}} \right)^2 R_{Th} = \frac{E_{Th}^2 R_{Th}}{4R_{Th}^2}$$

and

$$P_{L_{\max}} = \frac{E_{Th}^2}{4R_{Th}} \quad (\text{watts, W}) \quad (9.6)$$

For the Norton circuit of Fig. 9.78,


$$P_{L_{\max}} = \frac{I_N^2 R_N}{4} \quad (\text{W}) \quad (9.7)$$

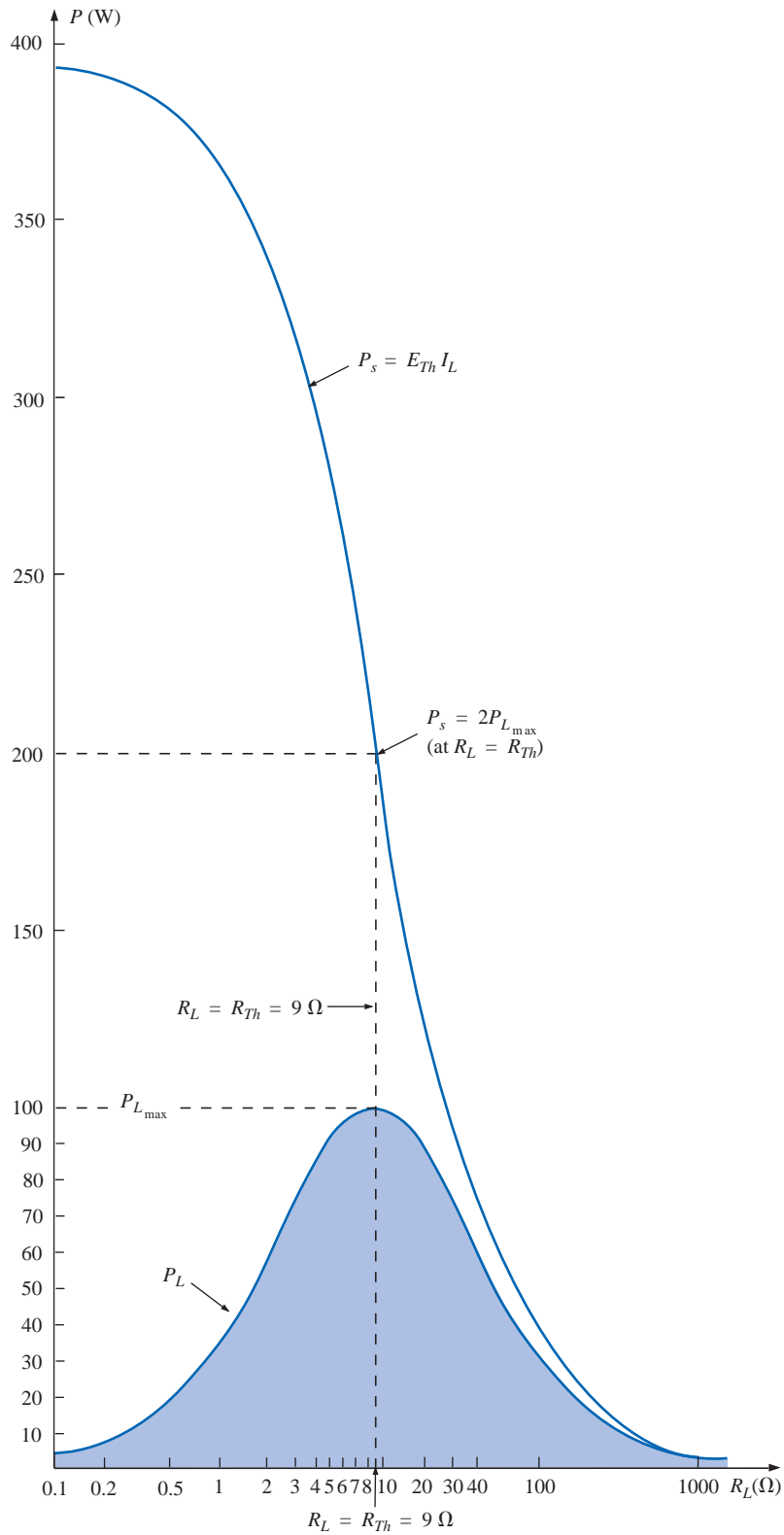

**FIG. 9.83**  
 $P_s$  and  $P_L$  versus  $R_L$  for the network of Fig. 9.79.



**EXAMPLE 9.14** A dc generator, battery, and laboratory supply are connected to a resistive load  $R_L$  in Fig. 9.84(a), (b), and (c), respectively.

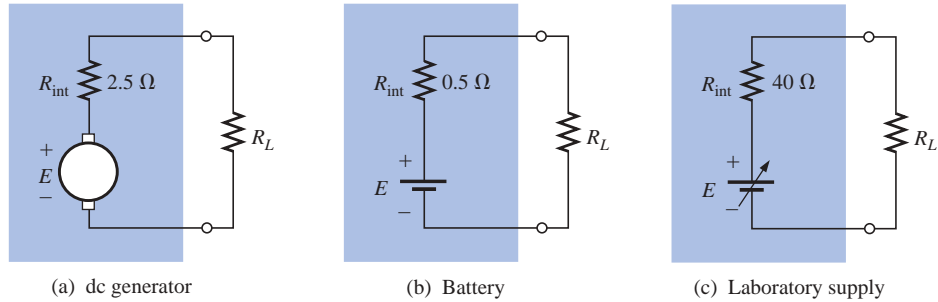

**FIG. 9.84**  
Example 9.14.

- For each, determine the value of  $R_L$  for maximum power transfer to  $R_L$ .
- Determine  $R_L$  for 75% efficiency.

**Solutions:**

- For the dc generator,

$$R_L = R_{Th} = R_{\text{int}} = 2.5 \, \Omega$$

For the battery,

$$R_L = R_{Th} = R_{\text{int}} = 0.5 \, \Omega$$

For the laboratory supply,

$$R_L = R_{Th} = R_{\text{int}} = 40 \, \Omega$$

- For the dc generator,

$$\eta = \frac{P_o}{P_s} \quad (\eta \text{ in decimal form})$$

$$\eta = \frac{R_L}{R_{Th} + R_L}$$

$$\eta(R_{Th} + R_L) = R_L$$

$$\eta R_{Th} + \eta R_L = R_L$$

$$R_L(1 - \eta) = \eta R_{Th}$$


and

$$\boxed{R_L = \frac{\eta R_{Th}}{1 - \eta}} \quad (9.8)$$


$$R_L = \frac{0.75(2.5 \, \Omega)}{1 - 0.75} = 7.5 \, \Omega$$

For the battery,


$$R_L = \frac{0.75(0.5 \, \Omega)}{1 - 0.75} = 1.5 \, \Omega$$

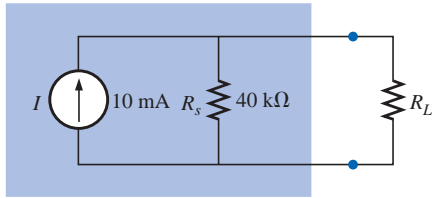


**FIG. 9.85**  
Example 9.15.

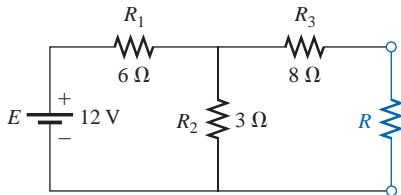


**FIG. 9.86**  
Example 9.16.

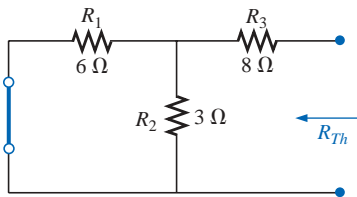

**FIG. 9.87**  
Determining  $R_{Th}$  for the network external to the resistor  $R$  of Fig. 9.86.

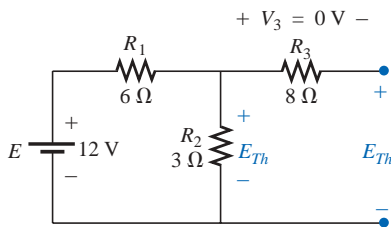

**FIG. 9.88**  
Determining  $E_{Th}$  for the network external to the resistor  $R$  of Fig. 9.86.

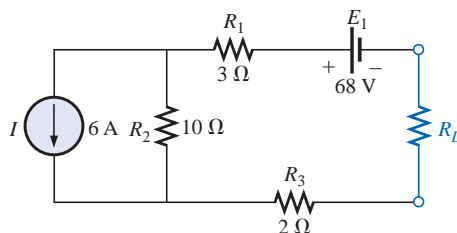

**FIG. 9.89**  
Example 9.17.

For the laboratory supply,

$$R_L = \frac{0.75(40 \Omega)}{1 - 0.75} = 120 \Omega$$

The results of Example 9.14 reveal that the following modified form of the **maximum power transfer theorem** is valid:

*For loads connected directly to a dc voltage supply, maximum power will be delivered to the load when the load resistance is equal to the internal resistance of the source; that is, when*

$$R_L = R_{int} \tag{9.9}$$

**EXAMPLE 9.15** Analysis of a transistor network resulted in the reduced configuration of Fig. 9.85. Determine the  $R_L$  necessary to transfer maximum power to  $R_L$ , and calculate the power of  $R_L$  under these conditions.

**Solution:** Eq. (9.4):

$$R_L = R_s = 40 \text{ k}\Omega$$

Eq. (9.7):

$$P_{L_{max}} = \frac{I_N^2 R_N}{4} = \frac{(10 \text{ mA})^2 (40 \text{ k}\Omega)}{4} = 1 \text{ W}$$

**EXAMPLE 9.16** For the network of Fig. 9.86, determine the value of  $R$  for maximum power to  $R$ , and calculate the power delivered under these conditions.

**Solution:** See Fig. 9.87.

$$R_{Th} = R_3 + R_1 \parallel R_2 = 8 \Omega + \frac{(6 \Omega)(3 \Omega)}{6 \Omega + 3 \Omega} = 8 \Omega + 2 \Omega$$

and

$$R = R_{Th} = 10 \Omega$$

See Fig. 9.88.

$$E_{Th} = \frac{R_2 E}{R_2 + R_1} = \frac{(3 \Omega)(12 \text{ V})}{3 \Omega + 6 \Omega} = \frac{36 \text{ V}}{9} = 4 \text{ V}$$

and, by Eq. (9.6),

$$P_{L_{max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(4 \text{ V})^2}{4(10 \Omega)} = 0.4 \text{ W}$$

**EXAMPLE 9.17** Find the value of  $R_L$  in Fig. 9.89 for maximum power to  $R_L$ , and determine the maximum power.

**Solution:** See Fig. 9.90.

$$R_{Th} = R_1 + R_2 + R_3 = 3 \Omega + 10 \Omega + 2 \Omega = 15 \Omega$$

and

$$R_L = R_{Th} = 15 \Omega$$



Note Fig. 9.91, where

$$V_1 = V_3 = 0 \text{ V}$$

and  $V_2 = I_2 R_2 = I R_2 = (6 \text{ A})(10 \Omega) = 60 \text{ V}$

Applying Kirchhoff's voltage law,

$$\sum_{\mathcal{C}} V = -V_2 - E_1 + E_{Th} = 0$$

and  $E_{Th} = V_2 + E_1 = 60 \text{ V} + 68 \text{ V} = 128 \text{ V}$

Thus,  $P_{L_{\max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(128 \text{ V})^2}{4(15 \Omega)} = 273.07 \text{ W}$

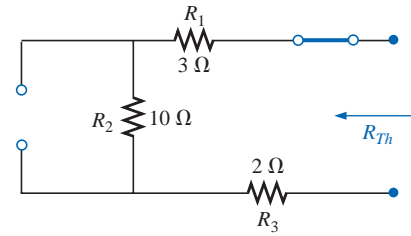


FIG. 9.90

Determining  $R_{Th}$  for the network external to the resistor  $R_L$  of Fig. 9.89.

## 9.6 MILLMAN'S THEOREM

Through the application of **Millman's theorem**, any number of parallel voltage sources can be reduced to one. In Fig. 9.92, for example, the three voltage sources can be reduced to one. This would permit finding the current through or voltage across  $R_L$  without having to apply a method such as mesh analysis, nodal analysis, superposition, and so on. The theorem can best be described by applying it to the network of Fig. 9.92. Basically, three steps are included in its application.

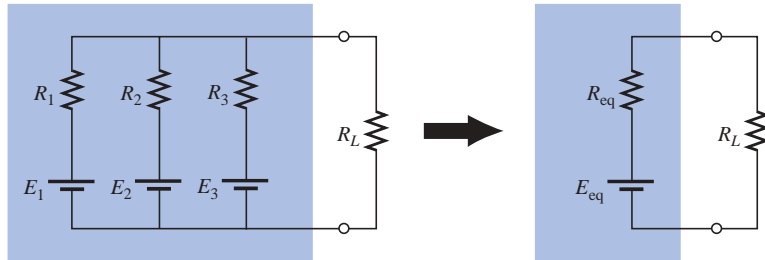


FIG. 9.92

Demonstrating the effect of applying Millman's theorem.

*Step 1:* Convert all voltage sources to current sources as outlined in Section 8.3. This is performed in Fig. 9.93 for the network of Fig. 9.92.

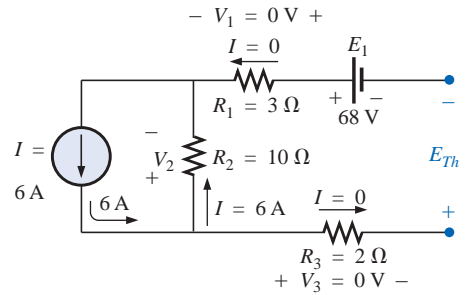


FIG. 9.91

Determining  $E_{Th}$  for the network external to the resistor  $R_L$  of Fig. 9.89.



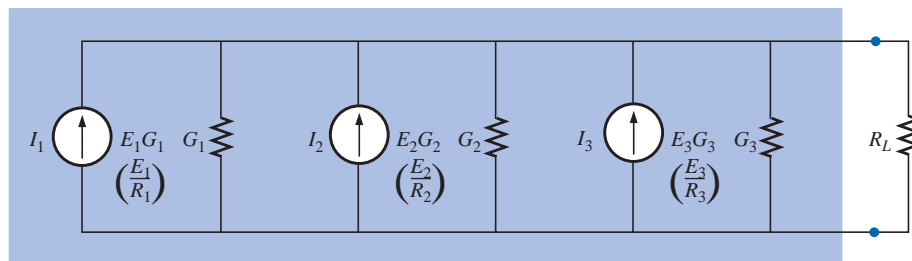


FIG. 9.93

Converting all the sources of Fig. 9.92 to current sources.

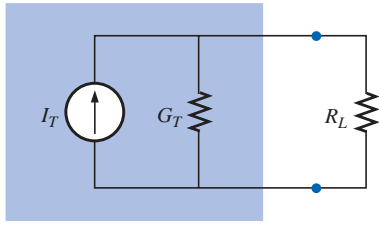

**FIG. 9.94**  
Reducing all the current sources of Fig. 9.93 to a single current source.

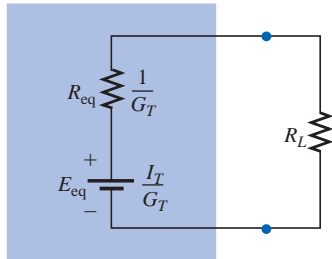

**FIG. 9.95**  
Converting the current source of Fig. 9.94 to a voltage source.

*Step 2:* Combine parallel current sources as described in Section 8.4. The resulting network is shown in Fig. 9.94, where

$$I_T = I_1 + I_2 + I_3 \quad \text{and} \quad G_T = G_1 + G_2 + G_3$$

*Step 3:* Convert the resulting current source to a voltage source, and the desired single-source network is obtained, as shown in Fig. 9.95.

In general, Millman's theorem states that for any number of parallel voltage sources,

$$E_{\text{eq}} = \frac{I_T}{G_T} = \frac{\pm I_1 \pm I_2 \pm I_3 \pm \dots \pm I_N}{G_1 + G_2 + G_3 + \dots + G_N}$$

or

$$E_{\text{eq}} = \frac{\pm E_1 G_1 \pm E_2 G_2 \pm E_3 G_3 \pm \dots \pm E_N G_N}{G_1 + G_2 + G_3 + \dots + G_N} \quad (9.10)$$

The plus-and-minus signs appear in Eq. (9.10) to include those cases where the sources may not be supplying energy in the same direction. (Note Example 9.18.)

The equivalent resistance is

$$R_{\text{eq}} = \frac{1}{G_T} = \frac{1}{G_1 + G_2 + G_3 + \dots + G_N} \quad (9.11)$$


In terms of the resistance values,

$$E_{\text{eq}} = \frac{\pm \frac{E_1}{R_1} \pm \frac{E_2}{R_2} \pm \frac{E_3}{R_3} \pm \dots \pm \frac{E_N}{R_N}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}} \quad (9.12)$$

and

$$R_{\text{eq}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}} \quad (9.13)$$

The relatively few direct steps required may result in the student's applying each step rather than memorizing and employing Eqs. (9.10) through (9.13).

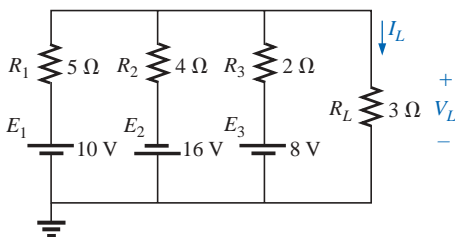

**FIG. 9.96**  
Example 9.18.

**EXAMPLE 9.18** Using Millman's theorem, find the current through and voltage across the resistor  $R_L$  of Fig. 9.96.

**Solution:** By Eq. (9.12),

$$E_{\text{eq}} = \frac{+\frac{E_1}{R_1} - \frac{E_2}{R_2} + \frac{E_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

The minus sign is used for  $E_2/R_2$  because that supply has the opposite polarity of the other two. The chosen reference direction is therefore



that of  $E_1$  and  $E_3$ . The total conductance is unaffected by the direction, and

$$E_{\text{eq}} = \frac{+\frac{10\text{ V}}{5\ \Omega} - \frac{16\text{ V}}{4\ \Omega} + \frac{8\text{ V}}{2\ \Omega}}{\frac{1}{5\ \Omega} + \frac{1}{4\ \Omega} + \frac{1}{2\ \Omega}} = \frac{2\text{ A} - 4\text{ A} + 4\text{ A}}{0.2\text{ S} + 0.25\text{ S} + 0.5\text{ S}}$$

$$= \frac{2\text{ A}}{0.95\text{ S}} = \mathbf{2.105\text{ V}}$$

with

$$R_{\text{eq}} = \frac{1}{\frac{1}{5\ \Omega} + \frac{1}{4\ \Omega} + \frac{1}{2\ \Omega}} = \frac{1}{0.95\text{ S}} = \mathbf{1.053\ \Omega}$$

The resultant source is shown in Fig. 9.97, and

$$I_L = \frac{2.105\text{ V}}{1.053\ \Omega + 3\ \Omega} = \frac{2.105\text{ V}}{4.053\ \Omega} = \mathbf{0.519\text{ A}}$$

with

$$V_L = I_L R_L = (0.519\text{ A})(3\ \Omega) = \mathbf{1.557\text{ V}}$$

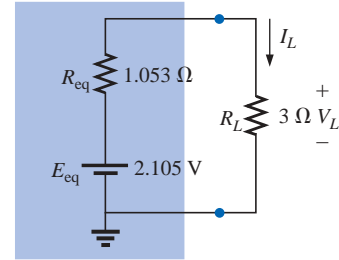


FIG. 9.97

The result of applying Millman's theorem to the network of Fig. 9.96.

**EXAMPLE 9.19** Let us now consider the type of problem encountered in the introduction to mesh and nodal analysis in Chapter 8. Mesh analysis was applied to the network of Fig. 9.98 (Example 8.12). Let us now use Millman's theorem to find the current through the 2- $\Omega$  resistor and compare the results.

**Solutions:**

- a. Let us first apply each step and, in the (b) solution, Eq. (9.12). Converting sources yields Fig. 9.99. Combining sources and parallel conductance branches (Fig. 9.100) yields

$$I_T = I_1 + I_2 = 5\text{ A} + \frac{5}{3}\text{ A} = \frac{15}{3}\text{ A} + \frac{5}{3}\text{ A} = \frac{20}{3}\text{ A}$$

$$G_T = G_1 + G_2 = 1\text{ S} + \frac{1}{6}\text{ S} = \frac{6}{6}\text{ S} + \frac{1}{6}\text{ S} = \frac{7}{6}\text{ S}$$

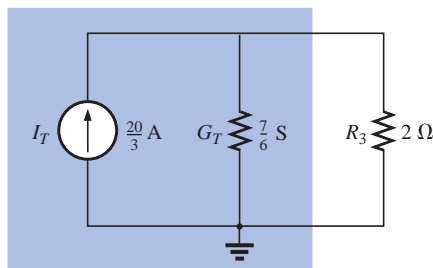


FIG. 9.100

Reducing the current sources of Fig. 9.99 to a single source.

Converting the current source to a voltage source (Fig. 9.101), we obtain

$$E_{\text{eq}} = \frac{I_T}{G_T} = \frac{\frac{20}{3}\text{ A}}{\frac{7}{6}\text{ S}} = \frac{(6)(20)}{(3)(7)}\text{ V} = \frac{\mathbf{40}}{\mathbf{7}}\text{ V}$$

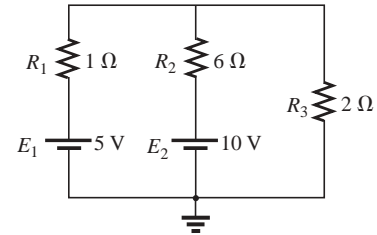


FIG. 9.98

Example 9.19.

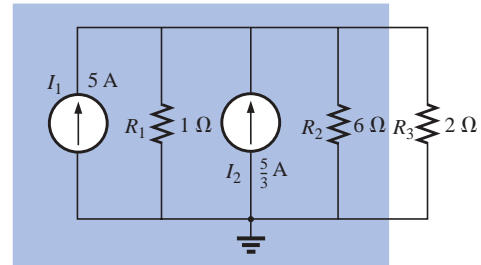


FIG. 9.99

Converting the sources of Fig. 9.98 to current sources.

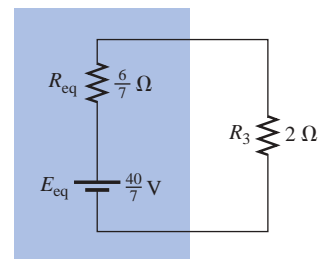


FIG. 9.101

Converting the current source of Fig. 9.100 to a voltage source.

and 
$$R_{\text{eq}} = \frac{1}{G_T} = \frac{1}{\frac{7}{6} \text{ S}} = \frac{6}{7} \Omega$$

so that

$$I_{2\Omega} = \frac{E_{\text{eq}}}{R_{\text{eq}} + R_3} = \frac{\frac{40}{7} \text{ V}}{\frac{6}{7} \Omega + 2 \Omega} = \frac{\frac{40}{7} \text{ V}}{\frac{6}{7} \Omega + \frac{14}{7} \Omega} = \frac{40 \text{ V}}{20 \Omega} = 2 \text{ A}$$

which agrees with the result obtained in Example 8.18.

b. Let us now simply apply the proper equation, Eq. (9.12):

$$E_{\text{eq}} = \frac{+\frac{5 \text{ V}}{1 \Omega} + \frac{10 \text{ V}}{6 \Omega}}{\frac{1}{1 \Omega} + \frac{1}{6 \Omega}} = \frac{\frac{30 \text{ V}}{6 \Omega} + \frac{10 \text{ V}}{6 \Omega}}{\frac{6}{6 \Omega} + \frac{1}{6 \Omega}} = \frac{40}{7} \text{ V}$$

and

$$R_{\text{eq}} = \frac{1}{\frac{1}{1 \Omega} + \frac{1}{6 \Omega}} = \frac{1}{\frac{6}{6 \Omega} + \frac{1}{6 \Omega}} = \frac{1}{\frac{7}{6} \text{ S}} = \frac{6}{7} \Omega$$

which are the same values obtained above.

The dual of Millman's theorem (Fig. 9.92) appears in Fig. 9.102. It can be shown that  $I_{\text{eq}}$  and  $R_{\text{eq}}$ , as in Fig. 9.102, are given by

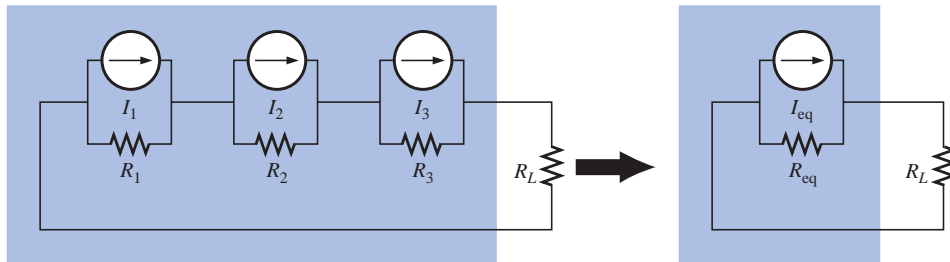


FIG. 9.102

The dual effect of Millman's theorem.

$$I_{\text{eq}} = \frac{\pm I_1 R_1 \pm I_2 R_2 \pm I_3 R_3}{R_1 + R_2 + R_3} \quad (9.14)$$

and

$$R_{\text{eq}} = R_1 + R_2 + R_3 \quad (9.15)$$

The derivation will appear as a problem at the end of the chapter.

## 9.7 SUBSTITUTION THEOREM


The **substitution theorem** states the following:

*If the voltage across and the current through any branch of a dc bilateral network are known, this branch can be replaced by any*




*combination of elements that will maintain the same voltage across and current through the chosen branch.*

More simply, the theorem states that for branch equivalence, the terminal voltage and current must be the same. Consider the circuit of Fig. 9.103, in which the voltage across and current through the branch  $a-b$  are determined. Through the use of the substitution theorem, a number of equivalent  $a-a'$  branches are shown in Fig. 9.104.

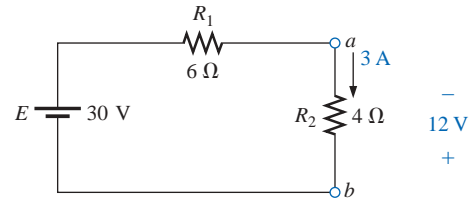

**FIG. 9.103**

*Demonstrating the effect of the substitution theorem.*

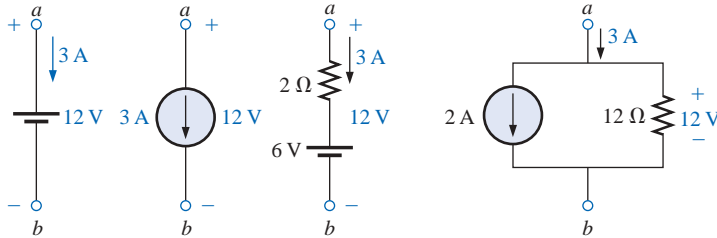


**FIG. 9.104**

*Equivalent branches for the branch  $a-b$  of Fig. 9.103.*

Note that for each equivalent, the terminal voltage and current are the same. Also consider that the response of the remainder of the circuit of Fig. 9.103 is unchanged by substituting any one of the equivalent branches. As demonstrated by the single-source equivalents of Fig. 9.104, *a known potential difference and current in a network can be replaced by an ideal voltage source and current source, respectively.*

Understand that this theorem cannot be used to *solve* networks with two or more sources that are not in series or parallel. For it to be applied, a potential difference or current value must be known or found using one of the techniques discussed earlier. One application of the theorem is shown in Fig. 9.105. Note that in the figure the known potential difference  $V$  was replaced by a voltage source, permitting the isolation of the portion of the network including  $R_3$ ,  $R_4$ , and  $R_5$ . Recall that this was basically the approach employed in the analysis of the ladder network as we worked our way back toward the terminal resistance  $R_5$ .

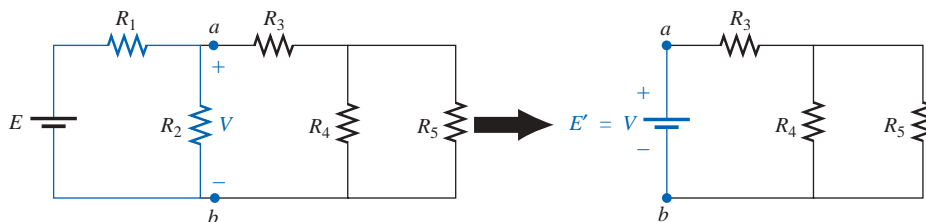

**FIG. 9.105**

*Demonstrating the effect of knowing a voltage at some point in a complex network.*

The current source equivalence of the above is shown in Fig. 9.106, where a known current is replaced by an ideal current source, permitting the isolation of  $R_4$  and  $R_5$ .

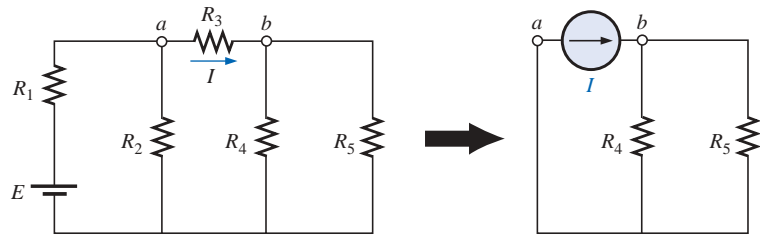


FIG. 9.106

Demonstrating the effect of knowing a current at some point in a complex network.

You will also recall from the discussion of bridge networks that  $V = 0$  and  $I = 0$  were replaced by a short circuit and an open circuit, respectively. This substitution is a very specific application of the substitution theorem.

### 9.8 RECIPROcity THEOREM

The **reciprocity theorem** is applicable only to single-source networks. It is, therefore, not a theorem employed in the analysis of multisource networks described thus far. The theorem states the following:

*The current  $I$  in any branch of a network, due to a single voltage source  $E$  anywhere else in the network, will equal the current through the branch in which the source was originally located if the source is placed in the branch in which the current  $I$  was originally measured.*

In other words, the location of the voltage source and the resulting current may be interchanged without a change in current. The theorem requires that the polarity of the voltage source have the same correspondence with the direction of the branch current in each position.

In the representative network of Fig. 9.107(a), the current  $I$  due to the voltage source  $E$  was determined. If the position of each is interchanged as shown in Fig. 9.107(b), the current  $I$  will be the same value as indicated. To demonstrate the validity of this statement and the theorem, consider the network of Fig. 9.108, in which values for the elements of Fig. 9.107(a) have been assigned.

The total resistance is

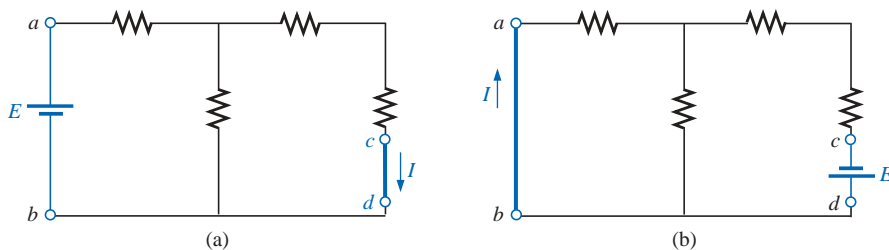
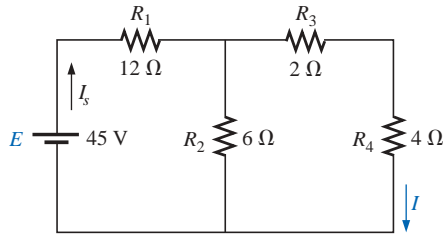


FIG. 9.107

Demonstrating the impact of the reciprocity theorem.


**FIG. 9.108**

Finding the current  $I$  due to a source  $E$ .

$$R_T = R_1 + R_2 \parallel (R_3 + R_4) = 12 \Omega + 6 \Omega \parallel (2 \Omega + 4 \Omega) \\ = 12 \Omega + 6 \Omega \parallel 6 \Omega = 12 \Omega + 3 \Omega = 15 \Omega$$

and 
$$I_s = \frac{E}{R_T} = \frac{45 \text{ V}}{15 \Omega} = 3 \text{ A}$$

with 
$$I = \frac{3 \text{ A}}{2} = 1.5 \text{ A}$$

For the network of Fig. 9.109, which corresponds to that of Fig. 9.107(b), we find


$$R_T = R_4 + R_3 + R_1 \parallel R_2 \\ = 4 \Omega + 2 \Omega + 12 \Omega \parallel 6 \Omega = 10 \Omega$$

and 
$$I_s = \frac{E}{R_T} = \frac{45 \text{ V}}{10 \Omega} = 4.5 \text{ A}$$


so that 
$$I = \frac{(6 \Omega)(4.5 \text{ A})}{12 \Omega + 6 \Omega} = \frac{4.5 \text{ A}}{3} = 1.5 \text{ A}$$

which agrees with the above.

The uniqueness and power of such a theorem can best be demonstrated by considering a complex, single-source network such as the one shown in Fig. 9.110.

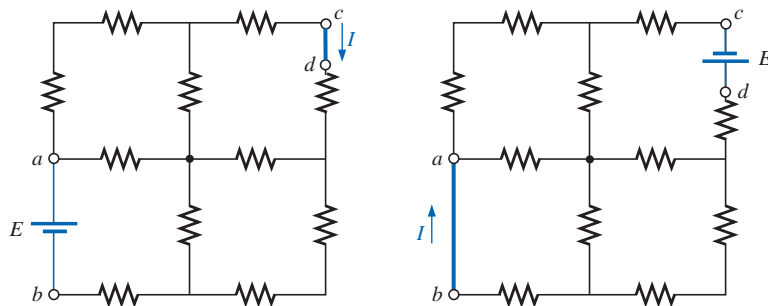
**FIG. 9.110**

Demonstrating the power and uniqueness of the reciprocity theorem.

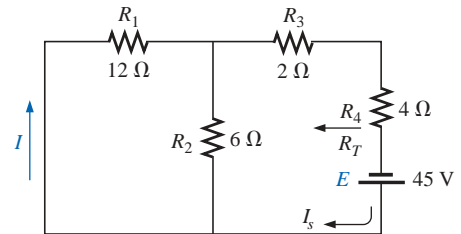
**FIG. 9.109**

Interchanging the location of  $E$  and  $I$  of Fig. 9.108 to demonstrate the validity of the reciprocity theorem.

## 9.9 APPLICATION

### Speaker System

One of the most common applications of the maximum power transfer theorem introduced in this chapter is to speaker systems. An audio amplifier (amplifier with a frequency range matching the typical range

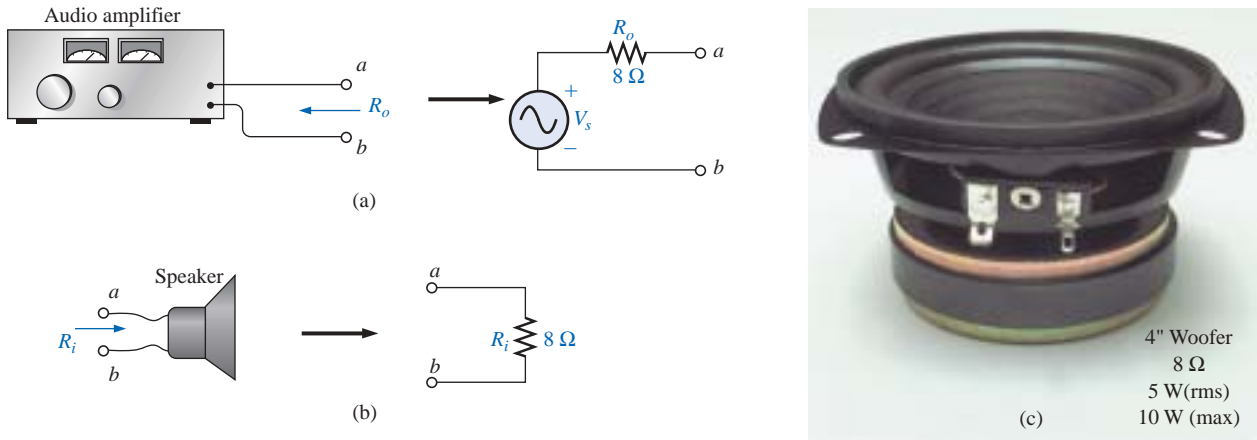


FIG. 9.111

Components of a speaker system: (a) amplifier; (b) speaker; (c) commercially available unit.

of the human ear) with an output impedance of  $8\ \Omega$  is shown in Fig. 9.111(a). *Impedance* is a term applied to opposition in ac networks—for the moment think of it as a resistance level. We can also think of impedance as the internal resistance of the source which is normally shown in series with the source voltage as shown in the same figure. Every speaker has an internal resistance that can be represented as shown in Fig. 9.111(b) for a standard  $8\text{-}\Omega$  speaker. Figure 9.111(c) is a photograph of a commercially available  $8\text{-}\Omega$  woofer (for very low frequencies). The primary purpose of the following discussion is to shed some light on how the audio power can be distributed and which approach would be the most effective.

Since the maximum power theorem states that the load impedance should match the source impedance for maximum power transfer, let us first consider the case of a single  $8\text{-}\Omega$  speaker as shown in Fig. 9.112(a) with an applied amplifier voltage of  $12\text{ V}$ . Since the applied voltage will split equally, the speaker voltage is  $6\text{ V}$ , and the power to the speaker is a maximum value of  $P = V^2/R = (6\text{ V})^2/8\ \Omega = 4.5\text{ W}$ .

If we have two  $8\text{-}\Omega$  speakers that we would like to hook up, we have the choice of hooking them up in series or parallel. For the series configuration of Fig. 9.112(b), the resulting current would be  $I = E/R = 12\text{ V}/24\ \Omega = 500\text{ mA}$ , and the power to each speaker would be  $P = I^2R = (500\text{ mA})^2(8\ \Omega) = 2\text{ W}$ , which is a drop of over 50% from the maximum output level of  $4.5\text{ W}$ . If the speakers are hooked up in parallel as shown in Fig. 9.112(c), the total resistance of the parallel combination is  $4\ \Omega$ , and the voltage across each speaker as determined by the voltage divider rule will be  $4\text{ V}$ . The power to each speaker is  $P = V^2/R = (4\text{ V})^2/8\ \Omega = 2\text{ W}$  which, interestingly enough, is the same power delivered to each speaker whether in series or parallel. However, the parallel arrangement is normally chosen for a variety of reasons. First, when the speakers are connected in parallel, if a wire should become disconnected from one of the speakers due simply to the vibration caused by the emitted sound, the other speakers will still be operating—perhaps not at maximum efficiency, but they will still be operating. If in series they would all fail to operate. A second reason relates to the general wiring procedure. When all of the speakers are in parallel, from various parts of a room all the red wires can be connected together and all the black wires together. If the speakers are in series, and if you

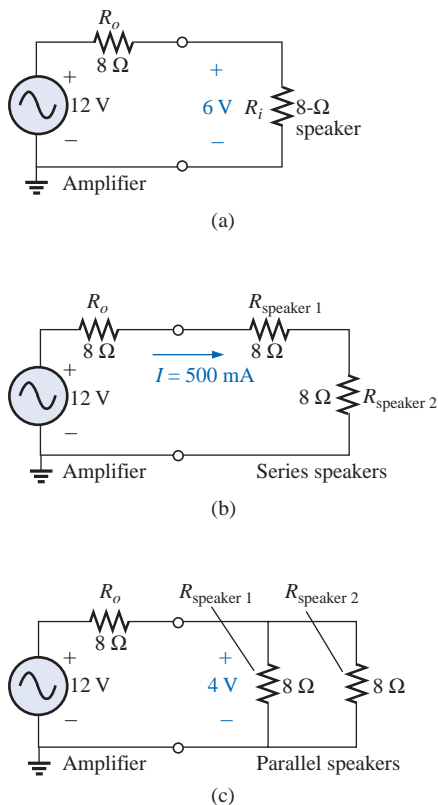



FIG. 9.112

Speaker connections: (a) single unit; (b) in series; (c) in parallel.



are presented with a bundle of red and black wires in the basement, you would first have to determine which wires go with which speakers.

Speakers are also available with input impedances of  $4\ \Omega$  and  $16\ \Omega$ . If you know that the output impedance is  $8\ \Omega$ , purchasing either two  $4\text{-}\Omega$  speakers or two  $16\text{-}\Omega$  speakers would result in maximum power to the speakers as shown in Fig. 9.113. The  $16\text{-}\Omega$  speakers would be connected in parallel and the  $4\text{-}\Omega$  speakers in series to establish a total load impedance of  $8\ \Omega$ .

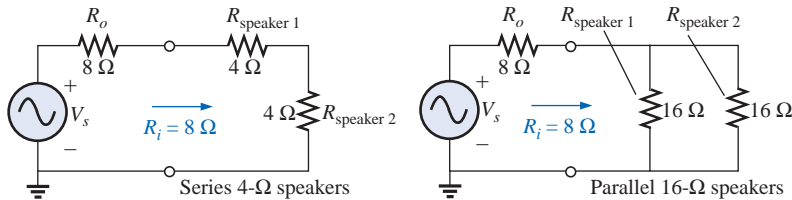

**FIG. 9.113**

*Applying  $4\text{-}\Omega$  and  $16\text{-}\Omega$  speakers to an amplifier with an output impedance of  $8\ \Omega$ .*

In any case, always try to match the total resistance of the speaker load to the output resistance of the supply. Yes, a  $4\text{-}\Omega$  speaker can be placed in series with a parallel combination of  $8\text{-}\Omega$  speakers for maximum power transfer from the supply since the total resistance will be  $8\ \Omega$ . However, the power distribution will not be equal, with the  $4\text{-}\Omega$  speaker receiving  $2.25\ \text{W}$  and the  $8\text{-}\Omega$  speakers each  $1.125\ \text{W}$  for a total of  $4.5\ \text{W}$ . The  $4\text{-}\Omega$  speaker is therefore receiving twice the audio power of the  $8\text{-}\Omega$  speakers, and this difference may cause distortion or imbalance in the listening area.

All speakers have maximum and minimum levels. A  $50\text{-W}$  speaker is rated for a maximum output power of  $50\ \text{W}$  and will provide that level on demand. However, in order to function properly, it will probably need to be operating at least at the  $1\text{-}$  to  $5\text{-W}$  level. A  $100\text{-W}$  speaker typically needs between  $5\ \text{W}$  and  $10\ \text{W}$  of power to operate properly. It is also important to realize that power levels less than the rated value (such as  $40\ \text{W}$  for the  $50\text{-W}$  speaker) will not result in an increase in distortion, but simply in a loss of volume. However, distortion will result if you exceed the rated power level. For example, if we apply  $2.5\ \text{W}$  to a  $2\text{-W}$  speaker, we will definitely have distortion. However, applying  $1.5\ \text{W}$  will simply result in less volume. A rule of thumb regarding audio levels states that the human ear can sense changes in audio level only if you double the applied power [a  $3\text{-dB}$  increase; decibels (dB) will be introduced in Chapter 23]. The doubling effect is always with respect to the initial level. For instance, if the original level were  $2\ \text{W}$ , you would have to go to  $4\ \text{W}$  to notice the change. If starting at  $10\ \text{W}$ , you would have to go to  $20\ \text{W}$  to appreciate the increase in volume. An exception to the above is at very low power levels or very high power levels. For instance, a change from  $1\ \text{W}$  to  $1.5\ \text{W}$  may be discernible, just as a change from  $50\ \text{W}$  to  $80\ \text{W}$  may be noticeable.

## 9.10 COMPUTER ANALYSIS

Once the mechanics of applying a software package or language are understood, the opportunity to be creative and innovative presents itself. Through years of exposure and trial-and-error experiences, professional



programmers develop a catalog of innovative techniques that are not only functional but very interesting and truly artistic in nature. Now that some of the basic operations associated with PSpice have been introduced, a few innovative maneuvers will be made in the examples to follow.

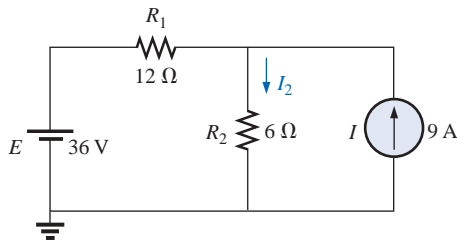


FIG. 9.114

Applying PSpice to determine the current  $I_2$  using superposition.

## PSpice

**Superposition** Let us now apply superposition to the network of Fig 9.114, which appeared earlier as Fig. 9.10 in Example 9.3, to permit a comparison of resulting solutions. The current through  $R_2$  is to be determined. Using methods described in earlier chapters for the application of PSpice, the network of Fig. 9.115 will result to determine the effect of the 36-V voltage source. Note that both **VDC** and **IDC** (flipped vertically) appear in the network. The current source, however, was set to zero simply by selecting the source and changing its value to 0 A in the **Display Properties** dialog box.

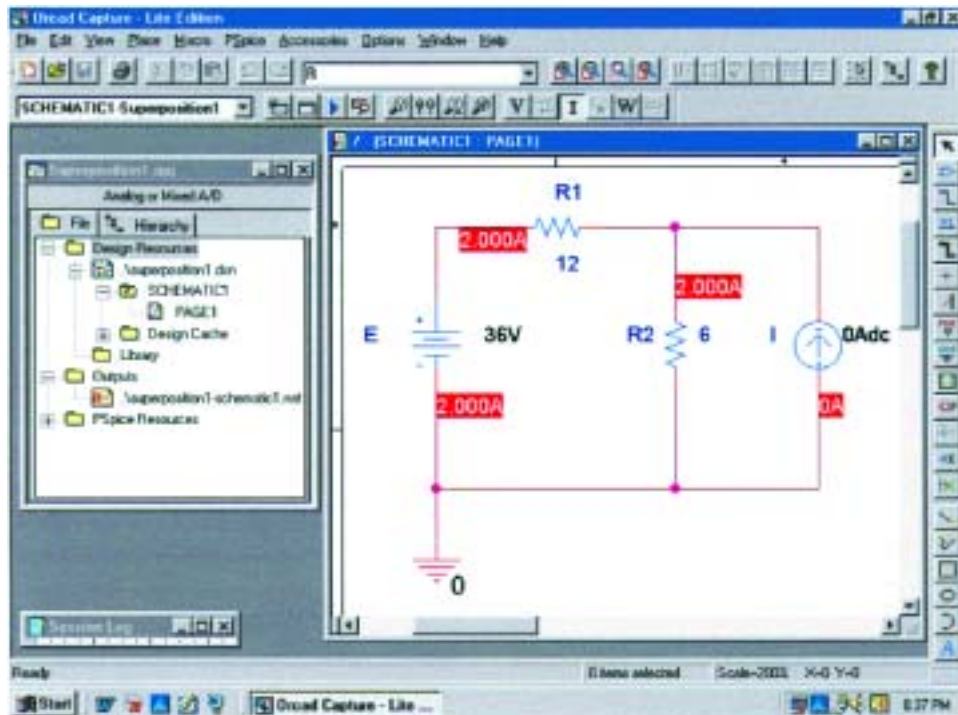


FIG. 9.115

Using PSpice to determine the contribution of the 36-V voltage source to the current through  $R_2$ .

Following simulation, the results appearing in Fig. 9.115 will result. The current through the 6- $\Omega$  resistor is 2 A due solely to the 36-V voltage source. Although direction is not indicated, it is fairly obvious in this case. For those cases where it is not obvious, the voltage levels can be displayed, and the direction would be from the point of high potential to the point of lower potential.

For the effects of the current source, the voltage source is set to 0 V as shown in Fig. 9.116. The resulting current is then 6 A through  $R_2$ , with the same direction as the contribution due to the voltage source.

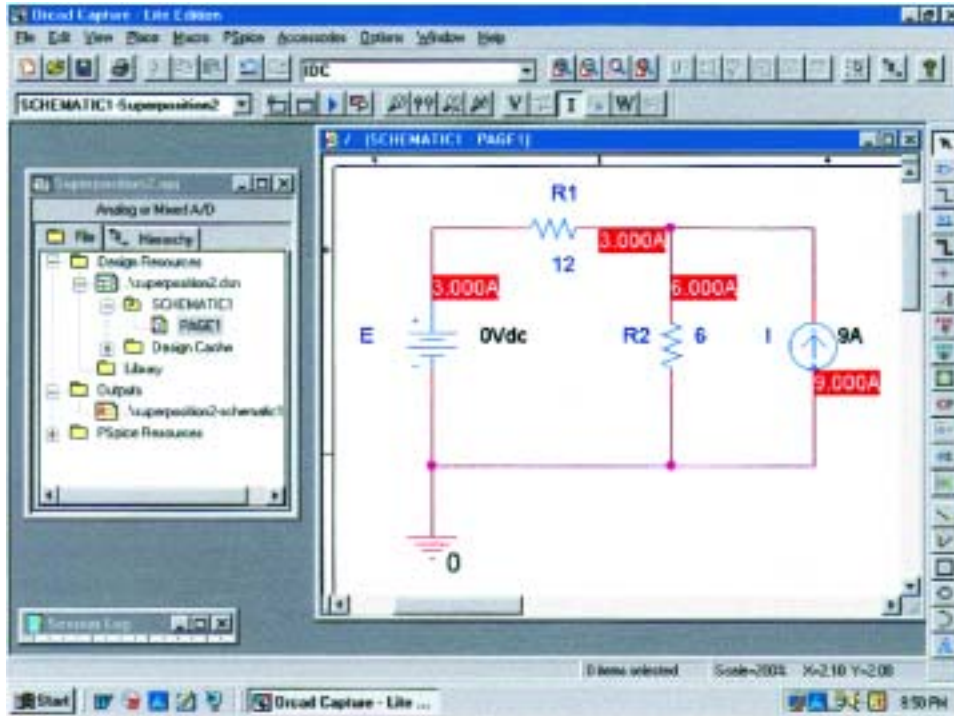


FIG. 9.116

Using PSpice to determine the contribution of the 9-A current source to the current through  $R_2$ .

The resulting current for the resistor  $R_2$  is the sum of the two currents:  $I_T = 2\text{ A} + 6\text{ A} = 8\text{ A}$ , as determined in Example 9.3.

**Thévenin's Theorem** The application of Thévenin's theorem requires an interesting maneuver to determine the Thévenin resistance. It is a maneuver, however, that has application beyond Thévenin's theorem whenever a resistance level is required. The network to be analyzed appears in Fig. 9.117 and is the same one analyzed in Example 9.10 (Fig. 9.49).

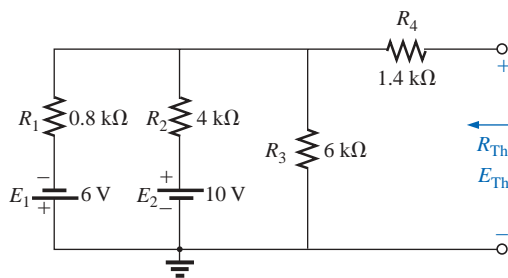


FIG. 9.117

Network to which PSpice is to be applied to determine  $E_{Th}$  and  $R_{Th}$ .

Since PSpice is not set up to measure resistance levels directly, a 1-A current source can be applied as shown in Fig. 9.118, and Ohm's law

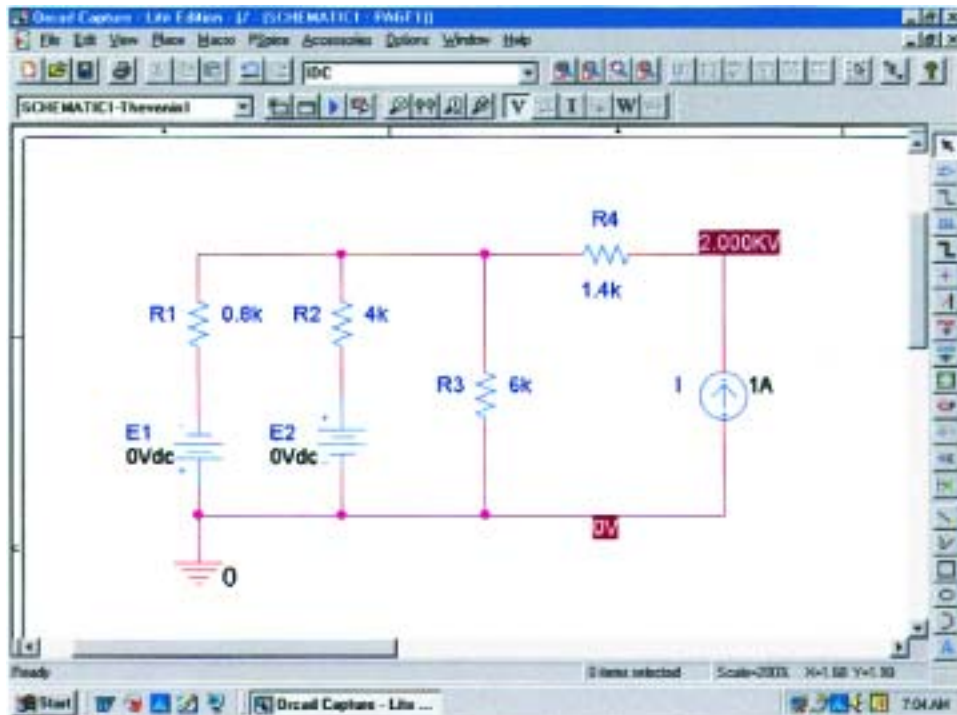


FIG. 9.118

Using PSpice to determine the Thévenin resistance of a network through the application of a 1-A current source.

can be used to determine the magnitude of the Thévenin resistance in the following manner:

$$|R_{Th}| = \left| \frac{V_s}{I_s} \right| = \left| \frac{V_s}{1 \text{ A}} \right| = |V_s|$$

In Eq. (9.16), since  $I_s = 1 \text{ A}$ , the magnitude of  $R_{Th}$  in ohms is the same as the magnitude of the voltage  $V_s$  (in volts) across the current source. The result is that when the voltage across the current source is displayed, it can be read as ohms rather than volts.

When PSpice is applied, the network will appear as shown in Fig. 9.118. The voltage source  $E_1$  and the current source are flipped using a right click on the source and using the **Mirror Vertically** option. Both voltage sources are set to zero through the **Display Properties** dialog box obtained by double-clicking on the source symbol. The result of the **Bias Point** simulation is 2 kV across the current source. The Thévenin resistance is therefore 2 k $\Omega$  between the two terminals of the network to the left of the current source (to match the results of Example 9.10). In total, by setting the voltage sources to 0 V, we have dictated that the voltage is the same at both ends of the voltage source, replicating the effect of a short-circuit connection between the two points.

For the open-circuit Thévenin voltage between the terminals of interest, the network must be constructed as shown in Fig. 9.119. The resistance of 1 T (= 1 million M $\Omega$ ) is considered large enough to represent an open circuit to permit an analysis of the network using PSpice. PSpice does not recognize floating nodes and would generate an error signal if a connection were not made from the top right node to ground. Both voltage sources are now set on their prescribed values, and a simulation will

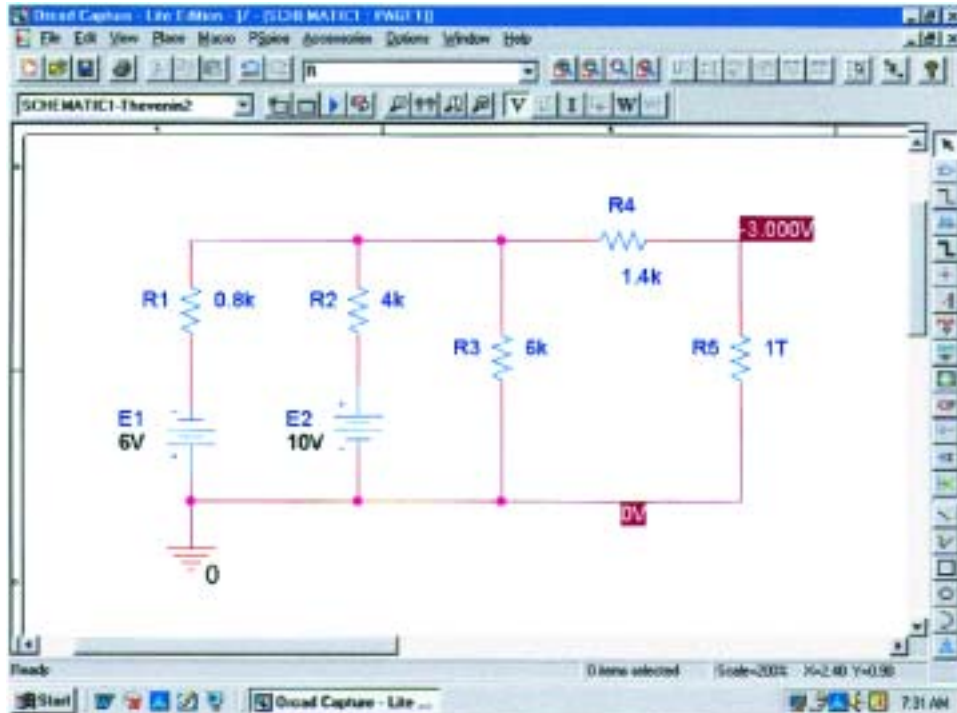


FIG. 9.119

Using PSpice to determine the Thévenin voltage for a network using a very large resistance value to represent the open-circuit condition between the terminals of interest.

result in 3 V across the 1-T resistor. The open-circuit Thévenin voltage is therefore 3 V which agrees with the solution of Example 9.10.

**Maximum Power Transfer** The procedure for plotting a quantity versus a parameter of the network will now be introduced. In this case it will be the output power versus values of load resistance to verify the fact that maximum power will be delivered to the load when its value equals the series Thévenin resistance. A number of new steps will be introduced, but keep in mind that the method has broad application beyond Thévenin's theorem and is therefore well worth the learning process.

The circuit to be analyzed appears in Fig. 9.120. The circuit is constructed in exactly the same manner as described earlier except for the value of the load resistance. Begin the process by starting a **New Project** called **MaxPower**, and build the circuit of Fig. 9.120. For the moment hold off on setting the value of the load resistance.

The first step will be to establish the value of the load resistance as a variable since it will not be assigned a fixed value. Double-click on the value of **RL** to obtain the **Display Properties** dialog box. For **Value**, type in **{Rval}** and click in place. The brackets (**not** parentheses) are required, but the variable does not have to be called **Rval**—it is the choice of the user. Next select the **Place part** key to obtain the **Place Part** dialog box. If you are not already in the **Libraries** list, choose **Add Library** and add **SPECIAL** to the list. Select the **SPECIAL** library and scroll the **Part List** until **PARAM** appears. Select it; then click **OK** to obtain a rectangular box next to the cursor on the

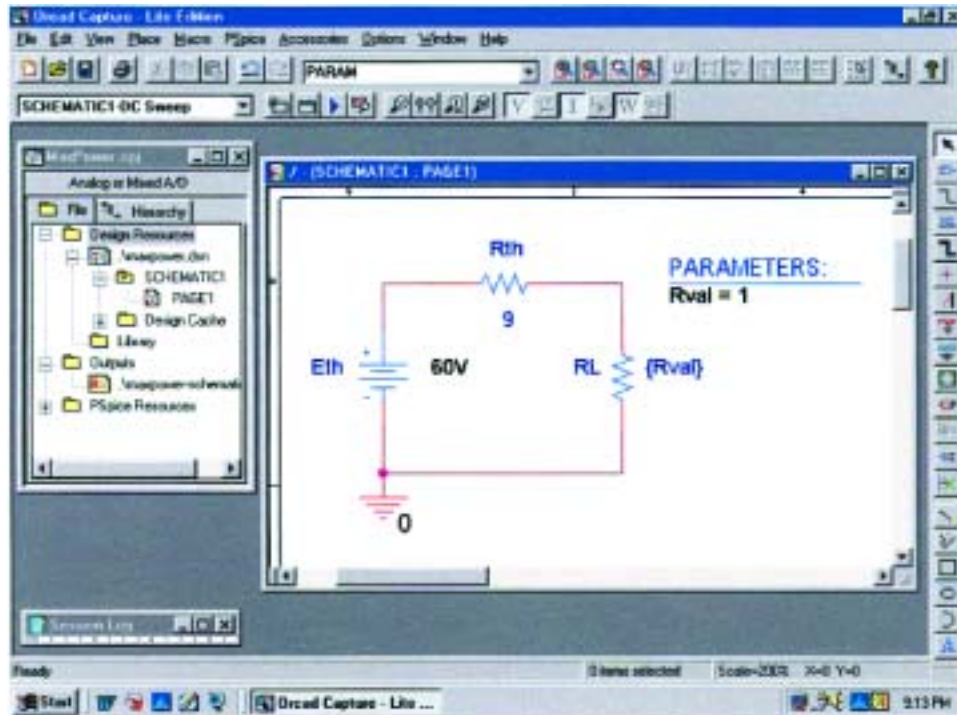



FIG. 9.120

Using PSpice to plot the power to  $R_L$  for a range of values for  $R_L$ .

screen. Select a spot near **Rval**, and deposit the rectangle. The result is **PARAMETERS:** as shown in Fig. 9.120.

Next double-click on **PARAMETERS:** to obtain a **Property Editor** dialog box which should have **SCHEMATIC1:PAGE1** in the second column from the left. Now select the **New Column** option from the top list of choices to obtain the **Add New Column** dialog box. Enter the **Name:Rval** and **Value:1** followed by an **OK** to leave the dialog box. The result is a return to the **Property Editor** dialog box but with **Rval** and its value (below **Rval**) added to the horizontal list. Now select **Rval/1** by clicking on **Rval** to surround **Rval** by a dashed line and add a black background around the **1**. Choose **Display** to produce the **Display Properties** dialog box, and select **Name and Value** followed by **OK**. Then exit the **Property Editor** dialog box (**X**) to obtain the screen of Fig. 9.120. Note that now the first value (1  $\Omega$ ) of **Rval** is displayed.

We are now ready to set up the simulation process. Select the **New Simulation Profile** key to obtain the **New Simulation** dialog box. Enter **DC Sweep** under **Name** followed by **Create**. The **Simulation Settings-DC Sweep** dialog box will appear. After selecting **Analysis**, select **DC Sweep** under the **Analysis type** heading. Then leave the **Primary Sweep** under the **Options** heading, and select **Global parameter** under the **Sweep variable**. The **Parameter name** should then be entered as **Rval**. For the **Sweep type**, the **Start value** should be 1  $\Omega$ ; but if we use 1  $\Omega$ , the curve to be generated will start at 1  $\Omega$ , leaving a blank from 0 to 1  $\Omega$ . The curve will look incomplete. To solve this problem, we will select 0.001  $\Omega$  as the **Start value** (very close to 0  $\Omega$ ) and the **End value** 30.001  $\Omega$  with an **Increment** of 1  $\Omega$ . The values of **RL** will therefore be 0.001  $\Omega$ , 1.001  $\Omega$ , 2.001  $\Omega$ , etc., although the plot

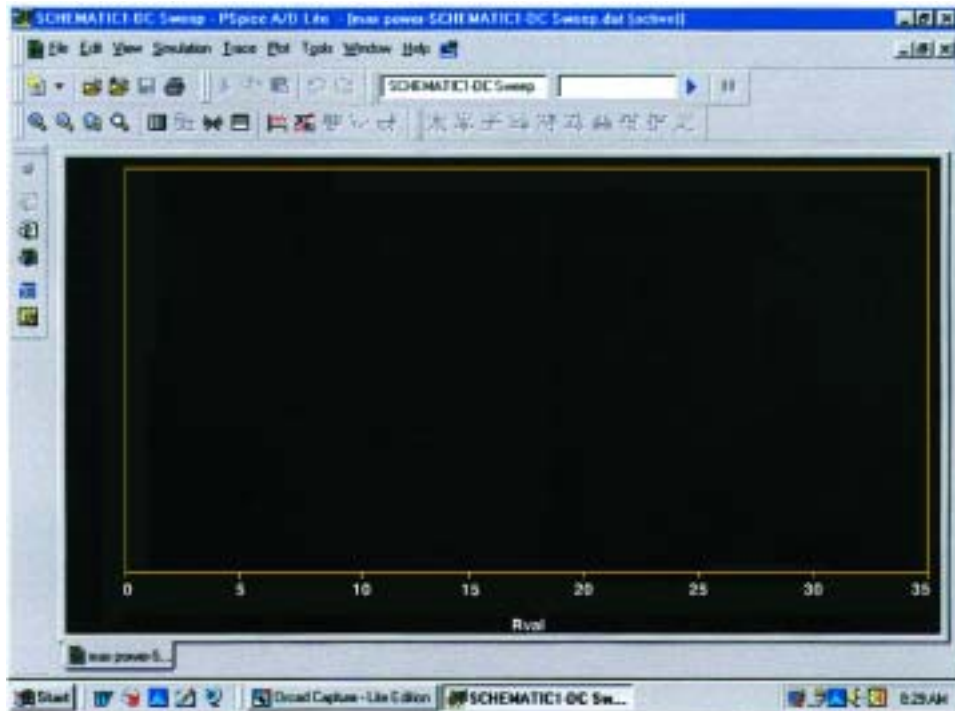
**FIG. 9.121**

*Plot resulting from the dc sweep of  $R_L$  for the network of Fig. 9.120 before defining the parameters to be displayed.*

will look as if the values were  $0\ \Omega$ ,  $1\ \Omega$ ,  $2\ \Omega$ , etc. Click **OK**, and select the **Run PSpice** key to obtain the display of Fig. 9.121.

First note that there are no plots on the graph and that the graph extends to  $35\ \Omega$  rather than  $30\ \Omega$  as desired. It did not respond with a plot of power versus **RL** because we have not defined the plot of interest for the computer. This is done by selecting the **Add Trace** key (the key in the middle of the lower toolbar that looks like a red sawtooth waveform) or **Trace-Add Trace** from the top menu bar. Either choice will result in the **Add Traces** dialog box. The most important region of this dialog box is the **Trace Expression** listing at the bottom. The desired trace can be typed in directly, or the quantities of interest can be chosen from the list of **Simulation Output Variables** and deposited in the **Trace Expression** listing. Since we are interested in the power to **RL** for the chosen range of values for **RL**, **W(RL)** is selected in the listing; it will then appear as the **Trace Expression**. Click **OK**, and the plot of Fig. 9.122 will appear. Originally, the plot extended from  $0\ \Omega$  to  $35\ \Omega$ . We reduced the range to  $0\ \Omega$  to  $30\ \Omega$  by selecting **Plot-Axis Settings-X Axis-User Defined 0 to 30-OK**.

Select the **Toggle cursor** key (which looks like a red curve passing through the origin of a graph), and then left-click the mouse. A vertical line and a horizontal line will appear, with the vertical line controlled by the position of the cursor. Moving the cursor to the peak value will result in **A1** = 9.0010 as the  $x$  value and 100.000 W as the  $y$  value as shown in the **Probe Cursor** box at the right of the screen. A second cursor can be generated by a right click of the mouse, which was set at **RL** =  $30.001\ \Omega$  to result in a power of 71.005 W. Notice also that the

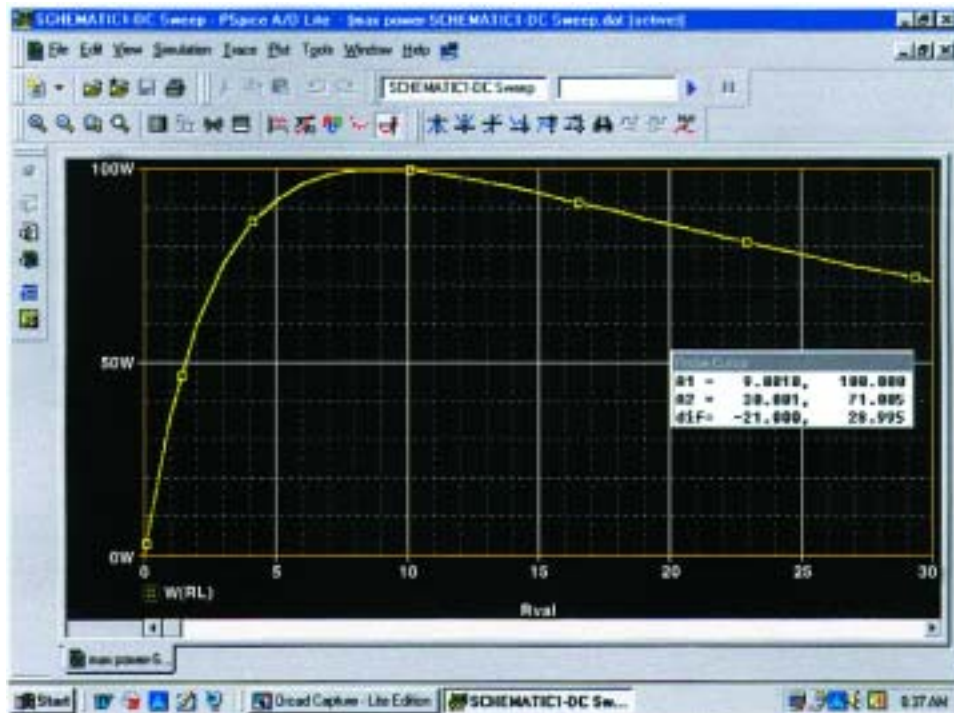


FIG. 9.122

A plot of the power delivered to  $R_L$  in Fig. 9.120 for a range of values for  $R_L$  extending from  $0\ \Omega$  to  $30\ \Omega$ .

plot generated appears as a listing at the bottom left of the screen as **W(RL)**.

Before leaving the subject, we should mention that the power to **RL** can be determined in more ways than one from the **Add Traces** dialog box. For example, first enter a minus sign because of the resulting current direction through the resistor, and then select **V2(RL)** followed by the multiplication of **I(RL)**. The following expression will appear in the **Trace Expression** box: **V2(RL)\*I(RL)**, which is an expression having the basic power format of  $P = V * I$ . Click **OK**, and the same power curve of Fig. 9.122 will appear. Other quantities, such as the voltage across the load and the current through the load, can be plotted against **RL** by simply following the sequence **Trace-Delete All Traces-Trace-Add Trace-V1(RL)** or **I(RL)**.

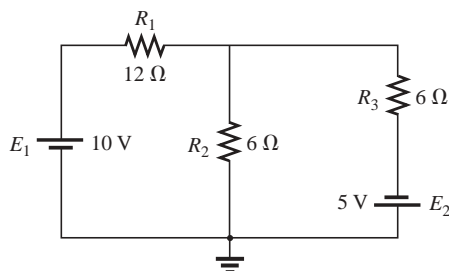


FIG. 9.123  
Problem 1.


## PROBLEMS

### SECTION 9.2 Superposition Theorem

1. a. Using superposition, find the current through each resistor of the network of Fig. 9.123.
- b. Find the power delivered to  $R_1$  for each source.
- c. Find the power delivered to  $R_1$  using the total current through  $R_1$ .
- d. Does superposition apply to power effects? Explain.




2. Using superposition, find the current  $I$  through the  $10\text{-}\Omega$  resistor for each of the networks of Fig. 9.124.

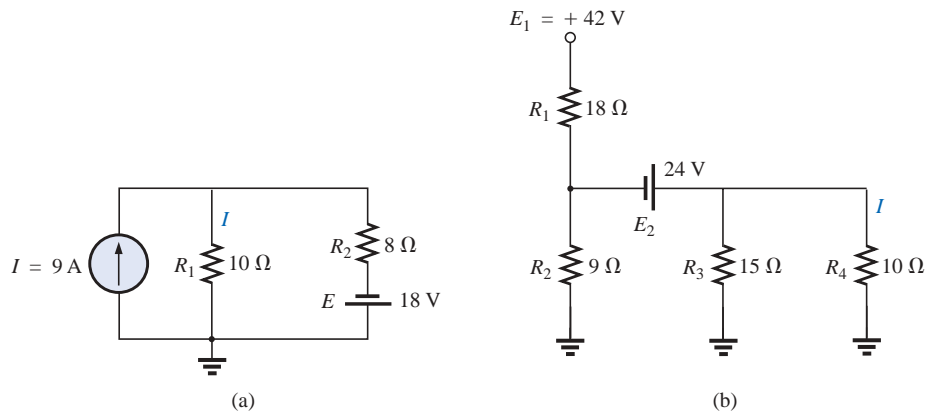


**FIG. 9.124**  
Problems 2 and 41.

- \* 3. Using superposition, find the current through  $R_1$  for each network of Fig. 9.125.

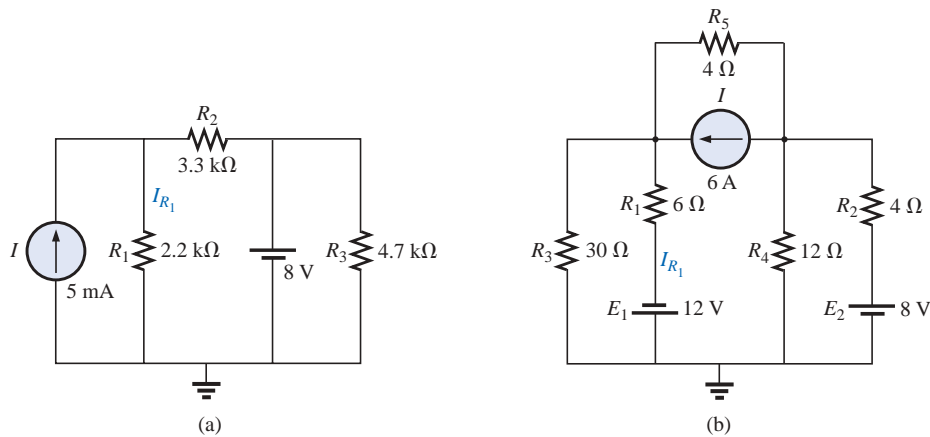

**FIG. 9.125**  
Problem 3.

4. Using superposition, find the voltage  $V_2$  for the network of Fig. 9.126.

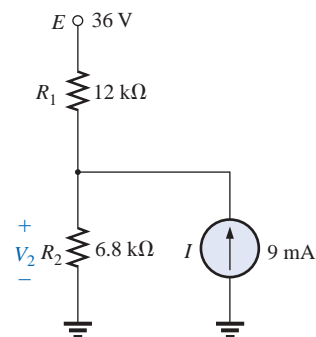


**FIG. 9.126**  
Problems 4 and 37.




**SECTION 9.3 Thévenin's Theorem**

5. a. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  of Fig. 9.127.
- b. Find the current through  $R$  when  $R$  is  $2\ \Omega$ ,  $30\ \Omega$ , and  $100\ \Omega$ .

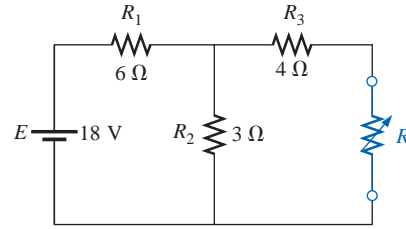


**FIG. 9.127**  
Problem 5.

6. a. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  in each of the networks of Fig. 9.128.
- b. Find the power delivered to  $R$  when  $R$  is  $2\ \Omega$  and  $100\ \Omega$ .

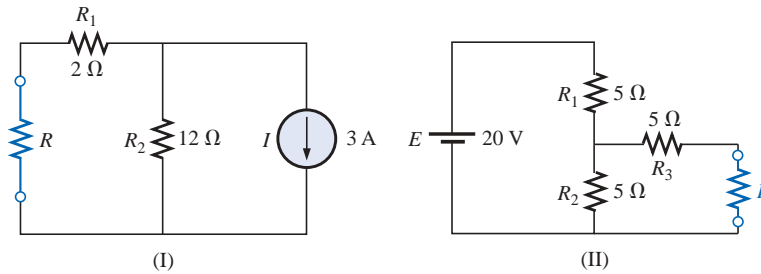

**FIG. 9.128**  
Problems 6, 13, and 19.

7. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  in each of the networks of Fig. 9.129.

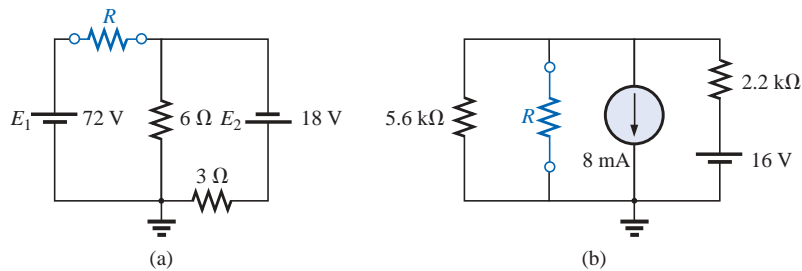

**FIG. 9.129**  
Problems 7, 14, and 20.



\* 8. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  in each of the networks of Fig. 9.130.

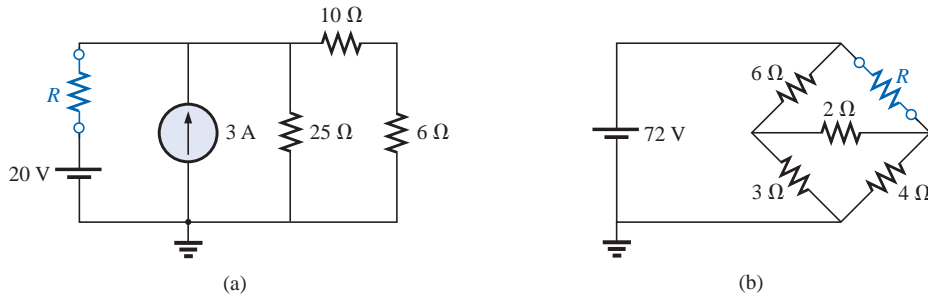


FIG. 9.130

Problems 8, 15, 21, 38, 39, and 42.

\* 9. Find the Thévenin equivalent circuit for the portions of the networks of Fig. 9.131 external to points  $a$  and  $b$ .

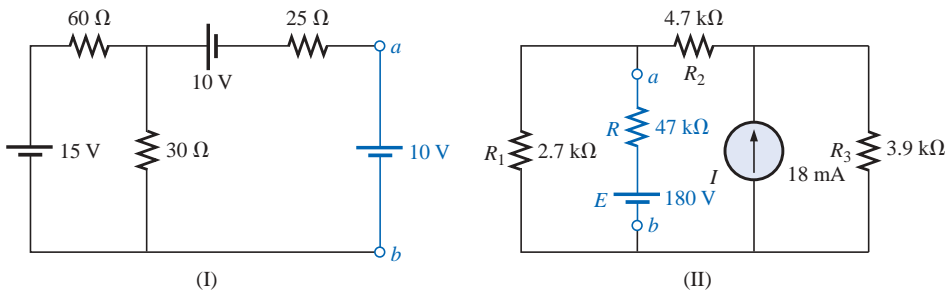


FIG. 9.131

Problems 9 and 16.

\*10. Determine the Thévenin equivalent circuit for the network external to the resistor  $R$  in both networks of Fig. 9.132.



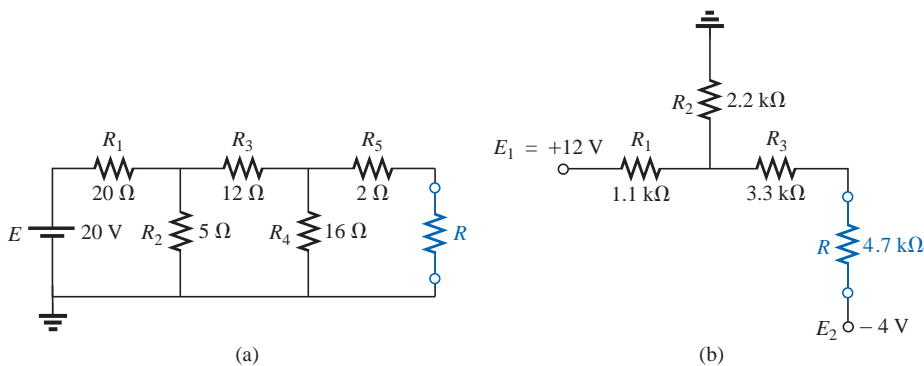


FIG. 9.132

Problems 10 and 17.

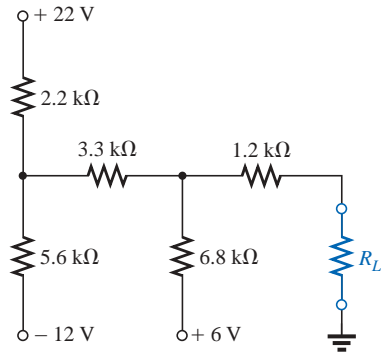

**FIG. 9.133**  
Problem 11.

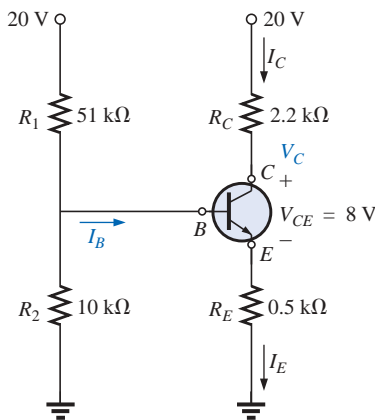

**FIG. 9.134**  
Problem 12.



- \*11. For the network of Fig. 9.133, find the Thévenin equivalent circuit for the network external to the load resistor  $R_L$ .
- \*12. For the transistor network of Fig. 9.134:
  - a. Find the Thévenin equivalent circuit for that portion of the network to the left of the base ( $B$ ) terminal.
  - b. Using the fact that  $I_C = I_E$  and  $V_{CE} = 8\text{ V}$ , determine the magnitude of  $I_E$ .
  - c. Using the results of parts (a) and (b), calculate the base current  $I_B$  if  $V_{BE} = 0.7\text{ V}$ .
  - d. What is the voltage  $V_C$ ?

**SECTION 9.4 Norton's Theorem**

- 13. Find the Norton equivalent circuit for the network external to the resistor  $R$  in each network of Fig. 9.128.
- 14. a. Find the Norton equivalent circuit for the network external to the resistor  $R$  for each network of Fig. 9.129.
- b. Convert to the Thévenin equivalent circuit, and compare your solution for  $E_{Th}$  and  $R_{Th}$  to that appearing in the solutions for Problem 7.
- 15. Find the Norton equivalent circuit for the network external to the resistor  $R$  for each network of Fig. 9.130.
- 16. a. Find the Norton equivalent circuit for the network external to the resistor  $R$  for each network of Fig. 9.131.
- b. Convert to the Thévenin equivalent circuit, and compare your solution for  $E_{Th}$  and  $R_{Th}$  to that appearing in the solutions for Problem 9.
- 17. Find the Norton equivalent circuit for the network external to the resistor  $R$  for each network of Fig. 9.132.
- 18. Find the Norton equivalent circuit for the portions of the networks of Fig. 9.135 external to branch  $a$ - $b$ .

**SECTION 9.5 Maximum Power Transfer Theorem**


- 19. a. For each network of Fig. 9.128, find the value of  $R$  for maximum power to  $R$ .
- b. Determine the maximum power to  $R$  for each network.
- 20. a. For each network of Fig. 9.129, find the value of  $R$  for maximum power to  $R$ .
- b. Determine the maximum power to  $R$  for each network.

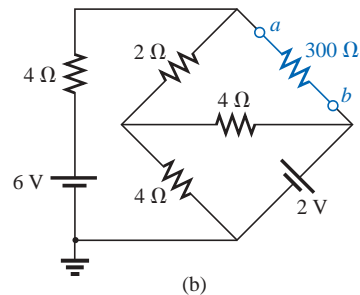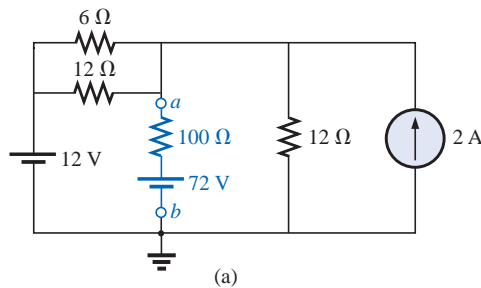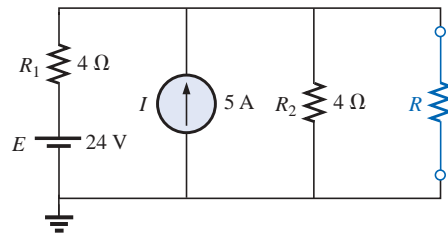

**FIG. 9.135**  
Problems 18 and 40.




21. For each network of Fig. 9.130, find the value of  $R$  for maximum power to  $R$ , and determine the maximum power to  $R$  for each network.
22. a. For the network of Fig. 9.136, determine the value of  $R$  for maximum power to  $R$ .  
 b. Determine the maximum power to  $R$ .  
 c. Plot a curve of power to  $R$  versus  $R$  for  $R$  equal to  $\frac{1}{4}$ ,  $\frac{1}{2}$ ,  $\frac{3}{4}$ , 1,  $1\frac{1}{4}$ ,  $1\frac{1}{2}$ ,  $1\frac{3}{4}$ , and 2 times the value obtained in part (a).



**FIG. 9.136**

Problems 22 and 43.


- \*23. Find the resistance  $R_1$  of Fig. 9.137 such that the resistor  $R_4$  will receive maximum power. Think!
- \*24. a. For the network of Fig. 9.138, determine the value of  $R_2$  for maximum power to  $R_4$ .  
 b. Is there a general statement that can be made about situations such as those presented here and in Problem 23?
- \*25. For the network of Fig. 9.139, determine the level of  $R$  that will ensure maximum power to the 100-Ω resistor.

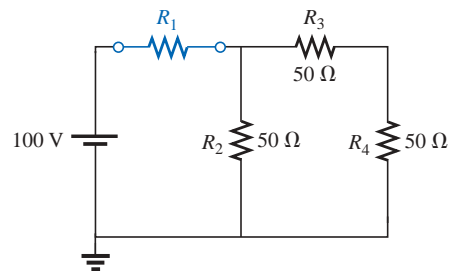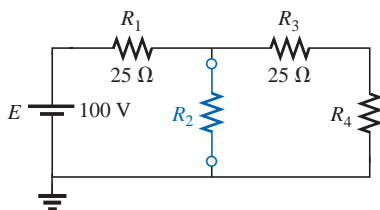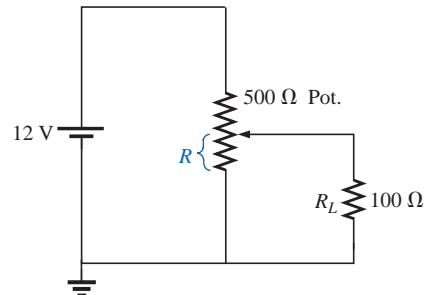
**FIG. 9.137**

Problem 23.


**FIG. 9.138**

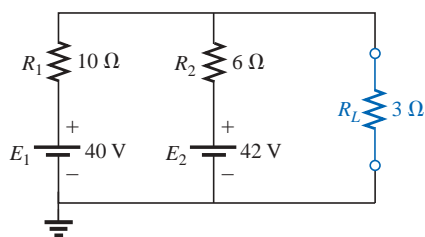
Problem 24.


**FIG. 9.139**


Problem 25.

### SECTION 9.6 Millman's Theorem


26. Using Millman's theorem, find the current through and voltage across the resistor  $R_L$  of Fig. 9.140.
27. Repeat Problem 26 for the network of Fig. 9.141.


**FIG. 9.140**

Problem 26.

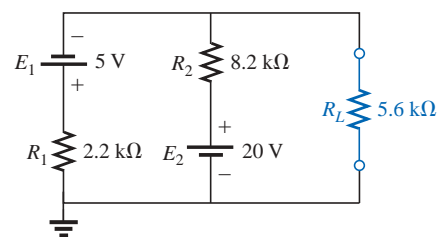

**FIG. 9.141**

Problem 27.

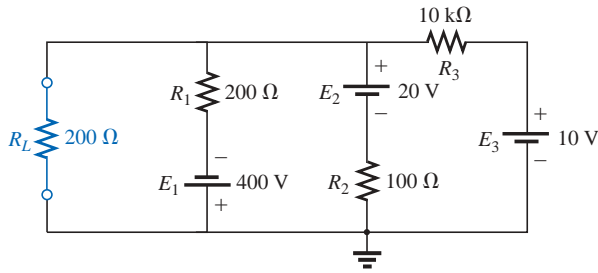


**FIG. 9.142**  
Problem 28.

28. Repeat Problem 26 for the network of Fig. 9.142.  
 29. Using the dual of Millman's theorem, find the current through and voltage across the resistor  $R_L$  of Fig. 9.143.

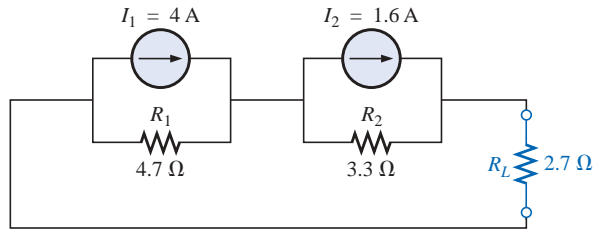


**FIG. 9.143**  
Problem 29.

- \*30. Repeat Problem 29 for the network of Fig. 9.144.

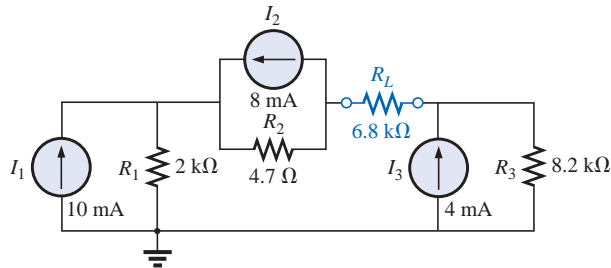


**FIG. 9.144**  
Problem 30.

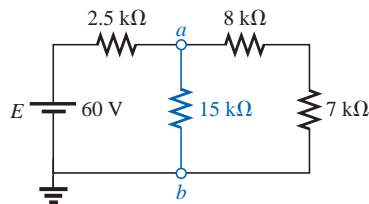


**FIG. 9.145**  
Problem 31.

**SECTION 9.7 Substitution Theorem**

31. Using the substitution theorem, draw three equivalent branches for the branch  $a-b$  of the network of Fig. 9.145.  
 32. Repeat Problem 31 for the network of Fig. 9.146.

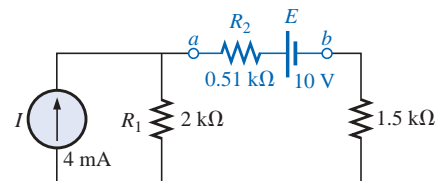

**FIG. 9.146**  
Problem 32.

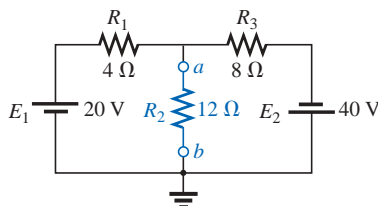


**FIG. 9.147**  
Problem 33.

- \*33. Repeat Problem 31 for the network of Fig. 9.147. Be careful!




**SECTION 9.8 Reciprocity Theorem**

34. a. For the network of Fig. 9.148(a), determine the current  $I$ .  
 b. Repeat part (a) for the network of Fig. 9.148(b).  
 c. Is the reciprocity theorem satisfied?

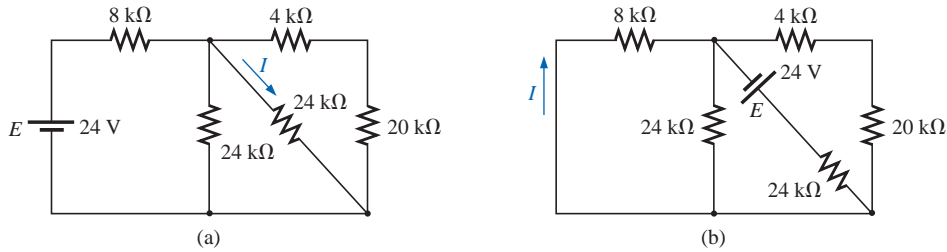


**FIG. 9.148**  
 Problem 34.

35. Repeat Problem 34 for the networks of Fig. 9.149.

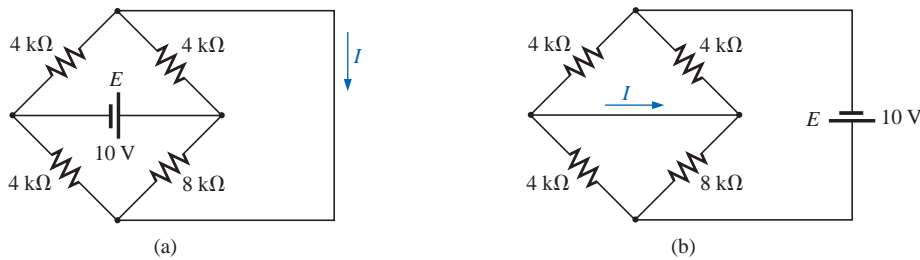

**FIG. 9.149**  
 Problem 35.

36. a. Determine the voltage  $V$  for the network of Fig. 9.150(a).  
 b. Repeat part (a) for the network of Fig. 9.150(b).  
 c. Is the dual of the reciprocity theorem satisfied?

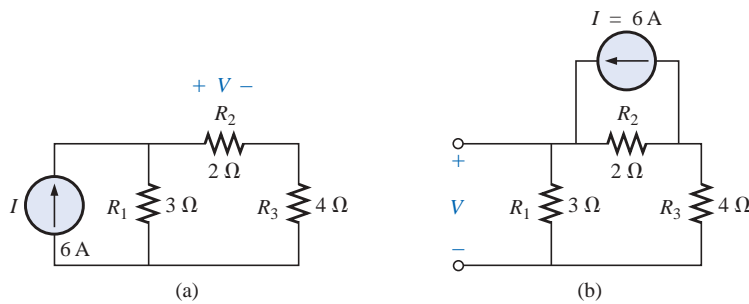

**FIG. 9.150**  
 Problem 36.

**SECTION 9.10 Computer Analysis**

**PSpice or Electronics Workbench**

37. Using schematics, determine the voltage  $V_2$  and its components for the network of Fig. 9.126.



38. Using schematics, determine the Thévenin equivalent circuit for the network of Fig. 9.130(b).
- \*39. a. Using schematics, plot the power delivered to the resistor  $R$  of Fig. 9.130(a) for  $R$  having values from  $1\ \Omega$  to  $50\ \Omega$ .
- b. From the plot, determine the value of  $R$  resulting in maximum power to  $R$  and the maximum power to  $R$ .
- c. Compare the results of part (a) to the numerical solution.
- d. Plot  $V_R$  and  $I_R$  versus  $R$ , and find the value of each under maximum power conditions.
- \*40. Change the  $300\text{-}\Omega$  resistor of Fig. 9.135(b) to a variable resistor, and plot the power delivered to the resistor versus values of the resistor. Determine the range of resis-

tance by trial and error rather than first performing a longhand calculation. Determine the Norton equivalent circuit from the results. The Norton current can be determined from the maximum power level.

#### Programming Language (C++, QBASIC, Pascal, etc.)

41. Write a program to determine the current through the  $10\text{-}\Omega$  resistor of Fig. 9.124(a) (for any component values) using superposition.
42. Write a program to perform the analysis required for Problem 8, Fig. 9.130(b), for any component values.
- \*43. Write a program to perform the analysis of Problem 22, and tabulate the power to  $R$  for the values listed in part (c).

## GLOSSARY

**Maximum power transfer theorem** A theorem used to determine the load resistance necessary to ensure maximum power transfer to the load.

**Millman's theorem** A method employing source conversions that will permit the determination of unknown variables in a multiloop network.

**Norton's theorem** A theorem that permits the reduction of any two-terminal linear dc network to one having a single current source and parallel resistor.

**Reciprocity theorem** A theorem that states that for single-source networks, the current in any branch of a network, due to a single voltage source in the network, will equal the current through the branch in which the source was originally located if the source is placed in the branch in which the current was originally measured.

**Substitution theorem** A theorem that states that if the voltage across and current through any branch of a dc bilateral network are known, the branch can be replaced by any combination of elements that will maintain the same voltage across and current through the chosen branch.

**Superposition theorem** A network theorem that permits considering the effects of each source independently. The resulting current and/or voltage is the algebraic sum of the currents and/or voltages developed by each source independently.

**Thévenin's theorem** A theorem that permits the reduction of any two-terminal, linear dc network to one having a single voltage source and series resistor.