

Appendix H



ANSWERS TO SELECTED ODD-NUMBERED PROBLEMS

Chapter 1

5. 3 h
7. CGS
9. MKS = CGS = 20°C
K = SI = 293.15
11. 45.72 cm
13. (a) 15×10^3 (b) 30×10^{-3}
(c) 7.4×10^6 (d) 6.8×10^{-6}
(e) 402×10^{-6} (f) 200×10^{-12}
15. (a) 10^4 (b) 10
(c) 10^9 (d) 10^{-2}
(e) 10 (f) 10^{31}
17. (a) 10^{-1} (b) 10^{-4}
(c) 10^9 (d) 10^{-9}
(e) 10^{42} (f) 10^3
19. (a) 10^6 (b) 10^{-2}
(c) 10^{32} (d) 10^{-63}
21. (a) 10^{-6} (b) 10^{-3}
(c) 10^{-8} (d) 10^9
(e) 10^{-16} (f) 10^{-1}
23. (a) 0.006 (b) 400
(c) 5000, 5, 0.005
(d) 0.0003, 0.3, 300
25. (a) 90 s (b) 144 s
(c) $50 \times 10^3 \mu\text{s}$
(d) 160 mm (e) 120 ns
(f) 41.898 days (g) 1.02 m
27. (a) 2.54 m (b) 1.219 m
(c) 26.7 N (d) 0.1348 lb
(e) 4921.26 ft
(f) 3.2187 m (g) 8530.17 yd
29. 670.62×10^6 mph
31. 2.045 s
33. 67.06 days
35. \$900
37. 345.6 m
39. 47.29 min/mile
41. (a) 4.74×10^{-3} Btu
(b) 7.098×10^{-4} m³
(c) 1.2096×10^5 s
(d) 2113.38 pints
43. 5.000
45. 2.949

Chapter 2

3. (a) 18 mN (b) 2 mN
(c) 180 μN
7. (a) 72 mN
(b) $Q_1 = 20 \mu\text{C}$, $Q_2 = 40 \mu\text{C}$
9. 3.1 A
11. 90 C

13. 0.5 A
15. 1.194 A > 1 A (yes)
17. (a) 1.248 million
(b) 0.936 million, sol. = (a)
19. 252 J
21. 4 C
23. 3.533 V
25. 5 A
27. 25 h
29. 0.773 h
31. 60 Ah:40 Ah = 1.5:1, 50% more
with 60 Ah
33. 545.45 mA, 129.6 kJ
43. 600 C

Chapter 3

1. (a) 500 mils (b) 10 mils
(c) 4 mils (d) 1000 mils
(e) 240 mils (f) 3.937 mils
3. (a) 0.04 in. (b) 0.03 in.
(c) 0.2 in. (d) 0.025 in.
(e) 0.00278 in. (f) 0.009 in.
5. 73.33 Ω
7. 3.581 ft
9. (a) $R_{\text{silver}} > R_{\text{copper}} > R_{\text{aluminum}}$
(b) silver 9.9 Ω ,
copper 1.037 Ω ,
aluminum 0.34 Ω
11. (a) 21.71 $\mu\Omega$ (b) 35.59 $\mu\Omega$
(c) increases (d) decreases
13. 942.28 m Ω
15. (a) #8: 1.1308 Ω . #18: 11.493 Ω
(b) #18: #8 = 10.164 1:1 \cong 10:1.
#18: #8 = 1:10.164 \cong 1:10
17. (a) 1.087 mA/CM
(b) 1.384 kA/in.²
(c) 3.6127 in.²
19. (a) 21.71 $\mu\Omega$ (b) 35.59 $\mu\Omega$
21. 0.15 in.
23. 2.409 Ω
25. 3.67 Ω
27. 0.046 Ω
29. (a) 40.29°C (b) -195.61°C
31. (a) $\alpha_{20} \cong 0.00393$
(b) 83.61°C
33. 1.751 Ω
35. 142.86
41. -30°C: 10.2 k Ω .
100°C: 10.15 k Ω
43. 6.5 k Ω
47. (a) Red Red Brown Silver
(b) Yellow Violet Red Silver

- (c) Blue Gray Orange Silver
(d) White Brown Green Silver
49. yes
51. (a) 0.1566 S (b) 0.0955 S
(c) 0.0219 S
57. (a) 10 fc: 3 k Ω . 100 fc: 0.4 k Ω
(b) neg. (c) no—log scales
(d) -321.43 Ω/fc

Chapter 4

1. 15 V
3. 4 k Ω
5. 72 mV
7. 54.55 Ω
9. 28.571 Ω
11. 1.2 k Ω
13. (a) 12.632 Ω (b) 4.1 MJ
17. 800 V
19. 1 W
21. (a) 57,600 J
(b) 16×10^{-3} kWh
23. 2 s
25. 196 μW
27. 4 A
29. 9.61 V
31. 0.833 A, 144.06 Ω
33. (a) 0.133 mA (b) 66.5 mAh
35. (c) \cong 70.7 mA
37. (a) 12 kW
(b) 10,130 W < 12,000 W (yes)
39. 16.34 A
41. (a) 238 W (b) 17.36%
43. (a) 1657.78 W
(b) 15.07 A
(c) 19.38 A
45. 65.25%
47. 80%
49. (a) 17.9%
(b) 76.73%, 328.66% increase
51. (a) 1350 J
(b) W doubles, P the same
53. 6.67 h
55. (a) 50 kW (b) 240.38 A
(c) 90 kWh
57. \$2.19

Chapter 5

1. (a) 20 Ω , 3 A
(b) 1.63 M Ω , 6.135 μA
(c) 110 Ω , 318.2 mA
(d) 10 k Ω , 12 mA

3. (a) 16 V (b) 4.2 V
 5. (a) 0.388 A (CW)
 (b) 2.087 A (CCW)
 7. (a) 5 V (b) 70 V
 9. 3.28 mA, 7.22 V
 11. (a) 70.6 Ω , 85 mA (CCW),
 $V_1 = 2.8045$ V,
 $V_2 = 0.4760$ V,
 $V_3 = 0.850$ V,
 $V_4 = 1.870$ V
 (b)–(c) $P_1 = 0.2384$ W,
 $P_2 = 0.0405$ W,
 $P_3 = 0.0723$ W,
 $P_4 = 0.1590$ W
 (d) all $\frac{1}{2}$ W
 13. (a) 225 Ω , 0.533 A
 (b) 8 W
 (c) 15 V
 15. All V_{ab}
 $+$ –
 (a) 66.67 V (b) -8 V
 (c) 20 V (d) 0.18 V
 17. (a) 12 V (b) 24 V
 (c) 60 Ω (d) 0.4 A
 (e) 60 Ω
 19. (a) $R_s = 80$ Ω
 (b) 0.2 W $< \frac{1}{4}$ W
 21. $R_1 = 3$ k Ω , $R_2 = 15$ k Ω
 23. (a) $R_1 = 0.4$ k Ω , $R_2 = 1.2$ k Ω ,
 $R_3 = 4.8$ k Ω
 (b) $R_1 = 0.4$ M Ω ,
 $R_2 = 1.2$ M Ω ,
 $R_3 = 4.8$ M Ω
 25. (a) I (CW) = 6.667 A,
 $V = 20$ V
 (b) I (CW) = 1 A,
 $V = 10$ V
 27. (a) 20 V, 26 V, 35 V,
 -12 V, 0 V
 (b) -6 V, -47 V, 9 V
 (c) -15 V, -38 V
 29. $V_0 = 0$ V, $V_4 = 10$ V,
 $V_7 = 4$ V, $V_{10} = 20$ V,
 $V_{23} = 6$ V, $V_{30} = -8$ V,
 $V_{67} = 0$ V, $V_{56} = -6$ V,
 $I(\text{up}) = 1.5$ A
 31. 2 Ω
 33. 100 Ω
 35. 1.52%

Chapter 6

1. (a) 2, 3, 4 (b) 2, 3 (c) 1, 4
 3. (a) 6 Ω , 0.1667 S
 (b) 1 k Ω , 1 mS
 (c) 2.076 k Ω , 0.4817 mS
 (d) 1.333 Ω , 0.75 S
 (e) 9.948 Ω , 100.525 mS
 (f) 0.6889 Ω , 1.4516 S

5. (a) 18 Ω (b) $R_1 = R_2 = 24$ Ω
 7. 120 Ω
 9. (a) 0.8571 Ω , 1.1667 S
 (b) $I_s = 1.05$ A, $I_1 = 0.3$ A,
 $I_2 = 0.15$ A, $I_3 = 0.6$ A
 (d) $P_1 = 0.27$ W,
 $P_2 = 0.135$ W,
 $P_3 = 0.54$ W,
 $P_{\text{del}} = 0.945$ W
 (e) $R_1, R_2 = \frac{1}{2}$ W, $R_3 = 1$ W
 11. (a) 66.67 mA (b) 225 Ω
 (c) 8 W
 13. (a) $I_s = 7.5$ A, $I_1 = 1.5$ A
 (b) $I_s = 9.6$ mA, $I_1 = 0.8$ mA
 15. 1260 W
 17. (a) 4 mA (b) 24 V
 (c) 18.4 mA
 19. (a) $I_1 = 3$ mA, $I_2 = 1$ mA,
 $I_3 = 1.5$ mA
 (b) $I_2 = 4$ μ A, $I_3 = 1.5$ μ A,
 $I_4 = 5.5$ μ A, $I_1 = 6$ μ A
 21. (a) $R_1 = 5$ Ω , $R_2 = 10$ Ω
 (b) $E = 12$ V, $I_2 = 1.333$ A,
 $I_3 = 1$ A, $R_3 = 12$ Ω ,
 $I = 4.333$ A
 (c) $I_1 = 64$ mA, $I_3 = 16$ mA,
 $I_2 = 20$ mA, $R = 3.2$ k Ω ,
 $I = 36$ mA
 (d) $E = 30$ V, $I_1 = 1$ A,
 $I_2 = I_3 = 0.5$ A,
 $R_2 = R_3 = 60$ Ω ,
 $P_{R_2} = 15$ W
 23. (a) $I_1 = 4$ A, $I_2 = 8$ A
 (b) $I_1 = 2$ A, $I_2 = 4$ A,
 $I_3 = 1$ A, $I_4 = 1.333$ A
 (c) $I_1 = 272.73$ mA,
 $I_2 = 227.27$ mA,
 $I_3 = 90.91$ mA,
 $I_4 = 500$ mA
 (d) $I_2 = 4.5$ A, $I_3 = 8.5$ A,
 $I_4 = 8.5$ A
 25. (a) $I = 4$ A, $I_2 = 4$ A,
 $I_1 = 3$ A
 27. $R_1 = 6$ k Ω , $R_2 = 1.5$ k Ω ,
 $R_3 = 0.5$ k Ω
 29. $I = 3$ A, $R = 2$ Ω
 31. (a) 6.13 V
 (b) 9 V
 (c) 9 V
 33. (a) 4 V (b) 3.997 V
 (c) 3.871 V (d) 3 V
 (e) R_m large as possible
 35. No! 4-V supply reversed

Chapter 7

1. (a) series: E , R_1 , and R_4 ,
 parallel: R_2 and R_3

- (b) series: E and R_1 ,
 parallel: R_2 and R_3
 (c) series: E , R_1 , and R_5 ;
 R_3 and R_4
 parallel: none
 (d) series: R_6 and R_7 ,
 parallel: E , R_1 , and R_4 ;
 R_2 and R_5
 3. (a) yes (KCL) (b) 3 A
 (c) yes (KCL) (d) 4 V
 (e) 2 Ω (f) 5 A
 (g) $P_1 = 12$ W, $P_2 = 18$ W,
 $P_{\text{del}} = 50$ W
 5. (a) 4 Ω
 (b) $I_s = 9$ A, $I_1 = 6$ A, $I_2 = 3$ A
 (c) 6 V
 7. $I_1 = 6$ A, $I_2 = 16$ A, $I_3 = 0.8$ A,
 $I = 22$ A
 9. (a) 4 A
 (b) $I_2 = 1.333$ A, $I_3 = 0.6665$ A
 (c) $V_a = 8$ V, $V_b = 4$ V
 11. (a) 5 Ω , 16 A
 (b) $I_{R_2} = 8$ A, $I_3 = I_9 = 4$ A
 (c) $I_8 = 1$ A (d) 14 V
 13. (a) $V_G = 1.9$ V, $V_s = 3.65$ V
 (b) $I_1 = I_2 = 7.05$ μ A,
 $I_D = 2.433$ mA
 (c) 6.268 V
 (d) 8.02 V
 15. (a) 0.6 A
 (b) 28 V
 17. (a) $I_2 = 1.667$ A, $I_6 = 1.111$ A,
 $I_8 = 0$ A
 19. (a) 1.882 Ω
 (b) $V_1 = V_4 = 32$ V
 (c) 8 A \leftarrow
 (d) 1.882 Ω
 21. (a) 6.75 A
 (b) 32 V
 23. 8.333 Ω
 25. (a) 24 A
 (b) 8 A
 (c) $V_3 = 48$ V, $V_5 = 24$ V,
 $V_7 = 16$ V
 (d) $P(R_7) = 128$ W,
 $P(E) = 5760$ W
 27. 4.44 W
 29. (a) 64 V
 (b) $R_{L_2} = 4$ k Ω ,
 $R_{L_3} = 3$ k Ω
 (c) $R_1 = 0.5$ k Ω ,
 $R_2 = 1.2$ k Ω ,
 $R_3 = 2$ k Ω
 31. (a) yes (b) $R_1 = 750$ Ω ,
 $R_2 = 250$ Ω
 (c) $R_1 = 745$ Ω , $R_2 = 255$ Ω
 33. (a) 1 mA (b) $R_{\text{shunt}} = 5$ m Ω
 35. (a) $R_s = 300$ k Ω
 (b) 20,000
 37. 0.05 μ A

Chapter 8

1. 28 V
3. (a) $I_1 = 12 \text{ A}$, $I_s = 11 \text{ A}$
(b) $V_s = 24 \text{ V}$, $V_3 = 6 \text{ V}$
5. (a) 3 A, 6 Ω (b) 4.091 mA, 2.2 k Ω
7. (a) 8 A (b) 8 A
9. 9.6 V, 2.4 A
11. (a) 5.4545 mA, 2.2 k Ω
(b) 17.375 V (c) 5.375 V
(d) 2.443 mA
13. (I) CW: $I_{R_1} = 1.445 \text{ mA}$;
down: $I_{R_3} = 9.958 \text{ mA}$;
CCW: $I_{R_2} = 8.513 \text{ mA}$
(II) CW: $I_{R_1} = 2.0316 \text{ mA}$;
left: $I_{R_2} = 0.8 \text{ mA}$;
CW: $I_{R_3} = I_{R_4} = 1.2316 \text{ mA}$
15. (d) left: 63.694 mA
17. (a) CW: $I_{R_1} = -\frac{1}{7} \text{ A}$;
CW: $I_{R_2} = -\frac{5}{7} \text{ A}$
 $I_{R_3} = \frac{4}{7} \text{ A}$ (down)
(b) CW: $I_{R_1} = -3.0625 \text{ A}$;
CW: $I_{R_3} = 0.1875 \text{ A}$
 $I_{R_2} = 3.25 \text{ A}$ (up)
19. (I) CW: $I_1 = 1.8701 \text{ A}$;
CW: $I_2 = -8.5484 \text{ A}$;
 $V_{ab} = -22.74 \text{ V}$
(II) CW: $I_2 = 1.274 \text{ A}$;
CW: $I_3 = 0.26 \text{ A}$;
 $V_{ab} = -0.904 \text{ V}$
21. (a) 72.16 mA, -4.433 V
(b) 1.953 A, -7.257 V
23. (a) All CW
 $I_1 = 0.0321 \text{ mA}$
 $I_2 = -0.8838 \text{ mA}$
 $I_3 = -0.968 \text{ mA}$
 $I_4 = -0.639 \text{ mA}$
(b) All CW
 $I_1 = -3.8 \text{ A}$
 $I_2 = -4.2 \text{ A}$
 $I_3 = 0.2 \text{ A}$
25. (a) CW,
 $I_1 = -\frac{1}{7} \text{ A}$, $I_2 = -\frac{5}{7} \text{ A}$
(b) CW,
 $I_1 = -3.0625 \text{ A}$,
 $I_2 = 0.1875 \text{ A}$
27. (I) (a) CW
(b) $I_1 = 1.871 \text{ A}$,
 $I_2 = -8.548 \text{ A}$
(c) $I_{R_1} = 1.871 \text{ A}$,
 $I_{R_2} = -8.548 \text{ A}$,
 $I_{R_3} = 10.419 \text{ A}$
29. $I_{5\Omega}$ (CW) = 1.9535 A,
 $V_a = -7.26 \text{ V}$
31. (a) All CW,
 $I_1 = 0.0321 \text{ mA}$,
 $I_2 = -0.8838 \text{ mA}$,
 $I_3 = -0.968 \text{ mA}$,
 $I_4 = -0.639 \text{ mA}$

- (b) All CW,
 $I_1 = 3.8 \text{ A}$, $I_2 = -4.2 \text{ A}$,
 $I_3 = 0.2 \text{ A}$
33. (I) (b) $V_1 = -14.86 \text{ V}$,
 $V_2 = -12.57 \text{ V}$
(c) $V_{R_1} = V_{R_4} =$
 $V_1 = -14.86 \text{ V}$,
 $V_{R_2} = V_2 = -12.57 \text{ V}$,
 $V_{R_3} = 9.71 \text{ V}$ (+ -)
(II) (b) $V_1 = -2.556 \text{ V}$,
 $V_2 = 4.03 \text{ V}$
(c) $V_{R_1} = V_1 = -2.556 \text{ V}$,
 $V_{R_2} = V_{R_5} = V_2 = 4.03 \text{ V}$,
 $V_{R_4} = V_{R_3} = V_2 - V_1$
 $= 6.586 \text{ V}$
35. (I) $V_1 = 7.238 \text{ V}$,
 $V_2 = -2.453 \text{ V}$,
 $V_3 = 1.405 \text{ V}$
(II) $V_1 = -6.64 \text{ V}$,
 $V_2 = 1.288 \text{ V}$,
 $V_3 = 10.676 \text{ V}$
37. (a) $V_1 = 10.083 \text{ V}$,
 $V_2 = 6.944 \text{ V}$,
 $V_3 = -17.056 \text{ V}$
(b) $V_1 = 48 \text{ V}$, $V_2 = 64 \text{ V}$
39. (b) (I) $V_1 = -14.86 \text{ V}$,
 $V_2 = -12.57 \text{ V}$
(II) $V_1 = -2.556 \text{ V}$,
 $V_2 = 4.03 \text{ V}$
(c) (I) $V_{R_1} = V_{R_4} = -14.86 \text{ V}$,
 $V_{R_2} = -12.57 \text{ V}$,
 $V_{R_3} = V_1 + 12 - V_2$
 $= 9.71 \text{ V}$
(II) $V_{R_1} = -2.556 \text{ V}$,
 $V_{R_2} = V_{R_5} = 4.03 \text{ V}$,
 $V_{R_3} = V_{R_4} = V_2 - V_1$
 $= 6.586 \text{ V}$
41. (I) $V_1 = -5.311 \text{ V}$,
 $V_2 = -0.6219 \text{ V}$,
 $V_3 = 3.751 \text{ V}$
 $V_{-5A} = -5.311 \text{ V}$
(II) $V_1 = -6.917 \text{ V}$,
 $V_2 = 12 \text{ V}$,
 $V_3 = 2.3 \text{ V}$,
 $V_{5A} = V_2 - V_1 = 18.917 \text{ V}$,
 $V_{2A} = V_3 - V_2 = -9.7 \text{ V}$
43. (b) $V_{R_5} = 0.1967 \text{ V}$
(c) no
(d) no
45. (b) $I_{R_s} = 0 \text{ A}$
(c) no
(d) no
47. (a) 3.33 mA
(b) 1.177 A
49. (a) 133.33 mA
(b) 7 A
51. (b) 0.833 mA
53. 4.2 Ω

Chapter 9

1. (a) CW: $I_{R_1} = \frac{5}{6} \text{ A}$, $I_{R_2} = 0 \text{ A}$,
CW: $I_{R_3} = \frac{5}{6} \text{ A}$
(b) $E_1: 5.33 \text{ W}$, $E_2: 0.333 \text{ W}$
(c) 8.333 W (d) no
3. (a) down: 4.4545 mA
(b) down: 3.11 A
5. (a) 6 Ω , 6 V
(b) 2 Ω : 0.75 A,
30 Ω : 0.1667 A,
100 Ω : 0.0566 A
7. (I) 2 Ω , 84 V (II) 1.579 k Ω ,
-1.149 V
9. (I) 45 Ω , -5 V (II) 2.055 k Ω ,
16.772 V
11. 4.041 k Ω , 9.733 V
13. (I): 14 Ω , 2.571 A,
(II): 7.5 Ω , 1.333 A
15. (a) 9.756 Ω , 0.95 A
(b) 2 Ω , 30 A
17. (a) 10 Ω , 0.2 A
(b) 4.033 k Ω , 2.9758 mA
19. (I) (a) 14 Ω
(b) 23.14 W
(II) (a) 7.5 Ω
(b) 3.33 W
21. (a) 9.756 Ω , 2.2 W
(b) 2 Ω , 450 W
23. 0 Ω
25. 500 Ω
27. 39.3 μA , 220 mV
29. 2.25 A, 6.075 V
35. (a) 0.357 mA (b) 0.357 mA
(c) yes

Chapter 10

1. $9 \times 10^3 \text{ N/C}$
3. 70 μF
5. 50 V/m
7. $8 \times 10^3 \text{ V/m}$
9. 937.5 pF
11. mica
13. (a) 10^6 V/m (b) 4.96 μC
(c) 0.0248 μF
15. 29,035 V
17. (a) 0.5 s (b) $20(1 - e^{-t/0.5})$
(c) $1\tau: 12.64 \text{ V}$, $3\tau: 19 \text{ V}$,
 $5\tau: 19.87 \text{ V}$
(d) $i_C = 0.2 \times 10^{-3} e^{-t/0.5}$
 $V_R = 20e^{-t/0.5}$
19. (a) 5.5 ms
(b) $100(1 - e^{-(5.5 \times 10^{-3})t})$
(c) $1\tau: 63.21 \text{ V}$, $3\tau: 95.02 \text{ V}$,
 $5\tau: 99.33 \text{ V}$
(d)
 $i_C = 18.18 \times 10^{-3} e^{-(5.5 \times 10^{-3})t}$
 $V_R = 60e^{-t/(5.5 \times 10^{-3})}$
21. (a) 10 ms

- (b) $50(1 - e^{-t/(10 \times 10^{-3})})$
 (c) $10 \times 10^{-3} e^{-t/(10 \times 10^{-3})}$
 (d) $v_C \cong 50 \text{ V}$, $i_C = 0 \text{ A}$
 (e) $v_C = 50 e^{-t/(4 \times 10^{-3})}$
 $i_C = -25 \times 10^{-3} e^{-t/(4 \times 10^{-3})}$
23. (a) $80(1 - e^{-t/(1 \times 10^{-6})})$
 (b) $0.8 \times 10^{-3} e^{-t/(1 \times 10^{-6})}$
 (c) $v_C = 80 e^{-t/(4.9 \times 10^{-6})}$
 $i_C = 0.163 \times 10^{-3} e^{-t/(4.9 \times 10^{-6})}$
25. (a) $10 \mu\text{s}$ (b) 3 kA (c) yes
27. (a) $v_C = 52 \text{ V} - 40 \text{ V} e^{-t/123.8\text{ms}}$
 $i_C = 2.198 \text{ mA} e^{-t/123.8\text{ms}}$
29. $1.386 \mu\text{s}$
31. $R = 54.567 \text{ k}\Omega$
33. (a) $v_C = 60(1 - e^{-t/0.2\text{s}})$,
 $0.5 \text{ s}: 55.07 \text{ V}$, $1 \text{ s}: 59.596 \text{ V}$
 $i_C = 60 \times 10^{-3} e^{-t/0.2\text{s}}$
 $0.5 \text{ s}: 4.93 \text{ mA}$,
 $1 \text{ s}: 0.404 \text{ mA}$
 $v_{R_1} = 60 e^{-t/0.2\text{s}}$
 $0.5 \text{ s}: 4.93 \text{ V}$, $1 \text{ s}: 0.404 \text{ V}$
 (b) $t = 0.405 \text{ s}$, 1.387 s longer
35. (a) 19.634 V
 (b) 2.31 s
 (c) 1.155 s
37. (a) $v_C = 3.275(1 - e^{-t/52.68\text{ms}})$
 $i_C = 1.216 \times 10^{-3} e^{-t/52.68\text{ms}}$
39. (a) $v_C = 27.2 - 25.2 e^{-t/18.26\text{ms}}$
 $i_C = 3.04 \text{ mA} e^{-t/18.26\text{ms}}$
41. $0-4 \text{ ms}: 0.3 \text{ mA}$,
 $4-6 \text{ ms}: 0.9 \text{ mA}$,
 $6-7 \text{ ms}: 3 \text{ mA}$,
 $7-10 \text{ ms}: 0 \text{ mA}$,
 $10-13 \text{ ms}: -3.2 \text{ mA}$,
 $13-15 \text{ ms}: 1.8 \text{ mA}$
43. $0-4 \text{ ms}: 0 \text{ V}$,
 $4-6 \text{ ms}: -8 \text{ V}$,
 $6-16 \text{ ms}: 20 \text{ V}$,
 $16-18 \text{ ms}: 0 \text{ V}$,
 $18-20 \text{ ms}: -12 \text{ V}$,
 $20-25 \text{ ms}: 0 \text{ V}$
45. $V_1 = 10 \text{ V}$, $Q_1 = 60 \mu\text{C}$,
 $V_2 = 6.67 \text{ V}$, $Q_2 = 40 \mu\text{C}$,
 $V_3 = 3.33 \text{ V}$, $Q_3 = 40 \mu\text{C}$
47. (a) 56.54 V
 (b) 42.405 V
 (c) 14.135 V
 (d) 43.46 V
 (e) 433.44 ms
49. 8640 pJ
51. (a) 5 J
 (b) 0.1 C
 (c) 200 A
 (d) 10 kW
 (e) 10 s

Chapter 11

1. $\Phi: 5 \times 10^4 \text{ maxwells}$,
 $5 \times 10^4 \text{ lines}$. $B: 8 \text{ gauss}$,
 51.616 lines
3. (a) 0.04 T
5. $952.4 \times 10^3 \text{ At/Wb}$
7. 2624.67 At/m
9. 2.133 A
11. (a) $N_1 = 60 \text{ t}$
 (b) $13.34 \times 10^{-4} \text{ Wb/Am}$
13. 2.687 A
15. 1.35 N
17. (a) 2.028 A (b) $\cong 2 \text{ N}$
19. $6.1 \times 10^{-3} \text{ Wb}$
21. (a) $B = 1.5(1 - e^{-H/700\text{At/m}})$
 (c) $H = -700 \log_e(1 - B/1.5 \text{ T})$
 (e) Eq: 40.1 mA

Chapter 12

1. 4.25 V
3. 14 turns
5. $15.65 \mu\text{H}$
7. (a) 2.5 V (b) 0.3 V
 (c) 200 V
9. $0-3 \text{ ms}: 0 \text{ V}$. $3-8 \text{ ms}: 1.6 \text{ V}$.
 $8-13 \text{ ms}: -1.6 \text{ V}$.
 $13-14 \text{ ms}: 0 \text{ V}$.
 $14-15 \text{ ms}: 8 \text{ V}$.
 $15-16 \text{ ms}: -8 \text{ V}$.
 $16-17 \text{ ms}: 0 \text{ V}$.
11. $0-5 \mu\text{s}: 4 \text{ mA}$. $10 \mu\text{s}: -8 \text{ mA}$.
 $12 \mu\text{s}: 4 \text{ mA}$. $12-16 \mu\text{s}: 4 \text{ mA}$.
 $24 \mu\text{s}: 0 \text{ mA}$.
13. (a) $2.27 \mu\text{s}$
 (b) $5.45 \times 10^{-3}(1 - e^{-t/2.27\mu\text{s}})$
 (c) $v_L = 12e^{-t/2.27\mu\text{s}}$
 $v_R = 12(1 - e^{-t/2.27\mu\text{s}})$
 (d) $i_L: 1\tau = 3.45 \text{ mA}$,
 $3\tau = 5.179 \text{ mA}$,
 $5\tau = 5.413 \text{ mA}$.
 $v_L: 1\tau = 4.415 \text{ V}$,
 $3\tau = 0.598 \text{ V}$,
 $5\tau = 0.081 \text{ V}$.
15. (a) $i_L = 4.186 \text{ mA} -$
 $3.814 \text{ mA} e^{-t/13.95\mu\text{s}}$
 $v_L = -32.8 \text{ V} e^{-t/13.95\mu\text{s}}$
17. (a) $v_L = 20 \text{ V} e^{-t/1\mu\text{s}}$
 $i_L = 2 \text{ mA}(1 - e^{-t/1\mu\text{s}})$
 (b) $i_L = 2 \text{ mA} e^{-t/0.5\mu\text{s}}$
 $v_L = -40 \text{ V} e^{-t/0.5\mu\text{s}}$
19. (a) $i_L = 6 \text{ mA}(1 - e^{-t/0.5\mu\text{s}})$
 $v_L = 12 \text{ V} e^{-t/0.5\mu\text{s}}$
 (b) $i_L = 5.188 \text{ mA} e^{-t/83.3\text{ns}}$
 $v_L = -62.256 \text{ V} e^{-t/83.3\text{ns}}$
21. $25.68 \mu\text{s}$
23. (a) $i_L = 3.638 \times$
 $10^{-3} (1 - e^{-t/6.676\mu\text{s}})$
 $v_L = 5.45 e^{-t/6.676\mu\text{s}}$

- (b) 2.825 mA , 1.2186 V
 (c) $i_L = 2.825 \times$
 $10^{-3} e^{-t/2.128\mu\text{s}}$
 $v_L = -13.27 e^{-t/2.128\mu\text{s}}$
25. (a) 0.243 V
 (b) 29.47 V
 (c) 18.96 V
 (d) 2.025 ms
27. (a) 20 V
 (b) $12 \mu\text{A}$
 (c) $5.376 \mu\text{s}$
 (d) 0.366 V
29. $i_L = -3.478 \text{ mA} -$
 $7.432 \text{ mA} e^{-t/173.9\mu\text{s}}$
 $v_L = 51.28 \text{ V} e^{-t/173.9\mu\text{s}}$
31. (a) 8 H
 (b) 4 H
33. $L: 4 \text{ H}$, 2 H
 $R: 5.7 \text{ k}\Omega$, $9.1 \text{ k}\Omega$
35. $V_1 = 16 \text{ V}$, $V_2 = 0 \text{ V}$,
 $I_1 = 4 \text{ mA}$
37. $V_1 = 10 \text{ V}$
 $I_1 = 2 \text{ A}$
 $I_2 = 1.33 \text{ A}$
39. $W_C = 360 \mu\text{J}$
 $W_L = 12 \text{ J}$
- ## Chapter 13
1. (a) 10 ms (b) 2 (c) 100 Hz
 (d) amplitude = 5 V ,
 $V_{p-p} = 6.67 \text{ V}$
3. 10 ms , 100 Hz
5. (a) 60 Hz (b) 100 Hz
 (c) 29.41 Hz (d) 40 kHz
7. 0.25 s
9. $T = 50 \mu\text{s}$
11. (a) $\pi/4$ (b) $\pi/3$ (c) $\frac{2}{3}\pi$
 (d) $\frac{3}{2}\pi$ (e) 0.989π (f) 1.228π
13. (a) 3.14 rad/s
 (b) $20.94 \times 10^3 \text{ rad/s}$
 (c) $1.57 \times 10^6 \text{ rad/s}$
 (d) 157.1 rad/s
15. (a) 120 Hz , 8.33 ms
 (b) 1.34 Hz , 746.27 ms
 (c) 954.93 Hz , 1.05 ms
 (d) $9.95 \times 10^{-3} \text{ Hz}$, 100.5 s
17. 104.7 rad/s
23. 0.4755 A
25. 11.537° , 168.463°
29. (a) v leads i by 10°
 (b) i leads v by 70°
 (c) i leads v by 80°
 (d) i leads v by 150°
31. (a) $v = 25 \sin(\omega t + 30^\circ)$
 (b)
 $i = 3 \times 10^{-3} \sin(6.28 \times 10^3 t - 60^\circ)$
33. $\frac{1}{3} \text{ ms}$
35. 0.388 ms
37. (a) 0.4 ms

- (b) 2.5 kHz
 (c) -25 mV
 39. (a) 1.875 V (b) -4.778 mA
 41. (a) 40 μ s
 (b) 25 kHz
 (c) 17.13 mV
 43. (a) 2 sin 377t
 (b) 100 sin 377t
 (c) 84.87 $\times 10^{-3}$ sin 377t
 (d) 33.95 $\times 10^{-6}$ sin 377t
 45. 2.16 V
 47. 0 V
 49. (a) $T = 40 \mu\text{s}$, $f = 25 \text{ kHz}$,
 $V_{\text{av}} = 20 \text{ mV}$,
 $V_{\text{rms}} = 34.6 \text{ mV}$
 (b) $T = 100 \mu\text{s}$, $f = 10 \text{ kHz}$,
 $V_{\text{av}} = -0.3 \text{ V}$,
 $V_{\text{rms}} = 367 \text{ mV}$

Chapter 14

3. (a) 3770 cos 377t
 (b) 452.4 cos(754t + 20°)
 (c) 4440.63 cos(157t - 20°)
 (d) 200 cos t
 5. (a) 210 sin 754t
 (b) 14.8 sin(400t - 120°)
 (c) 42 $\times 10^{-3}$ sin(ωt + 88°)
 (d) 28 sin(ωt + 180°)
 7. (a) 1.592 H (b) 2.654 H
 (c) 0.8414 H
 9. (a) 100 sin(ωt + 90°)
 (b) 8 sin(ωt + 150°)
 (c) 120 sin(ωt - 120°)
 (d) 60 sin(ωt + 190°)
 11. (a) 1 sin(ωt - 90°)
 (b) 0.6 sin(ωt - 70°)
 (c) 0.8 sin(ωt + 10°)
 (d) 1.6 sin(377t + 130°)
 13. (a) $\infty \Omega$ (b) 530.79 Ω
 (c) 265.39 Ω (d) 17.693 Ω
 (e) 1.327 Ω
 15. (a) 9.31 Hz (b) 4.66 Hz
 (c) 18.62 Hz (d) 1.59 Hz
 17. (a) 6 $\times 10^{-3}$ sin(200t + 90°)
 (b) 33.96 $\times 10^{-3}$ sin(377t + 90°)
 (c) 44.94 $\times 10^{-3}$ sin(374t + 300°)
 (d) 56 $\times 10^{-3}$ sin(ωt + 160°)
 19. (a) 1334 sin(300t - 90°)
 (b) 37.17 sin(377t - 90°)
 (c) 127.2 sin 754t
 (d) 100 sin(1600t - 170°)
 21. (a) C (b) L = 254.78 mH
 (c) R = 5 Ω
 25. 318.47 mH
 27. 5.067 nF
 29. (a) 0 W (b) 0 W
 (c) 122.5 W
 31. 192 W
 33. 40 sin(ωt - 50°)
 35. (a) 2 sin(157t - 60°)
 (b) 318.47 mH (c) 0 W
 37. (a) $i_1 = 2.828 \sin(10^4 t + 150^\circ)$,
 $i_2 = 11.312 \sin(10^4 t + 150^\circ)$
 (b) $i_s = 14.14 \sin(10^4 t + 150^\circ)$
 39. (a) 5 $\angle 36.87^\circ$
 (b) 2.83 $\angle 45^\circ$
 (c) 16.38 $\angle 77.66^\circ$
 (d) 806.23 $\angle 82.87^\circ$
 (e) 1077.03 $\angle 21.80^\circ$
 (f) 0.00658 $\angle 81.25^\circ$
 (g) 11.78 $\angle -49.82^\circ$
 (h) 8.94 $\angle 153.43^\circ$
 (i) 61.85 $\angle -104.04^\circ$
 (j) 101.53 $\angle -39.81^\circ$
 (k) 4326.66 $\angle 123.69^\circ$
 (l) 25.495 $\times 10^{-3} \angle -78.69^\circ$
 41. (a) 15.033 $\angle 86.19^\circ$
 (b) 60.208 $\angle 4.76^\circ$
 (c) 0.30 $\angle 88.09^\circ$
 (d) 2002.5 $\angle -87.14^\circ$
 (e) 86.182 $\angle 93.73^\circ$
 (f) 38.694 $\angle -94^\circ$
 43. (a) 11.8 + j 7
 (b) 151.9 + j 49.9
 (c) 4.72 $\times 10^{-6}$ + j 71
 (d) 5.2 + j 1.6
 (e) 209.3 + j 311
 (f) -21.2 + j 12
 (g) 7.03 + j 9.93
 (h) 95.698 + j 22.768
 45. (a) 6 $\angle -50^\circ$
 (b) 0.2 $\times 10^{-3} \angle 140^\circ$
 (c) 109 $\angle -230^\circ$
 (d) 76.471 $\angle -80^\circ$
 (e) 4 $\angle 0^\circ$
 (f) 0.71 $\angle -16.49^\circ$
 (g) 4.21 $\times 10^{-3} \angle 161.1^\circ$
 (h) 18.191 $\angle -50.91^\circ$
 47. (a) x = 4, y = 3
 (b) x = 4
 (c) x = 3, y = 6 or
 x = 6, y = 3
 (d) 30°
 49. (a) 56.569 sin(377t + 20°)
 (b) 169.68 sin 377t
 (c)
 11.314 $\times 10^{-3}$ sin(377t + 120°)
 (d) 7.07 sin(377t + 90°)
 (e) 1696.8 sin(377t - 120°)
 (f) 6000 sin(377t - 180°)
 51.
 $i_1 = 2.537 \times 10^{-5} \sin(\omega t + 96.79^\circ)$
 53. $i_T = 18 \times 10^{-3} \sin 377t$
 (c) 15.7 $\Omega \angle 90^\circ$
 (d) 265.25 $\Omega \angle -90^\circ$
 (e) 318.47 $\Omega \angle -90^\circ$
 (f) 200 $\Omega \angle 0^\circ$
 3. (a) 88 $\times 10^{-3}$ sin ωt
 (b) 9.045 sin(377t + 150°)
 (c) 2547.02 sin(157t - 50°)
 5. (a) 4.24 $\Omega \angle -45^\circ$
 (b) 3.04 k $\Omega \angle 80.54^\circ$
 (c) 1617.56 $\Omega \angle 88.33^\circ$
 7. (a) 10 $\Omega \angle 36.87^\circ$
 (c) I = 10 A $\angle -36.87^\circ$,
 $V_R = 80 \text{ V} \angle -36.87^\circ$,
 $V_L = 60 \text{ V} \angle 53.13^\circ$
 (f) 800 W (g) 0.8 lagging
 9. (a) 1660.27 $\Omega \angle -73.56^\circ$
 (b) 8.517 mA $\angle 73.56^\circ$
 (c) $V_R = 4.003 \text{ V} \angle 73.56^\circ$,
 $V_L = 13.562 \text{ V} \angle -16.44^\circ$
 (d) 34.09 mW, 0.283 leading
 11. (a) 3.16 k $\Omega \angle 18.43^\circ$
 (c) 3.18 μ F, 6.37 H
 (d) I = 1.3424 mA $\angle 41.57^\circ$,
 $V_R = 4.027 \text{ V} \angle 41.57^\circ$,
 $V_L = 2.6848 \text{ V} \angle 131.57^\circ$,
 $V_C = 1.3424 \text{ V} \angle -48.43^\circ$
 (g) 5.406 mW
 (h) 0.9487 lagging
 13. (a) 40 mH (b) 220 Ω
 15. (a) $V_1 = 37.97 \text{ V} \angle -51.57^\circ$,
 $V_2 = 113.92 \text{ V} \angle 38.43^\circ$
 (b) $V_1 = 55.80 \text{ V} \angle 26.55^\circ$,
 $V_2 = 12.56 \text{ V} \angle -63.45^\circ$
 17. (a) I = 39 mA $\angle 126.65^\circ$,
 $V_R = 1.17 \text{ V} \angle 126.65^\circ$,
 $V_C = 25.86 \text{ V} \angle 36.65^\circ$
 (b) 0.058 leading
 (c) 45.63 mW
 (g) $Z_T = 30 \Omega - j 512.2 \Omega$
 19. $Z_T = 3.2 \Omega + j 2.4 \Omega$
 25. (a) $Z_T = 3 \Omega + j 8 \Omega$,
 $Y_T = 41.1 \text{ mS} - j 109.5 \text{ mS}$
 (b) $Z_T = 60 \Omega - j 70 \Omega$,
 $Y_T = 7.1 \text{ mS} + j 8.3 \text{ mS}$
 (c) $Z_T = 200 \Omega - j 100 \Omega$,
 $Y_T = 4 \text{ mS} + j 2 \text{ mS}$
 27. (a) $Y_T = 538.52 \text{ mS} \angle -21.8^\circ$
 (c) E = 3.71 V $\angle 21.8^\circ$,
 $I_R = 1.855 \text{ A} \angle 21.8^\circ$,
 $I_L = 0.742 \text{ A} \angle -68.2^\circ$
 (f) 6.88 W
 (g) 0.928 lagging
 (h) e = 5.25 sin(377t + 21.8°),
 $i_R = 2.62 \sin(377t + 21.8^\circ)$,
 $i_L = 1.049 \sin(377t - 68.2^\circ)$,
 $i_s = 2.828 \sin 377t$
 29. (a) $Y_T = 129.96 \text{ mS} \angle -50.31^\circ$
 (c) $I_s = 7.8 \text{ A} \angle -50.31^\circ$,
 $I_R = 5 \text{ A} \angle 0^\circ$,
 $I_L = 6 \text{ A} \angle -90^\circ$

Chapter 15

1. (a) 6.8 $\Omega \angle 0^\circ$
 (b) 754 $\Omega \angle 90^\circ$

- (f) 300 W
 (g) 0.638 lagging
 (h) $e = 84.84 \sin 377t$,
 $i_R = 7.07 \sin 377t$,
 $i_L = 8.484 \sin(377t - 90^\circ)$,
 $i_S = 11.03 \sin(377t - 50.31^\circ)$
31. (a) $\mathbf{Y}_T = 0.416 \text{ mS} \angle 36.897^\circ$
 (c) $L = 10.61 \text{ H}$, $C = 1.326 \mu\text{F}$
 (d) $\mathbf{E} = 8.498 \text{ V} \angle -56.897^\circ$,
 $\mathbf{I}_R = 2.833 \text{ mA} \angle -56.897^\circ$,
 $\mathbf{I}_L = 2.125 \text{ mA} \angle -146.897^\circ$,
 $\mathbf{I}_C = 4.249 \text{ mA} \angle 33.103^\circ$
 (g) 24.078 mW
 (h) 0.8 leading
 (i)
 $e = 12.016 \sin(377t - 56.897^\circ)$,
 $i_R = 4 \sin(377t - 56.897^\circ)$,
 $i_L = 3 \sin(377t - 146.897^\circ)$,
 $i_C = 6 \sin(377t + 33.103^\circ)$
33. (a) $\mathbf{I}_1 = 18.09 \text{ A} \angle 65.241^\circ$,
 $\mathbf{I}_2 = 8.528 \text{ A} \angle -24.759^\circ$
 (b) $\mathbf{I}_1 = 11.161 \text{ A} \angle 0.255^\circ$,
 $\mathbf{I}_2 = 6.656 \text{ A} \angle 153.690^\circ$
39. (a) $R_p = 94.73 \Omega$,
 $X_p = 52.1 \Omega (C)$
 (b) $R_p = 4 \text{ k}\Omega$,
 $X_p = 4 \text{ k}\Omega (C)$
41. (a) $\mathbf{E} = 176.68 \text{ V} \angle 36.44^\circ$,
 $\mathbf{I}_R = 0.803 \text{ A} \angle 36.44^\circ$,
 $\mathbf{I}_L = 2.813 \text{ A} \angle -53.56^\circ$
 (b) 0.804 lagging
 (c) 141.86 W
 (f) $\mathbf{I}_C = 1.11 \text{ A} \angle 126.43^\circ$
 (g) $\mathbf{Z}_T = 142.15 \Omega + j 104.96 \Omega$
43. $R = 4 \Omega$, $X_L = 3.774 \Omega$

Chapter 16

1. (a) $1.2 \Omega \angle 90^\circ$
 (b) $10 \text{ A} \angle -90^\circ$
 (c) $10 \text{ A} \angle -90^\circ$
 (d) $\mathbf{I}_2 = 6 \text{ A} \angle -90^\circ$,
 $\mathbf{I}_3 = 4 \text{ A} \angle -90^\circ$
 (e) $60 \text{ V} \angle 0^\circ$
3. (a) $\mathbf{Z}_T = 3.87 \Omega \angle -11.817^\circ$,
 $\mathbf{Y}_T = 0.258 \text{ S} \angle 11.817^\circ$
 (b) $15.504 \text{ A} \angle 41.817^\circ$
 (c) $3.985 \text{ A} \angle 82.826^\circ$
 (d) $47.809 \text{ V} \angle -7.174^\circ$
 (e) 910.71 W
5. (a) $0.375 \text{ A} \angle 25.346^\circ$
 (b) $70.711 \text{ V} \angle -45^\circ$
 (c) 33.9 W
7. (a) $1.423 \text{ A} \angle 18.259^\circ$
 (b) $26.574 \text{ V} \angle 4.763^\circ$
 (c) 54.074 W
9. (a) $\mathbf{Y}_T = 0.099 \text{ S} \angle -9.709^\circ$
 (b) $\mathbf{V}_1 = 20.4 \text{ V} \angle 30^\circ$,
 $\mathbf{V}_2 = 10.887 \text{ V} \angle 58.124^\circ$
 (c) $1.933 \text{ A} \angle 11.109^\circ$

11. $33.201 \text{ A} \angle 38.89^\circ$
 13. 139.71 mW

Chapter 17

3. (a) $\mathbf{Z} = 21.93 \Omega \angle -46.85^\circ$,
 $\mathbf{E} = 10.97 \text{ V} \angle 13.15^\circ$
 (b) $\mathbf{Z} = 5.15 \Omega \angle 59.04^\circ$,
 $\mathbf{E} = 10.3 \text{ V} \angle 179.04^\circ$
5. (a) $5.15 \text{ A} \angle -24.5^\circ$
 (b) $0.442 \text{ A} \angle 143.48^\circ$
7. (a) $13.07 \text{ A} \angle -33.71^\circ$
 (b) $48.33 \text{ A} \angle -77.57^\circ$
9. $-3.165 \times 10^{-3} \text{ V} \angle 137.29^\circ$
11. $\mathbf{I}_{1\text{k}\Omega} = 10 \text{ mA} \angle 0^\circ$
 $\mathbf{I}_{2\text{k}\Omega} = 1.667 \text{ mA} \angle 0^\circ$
13. $\mathbf{I}_L = 1.378 \text{ mA} \angle -56.31^\circ$
15. (a) $\mathbf{V}_1 = 19.86 \text{ V} \angle 43.8^\circ$,
 $\mathbf{V}_2 = 8.94 \text{ V} \angle 106.9^\circ$
 (b) $\mathbf{V}_1 = 19.78 \text{ V} \angle 132.48^\circ$,
 $\mathbf{V}_2 = 13.37 \text{ V} \angle 98.78^\circ$
17. $\mathbf{V}_1 = 220 \text{ V} \angle 0^\circ$
 $\mathbf{V}_2 = 96.664 \text{ V} \angle -12.426^\circ$
 $\mathbf{V}_3 = 100 \text{ V} \angle 90^\circ$
19. (left) $\mathbf{V}_1 = 14.62 \text{ V} \angle -5.86^\circ$
 (top) $\mathbf{V}_2 = 35.03 \text{ V} \angle -37.69^\circ$
 (right) $\mathbf{V}_3 = 32.4 \text{ V} \angle -73.34^\circ$
 (middle) $\mathbf{V}_4 = 5.677 \text{ V} \angle 23.53^\circ$
21. $\mathbf{V}_1 = 4.372 \text{ V} \angle -128.66^\circ$
 $\mathbf{V}_2 = 2.253 \text{ V} \angle 17.628^\circ$
23. $\mathbf{V}_1 = -10.667 \text{ V} \angle 0^\circ$
 $\mathbf{V}_2 = -6 \text{ V} \angle 0^\circ$
25. $-2451.92\mathbf{E}_i$
27. (a) No
 (b) $1.76 \text{ mA} \angle -71.54^\circ$
 (c) $7.03 \text{ V} \angle -18.46^\circ$
29. Balanced
31. $R_x = R_2R_3/R_1$
 $L_x = R_2L_3/R_1$
33. (a) $11.57 \text{ A} \angle -67.13^\circ$
 (b) $36.9 \text{ A} \angle 23.87^\circ$

Chapter 18

1. (a) $6.095 \text{ A} \angle -32.115^\circ$
 (b) $3.77 \text{ A} \angle -93.8^\circ$
3. $i = 0.5 \text{ A} + 1.581 \sin(\omega t - 26.565^\circ)$
5. $6.261 \text{ mA} \angle -63.43^\circ$
7. $-22.09 \text{ V} \angle 6.34^\circ$
9. $19.62 \text{ V} \angle 53^\circ$
11. $\mathbf{V}_s = 10 \text{ V} \angle 0^\circ$
13. (a) $\mathbf{Z}_{Th} = 21.312 \Omega \angle 32.196^\circ$
 $\mathbf{E}_{Th} = 2.131 \text{ V} \angle 32.196^\circ$
 (b) $\mathbf{Z}_{Th} = 6.813 \Omega \angle -54.228^\circ$
 $\mathbf{E}_{Th} = 57.954 \text{ V} \angle 11.099^\circ$
15. (a) $\mathbf{Z}_{Th} = 4 \Omega \angle 90^\circ$
 $\mathbf{E}_{Th} = 4 \text{ V} + 10 \text{ V} \angle 0^\circ$
 (b) $\mathbf{I} = 0.5 \text{ A} + 1.11 \text{ A} \angle -26.565^\circ$

17. (a) $\mathbf{Z}_{Th} = 4.472 \text{ k}\Omega \angle -26.565^\circ$
 $\mathbf{E}_{Th} = 31.31 \text{ V} \angle -26.565^\circ$
 (b) $\mathbf{I} = 6.26 \text{ mA} \angle 63.435^\circ$
19. $\mathbf{Z}_{Th} = 4.44 \text{ k}\Omega \angle -0.031^\circ$
 $\mathbf{E}_{Th} = -444.45 \times 10^3 \text{ V} \angle 0.255^\circ$
21. $\mathbf{Z}_{Th} = 5.099 \text{ k}\Omega \angle -11.31^\circ$
 $\mathbf{E}_{Th} = -50 \text{ V} \angle 0^\circ$
23. $\mathbf{Z}_{Th} = -39.215 \Omega \angle 0^\circ$
 $\mathbf{E}_{Th} = 20 \text{ V} \angle 53^\circ$
25. $\mathbf{Z}_{Th} = 607.42 \Omega \angle 0^\circ$
 $\mathbf{E}_{Th} = 1.62 \text{ V} \angle 0^\circ$
27. (a) $\mathbf{Z}_N = 21.312 \Omega \angle 32.196^\circ$,
 $\mathbf{I}_N = 0.1 \text{ A} \angle 0^\circ$
 (b) $\mathbf{Z}_N = 6.813 \Omega \angle -54.228^\circ$,
 $\mathbf{I}_N = 8.506 \text{ A} \angle 65.324^\circ$
29. (a) $\mathbf{Z}_N = 9.66 \Omega \angle 14.93^\circ$,
 $\mathbf{I}_N = 2.15 \text{ A} \angle -42.87^\circ$
 (b) $\mathbf{Z}_N = 4.37 \Omega \angle 55.67^\circ$,
 $\mathbf{I}_N = 22.83 \text{ A} \angle -34.65^\circ$
31. (a) $\mathbf{Z}_N = 9 \Omega \angle 0^\circ$,
 $\mathbf{I}_N = 1.333 \text{ A} + 2.667 \text{ A} \angle 0^\circ$
 (b) $12 \text{ V} + 2.65 \text{ V} \angle -83.66^\circ$
33. $\mathbf{Z}_N = 5.1 \text{ k}\Omega \angle -11.31^\circ$,
 $\mathbf{I}_N = -1.961 \times 10^{-3} \text{ V} \angle 11.31^\circ$
35. $\mathbf{Z}_N = 5.1 \text{ k}\Omega \angle -11.31^\circ$,
 $\mathbf{I}_N = 9.81 \text{ mA} \angle 11.31^\circ$
37. $\mathbf{Z}_N = 6.63 \text{ k}\Omega \angle 0^\circ$
 $\mathbf{I}_N = 0.792 \text{ mA} \angle 0^\circ$
39. (a) $\mathbf{Z}_L = 8.32 \Omega \angle 3.18^\circ$,
 1198.2 W
 (b) $\mathbf{Z}_L = 1.562 \Omega \angle -14.47^\circ$,
 1.614 W
41. 40 k Ω , 25 W
43. (a) 9 Ω (b) 20 W
45. (a) 1.414 k Ω (b) 0.518 W
49. 25.77 mA $\angle 104.4^\circ$

Chapter 19

1. (a) 120 W
 (b) $Q_T = 0 \text{ VAR}$, $S_T = 120 \text{ VA}$
 (c) 0.5 A
 (d) $I_1 = \frac{1}{6} \text{ A}$, $I_2 = \frac{1}{3} \text{ A}$
3. (a) 400 W, -400 VAR (C),
 565.69 VA, 0.7071 leading
 (c) $5.66 \text{ A} \angle 135^\circ$
5. (a) 500 W, -200 VAR (C),
 538.52 VA
 (b) 0.928 leading
 (d) $10.776 \text{ A} \angle 21.875^\circ$
7. (a) $R: 200 \text{ W}$, $L, C: 0 \text{ W}$
 (b) $R: 0 \text{ VAR}$, $C: 80 \text{ VAR}$,
 $L: 100 \text{ VAR}$
 (c) $R: 200 \text{ VA}$, $C: 80 \text{ VA}$,
 $L: 100 \text{ VA}$
 (d) 200 W, 20 VAR (L),
 200.998 VA, 0.995 (lagging)
 (f) $10.05 \text{ A} \angle -5.73^\circ$

9. (a) $R: 38.99 \text{ W}, L: 0 \text{ W}, C: 0 \text{ W}$
 (b) $R: 0 \text{ VAR}, L: 126.74 \text{ VAR}, C: 46.92 \text{ VAR}$
 (c) $R: 38.99 \text{ VA}, L: 126.74 \text{ VA}, C: 46.92 \text{ VA}$
 (d) $38.99 \text{ W}, 79.82 \text{ VAR} (L), 88.83 \text{ VA}, 0.439 \text{ (lagging)}$
 (f) 0.31 J
 (g) $W_L = 0.32 \text{ J}, W_C = 0.12 \text{ J}$
11. (a) $\mathbf{Z} = 2.30 \Omega + j 1.73 \Omega$
 (b) 4000 W
13. (a) $900 \text{ W}, 0 \text{ VAR}, 900 \text{ VA}, 1$
 (b) $9 \text{ A } \angle 0^\circ$
 (d) $\mathbf{Z}_1: R = 0 \Omega, X_C = 20 \Omega$
 $\mathbf{Z}_2: R = 2.83 \Omega, X = 0 \Omega$
 $\mathbf{Z}_3: R = 5.66 \Omega, X_L = 4.717 \Omega$
15. (a) $1100 \text{ W}, 2366.26 \text{ VAR}, 2609.44 \text{ VA}, 0.4215 \text{ (leading)}$
 (b) $521.89 \text{ V } \angle -65.07^\circ$
 (c) $\mathbf{Z}_1: R = 1743.38 \Omega, X_C = 1307.53 \Omega$
 $\mathbf{Z}_2: R = 43.59 \Omega, X_C = 99.88 \Omega$
17. (a) 7.81 kVA
 (b) 0.640 (lagging)
 (c) 65.08 A
 (d) $1105 \mu\text{F}$
 (e) 41.67 A
19. (a) 128.14 W
 (b) $a-b: 42.69 \text{ W}, b-c: 64.03 \text{ W}, a-c: 106.72 \text{ W}, a-d: 106.72 \text{ W}, c-d: 0 \text{ W}, d-e: 0 \text{ W}, f-e: 21.34 \text{ W}$
21. (a) $5 \Omega, 132.03 \text{ mH}$
 (b) 10Ω
 (c) $15 \Omega, 262.39 \text{ mH}$

Chapter 20

1. (a) $\omega_s = 250 \text{ rad/s}, f_s = 39.79 \text{ Hz}$
 (b) $\omega_s = 3535.53 \text{ rad/s}, f_s = 562.7 \text{ Hz}$
 (c) $\omega_s = 21,880 \text{ rad/s}, f_s = 3482.31 \text{ Hz}$
3. (a) $X_L = 40 \Omega$
 (b) $I = 10 \text{ mA}$
 (c) $V_R = 20 \text{ mV}, V_L = 400 \text{ mV}, V_C = 400 \text{ mV}$
 (d) $Q_s = 20 \text{ (high)}$
 (e) $L = 1.27 \text{ mH}, C = 0.796 \mu\text{F}$
 (f) $BW = 250 \text{ Hz}$
 (g) $f_2 = 5.125 \text{ kHz}, f_1 = 4.875 \text{ kHz}$
5. (a) $BW = 400 \text{ Hz}$
 (b) $f_2 = 6200 \text{ Hz}, f_1 = 5800 \text{ Hz}$
 (c) $X_L = X_C = 45 \Omega$
 (d) $P_{\text{HPF}} = 375 \text{ mW}$

7. (a) $Q_s = 10$
 (b) $X_L = 20 \Omega$
 (c) $L = 1.59 \text{ mH}, C = 3.98 \mu\text{F}$
 (d) $f_2 = 2100 \text{ Hz}, f_1 = 1900 \text{ Hz}$
9. $L = 13.26 \text{ mH}, C = 27.07 \text{ nF}$
 $f_2 = 8460 \text{ Hz}, f_1 = 8340 \text{ Hz}$
11. (a) $f_s = 1 \text{ MHz}$
 (b) $BW = 160 \text{ kHz}$
 (c) $R = 720 \Omega, L = 0.7162 \text{ mH}, C = 35.37 \text{ pF}$
 (d) $R_f = 56.25 \Omega$
13. (a) $f_p = 159.155 \text{ kHz}$
 (b) $V_C = 4 \text{ V}$
 (c) $I_L = I_C = 40 \text{ mA}$
 (d) $Q_p = 20$
15. (a) $f_s = 11,253.95 \text{ Hz}$
 (b) $Q_f = 1.77 \text{ (no)}$
 (c) $f_p = 9,280.24 \text{ Hz}, f_m = 10,794.41 \text{ Hz}$
 (d) $X_L = 5.83 \Omega, X_C = 8.57 \Omega$
 (e) $Z_{T_p} = 12.5 \Omega$
 (f) $V_C = 25 \text{ mV}$
 (g) $Q_p = 1.46, BW = 6.356 \text{ kHz}$
 (h) $I_C = 2.92 \text{ mA}, I_L = 3.54 \text{ mA}$
17. (a) $X_C = 30 \Omega$
 (b) $Z_{T_p} = 225 \Omega$
 (c) $\mathbf{I}_C = 0.6 \text{ A } \angle 90^\circ, \mathbf{I}_L \cong 0.6 \text{ A } \angle -86.19^\circ$
 (d) $L = 0.239 \text{ mH}, C = 265.26 \text{ nF}$
 (e) $Q_p = 7.5, BW = 2.67 \text{ kHz}$
19. (a) $f_s = 7.118 \text{ kHz}, f_p = 6.647 \text{ kHz}, f_m = 7 \text{ kHz}$
 (b) $X_L = 20.88 \Omega, X_C = 23.94 \Omega$
 (c) $Z_{T_p} = 55.56 \Omega$
 (d) $Q_p = 2.32, BW = 2.865 \text{ kHz}$
 (e) $I_L = 99.28 \text{ mA}, I_C = 92.73 \text{ mA}$
 (f) $V_C = 2.22 \text{ V}$
21. (a) $f_p = 3558.81 \text{ Hz}$
 (b) $V_C = 138.2 \text{ V}$
 (c) $P = 691 \text{ mW}$
 (d) $BW = 575.86 \text{ Hz}$
23. (a) $X_L = 98.54 \Omega$
 (b) $Q_f = 8.21$
 (c) $f_p = 8.05 \text{ kHz}$
 (d) $V_C = 4.83 \text{ V}$
 (e) $f_2 = 8.55 \text{ kHz}, f_1 = 7.55 \text{ kHz}$
25. $R_s = 3.244 \text{ k}\Omega, C = 31.66 \text{ nF}$
27. (a) $f_p = 251.65 \text{ kHz}$
 (b) $Z_{T_p} = 4.444 \text{ k}\Omega$
 (c) $Q_p = 14.05$
 (d) $BW = 17.91 \text{ kHz}$
 (e) $20 \text{ nF}: f_p = 194.93 \text{ kHz}, Z_{T_p} = 49.94 \Omega, Q_p = 2.04, BW = 95.55 \text{ kHz}$
 (f) $1 \text{ nF}: f_p = 251.65 \text{ kHz}, Z_{T_p} = 13.33 \text{ k}\Omega, Q_p = 21.08, BW = 11.94 \text{ kHz}$

- (g) Network: $L/C = 100 \times 10^3$
 part (e): $L/C = 1 \times 10^3$
 part (f): $L/C = 400 \times 10^3$
 (h) yes, $L/C \uparrow, BW \downarrow$

Chapter 21

1. (a) 0.2 H
 (b) $e_p = 1.6 \text{ V}, e_s = 5.12 \text{ V}$
 (c) $e_p = 15 \text{ V}, e_s = 24 \text{ V}$
3. (a) 158.02 mH
 (b) $e_p = 24 \text{ V}, e_s = 1.8 \text{ V}$
 (c) $e_p = 15 \text{ V}, e_s = 24 \text{ V}$
5. (a) 3.125 V (b) $391.02 \mu\text{Wb}$
 7. 56.31 Hz
 9. 400Ω
 11. $12,000t$
 13. (a) 3
 (b) 2.78 W
15. (a) $360.56 \Omega \angle 86.82^\circ$
 (b) $332.82 \text{ mA } \angle -86.82^\circ$
 (c) $\mathbf{V}_{R_e} = 6.656 \text{ V } \angle -86.82^\circ, \mathbf{V}_{X_e} = 13.313 \text{ V } \angle 3.18^\circ, \mathbf{V}_{X_L} = 106.50 \text{ V } \angle 3.18^\circ$
19. 1.354 H
21. $\mathbf{I}_1(R_1 + j X_{L_1}) + \mathbf{I}_2(j X_m) = \mathbf{E}_1$
 $\mathbf{I}_1(j X_m) + \mathbf{I}_2(j X_{L_2} + R_2) = 0$
23. (a) 20 (b) 83.33 A (c) 4.167 A
 (d) $a = \frac{1}{20}, I_s = 4.167 \text{ A}, I_p = 83.33 \text{ A}$
25. (a) $25 \text{ V } \angle 0^\circ, 5 \text{ A } \angle 0^\circ$
 (b) $80 \Omega \angle 0^\circ$ (c) $20 \Omega \angle 0^\circ$
27. (a) $\mathbf{E}_2 = 40 \text{ V } \angle 60^\circ, \mathbf{I}_2 = 3.33 \text{ A } \angle 60^\circ, \mathbf{E}_3 = 30 \text{ V } \angle 60^\circ, \mathbf{I}_3 = 3 \text{ A } \angle 60^\circ$
 (b) $R_1 = 64.52 \Omega$
29. $[\mathbf{Z}_1 + \mathbf{X}_{L_1}]\mathbf{I}_1 - \mathbf{Z}_{M_{12}}\mathbf{I}_2 + \mathbf{Z}_{M_{13}}\mathbf{I}_3 = \mathbf{E}_1,$
 $\mathbf{Z}_{M_{12}}\mathbf{I}_1 - [\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{X}_{L_2}]\mathbf{I}_2 + \mathbf{Z}_2\mathbf{I}_3 = 0,$
 $\mathbf{Z}_{M_{13}}\mathbf{I}_1 - \mathbf{Z}_2\mathbf{I}_2 + [\mathbf{Z}_2 + \mathbf{Z}_4 + \mathbf{X}_{L_3}]\mathbf{I}_3 = 0$

Chapter 22

1. (a) 120.1 V (b) 120.1 V
 (c) 12.01 A (d) 12.01 A
3. (a) 120.1 V (b) 120.1 V
 (c) 16.98 A (d) 16.98 A
5. (a) $\theta_2 = -120^\circ, \theta_3 = 120^\circ$
 (b) $\mathbf{V}_{an} = 120 \text{ V } \angle 0^\circ, \mathbf{V}_{bn} = 120 \text{ V } \angle -120^\circ, \mathbf{V}_{cn} = 120 \text{ V } \angle 120^\circ$
 (c) $\mathbf{I}_{an} = 8 \text{ A } \angle -53.13^\circ, \mathbf{I}_{bn} = 8 \text{ A } \angle -173.13^\circ, \mathbf{I}_{cn} = 8 \text{ A } \angle 66.87^\circ$
 (e) 8 A (f) 207.85 V
7. $V_\phi = 127 \text{ V}, I_\phi = 8.98 \text{ A}, I_L = 8.98 \text{ A}$

9. (a) $E_{AN} = 12.7 \text{ kV} \angle -30^\circ$,
 $E_{BN} = 12.7 \text{ kV} \angle -150^\circ$,
 $E_{CN} = 12.7 \text{ kV} \angle 90^\circ$
 (b) $I_{an} = 11.285 \text{ A} \angle -97.54^\circ$,
 $I_{bn} = 11.285 \text{ A} \angle -217.54^\circ$,
 $I_{cn} = 11.285 \text{ A} \angle 22.46^\circ$
 (c) $I_L = I_\phi$
 (d) $V_{an} = 12,154.28 \text{ V} \angle -29.34^\circ$,
 $V_{bn} = 12,154.28 \text{ V} \angle -149.34^\circ$,
 $V_{cn} = 12,154.28 \text{ V} \angle 90.66^\circ$
11. (a) 120.1 V (b) 208 V
 (c) 13.364 A (d) 23.15 A
13. (a) $\theta_2 = -120^\circ$, $\theta_3 = +120^\circ$
 (b) $V_{ab} = 208 \text{ V} \angle 0^\circ$,
 $V_{bc} = 208 \text{ V} \angle -120^\circ$,
 $V_{ca} = 208 \text{ V} \angle 120^\circ$
 (d) $I_{ab} = 9.455 \text{ A} \angle 0^\circ$,
 $I_{bc} = 9.455 \text{ A} \angle -120^\circ$,
 $I_{ca} = 9.455 \text{ A} \angle 120^\circ$
 (e) 16.376 A (f) 120.1 V
15. (a) $\theta_2 = -120^\circ$, $\theta_3 = 120^\circ$
 (b) $V_{ab} = 208 \text{ V} \angle 0^\circ$,
 $V_{bc} = 208 \text{ V} \angle -120^\circ$,
 $V_{ca} = 208 \text{ V} \angle 120^\circ$
 (d) $I_{ab} = 86.67 \text{ A} \angle -36.87^\circ$,
 $I_{bc} = 86.67 \text{ A} \angle -156.87^\circ$,
 $I_{ca} = 86.67 \text{ A} \angle 83.13^\circ$
 (e) 150.11 A (f) 120.1 V
17. (a) $I_{ab} = 15.325 \text{ A} \angle -73.30^\circ$,
 $I_{bc} = 15.325 \text{ A} \angle -193.30^\circ$,
 $I_{ca} = 15.325 \text{ A} \angle 46.7^\circ$
 (b) $I_{Aa} = 26.54 \text{ A} \angle -103.31^\circ$,
 $I_{Bb} = 26.54 \text{ A} \angle 136.68^\circ$,
 $I_{Cc} = 26.54 \text{ A} \angle 16.69^\circ$
 (c) $E_{AB} = 17,013.6 \text{ V} \angle -0.59^\circ$,
 $E_{BC} = 17,013.77 \text{ V} \angle -120.59^\circ$,
 $E_{CA} = 17,013.87 \text{ V} \angle 119.41^\circ$
19. (a) 208 V (b) 120.09 V
 (c) 7.076 A (d) 7.076 A
21. $V_\phi = 69.28 \text{ V}$, $I_\phi = 2.89 \text{ A}$,
 $I_L = 2.89 \text{ A}$
23. $V_\phi = 69.28 \text{ V}$, $I_\phi = 5.77 \text{ A}$,
 $I_L = 5.77 \text{ A}$
25. (a) 440 V (b) 440 V
 (c) 29.33 A (d) 50.8 A
27. (a) $\theta_2 = -120^\circ$, $\theta_3 = +120^\circ$
 (b) $V_{ab} = 100 \text{ V} \angle 0^\circ$,
 $V_{bc} = 100 \text{ V} \angle -120^\circ$,
 $V_{ca} = 100 \text{ V} \angle 120^\circ$
 (d) $I_{ab} = 5 \text{ A} \angle 0^\circ$,
 $I_{bc} = 5 \text{ A} \angle -120^\circ$,
 $I_{ca} = 5 \text{ A} \angle 120^\circ$
 (e) 8.66 A
29. (a) $\theta_2 = -120^\circ$, $\theta_3 = 120^\circ$
 (b) $V_{ab} = 100 \text{ V} \angle 0^\circ$,
 $V_{bc} = 100 \text{ V} \angle -120^\circ$,
 $V_{ca} = 100 \text{ V} \angle 120^\circ$
- (d) $I_{ab} = 7.072 \text{ A} \angle 45^\circ$,
 $I_{bc} = 7.072 \text{ A} \angle -75^\circ$,
 $I_{ca} = 7.072 \text{ A} \angle 165^\circ$
 (e) 12.25 A
31. 2160 W, 0 VAR, 2160 VA,
 $F_p = 1$
33. 7210.67 W, 7210.67 VAR (C),
 10,197.42 VA, 0.707 leading
35. 7.263 kW, 7.263 kVAR,
 10.272 kVA, 0.707 lagging
37. 287.93 W, 575.86 VAR (L),
 643.83 VA, 0.4472 lagging
39. 900 W, 1200 VAR (L), 1500 VA,
 0.6 lagging
41. $Z_\phi = 12.98 \Omega - j 17.31 \Omega$
43. (a) 9237.6 V (b) 80 A
 (c) 1276.8 kW
 (d) 0.576 lagging
 (e) $I_{Aa} = 80 \text{ A} \angle -54.83^\circ$
 (f) $V_{an} = 7773.45 \text{ V} \angle -4.87^\circ$
 (g) $Z_\phi = 62.52 \Omega + j 74.38 \Omega$
 (h) F_p (entire system) = 0.576,
 F_p (load) = 0.643 (both lagging)
 (i) 93.98%
45. (b) $P_T = 5899.64 \text{ W}$,
 $P_{\text{meter}} = 1966.55 \text{ W}$
49. (a) 120.09 V
 (b) $I_{an} = 8.492 \text{ A}$, $I_{bn} = 7.076 \text{ A}$,
 $I_{cn} = 42.465 \text{ A}$
 (c) 4928.5 W, 4928.53 VAR (L),
 6969.99 VA, 0.7071 lagging
 (d) $I_{an} = 8.492 \text{ A} \angle -75^\circ$,
 $I_{bn} = 7.076 \text{ A} \angle -195^\circ$,
 $I_{cn} = 42.465 \text{ A} \angle 45^\circ$
 (e) $I_N = 34.712 \text{ A} \angle -42.972^\circ$
- (b) $0.1f_c: -5.71^\circ$, $0.5f_c: -26.57^\circ$,
 $f_c: -45^\circ$, $2f_c: -63.43^\circ$,
 $10f_c: -84.29^\circ$
21. $C = 0.265 \mu\text{F}$,
 250 Hz: $A_v = 0.895$,
 $\theta = -26.54^\circ$,
 1000 Hz: $A_v = 0.4475$,
 $\theta = -63.41^\circ$
23. (a) $f_c = 3.617 \text{ kHz}$,
 $f_c: A_v = 0.707$, $\theta = 45^\circ$,
 $2f_c: A_v = 0.894$, $\theta = 26.57^\circ$,
 $0.5f_c: A_v = 0.447$, $\theta = 63.43^\circ$,
 $10f_c: A_v = 0.995$, $\theta = 5.71^\circ$,
 $\frac{1}{10}f_c: A_v = 0.0995$,
 $\theta = 84.29^\circ$
25. $R = 795.77 \Omega \rightarrow 797 \Omega$,
 $f_c: A_v = 0.707$, $\theta = 45^\circ$,
 1 kHz: $A_v = 0.458$, $\theta = 63.4^\circ$,
 4 kHz: $A_v \cong 0.9$, $\theta = 26.53^\circ$
27. (a) $f_{c1} = 795.77 \text{ Hz}$,
 $f_{c2} = 1989.44 \text{ Hz}$,
 $f_{c1}: V_o = 0.656V_i$,
 $f_{c2}: V_o = 0.656V_i$,
 $f_{\text{center}} = 1392.60 \text{ Hz}$,
 $V_o = 0.711V_i$,
 500 Hz: $V_o = 0.516V_i$,
 4 kHz: $V_o = 0.437V_i$
 (b) $BW \cong 2.9 \text{ kHz}$,
 $f_{\text{center}} = 1.94 \text{ kHz}$
29. (a) $f_s = 100.658 \text{ kHz}$
 (b) $Q_s = 18.39$, $BW = 5473.52 \text{ Hz}$
 (c) $f_s: A_v = 0.93$,
 $f_1 = 97,921.24 \text{ Hz}$,
 $f_2 = 103,394.76 \text{ Hz}$,
 $f = 95 \text{ kHz}: A_v = 0.392$,
 $f = 105 \text{ kHz}: A_v = 0.5$
 (d) $f = f_s$, $V_o = 0.93 V$,
 $f = f_1 = f_2$, $V_o = 0.658 V$
31. (a) $Q_s = 12.195$
 (b) $BW = 410 \text{ Hz}$,
 $f_2 = 5205 \text{ Hz}$,
 $f_1 = 4795 \text{ Hz}$
 (c) $f_s: V_o = 0.024V_i$
 (d) $f_s: V_o$ still $0.024V_i$
33. (a) $f_p = 726.44 \text{ kHz}$ (stop-band)
 $f = 2.013 \text{ MHz}$ (pass-band)
35. (a–b) $f_c = 6772.55 \text{ Hz}$
 (c) $f_c: -3 \text{ dB}$, $\frac{1}{2}f_c: -6.7 \text{ dB}$,
 $2f_c: -0.969 \text{ dB}$,
 $\frac{1}{10}f_c: -20.04 \text{ dB}$,
 $10f_c: -0.043 \text{ dB}$
 (d) $f_c: 0.707$, $\frac{1}{2}f_c: 0.4472$,
 $2f_c: 0.894$
 (e) $f_c: 45^\circ$, $\frac{1}{2}f_c: 63.43^\circ$, $2f_c: 26.57^\circ$
37. (a–b) $f_c = 13.26 \text{ kHz}$
 (c) $f_c: -3 \text{ dB}$, $\frac{1}{2}f_c: -0.97 \text{ dB}$,
 $2f_c: -6.99 \text{ dB}$

Chapter 23

1. (a) left: 1.54 kHz,
 right: 5.623 kHz
 (b) bottom: 0.2153 V,
 top: 0.5248 V
3. (a) 1000 (b) 10^{12}
 (c) 1.585 (d) 1.096
 (e) 10^{10} (f) 1513.56
 (g) 10.023 (h) 1,258,925.41
5. 1.681
 7. -0.301
9. (a) 1.845
 (b) 18.45
11. 13.01
 13. 38.49
15. 24.08 dB_s
19. (a) $0.1f_c: 0.995$, $0.5f_c: 0.894$,
 $f_c: 0.707$, $2f_c: 0.447$,
 $10f_c: 0.0995$

- $\frac{1}{10}f_c$: -0.043 dB,
 $10f_c$: -20.04 dB
 (d) f_c : 0.707 , $\frac{1}{2}f_c$: 0.894 ,
 $2f_c$: 0.447
 (e) f_c : -45° , $\frac{1}{2}f_c$: -26.57° ,
 $2f_c$: -63.43°
39. (a) $f_1 = 663.15$ Hz, $f_c = 468.1$ Hz
 $0 < f < f_c$: $+6$ dB/octave,
 $f > f_c$: -3.03 dB
 (b) f_1 : 45° , f_c : 54.78° , $\frac{1}{2}f_1$: 63.43° ,
 $2f_1$: 84.29°
41. (a) $f_1 = 19,894.37$ Hz
 $f_c = 1,989.44$ Hz
 $0 < f < f_c$: 0 dB,
 $f_c < f < f_1$: -6 dB/octave,
 $f > f_1$: -20 dB
 (b) f_c : -39.29° ,
 10 kHz: -52.06° ,
 f_1 : -39.29°
43. (a) $f_1 = 964.58$ Hz,
 $f_c = 7,334.33$ Hz
 $0 < f < f_1$: -17.62 dB,
 $f_1 < f < f_c$: $+6$ dB/octave,
 $f > f_c$: 0 dB
 (b) f_1 : 39.35° , 1.3 kHz: 43.38° ,
 f_c : 39.35°
45. (a) $f = 180$ Hz $\cong -3$ dB,
 $f = 18$ kHz: -3.105 dB
 (b) 100 Hz: 97° ,
 1.8 kHz: $0.12^\circ \cong 0^\circ$,
 18 kHz: -61.8°
47. $A_v = -120/[(1 - j 50/f)(1 - j 200/f)(1 - jf/36 \text{ kHz})]$
49. $f_c = 2$ kHz, $0 < f < f_c$: 0 dB,
 $f > f_c$: -6 dB/octave
51. $f_1 = 1$ kHz, $f_2 = 2$ kHz,
 $f_3 = 3$ kHz
 $0 < f < f_1$: 0 dB,
 $f_1 < f < f_2$: $+6$ dB/octave
 $f_2 < f < f_3$: $+12$ dB/octave,
 $f > f_3$: 13.06 dB
53. (a) woofer: 0.673 , tweeter: 0.678
 (b) woofer: 0.015 , tweeter: 0.337
 (c) mid-range: $0.998 \cong 1$

Chapter 24

- (a) positive-going (b) 2 V
(c) 0.2 ms (d) 6 V (e) 6.5%
- (a) positive-going
(b) 10 mV
(c) 3.2 ms (d) 20 mV
(e) 3.4%
- V_2 of $(V_1 - V_2)/V = 0.1$ is
 13.571 mV
- (a) $120 \mu\text{s}$ (b) 8.333 kHz
(c) maximum = 440 mV,
minimum = 80 mV

9. prf = 125 kHz,
 duty cycle = 62.5%

- (a) $8 \mu\text{s}$
(b) $2 \mu\text{s}$
(c) 125 kHz
(d) 0 V
(e) 3.464 mV
- 18.88 mV
- 117 mV
- $v_o = 4(1 + e^{-t/20\text{ms}})$
- $i_C = -8 \times 10^{-3} e^{-t}$
- $i_C = 4 \times 10^{-3} e^{-t/0.2\text{ms}}$
(a) $5\tau = T/2$ (b) $5\tau = \frac{1}{5}(T/2)$
(c) $5\tau = 10(T/2)$
- $0 - T/2$: $v_C = 20$ V,
 $T/2 - T$: $v_C = 20e^{-t/\tau}$,
 $T - \frac{3}{2}T$: $v_C = 20(1 - e^{-t/\tau})$,
 $\frac{3}{2}T - T$: $v_C = 20e^{-t/\tau}$
- $Z_p = 4.573$ M $\Omega \angle -59.5^\circ$,
 $Z_s = 0.507$ M $\Omega \angle -59.5^\circ$

Chapter 25

- (I) a. no b. no c. yes d. no
e. yes
(II) a. yes b. yes c. yes d. yes
e. no
(III) a. yes b. yes c. no d. yes
e. yes
(IV) a. no b. no c. yes d. yes
e. yes
- (a) 19.04 V (b) 4.53 A
- 71.872 W
- (a) $i = 2 + 2.08 \sin(400t - 33.69^\circ) + 0.5 \sin(800t - 53.13^\circ)$
(b) 2.508 A
(c) $v_R = 24 + 24.96 \sin(400t + 33.69^\circ) + 6 \sin(800t - 53.13^\circ)$
(d) 30.092 A
(e) $v_L = 16.64 \sin(400t + 56.31^\circ) + 8 \sin(800t + 36.87^\circ)$
(f) 13.055 V (g) 75.481 W
- (a) $i = 1.2 \sin(400t + 53.13^\circ)$
(b) 0.848 A
(c) $v_R = 18 \sin(400t + 53.13^\circ)$
(d) 12.73 V
(e) $v_C = 18 + 23.98 \sin(400t - 36.87^\circ)$
(f) 24.73 V (g) 10.79 W
- $v_o = 2.257 \times 10^{-3} \sin(377t + 93.66^\circ) + 1.923 \times 10^{-3} \sin(754t + 1.64^\circ)$

17. $i_T = 30 + 30.27 \sin(20t + 7.59^\circ) + 0.5 \sin(40t - 30^\circ)$

Chapter 26

- $Z_i = 986.84 \Omega$
- (a) $I_{i1} = 10 \mu\text{A}$
(b) $Z_{i2} = 4.5$ k Ω
(c) $E_{i3} = 6.9$ V
- $Z_o = 44.59$ k Ω
- $Z_o = 10$ k Ω
- (a) $A_v = -392.98$
(b) $A_{vT} = -320.21$
- (a) $A_{vNL} = -2398.8$
(b) $E_i = 50$ mV
(c) $Z_i = 1$ k Ω
- (a) $A_G = 6.067 \times 10^4$
(b) $A_{GT} = 4.94 \times 10^4$
- (a) $A_{vT} = 1500$
(b) $A_{iT} = 187.5$
(c) $A_{i1} = 15$, $A_{i2} = 12.5$
(d) $A_{iT} = 187.5$
- (a) $z_{11} = (Z_1 Z_2 + Z_1 Z_3) / (Z_1 + Z_2 + Z_3)$,
 $z_{12} = Z_1 Z_3 / (Z_1 + Z_2 + Z_3)$,
 $z_{21} = z_{12}$,
 $z_{22} = (Z_1 Z_3 + Z_2 Z_3) / (Z_1 + Z_2 + Z_3)$
- (a) $y_{11} = (Y_1 Y_2 + Y_1 Y_3) / (Y_1 + Y_2 + Y_3)$,
 $y_{12} = -Y_1 Y_2 / (Y_1 + Y_2 + Y_3)$,
 $y_{21} = y_{12}$,
 $y_{22} = (Y_1 Y_2 + Y_2 Y_3) / (Y_1 + Y_2 + Y_3)$
- $h_{11} = Z_1 Z_2 / (Z_1 + Z_2)$,
 $h_{21} = -Z_1 / (Z_1 + Z_2)$,
 $h_{12} = Z_1 / (Z_1 + Z_2)$,
 $h_{22} = (Z_1 + Z_2 + Z_3) / (Z_1 Z_3 + Z_2 Z_3)$
- $h_{11} = (Y_1 + Y_2 + Y_3) / (Y_1 Y_2 + Y_1 Y_3)$,
 $h_{21} = -Y_2 / (Y_2 + Y_3)$,
 $h_{12} = Y_2 / (Y_2 + Y_3)$,
 $h_{22} = Y_2 Y_3 / (Y_2 + Y_3)$
- (a) 47.62 (b) -99
- $Z_i = 9,219.5 \Omega \angle -139.4^\circ$,
 $Z_o = 29.07$ k $\Omega \angle -86.05^\circ$
- $h_{11} = 2.5$ k Ω , $h_{12} = 0.5$,
 $h_{21} = -0.75$, $h_{22} = 0.25$ mS