

PROBLEM SOLUTIONS CHAPTER 10

SOLUTION 10.1 Using KCL, we can write

$$C \frac{dv_C}{dt} + \frac{v_C}{R} = i_{in}(t)$$

Dividing by C:

$$\frac{dv_C}{dt} + \frac{1}{RC} v_C = \frac{i_{in}(t)}{C}$$

We know that $i_{in}(t) = 20\sin(400t)$ mA, which can be represented by a complex exponential,

$i_{in}(t) = \text{Re}\left[20e^{j400t} e^{-j/2}\right]$ mA. For convenience we will simply let $i_{in}(t) = 20e^{j400t} e^{-j/2}$ mA, knowing that we must take the real part to complete our solution. The output voltage will also be represented as a complex exponential:

$$v_C(t) = V_m e^{j(400t + \phi)} = V_m e^{j400t} e^{j\phi}$$

Substituting this expression into the differential equation and canceling e^{j400t} :

$$j400V_m e^{j\phi} + \frac{V_m}{RC} e^{j\phi} = \frac{20 \times 10^{-3} e^{-j/2}}{C}$$

Thus

$$V_m e^{j\phi} \left(\frac{1}{RC} + j400 \right) = \frac{20 \times 10^{-3}}{C} \quad V_m e^{j\phi} = \frac{-j4000}{1000 + j400} = 3.714 \angle -111.8^\circ$$

where the values for $R = 100$ and $C = 5$ mF were substituted in. Thus,

$$V_m = 3.714$$

$$\phi = 0 - \tan^{-1} \frac{400}{1000} = -111.8^\circ$$

Taking into account a 90° phase shift we obtain

$$v_C(t) = 3.714 \cos(400t - 111.8^\circ) = 3.714 \sin(400t - 21.8^\circ) \text{ V}$$

and

$$i_{out}(t) = 18.57 \sin(400t - 21.8^\circ) \text{ mA}$$

SOLUTION 10.2 From KCL and component definitions:

$$i_{in}(t) - \frac{v_L}{25} - i_L = 0 \quad \frac{0.1}{25} \frac{di_L}{dt} + i_L = i_{in}(t) \quad \frac{di_L}{dt} + 250i_L = 250i_{in}(t)$$

We represent the input signal by the complex exponential: $i_{in}(t) = 0.2e^{j250t}$ A and the unknown current can be represented as $i_L(t) = I_L e^{j(250t+\phi)}$.

Substituting this into the differential equation and canceling e^{j250t} :

$$j250I_L e^{j\phi} + 250I_L e^{j\phi} = 50$$

Thus

$$I_L e^{j\phi} (j250 + 250) = 50 \quad I_L e^{j\phi} = \frac{50}{250 + j250} = 0.14142 \quad -45^\circ$$

and

$$I_L = 0.141, \phi = -45^\circ \quad i_L(t) = 0.141 \cos(250t - 45^\circ) \text{ A}$$

SOLUTION 10.3. Construct differential equation by KVL and device definitions:

$$v_{in}(t) - 0.5 \frac{di_L}{dt} - 200i_L = 0 \quad \frac{di_L}{dt} + 400i_L = 2v_{in}(t)$$

We represent $v_{in}(t)$ as the complex exponential function, $v_{in}(t) = 20e^{j400t}$ V. The current in the inductor has the form: $i_L = I_L e^{j(400t+\phi)}$. Substituting into the differential equation and canceling e^{j400t} :

$$j400I_L e^{j\phi} + 400I_L e^{j\phi} = 40$$

Thus

$$I_L e^{j\phi} (j\omega + 400) = 40 \quad I_L e^{j\phi} = \frac{40}{400 + j400} = 0.070711 \quad -45^\circ$$

and

$$I_L = 0.0707, \phi = -45^\circ, \quad i_L(t) = 70.7 \cos(400t - 45^\circ) \text{ mA}$$

Hence,

$$v_{out}(t) = 14.14 \cos(400t - 45^\circ) \text{ V}$$

SOLUTION 10.4. Construct differential equation using KVL and device definitions:

$$v_{in}(t) - v_C - C \frac{dv_C}{dt} R = 0 \quad RC \frac{dv_C}{dt} + v_C = v_{in}(t)$$

The output voltage is defined as:

$$v_{out}(t) = v_{in}(t) - v_C(t)$$

This means that finding v_C is enough to be able to obtain the output voltage. The input voltage is represented by the complex exponential:

$$v_{in}(t) = 20e^{j250t} e^{-j\pi/2} \text{ V}$$

and $v_C(t) = V_m e^{j(250t + \phi)}$. Substituting into the differential equation, dividing by e^{j250t} , and rearranging:

$$j250RCV_C e^{j\phi} + V_C e^{j\phi} = -j20 \quad V_C e^{j\phi} (j250RC + 1) = -j20$$

$$V_C e^{j\phi} = \frac{-j20}{1 + j} = 14.142 \angle -135^\circ$$

Now

$$V_{out} e^{j\theta} = -j20 - V_C e^{j\phi} \quad V_{out} e^{j\theta} = 10 - j10 = 14.142 \angle -45^\circ$$

Thus, in the time-domain,

$$v_{out}(t) = 14.142 \cos(250t - 45^\circ) \text{ V}$$

SOLUTION 10.5. The circuit is identical to that of problem 10.1. Thus,

$$RC \frac{dv_s}{dt} + v_s = Ri_s(t) \quad Ri_s(t) - RC \frac{dv_s}{dt} = v_s$$

Moreover, the complex exponential solution is given by

$$v_s(t) = V_m e^{j\phi} = 223.6 e^{-j63.43^\circ} \text{ V}$$

Hence

$$R - jRC 223.6 e^{-j63.43^\circ} = 223.6 e^{-j63.43^\circ} = 100 - j200$$

i.e.,

$$R - jRC(100 - j200) = R - 200RC - j100RC = 100 - j200$$

Thus $RC = 2$ s, $R = 100 + 200RC = 500$, and $C = 4$ mF.

SOLUTION 10.6. First use KVL

$$v_{in} - v_L - v_C - v_{out} = 0 \quad v_{in} - L \frac{di_L}{dt} - \frac{1}{C} \int i_L dt - Ri_L = 0$$

Differentiating this equation, rearranging, and dividing by L,

$$\frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L = \frac{1}{L} \frac{dv_{in}}{dt}$$

We represent the input signal with $\omega = 10^4$ as $v_{in}(t) = 100e^{j\omega t} e^{-j/2}$ V and $i_L(t) = I_L e^{j\omega t} e^{j\phi}$ A.

Substituting these two expressions into the differential equation and dividing out $e^{j\omega t}$:

$$-\omega^2 I_L e^{j\phi} + j \frac{R\omega}{L} I_L e^{j\phi} + \frac{1}{LC} I_L e^{j\phi} = \frac{-j100 \times j\omega}{L} \quad I_L e^{j\phi} \left[\frac{1}{LC} - \omega^2 + j \frac{R\omega}{L} \right] = 10^8$$

$$I_L e^{j\phi} = \frac{10^8}{-75 \times 10^6 + j10^8} = -0.48 - j0.64 = 0.8 \angle -126.87^\circ$$

Solving for the magnitude and angle (by hand or using MATLAB):

$$i_L(t) = 0.8 \cos(10,000t - 126.87^\circ) = 0.8 \sin(10,000t - 36.87^\circ) \text{ A}$$

and

$$v_{out}(t) = 80 \sin(10,000t - 36.87^\circ) \text{ V}$$

SOLUTION 10.7. Using standard reference directions, from KCL and component definitions,

$$i_{in} = i_R + i_L + i_C = \frac{v_{out}}{R} + i_L(0) + \frac{1}{L} \int_0^t v_{out}(\tau) d\tau + C \frac{dv_{out}}{dt}$$

Taking a second derivative and dividing by C yields

$$\frac{d^2 v_{out}}{dt^2} + \frac{1}{RC} \frac{dv_{out}}{dt} + \frac{1}{LC} v_{out} = \frac{1}{C} \frac{di_{in}}{dt}$$

We now let $\omega = 2500$ rad/s and represent $i_{in}(t)$ by the real part of the complex exponential $0.02e^{j\omega t}$.

Further we represent $v_{out}(t)$ as the real part of the complex exponential $V_m e^{j(\omega t + \phi)} = V_m e^{j\omega t} e^{j\phi}$.

Substituting these expressions into the differential equation and taking the indicated derivatives yields

$$V_m(j\omega)^2 e^{j\omega t} e^{j\phi} + \frac{V_m}{RC} j\omega e^{j\omega t} e^{j\phi} + \frac{1}{LC} V_m e^{j\omega t} e^{j\phi} = \frac{0.02}{C} j\omega e^{j\omega t}$$

Observe that $e^{j\omega t}$ cancels out on both sides of this equation producing

$$V_m e^{j\phi} \left(\frac{1}{LC} - \omega^2 + \frac{j\omega}{RC} \right) = \frac{j0.02\omega}{C}$$

Hence

$$V_m e^{j\phi} = \frac{j0.02\omega}{C \left(\frac{1}{LC} - \omega^2 + \frac{j\omega}{RC} \right)} = 1.28 + j0.96$$

This was obtained using MATLAB as follows:

```

»w = 2500;
»L = 40e-3;
»C = 1e-6;
»R = 100;
»Vout = j*0.02*w/(1/L - C*w^2 + j*w/R)
Vout = 1.2800e+00 + 9.6000e-01i

```

```

»magVout = abs(Vout)
magVout = 1.6000e+00
»angVout = angle(Vout)*180/pi
angVout = 3.6870e+01

```

Therefore

$$v_{out}(t) = 1.6\cos(2500t + 36.87^\circ) \text{ V}$$

SOLUTION 10.8. (a) From KCL: $3 \angle 15^\circ - 5 \angle 45^\circ - I = 0 \quad I = 3 \angle 15^\circ - 5 \angle 45^\circ$. In MATLAB,

```

»Ibar = 3*exp(j*15*pi/180) - 5*exp(j*45*pi/180)

```

$$I_{bar} = -6.3776e-01 - 2.7591e+00i$$

$$\gg \text{abs}(I_{bar})$$

$$\text{ans} = 2.8318e+00$$

$$\gg \text{angle}(I_{bar}) * 180 / \pi$$

$$\text{ans} = -1.0302e+02$$

Therefore,

$$i(t) = \text{Re}\{I_{bar}\} = 2.83 \cos(\omega t - 103^\circ) \text{ A}$$

(b) From KCL,

$$\gg I_{bar} = (1 + 2*j) - (-2 + j*6)$$

$$I_{bar} =$$

$$3.0000e+00 - 4.0000e+00i$$

$$\gg \text{abs}(I_{bar})$$

$$\text{ans} = 5$$

$$\gg \text{angle}(I_{bar}) * 180 / \pi$$

$$\text{ans} = -5.3130e+01$$

Therefore $i(t) = 5 \cos(50 t - 53^\circ) \text{ A}$.

SOLUTION 10.9. We define a Gaussian surface encompassing the three bottom nodes. Thus, KCL dictates that the sum of 4 currents be zero:

$$\gg I_{bar} = -(-2-j*8) + (3 + j*12) + 10$$

$$I_{bar} =$$

$$1.5000e+01 + 2.0000e+01i$$

$$\gg \text{abs}(I_{bar})$$

$$\text{ans} =$$

$$25$$

$$\gg \text{angle}(I_{bar}) * 180 / \pi$$

$$\text{ans} =$$

$$5.3130e+01$$

Therefore $i(t) = 25 \cos(1000t + 53.13^\circ) \text{ A}$.

SOLUTION 10.10. First represent the time-domain functions as phasors:

$$\mathbf{V}_1 = 2 \angle 0^\circ, \mathbf{V}_2 = 2\sqrt{2} \angle -45^\circ$$

Then, by KVL

$$\gg \mathbf{V}_1 = 2; \mathbf{V}_2 = 2\sqrt{2}\exp(-j\pi/4);$$

$$\gg \mathbf{V}_L = \mathbf{V}_1 - \mathbf{V}_2$$

$$\mathbf{V}_L =$$

$$0 + 2.0000e+00i$$

$$\text{Therefore, } \mathbf{V}_L = 2 \angle 90^\circ \text{ V and } v_L(t) = 2\cos(\omega t + 90^\circ) = -2\sin(\omega t) \text{ V}$$

SOLUTION 10.11. Apply KVL by simply following the loop defined by the independent voltage sources:

$$\mathbf{V}_x = 4j - 2j - 1 - 1 + (1 - j) - (1 + j) = -2$$

SOLUTION 10.12. First note that $\mathbf{I}_{\text{out}} = \frac{\mathbf{V}_R}{R}$. $\mathbf{V}_R = -j10 + (5 - j5) - 10$ $\mathbf{V}_R = -5 - j15 \text{ V}$.

$$\text{Thus, } \mathbf{I}_{\text{out}} = \frac{-5 - j15}{5} = -1 - j3 = 3.16 \angle -108.4^\circ \quad i_{\text{out}}(t) = 3.16\cos(500\pi t - 108.4^\circ) \text{ A.}$$

SOLUTION 10.13. Using a Gaussian surface,

$$\mathbf{I}_y = -(2 + j3) - (1 + j2) + (1 - j5) = -2 - j10 = 10.2 \angle -101.3^\circ \text{ A.}$$

Therefore, $i(t) = 10.2\cos(2000\pi t - 101.3^\circ) \text{ A}$. Now applying KVL,

$$\mathbf{V}_x = (2 + j2) + (2 + j3) - (1 - 4j) = 3 + 9j$$

$$\gg \mathbf{V}_x = 2 + 2*j + 2 + j*3 - 1 + 4*j$$

$$\mathbf{V}_x =$$

$$3.0000e+00 + 9.0000e+00i$$

$$\gg \text{abs}(\mathbf{V}_x)$$

$$\text{ans} =$$

$$9.4868e+00$$

$$\gg \text{angle}(\mathbf{V}_x) * 180 / \pi$$

ans =

7.1565e+01

Thus, $v_x(t) = 9.487\cos(2000\pi t + 71.6^\circ)$ V.

SOLUTION 10.14. (a) At $\omega = 1000\pi$ rad/s,

$$Y_C(j\omega) = j\omega C = j4.7 \times 10^{-3} \quad C = 1.496 \mu\text{F}$$

So, at $\omega = 50\pi$, $Y_C(j\omega) = j\omega C = j2.3499 \times 10^{-4} \text{ S}$ $Z_C(j\omega) = -j4255$.

(b) At $\omega = 1000\pi$ rad/s, $Z_L = j\omega L = j18.85$ $L = 6$ mH. Since impedance is proportional to frequency, multiplying the frequency by 20 means the impedance is multiplied by 20. Thus, at

$\omega = 20 \times (10^3)$ rad/s,

$$Z_L = j18.85 \times 20 = j377 \quad Y_L = -j2.652 \text{ mS}$$

SOLUTION 10.15. The input voltage phasor as $2 \angle 0^\circ$. By inspection:

$$\mathbf{I}_1 = j\omega C \mathbf{V}_C = j10 \times 0.1 \times 2 = j2$$

From the definition of a dependent V-source and an inductor:

$$\mathbf{I}_2 = \frac{5\mathbf{I}_1}{j\omega L} = \frac{j10}{j2} = 5$$

Finally,

$$\mathbf{V}_{\text{out}} = 5 \times 2(\mathbf{I}_1 + \mathbf{I}_2) = 10(5 + j2) = 50 + j20 = 53.85 \angle 21.8^\circ$$

$$v_{\text{out}}(t) = 53.85\cos(10t + 21.5^\circ) \text{ V}$$

SOLUTION 10.16. Using KCL and the definition of a resistor:

$$\mathbf{V}_{10} = 10(6 \angle 0^\circ - 3 \angle 90^\circ) = 10(6 - 3j) = 60 - j30 \text{ V}$$

Thus,

$$Z(j\omega_0) = \frac{60 - j30}{j3} = -10 - j20$$

And, the combination of this $Z(j\omega_0)$ with the $10 \text{ } \Omega$ resistance, at this frequency, is $10 - j5$.

$$\gg Z = -10 - j20; R = 10;$$

$$\gg Z_{\text{eq}} = R * Z / (R + Z)$$

$$Z_{\text{eq}} = 1.0000e+01 - 5.0000e+00i$$

$$\gg C = 1 / (-5 * j * 2000 * \pi)$$

$$C = 3.1831e-05$$

This is equivalent to a $10 \text{ } \Omega$ resistor in series with a $31.83 \text{ } \mu\text{F}$ capacitor.

SOLUTION 10.17.

$$\gg \omega = 2 * \pi * 60;$$

$$\gg V_L = 3 + 12 * \exp(-j * 30 * \pi / 180) + 6 - 12 * \exp(j * 30 * \pi / 180)$$

$$V_L = 9.0000e+00 - 1.2000e+01i$$

$$\gg Z_L = j * \omega / 60$$

$$Z_L = 0 + 6.2832e+00i$$

$$\gg I_L = V_L / Z_L$$

$$I_L = -1.9099e+00 - 1.4324e+00i$$

$$\gg \text{abs}(I_L)$$

$$\text{ans} = 2.3873e+00$$

$$\gg \text{angle}(I_L) * 180 / \pi$$

$$\text{ans} = -1.4313e+02$$

Therefore, $i_L(t) = 2.387 \cos(120 t - 143.1^\circ) \text{ A}$.

Solution 10.18 (a)

First represent the inputs with their phasors: $\mathbf{I}_{s1} = 10 \angle 30^\circ = 8.66 + j5$ and $\mathbf{V}_{s2} = 100 \angle 0^\circ$.

The admittance of the RC combination is: $Y_1 = \frac{1}{R} + j\omega C = 0.1 + j0.1$. Using superposition and noting that a 0-volt V-source is a short circuit and a 0-amp current source is an open circuit,

$$\mathbf{I}_x = Y_1 \mathbf{V}_{s2} - \mathbf{I}_{s1} = 1.3397 + j5 = 5.1764 \angle 75^\circ \text{ A}$$

Therefore,

$$i_x(t) = 5.176 \cos(100t + 75^\circ)$$

(b) Let i_{x1} be the contribution to i_x generated by the current source and i_{x2} the contribution generated by the voltage source. Then $i_{x1}(t) = -10 \cos(50t + 30^\circ) \text{ A}$, and $i_{x2}(t) = -14.142 \cos(100t + 45^\circ) \text{ A}$ since

```

»Vs2 = 100;
»w = 100;
»R = 10; C = 1e-3;
»Y1 = 1/R + j*w*C
Y1 =1.0000e-01 + 1.0000e-01i
»Ix2 = Y1*Vs2
Ix2 =1.0000e+01 + 1.0000e+01i
»abs(Ix2)
ans =1.4142e+01
»angle(Ix2)*180/pi
ans =45

```

Therefore $i_x(t) = -10\cos(50t + 30^\circ) - 14.142\cos(100t + 45^\circ)$ A.

Solution 10.19 First of all, write out the given values: $\omega = 200$ rad/s, $\mathbf{I}_1 = 0.5 \angle 90^\circ = 0.5j$ A, and

$\mathbf{V}_{s2} = 4 \angle 0^\circ$. From KVL $\mathbf{V}_{s1} = 3\mathbf{I}_1 + j\omega L\mathbf{I}_1 + \frac{\mathbf{I}_1}{j\omega C} + \mathbf{V}_{s2}$ which leads to:

```

»w = 200; I1 = 0.5j; Vs2 = 4;
»Vs1 = 3*I1 + j*w*0.04*I1 + I1/(j*w*1e-3) + Vs2
Vs1 =2.5000e+00 + 1.5000e+00i
»abs(Vs1)
ans =
2.9155e+00
»angle(Vs1)*180/pi
ans =
3.0964e+01

```

Therefore $v_{s1}(t) = 2.9155\cos(200t + 30.964^\circ)$ V.

Solution 10.20 The phasor for the input can be written as $\omega = 1000$ rad/s and $\mathbf{V}_{in} = 10 \angle 60^\circ = 5 + j8.66$ V. The currents can be obtained easily by applying Ohm's law for phasors:

$$\mathbf{I}_R = \frac{10 \angle 60^\circ}{500} = 0.02 \angle 60^\circ \text{ A}, \mathbf{I}_L = \frac{10 \angle 60^\circ}{j1000 \times 0.25} = 0.04 \angle -30^\circ \text{ A}, \text{ and}$$

$$\mathbf{I}_C = 10 \angle 60^\circ \times (j1000 \times 2 \times 10^{-6}) = 0.02 \angle 150^\circ \text{ A. Thus}$$

$$\mathbf{I}_{in} = 0.02 \angle 60^\circ + 0.04 \angle -30^\circ + 0.02 \angle 150^\circ = 0.0283 \angle 15^\circ \text{ A}$$

and

$$i_{in}(t) = 0.0283 \cos(1000t + 15^\circ) \text{ A}$$

using the following MATLAB code:

```

»Vin = 10*exp(j*60*pi/180)
Vin =5.0000e+00 + 8.6603e+00i
»R = 500; L = 0.25; C = 2e-6;
»w = 1e3;
»IR = Vin/500
IR =1.0000e-02 + 1.7321e-02i
»IL = Vin/(j*w*L)
IL =3.4641e-02 - 2.0000e-02i
»IC = j*w*C*Vin
IC =-1.7321e-02 + 1.0000e-02i
»Iin = IR + IL + IC
Iin =2.7321e-02 + 7.3205e-03i
»abs(Iin)
ans =2.8284e-02
»angle(Iin)*180/pi
ans =1.5000e+01

```

Solution 10.21 In MATLAB

```

»Iin = -100*j*1e-3; R = 100;
»L = 0.04; C = 2e-6; w = 2500;
»VR = R*Iin
VR =0 - 1.0000e+01i
»VL = j*w*L*Iin
VL =10
»VC = Iin/(j*w*C)
VC =-20
»Vin = VR + VL + VC

```

$V_{in} = -1.0000e+01 - 1.0000e+01i$

»abs(Vin)

ans = 1.4142e+01

»angle(Vin)*180/pi

ans = -135

Therefore, $v_{in}(t) = 14.14\cos(2500t - 135^\circ)$ V.

Solution 10.22 (a) Here, $i_1(t) = 0.6\cos(200t)$ A and $v_{out}(t) = 20\sin(200t) = 20\cos(200t - 90^\circ)$ V.

For $\omega = 200$ rad/s, the phasors are by inspection: $\mathbf{I}_1 = 0.6 \angle 0^\circ$ A, $\mathbf{V}_{out} = 20 \angle -90^\circ$ V.

(b) Write down the resistor, inductor, and capacitor current phasors, given \mathbf{V}_{out} :

$$\mathbf{I}_R = \frac{20 \angle -90^\circ}{1/0.03} = 0.6 \angle -90^\circ = -j0.6$$

$$\mathbf{I}_L = \frac{20 \angle -90^\circ}{j200 \times 0.1} = 1 \angle -180^\circ = -1$$

$$\mathbf{I}_C = 20 \angle -90^\circ \times (j200 \times 0.4 \times 10^{-3}) = 1.6 \angle 0^\circ$$

Now, by KCL

$$\mathbf{I}_2 = \mathbf{I}_R + \mathbf{I}_L + \mathbf{I}_C - \mathbf{I}_1 = -j0.6$$

where we have substituted the above values of branch currents. The time-domain function is:

$$i_2(t) = 0.6\cos(200t - 90^\circ) = 0.6\sin(200t)$$
 A

Solution 10.23 (a) $\omega = 400$ rad/s and $\mathbf{V}_{in} = 20 \angle 0^\circ$ V. We can easily use the voltage divider formula for phasors and substitute values to obtain:

$$\mathbf{V}_{out} = \frac{200}{200 + j\omega L} \mathbf{V}_{in} = \frac{20}{1 + j} = 14.14 \angle -45^\circ$$

in which case $v_{out}(t) = 14.14\cos(400t - 45^\circ)$ V

(b) $\omega = 250$ rad/s and $\mathbf{V}_{in} = 20 \angle -90^\circ = -j20$ V. Again, we can easily use voltage division:

$$\mathbf{V}_{out} = \frac{400}{400 + \frac{1}{j\omega C}} \mathbf{V}_{in} = \frac{20 \angle -90^\circ}{1 - j} = 14.14 \angle -45^\circ$$
 V

Thus, in the time-domain,

$$v_{out}(t) = 14.142\cos(250t - 45^\circ)$$
 V

Solution 10.24 (a) $\omega = 10,000$ rad/s and $\mathbf{V}_{in} = 100 \angle -90^\circ = -j100$ V. Apply the voltage divider formula:

$$\mathbf{V}_{out} = \frac{100}{100 + j\omega L + 1/j\omega C} \mathbf{V}_{in} = \frac{100}{100 + j100 - j0.25} \mathbf{V}_{in} = 80 \angle -126.87^\circ$$

The steady-state response is thus,

$$v_{out}(t) = 80\sin(10,000t - 36.87^\circ) \text{ V}$$

The phasor method provides for a much easier way of obtaining the steady-state response.

(b) Here, $\omega = 2500$ rad/s and $\mathbf{I}_{in} = 0.02 \angle 0^\circ$ A. Now, apply current division:

$$\mathbf{I}_R = \frac{0.01}{0.01 + j\omega C + 1/j\omega L} \mathbf{I}_{in} = \frac{0.01}{0.01 + j0.0025 - j0.01} \mathbf{I}_{in} = 0.016 \angle 36.86^\circ$$

By Ohm's law:

$$\mathbf{V}_{out} = 100\mathbf{I}_R = 1.6 \angle 36.87^\circ \text{ V}$$

Therefore

$$v_{out}(t) = 1.6\cos(2500t + 36.87^\circ) \text{ V}$$

Solution 10.25 (a) It is easier to find the admittance first:

$$Y_{in}(j100) = \frac{1}{j\omega L} + j\omega C = -j0.2 + j12.5 = j12.3$$

$$Z_{in}(j100) = -j0.0813$$

(b) $Y_{in}(j100) = \frac{1}{25j} = \frac{1}{j100 \times 0.05} + j100C$. Hence, in MATLAB,

$$\gg C = (1/(25*j) - 1/(j*w*L))/(j*100)$$

$$C = 1.6000e-03$$

Solution 10.26 (a)

$$Z_{in}(j\omega) = \frac{1}{j\omega C} + \frac{R \times j\omega L}{R + j\omega L} = \frac{-j}{\omega C} + \frac{j\omega RL}{R + j\omega L} = 9.975 - 0.0072^\circ$$

$$\gg R = 10; L = 0.1; C = 1e-3; w = 2e3;$$

$$\gg Z_{in} = -j/(w*C) + j*w*R*L/(R + j*w*L)$$

$$Z_{in} = 9.9751e+00 - 1.2469e-03i$$

»abs(Zin)

ans = 9.9751e+00

»angle(Zin)*180/pi

ans = -7.1620e-03

(b) As the frequency increases, the capacitor becomes a short circuit and the inductor becomes an open circuit. Thus, the impedance approaches R. Analytically,

$$\lim_{\omega} Z_{in}(j\omega) = \lim_{\omega} \frac{1}{j\omega C} + \lim_{\omega} \frac{R}{\frac{R}{j\omega L} + 1} = R$$

(c) $Z_{in}(j\omega) = \frac{-j}{\omega C} + \frac{j\omega RL(R - j\omega L)}{R^2 + \omega^2 L^2} = j \frac{\omega LR^2}{R^2 + \omega^2 L^2} - \frac{1}{\omega C} + \frac{R\omega^2 L^2}{R^2 + \omega^2 L^2}$. It follows that we must satisfy

$$\omega^2 LR^2 C = R^2 + \omega^2 L^2 \quad \text{or equivalently} \quad \omega^2 = \frac{R^2}{LR^2 C - L^2} = \frac{1}{LC \left(1 - \frac{L}{CR^2}\right)}$$

values $1 - \frac{L}{CR^2} = 0$; hence there is no finite value of frequency for which the impedance is real.

SOLUTION 10.27. We note that the input admittance is given by:

$$\begin{aligned} Y_{in}(j\omega) &= \frac{1}{100 + j\omega 0.1} + j\omega \times 10^{-6} = \frac{100 - j\omega 0.1}{10^4 + 0.01\omega^2} + j\omega \times 10^{-6} \\ &= \frac{100}{10^4 + 0.01\omega^2} + j\omega \times 10^{-6} - j \frac{\omega 0.1}{10^4 + 0.01\omega^2} \end{aligned}$$

Thus, must satisfy $10^5 = 10^4 + 0.01\omega^2$ or equivalently, $\omega = \sqrt{10^7 - 10^6} = 3000$ rad/s.

SOLUTION 10.28. (a) As usual we will use MATLAB.

»R1 = 20; R2 = 10;

»L = 0.04; C = 0.6e-3;

»w = 250;

$$\gg Y_{in} = 1/R_1 + 1/(R_2 + j\omega L) + j\omega C$$

$$Y_{in} = 1.0000e-01 + 1.0000e-01i$$

Hence

$$Y_{in}(j250) = 0.1 + j0.1 \text{ S}$$

(b) For this part we observe that

$$Y_{in}(j250) = \frac{1}{R_1} + \frac{1}{R_2 + j\omega L} + j\omega C = 0.1 - 0.05j + j250C$$

For this to be real, the imaginary part must be zero, i.e.,

$$C = \frac{0.05}{250} = \frac{1}{5000} = 0.2 \text{ mF}$$

Solution 10.29 (a) We can derive an expression for the input impedance by noting that it is the series combination of the resistance and the inductor/capacitor pair connected in parallel. Thus,

$$Z_{in}(j\omega) = R + \frac{\frac{1}{j\omega C} \times j\omega L}{\frac{1}{j\omega C} + j\omega L} = R - j \frac{\frac{L}{C}}{\omega L - \frac{1}{\omega C}}$$

Equating the real and imaginary parts of the given impedance, $R = 4$ and

$$\frac{-L}{\omega LC - 1/\omega} = \frac{-L}{2L - 0.25} = 2 \quad L = 0.1 \text{ H}$$

(b) At zero inductance, the above reactance is zero. Also, at $L = 0.125$, the denominator of the above reactance is zero, which means that the reactance is infinite.

Solution 10.30 (a) First derive an expression for the input impedance as a function of frequency:

$$Z_{in}(j\omega) = 5 + j\omega L + \frac{1}{j\omega C} = 5 + j\omega L - \frac{1}{\omega C}$$

We want the imaginary part to be equal to zero. Thus,

$$\omega L - \frac{1}{\omega C} = 0 \quad \omega^2 = \frac{1}{LC} \quad \omega = 2500 \text{ rad/s}$$

where we have substituted the values of L and C.

The magnitude of the impedance is minimum when the imaginary part is zero, and $Z_{in}(j2500) = 5$.

(b) Derive an expression for the admittance:

$$Y_{in}(\omega) = \frac{1}{5} + j\omega C + \frac{1}{j\omega L} = \frac{1}{5} + j\omega C - \frac{1}{\omega L}$$

Again, the imaginary part is equal to zero when $\omega = \frac{1}{\sqrt{LC}}$ or $\omega = 2500$, at which point the admittance is 0.2.

Solution 10.31 The input admittance is $Y_{in}(\omega) = \frac{1}{R} + j\omega C = 0.008 + j0.004$. Equating this to the given admittance at $\omega = 500$ yields $R = 125$, $C = 0.004$ or $C = 8 \mu\text{F}$.

Solution 10.32 Derive an expression for the admittance at $\omega = 1000$:

$$Y_{in}(j\omega) = \frac{1}{j\omega L} + \frac{0.25 \times j\omega C}{0.25 + j\omega C} = -j0.5 + \frac{j0.125}{0.25 + j0.5} = 0.2 - j0.4 \text{ S}$$

Note that this is equivalent to a 0.2 S conductance (i.e. 5 resistance) in parallel with a 2.5 mH inductance (at the given frequency!). Now, the impedance is:

$$Z_{in} = \frac{1}{0.2 - j0.4} = 1 + j2$$

This is equivalent to a resistance of 1 in series with a 2 mH inductance (at the given frequency).

Solution 10.33 The current is zero when the input impedance of the parallel combination of inductor and capacitor is infinite. The latter is given by:

$$Z_{LC}(j\omega) = \frac{\frac{1}{j\omega C} \times j\omega L}{\frac{1}{j\omega C} + j\omega L} = -j \frac{\frac{L}{C}}{\omega L - \frac{1}{\omega C}}$$

The magnitude of this is infinite when $\omega_r L - \frac{1}{\omega C} = 0$ $\omega_r^2 = \frac{1}{LC}$ $\omega_r = 15,811 \text{ rad/s}$. Observe that

$$\mathbf{I}_s = \frac{\mathbf{V}_s}{R + Z_{LC}(j\omega_r)} = 0$$

Hence $i_s(t) = 0$ at $\omega_r = 15,811$ rad/s. At this frequency, the voltage across the LC tank is equal to the input voltage (since there is no drop across the resistor).

Solution 10.34 (a) By inspection:

$$Z_{in} = \frac{2 \times j\omega 0.4}{2 + j\omega 0.4} = \frac{j\omega 0.8}{2 + j\omega 0.4}$$

$$Y_{in} = \frac{1}{R} + \frac{1}{j\omega L} = 0.5 - j \frac{2.5}{\omega}$$

(b) Use the current divider formula, and substitute the given frequency, to obtain:

$$\mathbf{I}_L = \frac{R}{R + j\omega L} \sqrt{2} = \frac{2\sqrt{2}}{2 + j2} = 1 \quad -45^\circ$$

and $i_L(t) = \cos(5t - 45^\circ)$ A.

Solution 10.35 (a) Using voltage division, $\mathbf{V}_{out} = \frac{R}{R - j/\omega C} \mathbf{V}_{in} = \frac{j\omega RC}{1 + j\omega RC} \mathbf{V}_{in}$ which

$$\mathbf{V}_{out} = 90^\circ - \phi_{in} - \tan^{-1}(\omega RC) \quad \text{and} \quad |\mathbf{V}_{out}| = \frac{\omega RC |\mathbf{V}_{in}|}{\sqrt{1 + \omega^2 R^2 C^2}}$$

(b) For this part, we need to make sure that $\tan^{-1}(\omega RC) = 45^\circ$ $\omega RC = 1$ $\omega = 1/RC$.

(c) At this frequency,

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\frac{1}{RC} RC}{\sqrt{1 + \frac{1}{R^2 C^2} R^2 C^2}} = \frac{1}{\sqrt{2}}$$

Solution 10.36 Here, $\omega = 1/RC$ and $\frac{\mathbf{V}_C}{\mathbf{V}_{in}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j}$. Therefore

$$\mathbf{V}_C = \frac{1}{1 + j} \mathbf{V}_{in} = 0.707 V_m \quad -45^\circ$$

The time-domain function is

$$v_C(t) = 0.707 V_m \cos \frac{1}{RC} t - 45^\circ \quad \text{V}$$

Solution 10.37 (a) The magnitude of the capacitor voltage is $10/14.14 = 0.707$ times the magnitude of the input signal. We just showed in the above problem that

$$\frac{V_C}{V_{in}} = \frac{1}{1 + j10RC} \quad \left| \frac{V_C}{V_{in}} \right| = \frac{1}{\sqrt{1 + 100R^2C^2}}$$

And we also showed that the ratio is 0.707 when the frequency is $1/RC$. So, $C = 1/(10R) = 0.01$ F.

(b) Again, from the results of the previous problem, the angle is -45 degrees.

Solution 10.38 $\omega = 1000$ rad/s and $I_{in} = 2 \angle 45^\circ$ A. The equivalent admittance is

$$Y_{eq}(j\omega) = \frac{1}{R} + j\omega C - \frac{1}{\omega L} = 0.25 + j(0.25 - 0.25) = 0.25 \text{ S}$$

In MATLAB

```
»Yeq = 0.25;
```

```
»Iin = 2*exp(j*pi/4)
```

```
Iin =
```

```
1.4142e+00 + 1.4142e+00i
```

```
»Vout = Iin/Yeq
```

```
Vout =
```

```
5.6569e+00 + 5.6569e+00i
```

```
»abs(Vout)
```

```
ans = 8
```

```
»angle(Vout)*180/pi
```

```
ans = 4.5000e+01
```

```
»% Using Current Division
```

```
»IL = (1/(j*1000*4e-3)/Yeq)*Iin
```

```
IL =
```

```
1.4142e+00 - 1.4142e+00i
```

```
»abs(IL)
```

```
ans = 2
```

```
»angle(IL)*180/pi
```

```
ans = -45
```

Therefore, $v_{out}(t) = 8\cos(1000t + 45^\circ)$ V and $i_L(t) = 2\cos(1000t - 45^\circ)$ A.

(b) If $\omega = 618$ rad/s, then

$$Y_{eq}(\omega) = \frac{1}{4} - j0.405 + j0.1545 = 0.25 - j0.25 = 0.3536 \quad -45^\circ$$

and

$$\gg V_{out} = I_{in}/Y_{eq}$$

Vout =

$$-3.4779e-04 + 5.6565e+00i$$

»abs(Vout)

ans =

$$5.6565e+00$$

»angle(Vout)*180/pi

ans =

$$9.0004e+01$$

»IL = Iin*(1/(j*618*4e-3))/Yeq

IL =

$$2.2882e+00 + 1.4069e-04i$$

»abs(IL)

ans =

$$2.2882e+00$$

»angle(IL)*180/pi

ans =

$$3.5228e-03$$

Therefore, $v_{out}(t) = 5.657\cos(1000t + 90^\circ) = -5.657\sin(1000t)$ V and $i_L(t) = 2.288\cos(1000t)$ A.

Solution 10.39 Write the input phasor: $\omega = 1000$ rad/s and $I_{in} = 0.01\sqrt{2} \quad 60^\circ$ A.

»w =1000;

»Iin = 0.01*sqrt(2)*exp(j*60*pi/180)

Iin =

$$7.0711e-03 + 1.2247e-02i$$

»Yeq = 1/500 + 1/(j*w*0.25) + j*w*2e-6

Yeq =

$$2.0000e-03 - 2.0000e-03i$$

»Vin = Iin/Yeq

```

Vin =
-1.2941e+00 + 4.8296e+00i
»abs(Vin)
ans =
    5
»angle(Vin)*180/pi
ans =
    1.0500e+02
»IR = Iin*(1/500)/Yeq
IR =
-2.5882e-03 + 9.6593e-03i
»abs(IR)
ans =
    1.0000e-02
»angle(IR)*180/pi
ans =
    1.0500e+02
»IL = Iin*(1/(j*w*0.25))/Yeq
IL =
    1.9319e-02 + 5.1764e-03i
»abs(IL)
ans =
    2.0000e-02
»angle(IL)*180/pi
ans =
    1.5000e+01
»IC = Iin*j*w*2e-6/Yeq
IC =
-9.6593e-03 - 2.5882e-03i
»abs(IC)
ans =
    1.0000e-02
»angle(IC)*180/pi
ans =
    -1.6500e+02

```

Therefore, $v_{in}(t) = 5\cos(1000t - 105^\circ)$ V, $i_C(t) = 0.01\cos(1000t - 165^\circ)$ A, $i_L(t) = 0.02\cos(1000t + 15^\circ)$ A, and $i_R(t) = 0.01\cos(1000t + 105^\circ)$ A.

SOLUTION 10.40. $\omega = 4$. Using voltage division

$$\mathbf{V}_1 = \frac{R}{R + \frac{1}{j\omega C} + j\omega L} \mathbf{V}_{in} = \frac{2}{2 - 4j + 2j} (-8j) = 5.657 \angle -45^\circ$$

Converting back to time:

$$v_{out}(t) = 5.657\cos(4t - 45^\circ) \text{ V}$$

SOLUTION 10.41. $\omega = 25$ rad/s, $\mathbf{V}_s = 10 \angle 0^\circ$ V. By voltage division,

$$\mathbf{V}_C = \frac{-j/0.02 \times 25}{10 + j0.08 \times 25 - j/0.02 \times 25} 10 \angle 0^\circ = -2j = 2 \angle -90^\circ$$

Thus, $v_C(t) = 2\cos(25t - 90^\circ)$ V.

SOLUTION 10.42. $\frac{|\mathbf{V}_{out}|}{|\mathbf{V}_{in}|} = \left| \frac{1}{3 + j8 + \frac{1}{j4C}} \right| = 0.2 \quad 25 = \left| 3 + j8 - \frac{1}{4C} \right|^2$

Thus $8 - \frac{1}{4C} = 25 - 9 \quad C = \frac{1}{16} = 0.0625$ F.

SOLUTION 10.43. Here, $\omega = 3.33 \times 10^3$ rad/s and $\mathbf{V}_{in} = 50 \angle 0^\circ$ V. Using phasors,

$$\mathbf{V}_R = \frac{400}{400 - \frac{j}{3.33 \times 10^3 \times 10^{-6}}} \times 50 = 40 \angle 36.897^\circ \text{ V}$$

and

$$\mathbf{V}_{out} = \frac{100\mathbf{V}_R / j\omega C}{100 + \frac{1}{j\omega C}} = \frac{100\mathbf{V}_R}{j100\omega C + 1} = 3985 \angle 32.1^\circ \text{ V}$$

Hence, $v_{out}(t) = 3985\cos(3.33 \times 10^3 t + 32.1^\circ)$ V.

SOLUTION 10.44. Here, $\omega = 10^4$ rad/s, $\mathbf{I}_{in} = 0.01 \angle 0^\circ$ A.

$$Z_1 = \frac{100 \times j\omega 0.1}{100 + j\omega 0.1} = 1 + j1000 \quad \mathbf{V}_L = Z_L \mathbf{I}_{in} = 0.01 \times Z_L = 0.01 + j10$$

Now, in MATLAB

```
»w=1e4; R = 100;L = 0.1; C = 0.1e-6;
```

```
»Z1 = R*j*w*L/(R+j*w*L)
```

```
Z1 = 9.9010e+01 + 9.9010e+00i
```

```
»Iin = 0.01;
```

```
»VL = Z1*Iin
```

```
VL =9.9010e-01 + 9.9010e-02i
```

```
»Z2 = 1/(1/R + j*w*C)
```

```
Z2 = 9.9010e+01 - 9.9010e+00i
```

```
»VC = Z2*VL
```

```
VC = 9.9010e+01 + 1.7764e-15i
```

```
»abs(VC)
```

```
ans = 9.9010e+01
```

```
»angle(VC)*180/pi
```

```
ans = 1.0280e-15
```

Thus, $v_C(t) = 99\cos(10000t)$ V.

SOLUTION 10.45. Here $\omega = 40$ rad/s and $\mathbf{V}_{in} = 120 \angle 0^\circ$. This problem is best done in MATLAB using parallel impedance computation, voltage division, and Ohm's law for phasors:

```
»R1 = 500; R2 = 80;
```

```
»C = 0.1e-3; L = 2;
```

```
»w = 40; Vin = 120;
```

```
»Z1 = R1/(j*w*C)/(R1 + 1/(j*w*C))
```

```
Z1 = 1.0000e+02 - 2.0000e+02i
```

```
»Z2 = R2*j*w*L/(R2 + j*w*L)
```

```
Z2 = 4.0000e+01 + 4.0000e+01i
```

```
» Use voltage division
```

```
»VC = Z1*Vin/(Z1+Z2)
```

```
VC = 1.2212e+02 - 3.1858e+01i
```

```
»abs(VC)
```

```
ans = 1.2621e+02
```

```
»angle(VC)*180/pi
```

```
ans = -1.4621e+01
```

```

» Use voltage division and Ohm's law for inductors
»VL = Z2*Vin/(Z1+Z2)
VL = -2.1239e+00 + 3.1858e+01i
»IL = VL/(j*w*L)
IL = 3.9823e-01 + 2.6549e-02i
»abs(IL)
ans = 3.9911e-01
»angle(IL)*180/pi
ans = 3.8141e+00

```

Therefore, $v_C(t) = 126.21\cos(40t - 14.621^\circ)$ V and $i_L(t) = 0.399\cos(40t + 3.814)$ A.

SOLUTION 10.46. Here $\omega = 40$ rad/s and $\mathbf{I}_{in} = 0.120 \angle 0^\circ$ A. This problem is best solved using MATLAB.

```

»w = 40; Iin = 0.12; R = 5;
»C = 0.004; L = 0.1;
»Y1 = 1/R + j*w*C
Y1 = 2.0000e-01 + 1.6000e-01i

```

```

»Y2 = 1/R + 1/(j*w*L)
Y2 = 2.0000e-01 - 2.5000e-01i

```

```

»% USING CURRENT DIVISION
»IL = Iin*Y2/(Y1 + Y2)
IL = 7.3171e-02 - 5.8537e-02i
»abs(IL)
ans = 9.3704e-02
»angle(IL)*180/pi
ans = -3.8660e+01

```

```

»% AGAIN USING CURRENT DIVISION
»IC = Iin*Y1/(Y1 + Y2)
IC = 4.6829e-02 + 5.8537e-02i

```

```

»% USING OHM'S LAW FOR CAPACITORS
»VC = IC/(j*w*C)
VC = 3.6585e-01 - 2.9268e-01i
»abs(VC)
ans = 4.6852e-01
»angle(VC)*180/pi
ans = -3.8660e+01


```

SOLUTION 10.47 Here, $\omega = 25$ rad/s and $\mathbf{I}_S = 2 \angle 0^\circ$ A. Now perform a source transformation. The combination of current source in parallel with resistor is changed into a voltage source in series with the same resistor. The voltage source value is: $\mathbf{V}_S = 1 \times \mathbf{I}_S = 2 \angle 0^\circ$ V. Apply Ohm's law to obtain:

$$\mathbf{I}_1 = \frac{2 \angle 0^\circ}{2 + \frac{1}{j25 \times 0.02}} = 0.5 + j0.5 = 0.707 \angle 45^\circ$$

Hence, $i_1(t) = 0.707\cos(25t + 45^\circ)$ A.

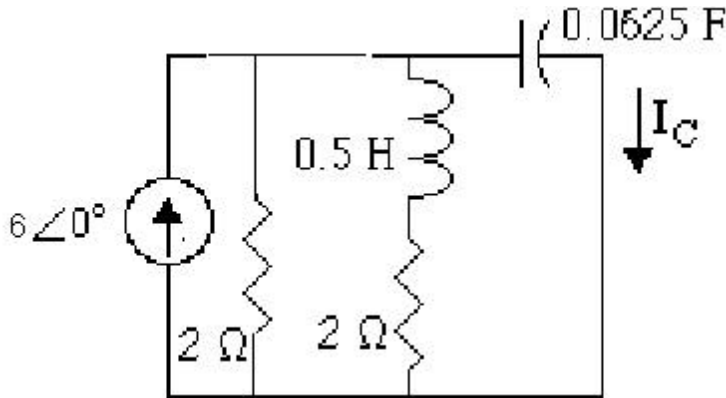SOLUTION 10.48 Apply a source transformation to obtain:



The impedance of the inductor branch is $Z_L(j4) = 2 + j4 \times 0.5 = 2 + j2$ and


$Y_L(j4) = \frac{1}{Z_L(j4)} = 0.25 - j0.25$ S. Now, the total admittance seen by the source:

$$Y_{eq}(j4) = \frac{1}{2} + j0.25 + Y_L(j4) = 0.75 \text{ S}$$

Thus, by inspection, $\mathbf{V}_C = \frac{6 \angle 0^\circ}{0.75} = 8 \angle 0^\circ$ V and $\mathbf{I}_C = 0.25 \angle 90^\circ \times 8 \angle 0^\circ = 2 \angle 90^\circ$ A. Therefore

$i_C(t) = 2\cos(4t + 90^\circ) = -2\sin(4t)$ A.

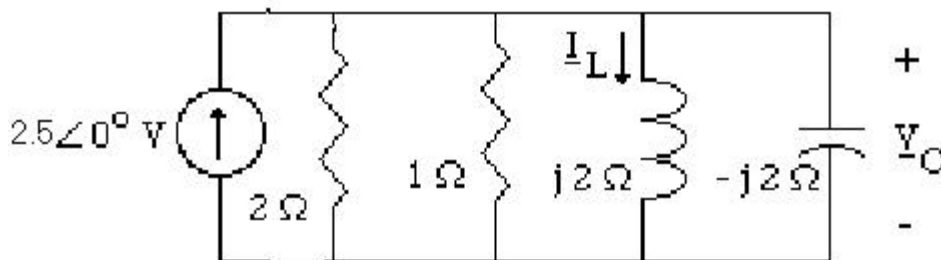SOLUTION 10.49. Apply a source transformation to obtain:



Then, by inspection, $Y_{eq}(j500) = \frac{1}{2} + \frac{1}{1} + \frac{1}{j2} - \frac{1}{j2} = 1.5$ S. Thus,

$$\mathbf{V}_C = \frac{2.5 \angle 0^\circ}{1.5} = 1.667 \angle 0^\circ \text{ V} = \mathbf{V}_L \quad \mathbf{I}_L = 1.667 / j2 = 0.833 \angle -90^\circ \text{ A}$$

In the time-domain:

$$v_C(t) = 1.667 \cos(500t) \text{ V and } i_L(t) = 0.833 \cos(500t - 90^\circ) = 0.833 \sin(500t) \text{ A.}$$