

Chapter 17/Problem 1

①

(a) Without L present and with $\hat{V}_1 = \hat{V}_{in}$

Fig
P17.1

$$Z(j\omega) = \frac{1}{j\omega C + \frac{1}{R_L}} = \frac{R_L}{1 + j\omega R_L C}$$

and

$$\hat{V}_{out} = \frac{-g_m R_L \hat{V}_{in}}{1 + j\omega R_L C}$$

with $\omega = 10^7 \text{ rad/s}$, $C = 40 \times 10^{-12} \text{ F}$, $g_m = 0.0045$ and $R_L = 40,000 \Omega$

$$\hat{V}_{out} = \frac{-0.004(40,000)\hat{V}_{in}}{1 + j(2\pi \times 10^7)(40,000)(40 \times 10^{-12})} = \frac{-160\hat{V}_{in}}{1 + j3.2\pi} = \frac{-160\angle 0^\circ \hat{V}_{in}}{100.54\angle 89.43^\circ}$$

$$\hat{V}_{out} = -1.592\angle 89.43^\circ \hat{V}_{in}$$

Set the reference for \hat{V}_{in} at 0°

$$\hat{V}_{out} = (-1.592\angle 89.53^\circ)(0.2\angle 0^\circ) = 0.318\angle 89.43^\circ$$

The magnitude of V_{out} is

$$|V_{out}| = 0.318$$

(b) Now with L present

$$Y(j\omega) = \frac{1}{j\omega L + j\omega C + \frac{1}{R_L}} = \frac{R_L - \omega^2 R_L L C + j\omega L}{j\omega R_L L}$$

With element values inserted

$$Y(j\omega) = \frac{40,000 - 1.6 \times 10^{-6} L \omega^2 + j\omega L}{j40,000 \omega L}$$

and

$$Z(j\omega) = \frac{j40,000 \omega L}{40,000 - 1.6 \times 10^{-6} L \omega^2 + j\omega L}$$

With

$$V_{out}(j\omega) = -Z(j\omega)g_m V_{in}(j\omega)$$

$V_{out}(j\omega)$ is maximized by making the denominator as small as possible

17/1 Cont'd

(2)

for $Z(j\omega)$

$$Z(j\omega) = \frac{j40,000\omega L}{40,000 - 1.6 \times 10^{-6} L \omega^2 + j\omega L}$$

Set

$$1.6 \times 10^{-6} L \omega^2 = 40,000$$

$$L = \frac{40,000}{1.6 \times 10^{-6} (2\pi \times 10^7)^2} = 6.332 \times 10^{-6} \text{ H} \leftarrow$$

Then with $L = 6.332 \times 10^{-6} \text{ H}$

$$\hat{V}_{out} = -0.004 Z(j\omega) \hat{V}_{in}$$

$$= -0.004 \left(\frac{j40,000}{j397.8} \right) \hat{V}_{in}$$

$$= -0.004 (100\sqrt{3}) \hat{V}_{in}$$

$$= -0.4021$$

Again with $\hat{V}_{in} = 0.2 \angle 0^\circ \text{ V}$

$$\hat{V}_{out} = (-0.4021)(0.2 \angle 0^\circ) \text{ V}$$

with

$$|\hat{V}_{out}| = -0.1206 \text{ V}$$

Compare this with part (a)

Chapter 17/Problem 2

By a voltage divider with L present

Pg
P17.2

$$Z_p(j\omega) = \frac{\frac{j\omega L}{j\omega C}}{j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{-j\frac{L}{C}}{\omega L - \frac{1}{\omega C}}$$

Then $\hat{V}_1 = \frac{Z_p(j\omega) \hat{V}_{in}}{R_s + Z_p(j\omega)} = \frac{\frac{-j\frac{L}{C} \hat{V}_{in}}{\omega L - \frac{1}{\omega C}}}{R_s + \frac{-j\frac{L}{C}}{\omega L - \frac{1}{\omega C}}} = \frac{\frac{-j\frac{L}{C} \hat{V}_{in}}{\omega L - \frac{1}{\omega C}}}{\frac{R_s(\omega L - \frac{1}{\omega C}) - j\frac{L}{C}}{\omega L - \frac{1}{\omega C}}}$

$$V_1 = \frac{\frac{L}{C} \hat{V}_{in}}{\frac{L}{C} - jR_s(\omega L - \frac{1}{\omega C})}$$

\hat{V}_{out} will be maximized when \hat{V}_1 is maximized
and this is accomplished by setting

$$\omega L - \frac{1}{\omega C} = 0$$

or setting

$$\omega_r = \omega_0 = \frac{1}{\sqrt{LC}}$$

with $\omega_r = 2\pi \times 10^7$ rad/s and $C = 20 \times 10^{-12}$ F

$$L = \frac{1}{\omega_r^2 C} = \frac{1}{(2\pi \times 10^7)^2 (20 \times 10^{-12})}$$

$$L = 1.267 \times 10^{-5} \text{ H}$$

Then

$$\hat{V}_{out} = -g_m R_s \hat{V}_{in} = (-0.004)(20,000) \hat{V}_{in}$$

$$= -80 \hat{V}_{in}$$

No value of V_{in} was given in the problem statement

Chapter 17 / Problem 3

(a) In fig 17.3a

$$Y_p(j\omega) = \frac{1}{R_2} + j\omega C + \frac{1}{j\omega L}$$

and

$$\begin{aligned} Z(j\omega) &= R_2 + Z_p(j\omega) \\ &= R_2 + \frac{1}{\frac{1}{R_2} + j(\omega C - \frac{1}{\omega L})} \end{aligned}$$

To make the impedance entirely real which is a condition of resonance

$$\omega C - \frac{1}{\omega L} = 0$$

$$\omega_r^2 = \frac{1}{LC}$$

$$\omega_r = \omega_0 = \frac{1}{\sqrt{LC}}$$

And then

$$Z(j\omega) = R_1 + R_2$$

(b) In fig 17.3b

$$Z_p(j\omega) = R_2 + j\omega L + \frac{1}{j\omega C}$$

$$Y_p = \frac{1}{R_2 + j(\omega L - \frac{1}{\omega C})}$$

and

$$Y_{in}(j\omega) = \frac{1}{R_1} + \frac{1}{R_2 + j(\omega L - \frac{1}{\omega C})}$$

Again, to make $Y(j\omega)$ entirely real

$$\omega_r = \omega_0 = \frac{1}{\sqrt{LC}}$$

and

$$Y'_{in}(j\omega) = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{And } Z_{in}(j\omega) = \frac{R_1 R_2}{R_1 + R_2}$$

Fig
P17.3a

Fig
P17.3b

Chapter 17 / Problem 4

$$\Re Z(j\omega_r) = \Re [Z(j\omega_r)] + \Im [Z(j\omega_r)]$$

The value of ω_r is found by setting $\Im [Z(j\omega_r)] = 0$ so that the impedance at resonance is entirely real.

$$\begin{aligned} Z_{in}(j\omega) &= \frac{a + j\omega}{B - \omega^2 + j4\omega} = \frac{(a + j\omega)(B - \omega^2 + j4\omega)}{(B - \omega^2 + j4\omega)(B - \omega^2 - j4\omega)} \\ &= \frac{(B - \omega^2)a - 4\omega^2 + j(8\omega - \omega^3 + 4a\omega)}{(B - \omega^2)^2 - 16\omega^2} \end{aligned}$$

Thus

$$\Re [Z_{in}(j\omega)] = \frac{(B - \omega^2)a - 4\omega^2}{(B - \omega^2)^2 - 16\omega^2}$$

and

$$\Im [Z_{in}(j\omega)] = \frac{8\omega - \omega^3 + 4a\omega}{(B - \omega^2)^2 - 16\omega^2}$$

(a) To find ω_r , set $\Im [Z_{in}(j\omega)] = 0$, with $a = 1$

$$8\omega - \omega^3 + 4a\omega = 0$$

$$\omega^2 = 4 - B = 4$$

$$\omega = \omega_r = 2 \text{ rad/s}$$

Then $Z_{in}(j\omega_r)$ is found from the real part, with $a = 1$

$$Z_{in}(j\omega_r) = \frac{(B - 4)(1) - 4(4)}{(B - 4)^2 - 16(4)} = \frac{4 - 16}{16 - 64} = \frac{-12}{-48} = \frac{1}{4} \Omega$$

(b) Look at part (a) where

$$8\omega_r - \omega_r^3 + 4a\omega_r = 0$$

and observe that to make ω_r real and positive

$$\omega_r^2 = 8 - 4a$$

$$8 - 4a = 0$$

$$a = 2$$

Hence

$$0 \leq a \leq 2$$

Chapter 17/Problem 5

Here

$$Y_W(s) = Cs + 1 + \frac{2s+1}{s^2+1}$$

$$= \frac{Cs^3 + Cs + s^2 + 2s + 2}{s^2+1}$$

Then

$$Y(j\omega) = \frac{2-\omega^2 + j(C\omega - C\omega^3 + 2\omega)}{1-\omega^2}$$

$$\operatorname{Re}[Y(j\omega)] = \frac{2-\omega^2}{1-\omega^2}$$

$$\operatorname{Im}[Y(j\omega)] = \frac{C(\omega - \omega^3) + 2\omega}{1-\omega^2}$$

Q8 $\omega_r = 3 \text{ rad/s}$, set $\operatorname{Im}[Y(j3)] = 0$

$$\frac{3C(1-9) + 2(3)}{1-9} = 0$$

$$-24C = -6$$

$$C = \frac{1}{4} \text{ F} \leftarrow$$

and obtain Y_W , use $\operatorname{Re}[Y_W(j\omega)]$

$$Y_W(j3) = \left. \frac{2-\omega^2}{1-\omega^2} \right|_{\omega=3 \text{ rad/s}} = \frac{2-9}{1-9} = \frac{-7}{-8} = \frac{7}{8} \text{ V}$$

Chapter 17/ Problem 6

Fig
P17.6

Equation (17.4) gives the resonant frequency

$$\omega_r = \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2}$$

$$LC = 2(0.02) = 0.04$$

$$\frac{R}{L} = \frac{2.8}{2} = 1.4$$

$$\omega_r = \sqrt{25 - (1.4)^2} = \sqrt{25 - 1.96} = \sqrt{23.04} = 4.8 \text{ rad/s}$$

Then from eq (17.5)

$$Z(j\omega_r) = \frac{L}{RC} = \frac{2}{2.8(0.02)} = 35.71 \Omega$$

Chapter 17 / Problem 7

①

Consider the parallel portion of the network with $C = 10 \mu\text{F}$ and $L = 0.1 \text{ H}$. Equations 17.4 and 17.5 indicate that

Fig
P17.7

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R_L^2}{L^2}}$$

and
$$Z_p(j\omega_r) = \frac{L}{R_L C}$$

with $LC = 0.1(10 \times 10^{-6}) = 1 \times 10^{-6}$

and $\frac{1}{LC} = 10^6$

$$\omega_r = \sqrt{10^6 - 100 R_L^2}$$

$$Z_p(j\omega_r) = \frac{10,000}{R_L} \Omega$$

At resonance, the total impedance (resistance) will be

$$Z_{in}(j\omega_r) = 125 \Omega + \frac{10,000}{R_L} \Omega$$


(a) when $R_L = 80 \Omega$

$$\omega_r = \sqrt{10^6 - 100(80)^2} = \sqrt{360,000} = 600 \text{ rad/s}$$

and

$$Z_{in}(j\omega_r) = 125 + \frac{10,000}{80} = 125 + 125 = 250 \Omega$$

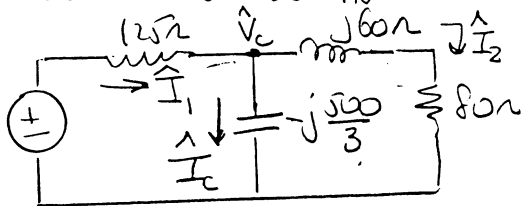The circuit with $\hat{V}_{in} = 250 \angle 0^\circ$ and at $\omega_r = 600 \text{ rad/s}$ is shown



$$\hat{I}_1 = \frac{250 \angle 0^\circ}{250} = 1 \angle 0^\circ \text{ A}$$

$$\hat{V}_C = 250 \angle 0^\circ - 125(1 \angle 0^\circ) = 125 \angle 0^\circ \text{ V}$$

$$\hat{I}_C = \frac{\hat{V}_C}{-j\frac{500}{3}} = \frac{125 \angle 0^\circ}{\frac{500}{3} \angle 90^\circ} = \frac{3}{4} \angle 90^\circ \text{ A}$$

and
$$\hat{I}_2 = \hat{I}_1 - \hat{I}_C = 1 \angle 0^\circ - \frac{3}{4} \angle 90^\circ = 1 + j0 - (0 + j\frac{3}{4}) = 1 - j\frac{3}{4} \text{ A}$$

or
$$\hat{I}_2 = 1.25 \angle -36.87^\circ \text{ A}$$

17/7 Cnctd
The power (in watts) delivered to $R_L = 60\Omega$ will be (2)

$$P_{60} = (1)^2(60) = 60W$$


(b) When $R_L = 60\Omega$

$$\omega_r = \sqrt{10^6 - 100(60)^2} = \sqrt{10^6 - 360,000} = \sqrt{640,000} = 800 \text{ rad/s}$$

and

$$Z_{in}(j\omega_r) = 125 + \frac{10,000}{60} = 291.67\Omega$$

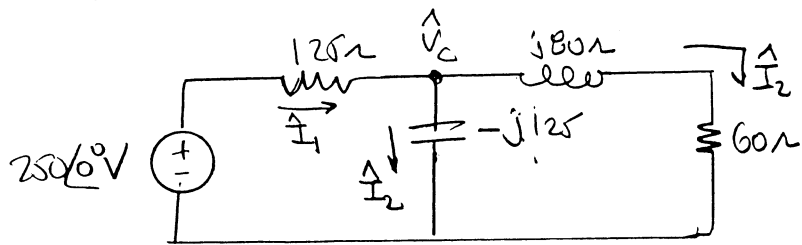The circuit at $\omega_r = 800 \text{ rad/s}$ is shown



$$\hat{I}_1 = \frac{250\angle 0^\circ}{291.67^\circ} = 0.857\angle 0^\circ$$

$$\hat{V}_c = 250\angle 0^\circ - (125\angle 0^\circ)(0.857\angle 0^\circ) = 142.86\angle 0^\circ$$

$$\hat{I}_c = \frac{\hat{V}_c}{-j125} = \frac{142.86\angle 0^\circ}{125\angle -90^\circ} = \frac{8}{7}\angle 90^\circ \text{ A}$$

$$\hat{I}_2 = \hat{I}_1 - \hat{I}_c = \frac{6}{7}\angle 0^\circ - \frac{8}{7}\angle 90^\circ = \frac{6}{7} - j\frac{8}{7}$$

or

$$\hat{I}_2 = \frac{10}{7}\angle -53.13^\circ \text{ A}$$

The power (in watt) delivered to $R_L = 60\Omega$ will be

$$P_{60} = \left(\frac{6}{7}\right)^2(60) = \frac{2160}{49} \text{ W}$$

Chapter 17/Problem 9

①

Fig
P17.9

Here

$$z(j\omega) = j\omega L + \frac{R}{R + \frac{1}{j\omega C}}$$

$$= j\omega L + \frac{R}{1 + j\omega RC}$$

$$= \frac{j\omega L - RLC\omega^2 + R}{1 + j\omega RC} \left[\frac{1 - j\omega RC}{1 - j\omega RC} \right]$$

$$= \frac{j\omega L - RLC\omega^2 + R + jR^2LC\omega^2 + j\omega^3 R^2 LC^2 - jR^2 C\omega}{1 + (\omega RC)^2}$$

$$\operatorname{Re}[z(j\omega)] = \frac{R}{1 + (\omega RC)^2}$$

$$\operatorname{Im}[z(j\omega)] = \frac{\omega L + \omega^3 R^2 LC^2 - \omega R^2 C}{1 + (\omega RC)^2}$$

From the imaginary part

$$\operatorname{Im}[z(j\omega_r)] = 0 = \omega_r^2 R^2 LC^2 - (R^2 C - L) = 0$$

$$\omega_r^2 = \frac{R^2 C - L}{R^2 LC^2} = \frac{1}{LC} - \frac{1}{R^2 C}$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{1}{R^2 C}} \quad \leftarrow$$

with

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_r = \sqrt{\frac{1}{LC} \left(1 - \frac{L}{R^2 C} \right)}$$

$$= \omega_0 \sqrt{1 - \frac{L}{R^2 C}}$$

17/9 Cont'd

(2)

From

$$\operatorname{Im}[z(j\omega_r)] = \frac{R}{1 + \omega_r^2(R^2C^2)}$$

$$= \frac{R}{1 + R^2C^2\left(\frac{1}{LC} - \frac{1}{R^2C^2}\right)}$$

$$= \frac{R}{1 + \frac{R^2C}{L} - 1} = \frac{RL}{R^2C} = \frac{L}{RC} \leftarrow$$



Chapter 17/Problem 11

Solution Available on Disc

Chapter 17 / Problem 12

①

For input across terminals a-b

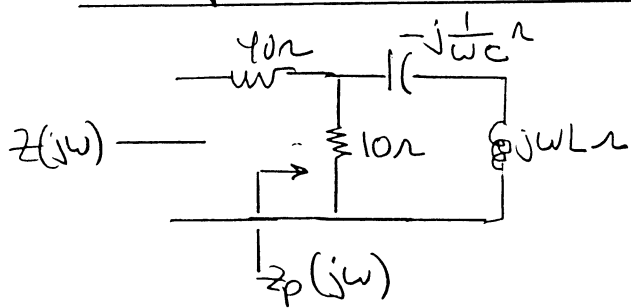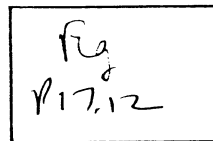

$$Y_p(j\omega) = \frac{1}{10} + \frac{1}{j\omega L - j\frac{1}{\omega C}}$$

$$= \frac{j10(\omega L - \frac{1}{\omega C}) + 10}{j10(\omega L - \frac{1}{\omega C})}$$

$$Z_p(j\omega) = \frac{j10(\omega L - \frac{1}{\omega C})}{10 + j10(\omega L - \frac{1}{\omega C})}$$

and

$$Z(j\omega) = 40\Omega + \frac{j10(\omega L - \frac{1}{\omega C})}{10 + j10(\omega L - \frac{1}{\omega C})}$$

To make $Z(j\omega)$ entirely resistive which is a condition of resonance, set


$$\omega L - \frac{1}{\omega C} = 0$$

$$\omega_r^2 = \frac{1}{LC}$$

and

$$\omega_r = \omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{0.8(0.002)}} = \sqrt{625} = 25 \text{ rad/s}$$

For input across terminals b-c

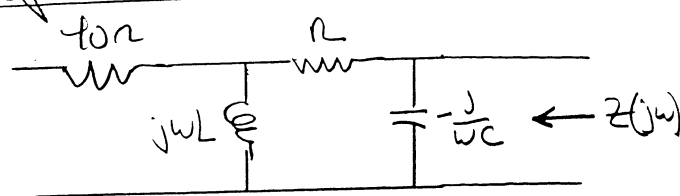

Observe that the 40 ohm resistor is not connected

$$Z(j\omega) = \frac{(R + j\omega L)(-j\frac{1}{\omega C})}{R + j(\omega L - \frac{1}{\omega C})} = \frac{\frac{L}{C} - j\frac{R}{\omega C}}{R + j(\omega L - \frac{1}{\omega C})}$$

$$\text{Let } A = \omega L - \frac{1}{\omega C}$$

17/12 Cont'd

(2)

$$z(j\omega) = \frac{\frac{L}{C} - j\frac{R}{\omega C}}{R + jA} \cdot \frac{R - jA}{R - jA} = \frac{R\frac{L}{C} - j\frac{L}{C}A - j\frac{R^2}{\omega C} + \frac{RA}{\omega C}}{R^2 + A^2}$$

$$\text{Im}[z(j\omega)] = -\frac{\left(\frac{L}{C}A + \frac{R^2}{\omega C}\right)}{R^2 + A^2}$$

For resonance, set $\text{Im}[z(j\omega)] = 0$

$$\frac{L}{C}A + \frac{R^2}{\omega C} = 0$$

$$\frac{L}{C}\left(\omega L - \frac{1}{\omega C}\right) = -\frac{R^2}{\omega C}$$

$$\frac{L}{C}\left(\frac{\omega^2 LC - 1}{\omega C}\right) = -\frac{R^2}{\omega C}$$


$$\frac{L^2}{C}\omega^2 = \frac{L}{C^2} - \frac{R^2}{C}$$

$$\omega^2 = \frac{C}{L^2} \left[\frac{L}{C^2} - \frac{R^2}{C} \right] = \frac{1}{LC} - \left(\frac{R}{L}\right)^2$$

$$\omega_r = \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2} = \sqrt{625 - 156.25}$$

$$\omega_r = \sqrt{468.75} = 21.65 \text{ rad/s}$$

For input across terminals a-c

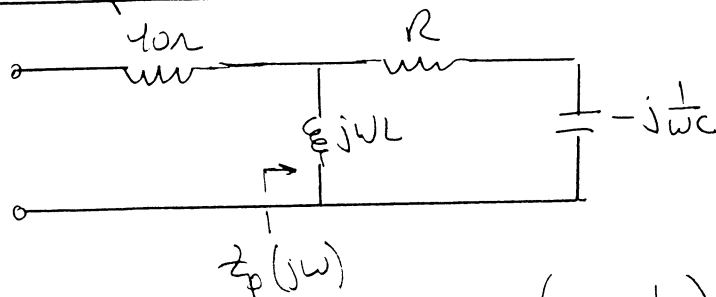

$$z_p(j\omega) = \frac{j\omega L \left(R - \frac{1}{j\omega C}\right)}{R + j\left(\omega L - \frac{1}{\omega C}\right)} = \frac{j\omega LR + \frac{L}{C}}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

let $A = \omega L - \frac{1}{\omega C}$

17/12 Cmtd

3

$$z_p(j\omega) = \frac{\frac{L}{C} + j\omega RL}{R + jA} \cdot \frac{R - jA}{R - jA}$$
$$= \frac{\frac{RL}{C} + j\omega R^2L - j\frac{L}{C}A + \omega RL A}{R^2 + A^2}$$

$$\text{Im}[z_p(j\omega)] = \frac{\omega R^2L - \frac{L}{C}A}{R^2 + A^2}$$

for resonance

$$\text{Im}[z_p(j\omega)] = 0 = \frac{\omega R^2L - \frac{L}{C}A}{R^2 + A^2}$$

$$\omega R^2L = \frac{L}{C} \left(\omega_r - \frac{1}{\omega_c} \right)$$
$$= \frac{L}{\omega_r C^2} (L C \omega_r^2 - 1)$$

$$\omega_r^2 R^2 C^2 = L C \omega_r^2 - 1$$

$$\omega_r^2 (L C - R^2 C^2) = 1$$

$$\omega_r^2 = \frac{1}{L C - (R C)^2} = \frac{1}{0,0016 - 0,0004}$$

$$\omega_r = \sqrt{\frac{1}{0,0012}} = \sqrt{833,33} = 28,87 \text{ rad/s}$$

Chapter 17 / Problem 17

For either figure

$$\omega_r^2 = \frac{1}{LC}$$

$$L = \frac{1}{\omega_r^2 C}$$

Fig
P17.15a

Fig
P17.15b

With

$$f_r = 10,000 \text{ Hz}$$

$$\omega_r = 2\pi(10,000) \text{ rad/s}$$

and $\omega_r^2 = 4\pi^2 \times 10^8 \text{ rad}^2/\text{s}^2$

Thus with $C = 10^{-7} \text{ F}$

$$L = \frac{10^{-7}}{4\pi^2 \times 10^8} = 2.533 \text{ mH}$$

Chapter 17 / Problem 16

(a) For Fig P17.16a use eq 17.4

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Fig
P17.16a

If $f_r = 1560 \text{ Hz}$, then

$$\omega_r = 2\pi(1560) = 9801.77 \text{ rad/s}$$

Fig
P17.16b

and

$$\omega_r^2 = 9.607468 \times 10^7 \text{ rad}^2/\text{s}^2$$

Then with $C = 10^{-7} \text{ F}$ and $R = 5 \Omega$

$$9.607468 \times 10^7 = \frac{10^7}{L} - \frac{2.601 \times 10^5}{L^2}$$

This leads to a quadratic

$$L^2 - 0.104086L + 2.707269 \times 10^{-3} = 0$$

There are two roots

$$L = 53.14 \text{ mH}$$

$$L = 50.94 \text{ mH}$$

(a) for Fig P.17.16b, it is shown in Problem 17.9 that

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{1}{R^2C^2}}$$

Then

$$9.607468 \times 10^7 = \frac{10^7}{L} - 3.944675 \times 10^8$$

$$L = \frac{10^7}{4.805422 \times 10^8} = 20.81 \text{ mH}$$

17/17

Bandwidth and Q

differ from answers
listed with problem statement

Chapter 17/Problem 16

The maximum value is at resonance

$$\omega_m = \omega_0 = 10^6 \text{ rad/s} = \frac{1}{\sqrt{LC}}$$

fig
P17.17

and

$$Z(\omega_m) = R = 20,000 \Omega \leftarrow$$

The magnitude at any ω is given by eq (17.9b).

$$10^{-8} = \frac{1}{\frac{1}{R^2} \pm (\omega C - \frac{1}{\omega L})^2}$$

$$= \frac{1}{2.5 \times 10^{-9} \pm (0.9 \times 10^6 C - \frac{1}{0.9 \times 10^6 L})^2}$$

$$10^{-8} = 2.5 \times 10^{-9} \pm (0.9 \times 10^6 C - \frac{1}{0.9 \times 10^6 L})^2$$

$$(7.5 \times 10^{-9})^{1/2} = \pm \frac{0.81 \times 10^{12} LC - 1}{0.9 \times 10^6 L}$$

with $LC = 10^{-12}$

$$(8.66 \times 10^{-5}) (0.9 \times 10^6 L) = \pm (0.810 - 1)$$

To make L real

$$77.94 L = 0.19$$

$$L = 0.002438 \quad (2.438 \mu\text{H}) \leftarrow$$

$$C = \frac{1}{L \omega_m^2} = \frac{10^{-12}}{0.002438} = 4.101 \times 10^{-10} \text{ F}$$

$$(410.2 \text{ pF}) \leftarrow$$

then

$$B_w = \frac{1}{RC} = \frac{1}{40000 (410.1 \times 10^{-12})} = 60,960 \text{ rad/s}$$

and

$$Q = \frac{\omega_m}{B_w} = \frac{10^6}{60,960} = 16.40$$

Chapter 17 / Problem 18

(a)

$$L = 100 \mu\text{H}$$

$$\omega_M = 2.08\pi \times 10^6 \text{ rad/s}$$

$$\beta_W = 2\pi \times 10^4 \text{ rad/s}$$

$$\omega_M = \frac{1}{LC}$$

$$\beta_W = \frac{1}{RC}$$

Fig
P17.18

$$C = \frac{1}{L\omega_M^2} = \frac{1}{(100 \times 10^{-6})(2.08\pi \times 10^6)^2} = 234.2 \times 10^{-12} \text{ F} \quad (234.2 \text{ pF})$$

$$R = \frac{1}{C\beta_W} = \frac{1}{(234.2 \times 10^{-12})(2\pi \times 10^4)} = 67,959 \Omega \quad (67.96 \text{ k}\Omega)$$

(b)

$$C = 250 \text{ pF}$$

$$\omega_M = 1.84\pi \times 10^6 \text{ rad/s}$$

$$\beta_W = 2\pi \times 10^4 \text{ rad/s}$$

$$L = \frac{1}{C\omega_M^2} = \frac{1}{(250 \times 10^{-12})(1.84\pi \times 10^6)^2} = 1.197 \times 10^{-7} \text{ H} \quad (119.7 \mu\text{H})$$

$$R = \frac{1}{C\beta_W} = \frac{1}{(250 \times 10^{-12})(2\pi \times 10^4)} = 63.66 \times 10^3 \Omega \quad (63.66 \text{ k}\Omega)$$

Chapter 17/Chapter 19

①

(a) Select $L = 300 \mu\text{H}$ (middle of range available)

Fig
P17.19

Specification:

low end

$$f_m = 550,000 \text{ Hz}; \quad \omega_m = 1.1\pi \times 10^6 \text{ rad/s}$$

high end

$$f_m = 1,650,000 \text{ Hz}; \quad \omega_m = 3.3\pi \times 10^6 \text{ rad/s}$$

For the low end

$$C = \frac{1}{L\omega_m^2} = \frac{1}{(300 \times 10^{-6})(1.1\pi \times 10^6)^2} = 279.12 \times 10^{-12} \text{ F}$$

For the high end

$$C = \frac{1}{L\omega_m^2} = \frac{1}{(300 \times 10^{-6})(3.3\pi \times 10^6)^2} = 31.01 \times 10^{-12} \text{ F}$$

∴ Select $C = 30 - 300 \text{ pF}$

$$f_m = 920,000 \text{ Hz}; \quad \omega_m = 1.84\pi \times 10^6 \text{ rad/s}$$

$$B_f = 20,000 \text{ Hz}; \quad B_\omega = 4\pi \times 10^4 \text{ rad/s}$$

Then

$$Q = \frac{\omega_m}{B_\omega} = 46 = R\sqrt{\frac{C}{L}}$$

with C tuned to

$$C = \frac{1}{L\omega_m^2} = \frac{1}{(300 \times 10^{-6})(1.84\pi \times 10^6)^2} = 99.76 \times 10^{-12} \text{ F}$$

$$R = 46\sqrt{\frac{L}{C}} = 46\sqrt{\frac{300 \times 10^{-6}}{99.76 \times 10^{-12}}} = 46\sqrt{3.007 \times 10^6}$$

$$R = 46(1734.2) = 79,771 \Omega = 79.77 \text{ k}\Omega$$

17/19 Cont'd
With the components of (b)

(2)

Low end

$$L = 300 \mu\text{H}$$

$$R = 79.77 \text{ k}\Omega$$

$$C = 279.1 \text{ pF}$$

$$\omega_m = 1.1\pi \times 10^6 \text{ rad/s}$$

$$\beta_{\omega} = \frac{1}{RC} = \frac{1}{(79.77 \times 10^3)(279.12 \times 10^{-12})} = 44.91 \times 10^3 \text{ rad/s}$$

$$f_{\beta} = \frac{44.91 \times 10^3}{2\pi} = 7.15 \times 10^3 \text{ Hz} \quad (7.15 \text{ kHz})$$

High end

$$L = 300 \mu\text{H}$$

$$R = 79.77 \text{ k}\Omega$$

$$C = 31.01 \text{ pF}$$

$$\omega_m = 3.3\pi \times 10^6 \text{ rad/s}$$

$$\beta_{\omega} = \frac{1}{(79.77 \times 10^3)(31.01 \times 10^{-12})} = 404.3 \times 10^3 \text{ rad/s}$$


$$f_{\beta} = \frac{404.3 \times 10^3}{2\pi} = 64.34 \text{ kHz}$$

Chapter 17/Problem 20

①

First make a voltage to current source transformation

Fig P17.20

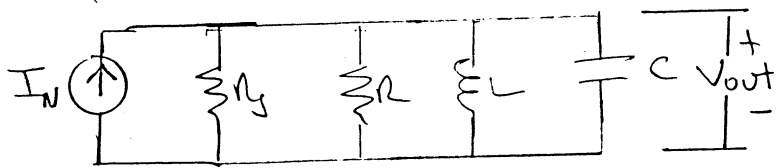

$$R_s = 40 \text{ k}\Omega$$

$$R = 10 \text{ k}\Omega$$

$$C = 1 \mu\text{F}$$

$$L = 0.01 \text{ H}$$

$$R_{eq} = \frac{R R_s}{R + R_s} = \frac{(10 \text{ k}\Omega)(40 \text{ k}\Omega)}{50 \text{ k}\Omega}$$

$$R_{eq} = 8 \text{ k}\Omega$$

$$(a) \quad f_m = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} = \frac{1}{2\pi} \frac{1}{(0.01)(1 \times 10^{-6})} = \frac{1}{2\pi} \frac{1}{\sqrt{10^{-8}}}$$

$$f_m = 1591.5 \text{ Hz}$$

$$|H(j\omega_m)| = \frac{V_{out}}{V_{in}} = \frac{R}{R_s + R} = \frac{10 \text{ k}\Omega}{50 \text{ k}\Omega} = 0.20$$

(b) The exact 3-dB bandwidth is

$$B_w = \frac{1}{R_{eq} C} = \frac{1}{(8000)(1 \times 10^{-6})} = 125 \text{ rad/s}$$

$$B_f = \frac{125}{2\pi} = 19.89 \text{ Hz}$$

(c) Approximate values

$$f_2, f_1 = 1591.5 \pm \frac{19.89}{2} = 1601.5, 1581.6$$

Exact values

$$f_2 = \frac{1}{2\pi} \left[\frac{1}{2R_{eq}C} + \sqrt{\left(\frac{1}{2R_{eq}C}\right)^2 + \frac{1}{LC}} \right]$$

with

$$R_{eq}C = 8000(1 \times 10^{-6}) = 0.008$$

$$\frac{1}{2R_{eq}C} = \frac{125}{2} = 62.50$$

17/20 Cont'd $LC = (0.01)(1 \times 10^{-6}) = 10^{-8}$

$$\frac{1}{LC} = 10^8$$

Let $\Lambda = \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} = \sqrt{(62.5)^2 + 10^8} = 10000.2$

Then $f_2 = \frac{1}{4\pi} [+62.5 + 10000.2] = \frac{1}{4\pi} (10062.7) = 1601.5$

$$f_1 = \frac{1}{2\pi} [-62.5 + 10000.2] = \frac{1}{2\pi} (9937.7) = 1581.6$$

Compare exact and approximate and find negligible difference

(d) $Q = \frac{W_m}{B_w} = \frac{f_m}{B_f} = \frac{1591.5}{19.89} = 80$

(e)

Chapter 17/Problem 21

Given data

$$f_r = 10,000 \text{ Hz}$$

$$\omega_0 = \omega_r = 20,000\pi \text{ rad/s}$$

$$C = 10^{-7} \text{ F}$$

$$B_f = 3000 \text{ Hz}$$

Then

$$L = \frac{1}{C\omega_0^2} = \frac{1}{(10^{-7})(20,000\pi)^2} = 2.533 \times 10^{-3} \text{ H} \quad (2.533 \text{ mH})$$

and

$$Q = \frac{\omega_0}{B_w} = \frac{f_0}{B_f} = \frac{10,000 \text{ Hz}}{3,000 \text{ Hz}} = \frac{10}{3} = \omega_r \sqrt{\frac{C}{L}}$$

$$R = \frac{10}{3} \sqrt{\frac{L}{C}} = \frac{10}{3} \sqrt{\frac{2.533 \times 10^{-3}}{1 \times 10^{-7}}}$$

$$R = \frac{10}{3} \sqrt{25,330} = \frac{10}{3} (159.16) = 530.5 \Omega \leftarrow$$

Fig
P17.21

Chapter 17/Problem 22

①

$$\text{Here } \omega_0 = \frac{1}{\sqrt{LC}}$$

Fig
P17.22

and

$$Z(j\omega) = R$$

so that with $\hat{I}_m = I_m \angle 0^\circ$

$$\hat{V}_C = \hat{V}_L = R I_m$$

$$(a) \quad w_C(t) = \frac{1}{2} C [v_C(t)]^2 = \frac{1}{2} C [R^2 I_m^2 \cos^2 \omega_0 t] = \frac{1}{2} C R^2 I_m^2 \cos^2 \omega_0 t \quad W$$

$$(b) \quad \text{With } v_L(t) = \frac{1}{L} \int v_C(t) dt = \frac{R I_m}{\omega_0 L} \sin \omega_0 t \quad A$$

then

$$w_L(t) = \frac{1}{2} L [i_L(t)]^2 = \frac{1}{2} L \left[\frac{R^2 I_m^2}{\omega_0^2 L^2} \sin^2 \omega_0 t \right]$$

$$w_L(t) = \frac{1}{2} \frac{R^2 I_m^2}{\omega_0^2 L} \sin^2 \omega_0 t \quad W$$

$$(c) \quad w_C(t) + w_L(t) = \frac{1}{2} R^2 I_m^2 C \left[\cos^2 \omega_0 t + \frac{1}{\omega_0^2 LC} \sin^2 \omega_0 t \right]$$

$$\text{But } \omega_0^2 = \frac{1}{LC}$$

so that with $\cos^2 \omega_0 t + \sin^2 \omega_0 t = 1$

$$w_C(t) + w_L(t) = \frac{1}{2} R^2 I_m^2 C$$

17/22 Cont'd

(2)

(d) Over one cycle between 0 and T (T is the period)

$$\begin{aligned}
 W_R(0, T) &= R \int_0^T i_R^2(t) dt = R \int_0^T I_m^2 \cos^2 \omega_0 t dt \\
 &= R I_m^2 \int_0^T \frac{1}{2} [t + \cos 2\omega_0 t] dt \\
 &= \frac{R I_m^2}{2} T + \frac{R I_m^2}{4\omega_0} [\sin 2\omega_0 t]_0^T \\
 &= \frac{R I_m^2}{2} T
 \end{aligned}$$

and with $T = \frac{2\pi}{\omega_0}$

$$W_R(0, T) = \frac{R I_m^2 \pi}{\omega_0}$$

(e)

$$Q = 2\pi \frac{\text{max energy stored}}{\text{energy dissipated over one period}}$$

$$= 2\pi \frac{\frac{1}{2} R I_m^2 C}{\frac{R I_m^2 \pi}{\omega_0}}$$

$$= 2\pi \frac{R^2 I_m^2 C \omega_0}{2 R I_m^2 \pi} = \omega_0 R C$$

also with

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 C = \frac{1}{\omega_0 L}$$

$$\text{and } Q = \frac{R}{\omega_0 L}$$

Chapter 17/Problem 24

With

$$f_0 = f_r = 10,000 \text{ Hz}$$

$$\omega_0 = \omega_r = 20,000\pi \text{ rad/s}$$

and

$$C = 1 \times 10^{-7} \text{ F}$$

Fig
P17.24

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$L = \frac{1}{\omega_0^2 C} = \frac{1}{(20,000\pi)^2 (1 \times 10^{-7})} = 2.533 \times 10^{-3} \text{ (2.533 mH)}$$

$$Q = \frac{\omega_m}{B_w} = \frac{f_0}{B_f} = \frac{10,000}{3,000} = \frac{10}{3}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$R = \frac{1}{Q} \sqrt{\frac{L}{C}} = \frac{3}{10} \sqrt{\frac{2.533 \times 10^{-3}}{1 \times 10^{-7}}} = 0.3 \sqrt{25330}$$

$$R = 47.75 \Omega$$

Chapter 17 / Problem 25

①

(a) By voltage division

Fig
P17.25

$$\begin{aligned}
 H(s) &= \frac{V_{out}(s)}{V_{in}(s)} = \frac{R_2}{Ls + R_1 + R_2 + \frac{1}{Cs}} \\
 &= \frac{R_2 Cs}{LCs^2 + (R_1 + R_2)s + 1} \\
 &= \frac{\frac{R_2}{L}s}{s^2 + \frac{R_1 + R_2}{L}s + \frac{1}{LC}}
 \end{aligned}$$

With component values

$$H(s) = \frac{200s}{s^2 + 250s + 10^6}$$

(b) The maximum voltage gain occurs at ω_m

$$\omega_m = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-6}}} = \frac{1}{10^{-3}} = 1000 \text{ rad/s}$$

$$H(j\omega_m) = \frac{200(j1000)}{10^6 - 10^6 + 250(j1000)} = \frac{200}{250} = 0.80$$

$$f_m = \frac{\omega_m}{2\pi} = \frac{1000}{2\pi} = 159.15 \text{ Hz}$$

(c) The exact value of the bandwidth is ($R = 160 + 40 = 200 \Omega$)

$$B_\omega = \frac{R}{L} = \frac{200}{0.8} = 250 \text{ rad/s}$$

$$B_f = \frac{B_\omega}{2\pi} = 39.79 \text{ Hz}$$

(d) The exact values of the half power frequencies depend on Q_0

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{200} \sqrt{\frac{0.8}{1.25 \times 10^{-6}}} = \frac{1}{200} \sqrt{64 \times 10^6}$$

$$Q = \frac{800}{200} = 4$$

~~25/25~~ 25/25 Cont'd

(2)

$$\begin{aligned} \omega_2 &= \omega_n \left[\sqrt{1 + \left(\frac{1}{2Q}\right)^2} + \frac{1}{2Q} \right] \\ &= 1000 \left[\sqrt{1 + \frac{1}{64}} + \frac{1}{8} \right] = 1000 \left[\sqrt{1.01563} + 0.125 \right] \end{aligned}$$

$$\omega_2 = 1000(1.00778 + 0.125) = 1132.78 \text{ rad/s}$$

$$\omega_1 = 1000(1.00778 - 0.125) = 882.78 \text{ rad/s}$$

$$f_2 = \frac{1132.78}{2\pi} = 180.29 \text{ Hz}$$

$$f_1 = \frac{882.78}{2\pi} = 140.50 \text{ Hz}$$

$$\text{Note that } \beta_f = f_2 - f_1 = 39.79 \text{ Hz} \checkmark$$

(e) From part (d)

$$Q = 4$$

Chapter 25 / Problem 26

(a) From Problem 25

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{R_2 s}{L}}{s^2 + \frac{R_1 + R_2}{L}s + \frac{1}{LC}}$$

With component values

$$H(s) = \frac{250s}{s^2 + 312.5s + 1.5625 \times 10^6}$$

(b)

$$\omega_m = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1.28(0.5 \times 10^{-6})}} = \frac{1}{\sqrt{0.64 \times 10^{-6}}} = \frac{1}{0.8 \times 10^{-3}} = 1250 \text{ rad/s}$$

$$f_m = \frac{1250}{2\pi} = 198.94 \text{ Hz}$$

$$H(j\omega_m) = \frac{250(j1250)}{1.5625 \times 10^6 - 1.5625 \times 10^6 + 312.5(j1250)} = \frac{250}{312.5} = 0.8$$

(c) With $R = R_1 + R_2 = 80 + 320 = 400 \Omega$

$$\beta_w = \frac{R}{L} = \frac{400}{1.28} = 312.5 \text{ rad/s}$$

$$\beta_f = \frac{312.5}{2\pi} = 49.74 \text{ Hz}$$

(d)

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{400} \sqrt{\frac{1.28}{0.5 \times 10^{-6}}} = \frac{1}{400} \sqrt{2.56 \times 10^6}$$

$$Q = \frac{1600}{400} = 4$$

$$\omega_2 = 1250(1.00778 + 0.125) = 1415.98 \text{ rad/s}$$

$$\omega_1 = 1250(1.00778 - 0.125) = 1103.48 \text{ rad/s}$$

$$f_2 = \frac{1415.98}{2\pi} = 225.36 \text{ Hz}$$

$$f_1 = \frac{1103.48}{2\pi} = 175.62 \text{ Hz}$$

Note that

$$\beta_f = f_2 - f_1 = 49.74 \text{ Hz} \checkmark$$

Chapter 17 / Problem 27

①

Fig
P17.27

$$(a) \quad I_L(s) = \frac{V_s(s)}{Ls + R + \frac{1}{Cs}}$$

$$= \frac{CsV_s(s)}{LCS^2 + RCS + 1}$$

$$H_1(s) = \frac{I_L(s)}{V_s(s)} = \frac{S}{L(S^2 + \frac{R}{L}S + \frac{1}{LC})}$$

then by voltage division

$$V_C(s) = \frac{\frac{1}{Cs} V_s(s)}{Ls + R + \frac{1}{Cs}} = \frac{\frac{1}{Cs} V_s(s)}{\frac{LCS^2 + RCS + 1}{Cs}}$$

$$H_2(s) = \frac{\frac{1}{LC}}{L(S^2 + \frac{R}{L}S + \frac{1}{LC})}$$

$$(b) \quad H_1(j\omega) = \frac{j\omega}{L(-\frac{1}{LC} - \omega^2) + j\frac{R}{L}\omega}$$

To make $|H_1(j\omega)|$ maximum set

$$\omega_m^2 = \frac{1}{LC}$$

$$\omega_m = \frac{1}{\sqrt{LC}}$$

then

$$H_1(\omega_m) = \frac{j\omega_m}{L \frac{R}{L} j\omega_m} = \frac{1}{R}$$

$$B\omega = \frac{R}{L}$$

and

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Chapter 17/27 Cont'd

(2)

(c)

$$|H_2(j\omega)| = \frac{\frac{1}{LC}}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{R}{L}\omega\right)^2}}$$

$$|H_2(j\omega)|^2 = \frac{\left(\frac{1}{LC}\right)^2}{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{R}{L}\omega\right)^2} = \frac{1}{(1 - LC\omega^2)^2 + (RC\omega)^2}$$

To maximize $|H_2(j\omega)|$ minimize

$$\phi(c) = (1 - LC\omega^2)^2 + (RC\omega)^2$$

$$\frac{d\phi(c)}{dc} = 2(\omega^2 LC - 1)LC\omega^2 + 2C(R\omega)^2 = 0$$

$$C = \frac{L}{R^2(\omega L)^2} = \frac{1}{L\omega^2} \left[\frac{1}{\frac{R^2}{L\omega^2} + 1} \right]$$

The Q of the coil is defined as

$$Q_{\text{coil}} = \frac{\omega L}{R}$$

and if Q_{coil} is high

$$C = \frac{1}{L\omega^2} \left[\frac{1}{(Q_{\text{coil}})^2 + 1} \right] \rightarrow \frac{1}{L\omega^2}$$

then with

$$\frac{1}{LC} = \frac{1}{L\left(\frac{1}{L\omega^2}\right)} = \omega^2$$

$$|H_2(j\omega)|_{\text{max}} = \frac{\omega^2}{\sqrt{(\omega^2 - \omega^2)^2 + \left(\frac{R}{L}\omega\right)^2}} = \frac{\omega^2}{\frac{R}{L}\omega} = \frac{\omega L}{R} = Q_{\text{coil}}$$

$$\text{Thus } |V_{\text{out}}|_{\text{max}} = |V_C|_{\text{max}} = Q_{\text{coil}} |V_s|$$

Chapter 17 / Problem 29

In example 17.10, it is shown that

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{s}{R_1 C_2}}{s^2 + \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2}\right)s + \frac{1}{R_1 R_2 C_1 C_2}}$$

Fig
P17.29

This is in the form of eq (17.18)

$$H(s) = K \frac{s}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

With $f_m = 1000$ Hz and $B_f = 12.5$ Hz, then by eqs (17.19a) and (17.19d)

$$\omega_m = \omega_p = \frac{1}{R_1 R_2 C_1 C_2} = 2000\pi \text{ rad/s}$$

and

$$B_w = \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} = 25\pi \text{ rad/s}$$

Let $C_1 = C_2 = 1 \mu\text{F}$ (10^{-6} F)

Then

$$B_w = 25\pi = \frac{2 \times 10^6}{R_2}$$

$$R_2 = \frac{2 \times 10^6}{25\pi} = 25,465 \Omega \quad (25.46 \text{ k}\Omega)$$

and


$$\frac{1}{R_1 R_2 C_1 C_2} = 2000\pi$$

$$\frac{10^{12}}{R_1 (25,465)} = 2000\pi$$

$$R_1 = \frac{10^{12}}{2000\pi (25,465)} = 6250 \Omega$$

Chapter 17/Problem 30

①

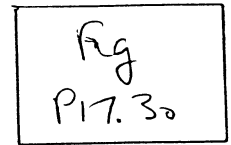

(a)

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{z_1(s)}{z_2(s)} = -\frac{Y_{1W}(s)}{Y_2(s)}$$

$$H(s) = -\frac{\frac{1}{R_1}}{Cs + \frac{1}{R_2} + \frac{1}{Cs}} = -\frac{\frac{Ls}{R_1}}{LCs^2 + \frac{L}{R_2}s + 1} = -\frac{s}{R_1C(s^2 + \frac{1}{R_2C}s + \frac{1}{LC})}$$

This is in the form

$$H(s) = K \frac{s}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

(b) Here

$$K = -\frac{1}{R_1C}$$

$$\zeta = \frac{1}{2R_2C}$$

and

$$\omega_p^2 = \frac{1}{LC} \rightarrow \omega_p = \frac{1}{\sqrt{LC}}$$

$$\beta_w = 2\zeta\omega_p = \frac{1}{R_2C}$$

$$Q = Q_p = \frac{\omega_p}{\beta_w} = \frac{\frac{1}{\sqrt{LC}}}{\frac{1}{R_2C}} = R_2\sqrt{\frac{C}{L}}$$

(c) From eq (17.19c)

$$\begin{aligned} \omega_1, \omega_2 &= \pm\zeta\omega_p + \sqrt{\zeta^2\omega_p^2 + \omega_p^2} = \pm\zeta\omega_p + \omega_p\left(\sqrt{1 + \left(\frac{1}{2Q_p}\right)^2} \pm \frac{1}{2Q_p}\right) \\ &= \pm\frac{1}{2R_2C} + \frac{1}{\sqrt{LC}}\left(\sqrt{1 + \frac{4L}{R_2^2C}} \pm \frac{2}{R_2}\sqrt{\frac{L}{C}}\right) \end{aligned}$$


17/30 cont'd
(d) one zero at $s_z = 0$

Two poles

$$s^2 + 2\sigma_p + \omega_p^2 = 0$$

$$s^2 + 2\sigma_p + \sigma_p^2 + \omega_d^2 - \sigma_p^2 = 0$$

$$(s + \sigma_p)^2 + \omega_d^2 = 0$$

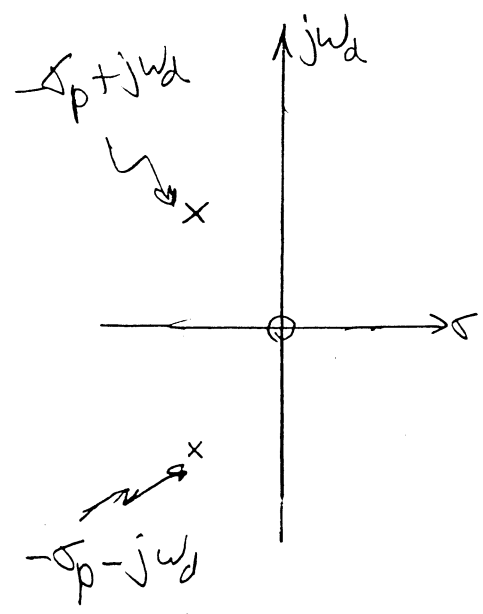

If $\omega_p > \sigma_p$, then $\omega_d^2 = \omega_p^2 - \sigma_p^2 > 0$

and $s_{1,2} = -\sigma_p \pm j\omega_d$

(e) With $\omega_m = \omega_p$ [eq (17.19a)], eq (17.19b) gives

$$H_m = |H(j\omega)|_{max} = \frac{|K|Q_p}{\omega_m} = \frac{\left(\frac{1}{R_w C}\right)\left(R + \sqrt{\frac{L}{C}}\right)}{\frac{1}{\sqrt{LC}}} = \frac{R + L}{R_w C}$$

(f) If $v_{in}(t) = 100 \sin 10^3 t$ mV

$$|V_{in}| = 100$$

$$H(j1000) = \frac{j10^3}{R_w C \left(\frac{1}{LC} - 10^6 + j\frac{10^3}{R_f C} \right)}$$

$$|H(j1000)| = \frac{10^3}{R_w C \sqrt{\left(\frac{1}{LC} - 10^6\right)^2 + 10^6 \left(\frac{1}{R_f C}\right)^2}}$$

and

$$|N_{out}| = \frac{10^5}{R_w C \sqrt{\left(\frac{1}{LC} - 10^6\right)^2 + 10^6 \left(\frac{1}{R_f C}\right)^2}}$$

Chapter 17 / Problem 31

(1)

(a)
$$H(s) = K \frac{s+a}{s^2+2\zeta\omega_p s+\omega_p^2}$$

$$|H(j\omega)| = K \sqrt{\frac{a^2+\omega^2}{(\omega_p^2-\omega^2)^2+4\zeta^2\omega^2}}$$

The radical is a nuisance

$$|H(j\omega)|^2 = K^2 \left[\frac{a^2+\omega^2}{(\omega_p^2-\omega^2)^2+4\zeta^2\omega^2} \right]$$

Note that the bracketed term is a function of ω^2 . In

the optimization process

$$\frac{d+(w^2)}{dw^2} = 0$$

the factor K need not be considered

$$\frac{d+(w^2)}{dw^2} = v du - u dv = 0$$

$$0 = \frac{1}{[(\omega_p^2-\omega^2)^2+4\zeta^2\omega^2]} - \frac{(a^2+\omega^2)[-2(\omega_p^2-\omega^2)+4\zeta^2]}{[(\omega_p^2-\omega^2)^2+4\zeta^2\omega^2]^2}$$

As long as

$$(\omega_p^2-\omega^2)^2+4\zeta^2\omega^2 \neq 0$$

this can be written as

$$(\omega_p^2-\omega^2)^2+4\zeta^2\omega^2 - (a^2+\omega^2)[-2(\omega_p^2-\omega^2)+4\zeta^2] = 0$$

$$\omega_p^4 - 2\omega_p^2\omega^2 + \omega^4 + 4\zeta^2\omega^2 + 4\zeta^2\omega^2 + 2(a^2+\omega^2)(\omega_p^2-\omega^2) - 4(a^2+\omega^2)\zeta^2 = 0$$

Let

$$\omega_p^4 - 2\omega_p^2\omega^2 + \omega^4 + 4\zeta^2\omega^2 = A$$

$$\begin{aligned} A + 2a^2\omega_p^2 - 2a^2\omega^2 + 2\omega_p^2\omega^2 - 2\omega^4 - 4a^2\zeta^2 - 4\zeta^2\omega^2 \\ = -\omega^4 - 2a^2\omega^2 + \omega_p^4 + 2a^2\omega_p^2 - 4a^2\zeta^2 \end{aligned}$$

17/31 Cont'd

(2)

This reduces to

$$w^4 + 2a^2w^2 = w_p^4 + 2a^2w_p^2 - 4a^2\sigma_p^2$$

and after a^4 is added to both side of the equation

$$w^4 + 2a^2w^2 + a^4 = w_p^4 + 2a^2w_p^2 - 4a^2\sigma_p^2 + a^4$$

completing the square gives

$$w^2 = -a^2 \pm \sqrt{(w_p^2 + a^2)^2 - (2a\sigma_p)^2}$$

and to produce a positive value of w

$$w = \sqrt{-a^2 + \sqrt{(w_p^2 + a^2)^2 - (2a\sigma_p)^2}}$$

$$\begin{aligned} \text{(b)} \quad \frac{1}{H(s)} &= \frac{s^2 + 2\sigma_p s + w_p^2}{K(s+a)} = \frac{s^2 + 2\sigma_p(s+a) - 2\sigma_p a + w_p^2}{K(s+a)} \\ &= \frac{2\sigma_p}{K} + \frac{s^2 - 2\sigma_p a + w_p^2}{K(s+a)} \end{aligned}$$

The first term is entirely real. For zero phase shift, the second term must be real. Hence with

$$\frac{1}{H_1(s)} = \frac{s^2 - 2\sigma_p a + w_p^2}{K(s+a)}$$

and

$$\frac{1}{H_1(jw)} = \frac{w_p^2 - w^2 + 2\sigma_p a}{K(a + jw)} \left[\frac{a - jw}{a + jw} \right]$$

So that

$$\text{Im} \left[\frac{1}{H_1(jw)} \right] = \frac{w^3 - ww_p^2 + 2\sigma_p aw}{K(a^2 + w^2)}$$

For $\text{Im}\left[\frac{1}{H(j\omega)}\right] = 0$ 17/31 Cont'd

(3)

$$\omega^2 = \omega_p^2 + 2\zeta_p a$$

and

$$\omega = \sqrt{\omega_p^2 + 2\zeta_p a}$$

This is subject to

$$\omega_p^2 \geq 2\zeta_p a$$

Problem ~~17/33~~ 17/33

Text lists solution for ~~part (a)~~
part (b)

$$\omega_m = 8.55 \text{ rad/s}$$

We get

$$\omega_m = 9.01 \text{ rad/s}$$

We did get

$$\omega_1 = 8.55 \text{ rad/s}$$

for lower half power frequency

Chapter 17/Problem 33

①

(a) From fig P.17.32 and Problem 32

$$H(s) = Z_w(s) = \frac{\frac{1}{C} \left(s + \frac{R_s}{L} \right)}{s^2 + \left(\frac{1}{R_p C} + \frac{R_s}{L} \right) s + \left(1 + \frac{R_s}{R_p} \right) \frac{1}{LC}}$$

and with the given circuit element

$$\frac{1}{R_p C} = \frac{1}{50(1/4)} = \frac{4}{50} = 0.08$$

$$\frac{R_s}{L} = \frac{0.08}{1/4} = 0.32$$

$$\frac{1}{R_p C} + \frac{R_s}{L} = 0.08 + 0.32 = 0.40$$

$$\frac{R_s}{R_p} = \frac{0.08}{50} = 0.0016$$

$$\frac{1}{LC} = \frac{1}{(1/4)(1/4)} = 16$$

$$\left(1 + \frac{R_s}{R_p} \right) \frac{1}{LC} = (1.0016)(16) = 16.0256$$

$$H(s) = \frac{4(s + 0.32)}{s^2 + 0.40s + 16.0256}$$

This is in the form

$$H(s) = K \frac{s+a}{s^2 + 2\sigma_p s + \omega_p^2}$$

where

$$K = 4$$

$$a = 0.32$$

$$\sigma_p = \frac{0.40}{2} = 0.20$$

$$\omega_p^2 = 16.0256$$

and

$$\omega_p = 4.0032$$

17/33 Cont'd

(a) With

$$Q_p = \frac{W_p}{\Delta\omega_p}$$

$$Q_p = \frac{W_p}{2\Delta\omega_p} = \frac{9.0072}{0.90} = 10.008 > 10$$

and the circuit is high Q. Moreover, $a \leq W_p$

$$0.72 \leq 9.0072$$

(b) Using eq (17.28)

$$\omega_m = \sqrt{-a^2 + \sqrt{(W_p^2 + a^2)^2 - (2\zeta\omega_p a)^2}}$$

$$= \sqrt{-(0.72)^2 + \sqrt{[8.11296 + (0.72)^2]^2 - [2(0.45)(0.72)]^2}}$$

$$= \sqrt{-0.5184 + \sqrt{(8.6480)^2 - (0.648)^2}}$$

$$= \sqrt{-0.5184 + \sqrt{665.976}} = \sqrt{-0.5184 + 81.6454}$$

$$= \sqrt{81.1270} = 9.0071 \approx 9.0072$$

Hence

$$\omega_m \approx W_p$$

Then the maximum gain derives from eq (17.30)

$$H_m \approx \frac{|K|}{2\zeta\omega_p} = \frac{9}{0.90} = 10$$

(c) From eq (17.30)

$$\beta_{\omega} \approx 2\zeta\omega_p = 2(0.45) = 0.90 \text{ rad/s}$$

$$\omega_1 \approx \omega_m - \frac{\beta_{\omega}}{2} = 9.0071 - 0.45 = 8.557 \text{ rad/s}$$

$$\omega_2 = \omega_m + \frac{\beta_{\omega}}{2} = 9.0071 + 0.45 = 9.457 \text{ rad/s}$$

$$(d) |V_{out}(j\omega_m)| = |I_{in}(j\omega_m)| H_m = (1)(10) = 10V$$

Chapter 17/Problem 34

This is a repeat of Problem 33 with different circuit elements ①

$$\frac{1}{R_p C} = \frac{10^9}{60,000} = 16,667$$

$$\frac{R_s}{L} = \frac{25}{0,001} = 25,000$$

$$\frac{1}{R_p C} + \frac{R_s}{L} = 41667$$

$$\frac{R_s}{R_p} = \frac{25}{60000} = 4.167 \times 10^{-4}$$

$$\frac{1}{LC} = \frac{10^9}{0,001} = 1 \times 10^{12}$$

$$\left(1 + \frac{R_s}{R_p}\right) \frac{1}{LC} = (1.000417)(1 \times 10^{12}) = 1.000417 \times 10^{12}$$

$$H(s) = \frac{10^9(s + 25,000)}{s^2 + 41,667s + 1.000417 \times 10^{12}}$$

This is in the form

$$H(s) = \frac{K(s+a)}{s^2 + 2\zeta_p s + \omega_p^2}$$

where

$$K = 10^9$$

$$a = 25,000$$

$$\zeta_p = 20,833$$

$$\omega_p^2 = 1.000417 \times 10^{12}$$

and

$$\omega_p = 1.00021 \times 10^6$$

17/34 Cont'd

$$(a) \text{ With } \zeta_p = \frac{W_p}{Q_p}$$

$$Q_p = \frac{W_p}{2\zeta_p} = \frac{1.00021 \times 10^6}{41,667} = 24.01 > 10$$

and the circuit is underdamped high Q. Moreover $a \leq W_p$
 $25,000 \leq 1.00021 \times 10^6$

(b) Using eq (17.28)

$$\begin{aligned} \omega_m &= \sqrt{-a^2 + \sqrt{(W_p^2 + a^2)^2 - (2\zeta_p a)^2}} \\ &= \sqrt{-(25,000)^2 + \sqrt{[1.000417 \times 10^{12} + (25,000)^2]^2 - [2(25,833)(25,000)]^2}} \\ &= \sqrt{6.25 \times 10^8 + \sqrt{(1.00104 \times 10^{12})^2 - (1.04165 \times 10^9)^2}} \\ &= \sqrt{6.25 \times 10^8 + \sqrt{1.00209 \times 10^{24} - 1.08503 \times 10^{18}}} \\ &= \sqrt{6.25 \times 10^8 + \sqrt{1.00208 \times 10^{24}}} \\ &= \sqrt{6.25 \times 10^8 + 1.00104 \times 10^{12}} = \sqrt{1.00167 \times 10^{12}} \end{aligned}$$

$$\omega_m = 1.00083 \times 10^6 \approx W_p$$

(c) The maximum gain derive from eq (17.28)

$$H_m = \frac{|K|}{2\zeta_p} = \frac{10^9}{41,667} = 24,000$$

(d) From eq (17.30)

$$\beta_w = 2\zeta_p = 41,667 \text{ rad/s}$$

$$\omega_1 = \omega_m - \frac{\beta_w}{2} = 1.00083 \times 10^6 - \frac{41,667}{2} = 979,996 \text{ rad/s}$$

$$\omega_2 = \omega_m + \frac{\beta_w}{2} = 1.00083 \times 10^6 + \frac{41,667}{2} = 1,021,663 \text{ rad/s}$$


$$(e) |V_{out}(j\omega_m)| = |I_w(j\omega_m)| H_m = (1)(24,000) = 24,000 \checkmark$$

Chapter 17/Problem 35

1

(a) Remove R_p from consideration

Fig
P17.32

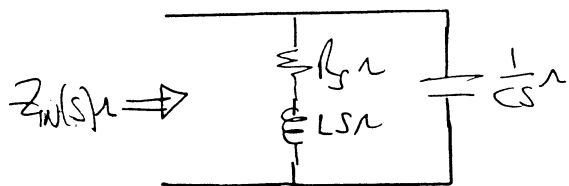

$$Y_{in}(s) = Cs + \frac{1}{Ls + R_s} = \frac{Lcs^2 + R_scs + 1}{Ls + R_s}$$

$$Z_{in}(s) = \frac{L(s + \frac{R_s}{L})}{LC(s^2 + \frac{R_s}{L}s + \frac{1}{LC})} = \frac{\frac{1}{C}(s + \frac{R_s}{L})}{s^2 + \frac{R_s}{L}s + \frac{1}{LC}}$$

Then

$$Z_{in}(j\omega) = \frac{\frac{1}{C}(\frac{R_s}{L} + j\omega)}{\frac{1}{LC} - \omega^2 + j\frac{R_s\omega}{L}}$$

With

$$A = \frac{1}{LC} - \omega^2$$

$$Z_{in}(j\omega) = \frac{\frac{1}{C}(\frac{R_s}{L} + j\omega)}{(A + j\frac{R_s\omega}{L})} \left[\frac{A - j\frac{R_s\omega}{L}}{A - j\frac{R_s\omega}{L}} \right]$$

$$\text{Im}[Z(j\omega)] = \frac{\omega A - \frac{1}{C}(\frac{R_s}{L})^2 \omega}{A^2 + (\frac{R_s}{L})^2}$$

With

$$\text{Im}[Z(j\omega)] = 0 = \frac{\omega_r}{C} \left(\frac{1}{LC} - \omega_r^2 \right) + \frac{1}{C} \left(\frac{R_s}{L} \right)^2 \omega_r = 0$$

$$\frac{1}{LC} - \omega_r^2 = \left(\frac{R_s}{L} \right)^2$$

$$\frac{1}{LC} = \frac{R_s^2}{L^2} + \omega_r^2$$

at $\omega_r = 2\pi \times 10^5$ rad/s

$$Q_{coil} = \frac{\omega_r L}{R_s} = \frac{2\pi \times 10^5 L}{R_s} = 40$$

$$\frac{R_s}{L} = \frac{2\pi \times 10^5}{40} = 1.571 \times 10^4$$

17/35 Cont'd

(2)

So that

$$\begin{aligned}\frac{1}{LC} &= \left(\frac{R_s}{L}\right)^2 + \omega^2 \\ &= (1.571 \times 10^4)^2 + (6.283 \times 10^5)^2 \\ &= 3.950 \times 10^{11}\end{aligned}$$

$$\frac{1}{C} = 3.950 \times 10^8$$

and

$$C = 2.531 \times 10^{-9} \quad (2.531 \text{ nF})$$

(b) With R_p back in the circuit, the transfer function is given in the problem statement of Problem 33. It is in the form

$$H(s) = \frac{\frac{1}{C} \left(s + \frac{R_s}{L}\right)}{s^2 + 2\zeta_p s + \omega_p^2}$$

For the bandwidth to be approximately $B_w = 20,000 \pi \text{ rad/s}$ and width

$$2\zeta_p = \frac{1}{R_p C} + \frac{R_s}{L}$$

then

$$20,000 \pi = \frac{1}{R_p C} + 1.571 \times 10^4$$

$$\begin{aligned}\frac{1}{R_p C} &= 6.283 \times 10^4 - 1.571 \times 10^4 \\ &= 47,122\end{aligned}$$

and

$$R_p = \frac{1}{47,122 C} = \frac{10^9}{47,122(2.531)} = 8385 \Omega$$

17/30 Cont'd

③

Then

$$Q_p = Q_{in} = \frac{W_m}{B_w} = \frac{2\pi(100,000)}{2\pi(10,000)} = 10$$

and this is high Q

Q 17/36

I am getting

$$Q_{cr} < 10$$

for the lower value of $C = 8.174 \text{ nF}$


Is it possible that

$L = 10 \mu\text{H}$ is erroneous?

Chapter 17 / Problem 36

A maximum $|V_{out}|$ occurs in the circuit

Fig
P17.36

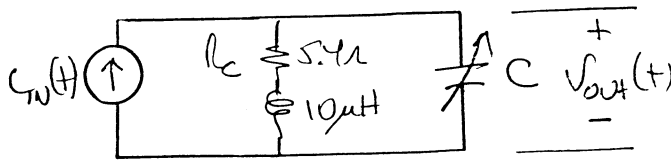

when, as shown in problem 35

$$\omega_r = \sqrt{\frac{1}{LC} - \left(\frac{R_c}{L}\right)^2} \approx C = \frac{1}{L \left[\left(\frac{R_c}{L}\right)^2 + \omega_r^2 \right]}$$

with

$$\frac{R_c}{L} = \frac{5.4}{10^{-5}} = 5.4 \times 10^5$$

$$C = \frac{10^5}{(2.916 \times 10^{11} + \omega_r^2)}$$

At $\omega_r = 1.1\pi \times 10^6 \text{ rad/s}$ (550 kHz) calling $C = C_0$

$$C_0 = \frac{10^5}{(1.1\pi \times 10^6)^2 + 2.916 \times 10^{11}} = \frac{10^5}{1.223 \times 10^{13}}$$

$$C_0 = 8.174 \times 10^{-9} \text{ F} \quad (8.174 \text{ nF})$$

At $\omega_r = 3.3\pi \times 10^6 \text{ rad/s}$ (1650 kHz) calling $C = C_1$

$$C_1 = \frac{10^5}{(3.3\pi \times 10^6)^2 + 2.916 \times 10^{11}} = \frac{10^5}{1.078 \times 10^{14}}$$

$$C_1 = 9.279 \times 10^{-10} \text{ F} \quad (92.789 \text{ nF})$$

The range

$$C_0 \leq C \leq C_1$$

is

$$8.174 \text{ nF} \leq C \leq 92.789 \text{ nF}$$

17/36 Cont'd

(2)

For the full circuit shown in Fig P17.36, the transfer function can be written as

$$H(s) = \frac{K(s+a)}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

and for high Q $\omega_m \approx \omega_p$ and $a \ll \omega_p$

Here

$$a = \frac{R_c}{L} = \frac{5.4}{10^{-5}} = 5.4 \times 10^5$$

$$2\zeta\omega_p = \frac{1}{RC} + \frac{R_c}{L} = \frac{1}{10,000C} + 5.4 \times 10^5$$

$$\omega_p^2 = \left(1 + \frac{R_c}{R}\right) \frac{1}{LC} = 1,000,054 \left(\frac{10^5}{C}\right) = \frac{100,0054}{C}$$

At $C = C_0$ (550 kHz)

$$\beta\omega = 2\zeta\omega_p = \frac{10^9}{10,000(8.174)} + 5.4 \times 10^5$$

$$= 1.224 \times 10^4 + 5.4 \times 10^5$$

$$= 5.522 \times 10^5 \text{ rad/s}$$

$$\omega_p = \sqrt{\frac{100,0054}{8.174 \times 10^{-9}}} = \sqrt{1.2241 \times 10^{13}} = 3.4986 \times 10^6 \text{ rad/s}$$

Note that with $\omega_m = 1.1\pi \times 10^5 = 3.416 \times 10^6 \text{ rad/s}$

$$\omega_m \approx \omega_p$$

With $\omega_m \approx \omega_p$

$$Q_{cir} = \frac{\omega_m}{2\zeta\omega_p} = \frac{3.498 \times 10^6}{5.522 \times 10^5} = 6.338$$

$$Q_{cir} < 10$$

Chapter 17 / Problem 37

①

(a)

$$I_L(s) = Y_{in}(s) V_{in}(s)$$

$$H(s) = Y_{in}(s) = \frac{V_{in}(s)}{I_L(s)}$$

Fig
P17.27

$$Z_{in}(s) = Ls + \frac{1}{Cs + \frac{1}{R}} = Ls + \frac{R}{RCs + 1} = \frac{RLCs^2 + Ls + R}{RCs + 1}$$

$$Z(s) = \frac{RLC(s^2 + \frac{1}{RC}s + \frac{1}{LC})}{RC(s + \frac{1}{RC})} = \frac{L(s^2 + \frac{1}{RC}s + \frac{1}{LC})}{s + \frac{1}{RC}}$$

$$H(s) = Y(s) = \frac{\frac{1}{L}(s + \frac{1}{RC})}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

This is in the form

$$H(s) = Y(s) = \frac{K(s+a)}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

(b) With the given circuit elements

$$a = \frac{1}{RC} = \frac{10^5}{2000} = 50$$

$$2\zeta\omega_p = 50$$

$$\zeta\omega_p = 25$$

$$\omega_p^2 = \frac{1}{LC} = 10^6$$

$$\omega_p = 1000 \text{ rad/s}$$

$$K = \frac{1}{L} = \frac{1}{0.1} = 10$$

$$Q_p = \frac{\omega_p}{2\zeta\omega_p} = \frac{1000}{50} = 20 > 10$$

This is indeed high Q. Moreover

$$a \ll \omega_p \quad (\zeta_0 < 1000)$$

17/37 Cont'd

(2)

$$\begin{aligned} (e) \quad \omega_m &= \sqrt{-a^2 + \sqrt{[\omega_p^2 + a^2]^2 - (2\zeta\omega_p a)^2}} \\ &= \sqrt{-2500 + \sqrt{(10^6 + 2500)^2 - (2500)^2}} \\ &= \sqrt{-2500 + \sqrt{1.0050 \times 10^{12} - 6.25 \times 10^6}} \\ &= \sqrt{-2500 + 1.002497 \times 10^6} = \sqrt{9.9999 \times 10^5} \\ \omega_m &= 999.99 \text{ rad/s} \approx \omega_p \end{aligned}$$

Thus

$$\zeta \omega_m = \frac{|K|}{2\zeta\omega_p} = \frac{10}{50} = 0.20$$

$$(d) \quad \beta_w \approx 2\zeta\omega_p = 50 \text{ rad/sec}$$

$$\omega_2 = \omega_m + \frac{\beta_w}{2} = 1000 + 25 = 1025 \text{ rad/s}$$

$$\omega_1 = \omega_m - \frac{\beta_w}{2} = 1000 - 25 = 975 \text{ rad/s}$$

Chapter 17 / Problem 38

(1)

(a) $H(s) = \frac{I_{out}(s)}{V_{in}(s)} = Y(s) = \frac{1}{Z(s)}$

Fig
P17.38

$$Z(s) = Ls + R_s + \frac{R_L}{\frac{1}{Cs}}$$

$$= Ls + R_s + \frac{R_L}{R_L + \frac{1}{Cs}} = \frac{RLCs^2 + (R_L R_s C + L)s + R_L + R_s}{R_L Cs + 1}$$

$$H(s) = Y(s) = \frac{\frac{1}{L}(s + \frac{1}{R_L C})}{s^2 + (\frac{1}{R_L C} + \frac{R_s}{L})s + \frac{1}{LC}(1 + \frac{R_s}{R_L})}$$

(b) With the circuit elements inserted

$$R_L C = 200(10 \times 10^{-6}) = 0.002$$

$$\frac{1}{R_L C} = \frac{1}{0.002} = 500 \quad \frac{R_s}{R_L} = \frac{0.5}{200} = 2.5 \times 10^{-3}$$

$$\frac{R_s}{L} = \frac{0.50}{0.001} = 500$$

$$\frac{1}{LC} = \frac{1}{0.001(10 \times 10^{-6})} = 10^8$$

$$\left(1 + \frac{R_s}{R_L}\right) \left(\frac{1}{LC}\right) = 1.0025 \times 10^8$$

and the transfer function becomes

$$H(s) = \frac{1000(s + 500)}{s^2 + 1000s + 1.0025 \times 10^8}$$

This is in the form

$$H(s) = \frac{K(s+a)}{s^2 + 2\zeta_p s + \omega_p^2}$$

and if $Q_{arc} \approx Q_p > 10$, the approximations of eqs (17.28) through (17.30) apply

$$Q_p = \frac{\omega_p}{2\zeta_p} = \frac{\sqrt{1.0025 \times 10^8}}{1000} = \frac{10012.5}{1000} = 10.01 > 10$$

17/38 Cont'd

(2)

Moreover

$$a = 500 \ll \omega_p = 10012.5$$

(c) For the exact value of ω_m , use eq (17.28)

$$\begin{aligned}\omega_m^2 &= -a^2 + \sqrt{(\omega_p^2 + a^2)^2 - (2\zeta\omega_p a)^2} \\ &= -2.5 \times 10^5 + \sqrt{(1.0025 \times 10^8 + 2.5 \times 10^5)^2 - [2(0.001)(500)]^2} \\ &= -2.5 \times 10^5 + \sqrt{1.0100 \times 10^{16} - 2.5 \times 10^{11}} \\ &= -2.5 \times 10^5 + \sqrt{1.0100 \times 10^{16}} \\ &= -2.5 \times 10^5 + 1.004988 \times 10^8 \\ \omega_m &= 1.002488 \times 10^8\end{aligned}$$

$$\omega_m = 10012.4 \text{ rad/s} \approx \omega_p = 10012.5 \text{ rad/s}$$

The maximum gain is

$$M_m = \frac{|K|}{2\zeta\omega_p} = \frac{1000}{1000} = 1.00$$

(d) $B_w = 2\zeta\omega_p = 1000 \text{ rad/s}$

$$\omega_1 = \omega_m - \frac{1000}{2} = 10012.4 - 500 = 9512.4 \text{ rad/s}$$

$$\omega_2 = \omega_m + \frac{1000}{2} = 10012.4 + 500 = 10512.4 \text{ rad/s}$$

Chapter 17/Problem 39

(a) Figure P17.39 is identical to Fig P17.38 with the exception that R_L in Fig P17.38 is R_p in Fig P17.39. The transfer function developed in Problem 38 is displayed in the statement of Problem 38.

Fig
P17.39

$$H(s) = Y(s) = \frac{\frac{1}{L} \left(s + \frac{1}{R_p C} \right)}{s^2 + \left(\frac{1}{R_p C} + \frac{R_s}{L} \right) s + \frac{1}{LC} \left(1 + \frac{R_s}{R_p} \right)}$$

With the circuit elements inserted

$$R_p C = 1600(0.00125) = 2$$

$$\frac{1}{R_p C} = 0.50$$

$$\frac{R_s}{L} = \frac{1}{0.5} = 2$$

$$\frac{1}{LC} = \frac{1}{0.5(0.00125)} = 1600$$

$$\frac{R_s}{R_p} = \frac{1}{1600} = 0.000625$$

$$\left(1 + \frac{R_s}{R_p} \right) \frac{1}{LC} = (1.000625) 1600 = 1601$$

and the transfer function becomes

$$H(s) = \frac{2(s + 0.50)}{s^2 + 2.5s + 1601}$$

This is in the form

$$H(s) = \frac{K(s + a)}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

Here

$$Q_p = \frac{\omega_p}{2\zeta\omega_p} = \frac{40.012}{2.5} = 16.005$$

This is high Q and

$$Q = 0.5 \ll \omega_p = 40.0012$$

Equation (17.28) through (17.30) apply

17/39 Cont'd

(2)

$$\begin{aligned}\omega_m^2 &= -a^2 + \sqrt{(\omega_p^2 + a^2) - (2\zeta pa)^2} \\ &= -0.25 + \sqrt{(1601 + 0.25)^2 - [2(2.5)(0.5)]^2} \\ &= -0.25 + \sqrt{2.564 \times 10^6 - 6.25} \\ &= -0.25 + 1601.25 = 1600 \\ \omega_m &= 40 \text{ rad/s} \approx \omega_p\end{aligned}$$

The maximum gain is

$$K = \frac{1/L}{2\zeta p} = \frac{2}{2.5} = 0.80$$

(d)

$$\begin{aligned}\beta_w &= 2\zeta p = 2.5 \text{ rad/s} \\ \omega_2 &= 40 + \frac{\beta_w}{2} = 40 + 1.25 = 41.25 \text{ rad/s} \\ \omega_1 &= 40 - \frac{\beta_w}{2} = 40 - 1.25 = 38.75 \text{ rad/s}\end{aligned}$$

(e) With $\omega_0 \approx \omega_p \approx \omega_m$

$$\begin{aligned}Q_{\text{cir}} &\approx \frac{\omega_0}{\frac{1}{R_p C} + \frac{R_s}{L}} \\ \frac{1}{Q_{\text{cir}}} &\approx \frac{R_s}{\omega_0 L} + \frac{1}{R_p C \omega_0} = \frac{1}{Q_{\text{coil}}} + \frac{1}{Q_{\text{cap}}} \\ &\approx \frac{Q_{\text{cap}} + Q_{\text{coil}}}{Q_{\text{cap}} Q_{\text{coil}}}\end{aligned}$$

and finally

$$Q_{\text{cir}} \approx \frac{Q_{\text{cap}} Q_{\text{coil}}}{Q_{\text{cap}} + Q_{\text{coil}}}$$

Chapter 17/Problem 10

①

Fig
P17.10

(a)

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} = Z(s) = \frac{1}{Y(s)}$$

$$Y(s) = \frac{1}{Ls + R_s} + Cs + \frac{1}{R_p}$$

$$= \frac{1}{Ls + R_s} + \frac{R_p Cs + 1}{R_p}$$

$$= \frac{R_p L Cs^2 + (L + R_p R_s C)s + R_s + R_p}{R_p (Ls + R_s)}$$

$$Z(s) = \frac{\frac{1}{C} \left(s + \frac{R_s}{L} \right)}{s^2 + \left(\frac{1}{R_p C} + \frac{R_s}{L} \right) s + \frac{1}{LC} \left(1 + \frac{R_s R_p}{L} \right)}$$

With circuit elements inserted

$$\frac{R_s}{L} = \frac{2/3}{0.0005} = 1.333 \times 10^3$$

$$\frac{1}{R_p C} = \frac{10^6}{1200(1.25)} = 6.667 \times 10^2$$

$$\frac{R_s}{R_p} = \frac{2/3}{1200} = 5.556 \times 10^{-4}$$

$$\frac{1}{LC} = \frac{10^6}{5 \times 10^{-7}(1.25)} = 1.600 \times 10^9$$

Then

$$H(s) = \frac{8 \times 10^5 (s + 1.333 \times 10^3)}{s^2 + 2000s + 1.60089 \times 10^9}$$

and this is in the form

$$H(s) = \frac{K(s+a)}{s^2 + 2\zeta\omega_p + \omega_p^2}$$

17/40 Cont'd

(2)

$$(b) Q_p = \frac{\omega_p}{2\zeta_p} = \frac{\sqrt{1.60089 \times 10^9}}{2000} = 20.01 > 10$$

This is a high Q circuit and

$$a = 1333 \ll \omega_p = 40011$$

(c) The exact value of ω_m derives from eq (17.20)

$$\begin{aligned}\omega_m^2 &= -a^2 + \sqrt{(\omega_p^2 + a^2)^2 - (2\zeta_p a)^2} \\ &= -1.777 \times 10^6 + \sqrt{(1.60089 \times 10^9 + 1.777 \times 10^6)^2 - (2.667 \times 10^6)^2} \\ &= -1.777 \times 10^6 + \sqrt{2.569 \times 10^{18} - 7.108 \times 10^{12}} \\ &= -1.777 \times 10^6 + \sqrt{2.569 \times 10^{18}} \\ &= -1.777 \times 10^6 + 1.603 \times 10^9 \\ &= 1.601 \times 10^9\end{aligned}$$

$$\begin{aligned}\omega_m &= 4.0011 \times 10^4 \text{ rad/s} \approx \omega_p = 4.0011 \times 10^4 \\ &(40011.10 \approx 40011.12)\end{aligned}$$

Hence $\omega_m = 40011 \text{ rad/s}$ and

$$H = \frac{K}{2\zeta_p} = \frac{8 \times 10^5}{2000} = 400 \Omega$$

$$(d) B_w \approx 2\zeta_p = 2000 \text{ rad/s}$$

$$\omega_2 = \omega_m + \frac{B_w}{2} = 40,011 + 1000 = 41,011 \text{ rad/s}$$

$$\omega_1 = \omega_m - \frac{B_w}{2} = 40,011 - 1000 = 39,011 \text{ rad/s}$$

17/40 Cont'd

$$Q_{ur} = Q_p = \frac{\frac{1}{L} \sqrt{1 + \frac{R_p}{R_s}}}{\left(\frac{R_s}{L} + \frac{1}{R_p C}\right)} \approx \frac{\omega_0}{\left(\frac{R_s}{L} + \frac{1}{R_p C}\right)}$$

$$\begin{aligned} \frac{1}{Q_{ur}} &\approx \frac{\frac{R_s}{L} + \frac{1}{R_p C}}{\omega_0} = \frac{R_s}{L \omega_0} + \frac{1}{R_p C \omega_0} \\ &= \frac{1}{Q_{coil}} + \frac{1}{Q_{cap}} = \frac{Q_{coil} + Q_{cap}}{Q_{coil} Q_{cap}} \end{aligned}$$

Thus

$$Q_{ur} = Q_p \approx \frac{Q_{coil} Q_{cap}}{Q_{coil} + Q_{cap}}$$

Chapter 17 / Problem 41

Fig
P17.41

(a) $Q = \frac{f_r}{B_f} = \frac{1600}{80} = 20$ (high Q)

(b) $Y(s) = Cs + \frac{1}{Ls + R} = \frac{LCs^2 + RCs + 1}{Ls + R} = \frac{C(s^2 + \frac{R}{L}s + \frac{1}{LC})}{s + \frac{R}{L}}$

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} = \frac{\frac{1}{L}(s + \frac{R}{L})}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

This is in the form

$$H(s) = \frac{K(s+a)}{s^2 + 2\zeta\omega_p + \omega_p^2}$$

(c) Because the circuit is high Q

$$\omega_p \approx \omega_n \approx \omega_0$$

$$\frac{1}{LC} = \omega_r^2$$

$$\frac{1}{LC} = (3200\pi)^2$$

$$L = \frac{1}{(3200\pi)^2 C}$$

and with $C = 1 \times 10^{-6} \text{ F}$

$$L = \frac{10^6}{(1.0126 \times 10^8)^2} = 9.89 \times 10^{-3} \text{ (9.89 mH)}$$

$$B'_w = 2\zeta\omega_p = \frac{R}{L} = 160\pi = 502.65$$

$$R = (502.65)(9.89 \times 10^{-3}) = 4.97 \Omega$$

Chapter 17/Problem 42

1

Fig
P17.42

(a) $H(s) = \frac{V_{out}}{V_{in}}$

By voltage division

$$Y_p(s) = Cs + \frac{1}{Ls+R} = \frac{Lcs^2 + Rcs + 1}{Ls+R}$$

$$Z_p(s) = \frac{1}{Y_p(s)} = \frac{Ls+R}{Lcs^2 + Rcs + 1}$$

$$Z_T(s) = R_s + \frac{Ls+R}{Lcs^2 + Rcs + 1} = \frac{R_s Lcs^2 + (R_s R + L)s + R_s + R}{Lcs^2 + Rcs + 1}$$

$$H(s) = \frac{Z_p(s)}{Z_T(s)} = \frac{Ls+R}{R_s Lcs^2 + (R_s R + L)s + R_s + R} = \frac{\frac{1}{R_s C} (s + \frac{R}{L})}{s^2 + (\frac{R}{L} + \frac{1}{R_s C})s + (1 + \frac{R}{R_s}) \frac{1}{LC}}$$

(b) First insert the given element values

$$R_s C = \frac{5}{3}$$

$$\frac{1}{LC} = 1$$

$$\frac{1}{R_s C} = \frac{3}{5} = 0.6$$

$$\frac{R}{R_s} = \frac{4/5}{5/3} = 0.48$$

$$\frac{R}{L} = 0.8$$

$$\frac{R}{L} + \frac{1}{R_s C} = 0.8 + 0.6 = 1.4$$

$$H(s) = \frac{0.6(s+0.8)}{s^2 + 1.4s + 1.48}$$

(c) $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{1} = 1 \text{ rad/s}$

(d) Consider only R, L and C and observe that the circuit is identical to the one in Example 17.3.

Equation 17.4 gives

$$\omega_r = \omega_0 \sqrt{1 - \frac{CR^2}{L}} = 1 \sqrt{1 - \frac{1(0.8)^2}{1}}$$

$$= 1 \sqrt{1 - 0.64} = 1 \sqrt{0.36} = 0.6 \text{ rad/s}$$

17/42 Cont'd

(2)

Alternatively, a resonance for $Z_p(j\omega)$ will produce a resonance for the entire circuit. With $RC = 0.8$

$$Z_p(s) = \frac{s + 0.8}{s^2 + 0.8s + 1}$$

$$\begin{aligned} Z(j\omega) &= \frac{0.8 + j\omega}{1 - \omega^2 + j0.8\omega} \frac{(1 - \omega^2) - j0.8\omega}{(1 - \omega^2) - j0.8\omega} \\ &= \frac{(0.8 + j\omega)[(1 - \omega^2) - j0.8\omega]}{(1 - \omega^2)^2 + 0.64\omega^2} \end{aligned}$$

Set $\text{Im}[Z(j\omega)] = 0$

$$\omega(1 - \omega^2) - 0.64\omega = 0$$

$$1 - \omega^2 = 0.64$$

$$\omega^2 = 0.36$$

$$\omega = 0.60 \text{ rad/s}$$

(c)

$$H(j\omega) = \frac{0.60(0.80 + j\omega)}{1.48 - \omega^2 + j1.4\omega}$$

$$|H(j\omega)| = \frac{0.60\sqrt{\omega^2 + 0.64}}{\sqrt{(1.48 - \omega^2)^2 + 1.96\omega^2}}$$

with $z = \omega^2$

$$|H(j\omega)|^2 = \frac{0.36(z + 0.64)}{(1.48 - z)^2 + 1.96z}$$

$$= \frac{0.36(z + 0.64)}{z^2 - z + 2.1904}$$

To find z_{\max} (or z_{\min})

$$d\{|H(j\omega)|^2\} = \frac{0.36(z^2 - z + 2.1904) - 0.36(z + 0.64)(2z - 1)}{z^2 - z + 2.1904} =$$

17/42 Cont'd

(3)

$$\dots (z^2 - z + 2.1904) - (z + 0.64)(2z - 1) = 0$$

$$z^2 - z + 2.1904 = 0$$

Solving

$$\omega_r^2 = z = 1.1600$$

$$\omega_r = \sqrt{1.1600} = 1.077 \text{ rad/s}$$

(iv)

$$\omega_p = \sqrt{\left(1 + \frac{R}{R_S}\right) \frac{1}{LC}} = \sqrt{(1 + 0.48)} = \sqrt{1.48} = 1.2166 \text{ rad/s}$$

17.43

Everything fine except for
 ω_r

Test set $\omega_r = 0.9802 \text{ rad/s}$

We get $\omega_r = 0.9220 \text{ rad/s}$

Chapter 17/Problem 43

①

(a) In a demonstration that

$$H(s) = \frac{\frac{1}{C} \left(s + \frac{R_s}{L} \right)}{s^2 + \left(\frac{1}{R_p C} + \frac{R_s}{L} \right) s + \left(1 + \frac{R_s}{R_p} \right) \frac{1}{LC}}$$

Fig
P17.43

see the solution to Problem 32.

(b) With the given circuit elements

$$R_p C = 10 \qquad \frac{1}{LC} = 1$$

$$\frac{1}{R_p C} = 0.10 \qquad \frac{R_s}{R_p} = \frac{0.8}{10} = 0.08$$

$$\frac{R_s}{L} = 0.80 \qquad \frac{1}{R_p C} + \frac{R_s}{L} = 0.10 + 0.80 = 0.90$$

$$H(s) = \frac{s + 0.80}{s^2 + 0.9s + 1.08} = \frac{s + a}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

$$\omega_0 = \frac{1}{LC} = 1 \text{ rad/s} \leftarrow$$

$$\omega_p = \sqrt{1.08} = 1.0392 \text{ rad/s} \leftarrow$$

$$\omega_d = \sqrt{\omega_p^2 - \zeta^2} = \sqrt{1.08 - (0.45)^2} = \sqrt{1.08 - 0.2025}$$

$$\omega_d = \sqrt{0.8775} = 0.9367 \text{ rad/s} \leftarrow$$

For ω_r , observe that the circuit is resistive when the parallel portion of the circuit is at its ω_r . Using eq (17.4) gives

$$\begin{aligned} \omega_r &= \omega_0 \sqrt{1 - \frac{C R_s^2}{L}} = 1 \sqrt{1 - \frac{(0.8)^2}{1}} \\ &= \sqrt{1 - 0.64} = \sqrt{0.36} = 0.60 \text{ rad/s} \end{aligned}$$

17/43 Cont'd

2

$$H(j\omega) = \frac{0.80 + j\omega}{1.08 - \omega^2 + j0.9\omega}$$

$$|H(j\omega)| = \frac{\sqrt{\omega^2 + 0.64}}{\sqrt{(1.08 - \omega^2)^2 + 0.81\omega^2}}$$

with $z = \omega^2$

$$|H(j\omega)|^2 = \frac{z + 0.64}{z^2 - 2.16z + 1.1664 + 0.81z} = \frac{z + 0.64}{z^2 - 1.35z + 1.1664}$$

To find $|H(j\omega)|^2$ max or min, take

$$\frac{d\{|H(j\omega)|^2\}}{dz} = \frac{(z^2 - 1.35z + 1.1664) \cdot 1 - (z + 0.64)(2z - 1.35)}{(z^2 - 1.35z + 1.1664)^2} = 0$$

$$z^2 + 1.28z - 2.0304 = 0$$

Solving

$$\omega_r^2 = z = 1.8441$$

$$\omega_r = 0.9220 \text{ rad/s}$$

Chapter 17/Problem 44

(1)

In the circuit in Fig P.17.43, the transfer function, developed in Problem 32 is

$$H(s) = \frac{\frac{1}{C}(s + \frac{R_p}{L})}{s^2 + (\frac{1}{R_p C} + \frac{R_p}{L})s + (1 + \frac{R_p}{R_p})\frac{1}{LC}}$$

With the circuit element (without the value of C) given in Problem 17.43

$$H(s) = \frac{\frac{1}{C}(s + 0.80)}{s^2 + (\frac{0.1}{C} + 0.80)s + \frac{1.08}{C}}$$

Multiplication by C throughout gives

$$H(s) = \frac{s + 0.80}{Cs^2 + (0.80C + 0.10)s + 1.08}$$

With $i_{in}(t) = 2 \cos t$, it is observed that

$$|I_{in}| = 2A \text{ and } \omega = 1 \text{ rad/s}$$

Thus

$$|V_{out}| = |H(j\omega)| |I_{in}| = 2 |H(j\omega)|$$

With $\omega = 1 \text{ rad/s}$

$$H(j\omega) = \frac{\sqrt{0.80 + j}}{\sqrt{(1.08 - C)^2 + (0.80C + 0.10)^2}}$$

and

$$\begin{aligned} |H(j\omega)|^2 &= \frac{1.64}{(1.08 - C)^2 + (0.80C + 0.10)^2} \\ &= \frac{1}{C^2 - 1.2195C + 0.7113} \end{aligned}$$

17/44 Cont'd

(2)

$|H(j\omega)|$ can be maximized by minimizing

$$P(c) = c^2 - 1.2195c + 0.7113$$

$$\frac{dP(c)}{dc} = 2c - 1.2195 = 0$$

$$2c = 1.2195$$

$$c = 0.6098 \text{ F}$$

17/45

$$\text{dB } R = 50 \Omega \quad Z_{sp} = 500$$

$$Q_p = \frac{1000}{500} = 2$$

This is not high Q_p

I made $R = 5 \Omega$ so that

$$Z_{sp} = 50$$

and $Q_p = 20$

Chapter 17 / Problem 45

①

(a) By voltage division

Fig
P17.45

$$H(s) = \frac{V_e(s)}{V_f(s)} = \frac{\frac{1}{Cs}}{Ls + R + \frac{1}{Cs}} = \frac{1}{LCs^2 + RCs + 1}$$

$$H(s) = \frac{Kc}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

(b) with the given circuit elements inserted

$$\frac{R}{L} = \frac{5}{0.1} = 50$$

$$\frac{1}{LC} = \frac{10^6}{0.1(10)} = 10^6$$

$$H(s) = \frac{10^6}{s^2 + 50s + 10^6}$$

In the form

$$H(s) = \frac{K}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

$$K = 10^6$$

$$2\zeta\omega_p = 50$$

and

$$\omega_p^2 = 10^6$$

$$Q_p = \frac{\omega_p}{2\zeta\omega_p} = \frac{\sqrt{10^6}}{50} = \frac{1000}{50} = 20 > 10 \text{ (high } Q)$$

(c) By eq (17.34)

$$\omega_m = \omega_p \sqrt{1 - \frac{1}{2Q_p^2}} = 1000 \sqrt{1 - \frac{1}{2(20)^2}} = 1000 \sqrt{1 - 0.00125} = 1000 \sqrt{0.99875}$$

$$= 1000(0.9994) = 999.4$$

$$\omega_m \approx \omega_p$$

$$H_m = \frac{|K|}{2\zeta\omega_p} = \frac{10^6}{50} = 20,000$$

17/46 Cont'd

(2)

(d) $\beta\omega = 2\zeta\omega_p = 50 \text{ rad/sec}$.

$$\omega_2 = \omega_p + \zeta\omega_p = 1000 + 25 = 1025 \text{ rad/s}$$


$$\omega_1 = \omega_p - \zeta\omega_p = 1000 - 25 = 975 \text{ rad/s}$$

Chapter 17 / Problem 46

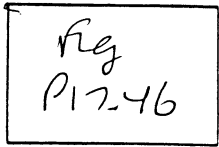(a) By current division

$$H(s) = \frac{I_L(s)}{I_w(s)} = \frac{\frac{1}{s}}{Cs + \frac{1}{R} + \frac{1}{s}} = \frac{\frac{1}{s}}{\frac{RLCs^2 + Ls + R}{s}}$$

$$H(s) = \frac{\frac{1}{RC}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$



which is in the form

$$H(s) = \frac{K}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

(b) With the network elements inserted

$$RC = 4000(10 \times 10^{-6}) = 0.04$$

$$\frac{1}{RC} = 25 = 2\zeta\omega_p$$

$$\omega_p^2 = \frac{1}{LC} = \frac{10^6}{0.1(10)} = 10^6$$

$$\omega_p = 1000 \text{ rad/s}$$

$$Q_p = \frac{\omega_p}{2\zeta\omega_p} = \frac{1000}{25} = 40 > 10 \text{ (This is high } Q)$$

$$K = 10^6$$

(c) By eq (17.34)

$$\omega_m = \omega_p \sqrt{1 - \frac{1}{2(Q_p)^2}} = 1000 \sqrt{1 - \frac{1}{3200}}$$

$$= 1000 \sqrt{1 - 3.125 \times 10^{-4}} = 1000 \sqrt{0.9969 \times 10^{-1}}$$

$$= 1000(0.9998) = 999.8$$

$$\omega_m \approx \omega_p$$

$$\omega_m = \frac{|K|}{2\zeta\omega_p} = \frac{10^6}{25} = 40,000$$

(d)

$$B\omega = 2\zeta\omega_p = 25 \text{ rad/s}$$

$$\omega_2 = \omega_p + \zeta\omega_p = 1000 + 12.5 = 1012.5 \text{ rad/s}$$

$$\omega_1 = \omega_p - \zeta\omega_p = 1000 - 12.5 = 987.5 \text{ rad/s}$$

Chapter 17 / Problem 47

①

(a) With the given circuit elements inserted,

Fig
P17.47

$$R_1 R_2 C_1 C_2 = (50,000)(0.2 \times 10^{-6})(0.5 \times 10^{-9}) \\ = 2.500 \times 10^{-7}$$

$$\frac{1}{R_1 R_2 C_1 C_2} = 4 \times 10^6$$

$$\frac{1}{R_1 C_1} = \frac{10^6}{(0.2)(50,000)} = 100$$

$$\frac{1}{R_2 C_1} = 100$$

$$\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} = 2(100) = 200$$

Hence

$$H(s) = \frac{4 \times 10^6}{s^2 + 200s + 4 \times 10^6}$$

and in the form

$$H(s) = \frac{K}{s^2 + 2\zeta\omega_p s + \omega_p^2}$$

Hence

$$K = 4 \times 10^6 \leftarrow$$

$$2\zeta\omega_p = 200$$

$$\omega_p^2 = 4 \times 10^6$$

$$\omega_p = 2000 \leftarrow$$

(b)

$$Q_p = \frac{\omega_p}{2\zeta\omega_p} = \frac{2000}{200} = 10 \leftarrow$$

(c) By eq (17.34)

$$\omega_m = \omega_p \sqrt{1 - \frac{1}{2(Q_p)^2}} = 2000 \sqrt{1 - \frac{1}{200}} = 2000 \sqrt{0.995}$$

$$\omega_m = 2000(0.9975) = 1995$$

$$H_m = \frac{|K|}{2\zeta\omega_p} = \frac{4 \times 10^6}{200} = 20,000$$

17/47 Cont'd

(2)

(d)

$$BW = 2\sigma_p = 200 \text{ rad/s}$$

$$\omega_2 = \omega_p + \sigma_p = 1995 + 100 = 2095 \text{ rad/s}$$

$$\omega_1 = \omega_p - \sigma_p = 1995 - 100 = 1895 \text{ rad/s}$$

Chapter 17 / Problem 50

(a) By voltage division

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{R}{sL + R + \frac{1}{Cs}} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L} + \frac{1}{LC}}$$

Fig
P17.50

Using the given circuit elements

$$H(s) = \frac{0.15}{s^2 + 0.15 + \frac{1}{4}}$$

(b) To obtain $R = 50$, make

$$K_m = \frac{50}{0.05} = 1000$$

$$K_f = \frac{1600\pi}{\frac{1}{\sqrt{LC}}} = \frac{3200\pi}{\frac{1}{2}} = 6400\pi$$

(c) new values, denoted by subscript n

$$R_n = 50 \Omega$$

$$L_n = \frac{K_m}{K_f} (0.5) = \frac{1000}{6400\pi} (0.5) = 0.0249 \text{ H}$$

$$C_n = \frac{1}{K_m K_f} C = \frac{8 \text{ F}}{6.4 \times 10^6 \pi} = 0.3979 \mu\text{F}$$

This make

$$H(s) = \frac{2010.65}{s^2 + 2010.65s + 1.0106 \times 10^8}$$

Notice that the center frequency is

$$f_c = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} = \frac{1}{2\pi} \sqrt{1.0106 \times 10^8} = 1600 \text{ Hz}$$

17/50 Cont'd

(2)

(d) With

$$H(s) = \frac{0.1s}{s^2 + 0.1s + 0.25}$$

and pole-zero location

$$z = 0$$

$$p_1, p_2 = -0.05 \pm j0.4975$$

the new pole locations will be

$$K_f(p_1, p_2) = 6400\pi (-0.05 \pm j0.4975) \\ = -1005.3 \pm j10002.7$$

Now check the poles of the new $H(s)$

$$H(s) = \frac{2010.6s}{s^2 + 2010.6s + 1.0106 \times 10^8}$$

$$= \frac{2010.6s}{(s + 1005.3 + j10002.7)(s + 1005.3 - j10002.7)}$$

and notice that the new magnitude is

$$2010.6 = K_f(0.1) \\ = 0.1(6400\pi) \\ = 640\pi \\ = 2010.6$$

Chapter 17 / Problem 51

①

$$(a) \quad z(s) = \frac{K}{(s-p_1)(s-p_2)} = \frac{K_m K}{\left(\frac{s}{K_f} - p_1\right)\left(\frac{s}{K_f} - p_2\right)} = \frac{K_m K_f^2 K}{(s - K_f p_1)(s - K_f p_2)}$$

The new pole locations are
 $K_f p_1$ and $K_f p_2$

The new gain constant is
 $K_m K_f^2 K$

The new impedance function is

$$z(s) = \frac{K_m K_f^2 K}{(s - K_f p_1)(s - K_f p_2)}$$

$$(b) \quad z(s) = K \frac{s - z_1}{(s-p_1)(s-p_2)} = \frac{K_m K_f (s - K_f z_1)}{(s - K_f p_1)(s - K_f p_2)}$$

The new pole locations are
 $K_f p_1$ and $K_f p_2$

The new zero location is
 $K_f z_1$

The new gain constant is
 $K_m K_f K$

The new impedance function is

$$z(s) = \frac{K_m K_f (s - K_f z_1)}{(s - K_f p_1)(s - K_f p_2)}$$

12/51 Cont'd

(2)

$$(c) \quad z(s) = K \frac{(s-z_1)(s-z_2)}{(s-p_1)(s-p_2)}$$

The new pole locations are

$$K+p_1 \text{ and } K+p_2$$

The new zero locations are

$$K+z_1 \text{ and } K+z_2$$

The new gain constant is

$$K_n K$$

The new impedance function is

$$z(s) = K_n K \frac{(s-K+z_1)(s-K+z_2)}{(s-K+p_1)(s-K+p_2)}$$

Chapter 17/Problem 52

(a)
$$Y(s) = \frac{60}{(s+5)(s+6)}$$

$$K_f = 2000\pi$$

$$K_M = 20$$

New poles are at

$$p_1 = 10,000\pi \text{ and } p_2 = 12,000\pi$$

The new gain constant is

$$\frac{K_f^2}{K_M} (60) = \frac{(2000\pi)^2}{20} = 120\pi^2 \times 10^5$$

The new admittance function is

$$Y(s) = \frac{120\pi^2 \times 10^5}{(s+10,000\pi)(s+12,000\pi)}$$

(b)
$$Y(s) = 120 \frac{s+1}{(s+5)(s+6)}$$

New poles are at

$$p_1 = 10,000\pi \text{ and } p_2 = 12,000\pi$$

New zeros are at

$$z_1 = 2000\pi$$

The new gain constant is

$$\frac{K_f}{K_M} (120) = 1.2\pi \times 10^4$$

The new admittance function is

$$Y(s) = \frac{1.2\pi \times 10^4 (s+2000\pi)}{(s+10,000\pi)(s+12,000\pi)}$$

Chapter 17/Problem 52 Cont'd

(2)

(c)
$$Y(s) = 120 \frac{(s+2)(s+5)}{(s+1)(s+10)}$$

New poles are at

$$p_1 = 8000\pi \quad \text{and} \quad p_2 = 20,000\pi$$

New zeroes are at

$$z_1 = 4000\pi \quad \text{and} \quad z_2 = 10,000\pi$$

The new gain constant is

$$\frac{120}{K_M} = \frac{120}{20} = 6$$

The new admittance function is

$$Y(s) = 6 \frac{(s+4000\pi)(s+10,000\pi)}{(s+8000\pi)(s+20,000\pi)}$$

(d)

$$Y(s) = \frac{s^2 - 4s + 8}{s^2 + 4s + 8} = \frac{(s+2+j2)(s+2-j2)}{(s-2+j2)(s-2-j2)}$$

New poles are at

$$p_1 = +4000\pi - j4000\pi \quad \text{and} \quad p_2 = 4000\pi + j4000\pi$$

New zeroes are at

$$z_1 = -4000\pi - j4000\pi \quad \text{and} \quad z_2 = -4000\pi + j4000\pi$$

The new gain constant is

$$\frac{1}{K_M} = \frac{1}{20}$$

The new admittance function is

$$Y(s) = \frac{1}{20} \left(\frac{s^2 - 4s + 8}{s^2 + 4s + 8} \right)$$

Chapter 17 / Problem 54

Because each $H(s)$ is a voltage ratio, the magnitude ratio, K_M , has no effect. With K_f as the frequency ratio

$$(a) \quad H(s) = \frac{K_f^3 k}{(s - K_f p_1)(s - K_f p_2)(s - K_f p_3)}$$

$$(b) \quad H(s) = \frac{K_f^2 k (s - K_f z_1)}{(s - K_f p_1)(s - K_f p_2)(s - K_f p_3)}$$

$$(c) \quad H(s) = \frac{K_f k (s - K_f z_1)(s - K_f z_2)}{(s - K_f p_1)(s - K_f p_2)(s - K_f p_3)}$$