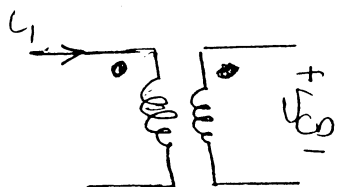


Chapter 18/Problem 1


Because $i_1(t) = 2t u(t)$ with positive current at point -A, then, because v_{C0} is $20 u(t)$, the dots are placed at point -A and -C

Fig
P.19.1



$$M = M_{21} = \frac{|v_2(t)|}{\left| \frac{di_1}{dt} \right|} = \frac{20}{2} = 10 \text{ H}$$

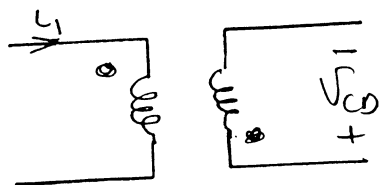When v_{C0} is $-20 u(t)$, then the dots on coil-2 are reversed to appear at point -A and -B



$$M = M_{21} = \frac{|v_2(t)|}{\left| \frac{di_1}{dt} \right|} = \frac{20}{2} = 10 \text{ H}$$

Chapter 18/Problem 2

The waveform can be broken into components

$$i_1 = -2t \text{ A}; \quad v_2(t) = 4 \text{ V} \quad 0 < t < \frac{1}{2}$$

$$i_1 = 2t \text{ A}; \quad v_2(t) = -4 \text{ V} \quad \frac{1}{2} < t < \frac{3}{2}$$

$$i_1 = -2t \text{ A}; \quad v_2(t) = 4 \text{ V} \quad \frac{3}{2} < t < \frac{5}{2}$$

Fig
P18.2a

Fig
P18.2b

Fig
P18.2c

(a) The opposite polarity of $i_1(t)$ and $v_2(t)$ indicated here shows that the dots should be placed at terminals -A and -D (or terminal -B and -C)

$$v_2(t) = M \frac{di_1}{dt}$$

$$4 = M(-2)$$

$$M = \frac{4}{-2} = -2 \text{ H}$$

(b) $i_1(t) = 2(1 - e^{-100t})u(t) \text{ A}$

$$v_2(t) = -M \frac{di_1}{dt}$$

$$= -M \frac{d}{dt} [2(1 - e^{-100t})]$$

$$= -2(200e^{-100t})$$

$$= -400e^{-100t}u(t) \text{ V}$$

Chapter 18/Problem 3

(a)

(i) For the dots at points -A and -C

$$v_2(t) = M \frac{d\dot{y}}{dt}$$

(ii) For the dots at points -A and -D

$$v_2(t) = -M \frac{d\dot{y}}{dt}$$

(iii) For the dots at points -B and -C

$$v_2(t) = -M \frac{d\dot{y}}{dt}$$

(iv) For the dot at point -B and -D

$$v_2(t) = M \frac{d\dot{y}}{dt}$$

(b) The foregoing development constitutes the sought after verification

Fig
P18.3

Chapter 18/Problem 4

(a)

For Fig P18.4a

$$v_x = 2i_a + 4 \frac{di_a}{dt} + 2 \frac{di_b}{dt}$$

$$v_y = 3 \frac{di_b}{dt} + 2 \frac{di_a}{dt}$$

For Fig P18.4b

$$v_x = R_1 i_a + L_1 \frac{di_a}{dt} - M \frac{di_b}{dt}$$

$$v_y = L_2 \frac{di_b}{dt} - M \frac{di_a}{dt}$$

Fig
P18.4a

Fig
P18.4b

(b) For Fig P18.4a

$$V_x(s) = (4s + 2)I_a(s) + 2sI_b(s) + 4i_a(0^+) + 2i_b(0^+)$$

$$V_y(s) = 3sI_b(s) + 2sI_a(s) + 3i_b(0^+) + 2i_a(0^+)$$

For Fig P18.4b

$$V_x(s) = (L_1 s + R_1)I_a(s) - MsI_b(s) + L_1 i_a(0^+) - M i_b(0^+)$$

$$V_y(s) = L_2 s I_b(s) - Ms I_a(s) + L_2 i_b(0^+) - M i_a(0^+)$$

Chapter 18 / Problem 5

(a) For Fig P18.5a

$$v_x = 2i_a + 4 \frac{di_a}{dt} - 2 \frac{di_b}{dt}$$

$$v_y = 3 \frac{di_b}{dt} - 2 \frac{di_a}{dt}$$

Fig
P18.5a

Fig
P18.5b

For Fig P18.5b

$$v_x = R_1 i_a + L_1 \frac{di_a}{dt} + M \frac{di_b}{dt}$$

$$v_y = L_2 \frac{di_b}{dt} + M \frac{di_a}{dt}$$

(b) For Fig P18.5a

$$v_x(s) = 2I_a(s) + 4sI_a(s) - 2sI_b(s) + 4i_a(0^-) - 2i_b(0^-)$$

$$v_y(s) = 3sI_b(s) - 2sI_a(s) + 3i_b(0^-) - 2i_a(0^-)$$

For Fig P18.5b

$$v_x(s) = (L_1 s + R_1)I_a(s) + MsI_b(s) + L_1 i_a(0^-) + M i_b(0^-)$$

$$v_y(s) = L_2 s I_b(s) + Ms I_a(s) + L_2 i_b(0^-) + M i_a(0^-)$$

Chapter 18/Problem 6

Fig
P18.6

Write by inspection

$$l_a - i_b + 2\left(\frac{di_a}{dt} - \frac{di_b}{dt}\right) - \frac{di_c}{dt} = v_w(t)$$

$$2\left(\frac{di_b}{dt} - \frac{di_a}{dt}\right) + \frac{di_c}{dt} + i_b - i_c + i_b = 0$$

$$l_c - l_a + l_c - i_b + 2\frac{di_c}{dt} + \frac{di_b}{dt} - \frac{di_a}{dt} = 0$$

or

$$l_a + 2\frac{di_a}{dt} - i_b - 2\frac{di_b}{dt} - \frac{di_c}{dt} = v_w(t)$$

$$-2\frac{di_a}{dt} + 2i_b + 2\frac{di_b}{dt} - i_c + \frac{di_c}{dt} = 0$$

$$-i_a - \frac{di_a}{dt} - i_b + \frac{di_b}{dt} + 2i_c + 2\frac{di_c}{dt} = 0$$

Chapter 18/Problem 7

For Fig P18.7a

$$V = 3 \frac{di}{dt} + 2.5 \frac{di}{dt} + 5 \frac{di}{dt} + 2.5 \frac{di}{dt}$$

with

$$V = L_{eq} \frac{di}{dt}$$

observe that

$$L_{eq} = 3 + 2.5 + 5 + 2.5 = 13H$$

For Fig P18.7b

$$V = 3 \frac{di}{dt} - 2.5 \frac{di}{dt} + 5 \frac{di}{dt} - 2.5 \frac{di}{dt}$$

with

$$V = L_{eq} \frac{di}{dt}$$

then

$$L_{eq} = 3 - 2.5 + 5 - 2.5 = 3H$$

Fig
P18.7a

Fig
P18.7b

Chapter 18/Problem 8

For Fig P18.8a

$$V_{in}(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$0 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

From the second

$$\frac{di_2}{dt} = -\frac{M}{L_2} \frac{di_1}{dt}$$

and with this in the first

$$V_{in}(t) = L_{eq} \frac{di_1}{dt} = \left(L_1 - \frac{M^2}{L_2} \right) \frac{di_1}{dt}$$

$$L_{eq} = L_1 - \frac{M^2}{L_2}$$

For Fig P18.8b

$$V_{in}(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$0 = (L_2 + L_3) \frac{di_2}{dt} + M \frac{di_1}{dt}$$

From the second

$$\frac{di_2}{dt} = -\frac{M}{L_2 + L_3} \frac{di_1}{dt}$$

and with this in the first

$$V_{in}(t) = L_{eq} \frac{di_1}{dt} = \left(L_1 - \frac{M^2}{L_2 + L_3} \right) \frac{di_1}{dt}$$

and

$$L_{eq} = L_1 - \frac{M^2}{L_2 + L_3}$$

These results are independent of the dot positions.

Fig
P18.8a

Fig
P18.8b

Chapter 18 / Problem 9

$$V_{in}(s) = (L_a + L_1) s I_1(s) + M s I_2(s)$$

$$0 = (L_2 + L_3) s I_2(s) + M s I_1(s)$$

Fig
P18.9

From the second

$$I_2(s) = -\frac{M}{L_2 + L_3} I_1(s)$$

and with this in the first

$$V_{in}(s) = Z_{in}(s) I_1(s) = \left(L_a + L_1 - \frac{M^2}{L_2 + L_3} \right) s I_1(s)$$

This makes

$$Z_{in}(s) = \left(L_a + L_1 - \frac{M^2}{L_2 + L_3} \right) s$$

Chapter 18/Problem 10

①

Treat these as problems in loop analysis
 For Fig P18.10a

Fig
 P18.10a

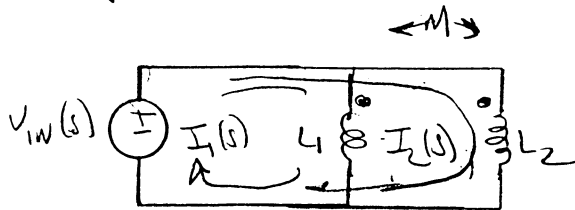


Fig
 P18.10b

Using V_{1W} , I_1 and I_2 for $V_{1W}(s)$, $I_1(s)$ and $I_2(s)$
 leads to

$$V_{1W} = L_1 s I_1 + M s I_2$$

$$V_{1W} = M s I_1 + L_2 s I_2$$

In matrix form

$$s \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_{1W} \\ V_{1W} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{\begin{bmatrix} L_2 & -M \\ -M & L_1 \end{bmatrix}}{s(L_1 L_2 - M^2)} \begin{bmatrix} V_{1W} \\ V_{1W} \end{bmatrix}$$

$$I_1 = \frac{(L_2 - M) V_{1W}}{s(L_1 L_2 - M^2)}$$

$$I_2 = \frac{(L_1 - M) V_{1W}}{s(L_1 L_2 - M^2)}$$

Then by KCL

$$I = I_1 + I_2 = \frac{L_1 + L_2 - 2M}{L_1 L_2 - M^2} \frac{V_{1W}}{s}$$

and with $V_{1W} = L_{eq} s I$

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

18/10 Circuit

(2)

(b) If the dots are reversed, then

$$V_{1W} = L_1 s I_1 - M s I_2$$

$$V_{1W} = -M s I_1 + L_2 s I_2$$

$$s \begin{bmatrix} L_1 & -M \\ -M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_{1W} \\ V_{1W} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{\begin{bmatrix} L_2 & M \\ M & L_1 \end{bmatrix}}{s(L_1 L_2 - M^2)} \begin{bmatrix} V_{1W} \\ V_{1W} \end{bmatrix}$$

$$I_1 = \frac{L_2 + M}{L_1 L_2 - M^2} \frac{V_{1W}}{s}$$

$$I_2 = \frac{L_1 + M}{L_1 L_2 - M^2} \frac{V_{1W}}{s}$$

$$I_1 + I_2 = \frac{L_1 + L_2 + 2M}{L_1 L_2 - M^2} \frac{V_{1W}}{s}$$

which makes

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 L_2 + 2M}$$

Chapter 18/Problem 11

(a) For Fig 18.11a, with

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

$$Z_{in}(s) = \frac{R L_{eq} s}{R + L_{eq} s}$$

This is the answer given but

$$Z_{in}(s) = \frac{\frac{L_1 + L_2 - 2M}{s(L_1 L_2 - M^2)} R}{R + \frac{s(L_1 L_2 - M^2)}{L_1 + L_2 - 2M}}$$

$$Z_{in}(s) = \frac{R(L_1 L_2 - M^2) s}{R(L_1 + L_2 - 2M) + (L_1 L_2 - M^2) s}$$

Fig
18.11a

Fig
18.11b

(b) For Fig 18.11b with

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

$$Z_{in}(s) = \frac{R L_{eq} s}{R + L_{eq} s}$$

$$= \frac{\frac{L_1 + L_2 + 2M}{s(L_1 L_2 - M^2)} R}{R + \frac{s(L_1 L_2 - M^2)}{L_1 + L_2 + 2M}}$$

$$= \frac{R(L_1 + L_2 - M^2) s}{R(L_1 + L_2 + 2M) + (L_1 L_2 - M^2) s}$$

18/12

Please be careful

Somehow, this one

has a peculiar aroma
associated with it

Chapter 18/Problem 12

The mesh equations in the s -domain with V_{in} , I_a , I_b and I_c used for $V_{in}(s)$, $I_a(s)$, $I_b(s)$ and $I_c(s)$ are

Fig
P18.6

$$\begin{aligned} (2s+1)I_a - (2s+1)I_b - sI_c &= V_{in} \\ -2sI_a + (2s+2)I_b + (s-1)I_c &= 0 \\ -(s+1)I_a + (s-1)I_b + (2s+2)I_c &= 0 \end{aligned}$$

Solve for I_a

$$I_a = \frac{\begin{vmatrix} V_{in} & -(2s+1) & -s \\ 0 & 2s+2 & s+1 \\ 0 & s-1 & 2s+2 \end{vmatrix}}{\begin{vmatrix} 2s+1 & -(2s+1) & -s \\ -2s & 2s+2 & s+1 \\ -(s+1) & s-1 & 2s+2 \end{vmatrix}} = \frac{(3s^2 + 8s + 5)V_{in}}{21s^3 + 29s^2 + 22s + 8}$$

Then

$$Z_{in}(s) = \frac{V_{in}(s)}{I_a(s)} = \frac{21s^3 + 29s^2 + 22s + 8}{3s^2 + 8s + 5}$$

Chapter 18/Problem 15

①

In the aiding configuration

$$L_{eq} = L_1 + L_2 + 2M = 3.7$$

In the opposing configuration

$$L_{eq} = L_1 + L_2 - 2M = 0.25$$

Adding and subtracting these give

$$2(L_1 + L_2) = 6.2$$

$$L_1 + L_2 = 3.1$$

And

$$4M = 1.2$$

$$M = 0.3H \leftarrow$$

The parallel combination L_{eq} with dotted terminals connected together is given by part (c) of Problem 10

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{121}{250}$$

$$= \frac{L_1 L_2 - 0.09}{3.1 - 0.6} = \frac{121}{250}$$

$$L_1 L_2 = 1.30$$

Then with

$$L_2 = 3.10 - L_1$$

$$L_1(3.10 - L_1) = 1.30$$

$$-L_1^2 + 3.10L_1 - 1.30 = 0$$

$$L_1^2 - 3.10L_1 + 1.30 = 0$$

$$(L_1 - 2.60)(L_2 - 0.50) = 0$$

$$L_1 = 2.60 \leftarrow$$

$$L_2 = 0.50 \leftarrow$$

Note

$$L_1 > L_2$$

Chapter 18/Problem 16

The open circuit at the right hand terminal means that the 1H inductor makes no contribution to the current through the 0.2H inductor.

Fig
P18.16

Thus, by voltage division

$$V_2(s) = \frac{0.2s}{0.2s + 200} V_{in}(s)$$

with $V_{in}(t) = 10u(t) \text{ V}$

$$V_{in}(s) = \frac{0.2s}{0.2s + 200} \frac{10}{s} = \frac{2}{s + 1000}$$

and

$$V_w(t) = 2e^{-1000t} u(t) \text{ V}$$

Chapter 18 / Problem 17

Fig
P18.17

(a) The open circuit at the right hand terminals means that the $5H$ inductor make no contribution to the current through the $0.2H$ inductor.

Thus, by voltage division

$$V_2(s) = \frac{0.2s}{0.2s + 200} V_{in}(s)$$

with $V_{in}(t) = 12u(t)$

$$V_2(s) = \frac{0.2s}{0.2s + 200} \cdot \frac{12}{s} = \frac{2.4}{s + 1000}$$

and
$$v_2(t) = 2.4 e^{-1000t} u(t) \text{ V}$$

The time constant is $T = 1 \text{ ms}$

(b) If $V_{in}(t) = -12u(-t)$, linearity gives

$$v_2(t) = -2.4 e^{+1000t} u(-t) \text{ V}$$

(c) If $V_{in}(t) = -6u(-t) + 6u(t)$ V, linearity and superposition gives

$$v_2(t) = -1.2 e^{+1000t} u(-t) + 1.2 e^{-1000t} u(t) \text{ V}$$

Chapter 18/Problem 18

With the open circuit at the right hand terminals, the 2H inductor at the right makes no mutual inductive contribution to the current through the 1H inductor. Because of this, it doesn't matter where the dot on the 1H inductor is placed.

Fig
P18.18

(a) and (b) will have the same zero-state response.

By voltage division

$$V_{out}(s) = \frac{s}{s+1} V_{in}(s)$$

with $V_{in}(t) = 10e^{-2t} u(t) V$

$$V_{out}(s) = \frac{10s}{(s+1)(s+2)} = \frac{K_1}{s+1} + \frac{K_2}{s+2}$$

$$K_1 = \left. \frac{10s}{s+2} \right|_{s=-1} = \frac{-10}{1} = -10$$


$$K_2 = \left. \frac{10s}{s+1} \right|_{s=-2} = \frac{-20}{-1} = 10$$

$$V_{out}(s) = 10 \left[\frac{1}{s+2} - \frac{1}{s+1} \right]$$

$$V_{out}(t) = 10 (e^{-2t} - e^{-t}) u(t) V$$

Chapter 18/Problem 19

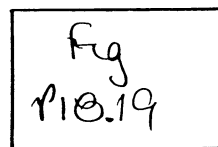With the open circuit at the left terminals, the 0.1 H inductor at the left makes no contribution to the current through the 0.2 H inductor. Thus, it doesn't matter where the dot is placed on the 0.1 H inductor.



(a) and (b) will have the same zero-state response

$$i_w(t) = 10 u(t) \text{ mA}$$

$$Y(s) = Cs + \frac{1}{Ls} = \frac{LCS^2 + 1}{Ls} = \frac{C(s^2 + \frac{1}{LC})}{s}$$

and with $L = 0.2 \text{ H}$ and $C = 0.1 \text{ F}$

$$Z(s) = \frac{10s}{s^2 + 50}$$

and

$$V_{out}(s) = Z(s) I_w(s)$$

$$I_w(s) = \frac{10}{s}$$

$$V_{out}(s) = \frac{100}{s^2 + 50} = \frac{100}{\sqrt{50}} \frac{\sqrt{50}}{s^2 + 50}$$

$$V_{out}(s) = 10\sqrt{2} \sin(2.071 t) u(t) \text{ mA}$$

Chapter 18/Problem 20

①

Because the left hand end of the circuit has an open circuit, the 0.1H inductor makes no contribution on $V_{out}(t)$.

Fig
P18.20

For both part (a) and part (b)

$$Y(s) = \frac{8}{5s} + \frac{s}{10} + 1 = \frac{5s^2 + 50s + 80}{50s}$$

and

$$Z(s) = \frac{10s}{s^2 + 10s + 16} \Omega$$

(a) with $i_w(t) = 10u(t) \text{ mA}$

$$I_w(s) = \frac{10}{s}$$

$$V_{out}(s) = Z(s)I_w(s) = \frac{100}{s^2 + 10s + 16} = \frac{100}{(s+2)(s+8)} = \frac{K_1}{s+2} + \frac{K_2}{s+8}$$

$$K_1 = \frac{100}{s+8} \Big|_{s=-2} = \frac{100}{6} = \frac{50}{3}$$

$$K_2 = \frac{100}{s+2} \Big|_{s=-8} = \frac{100}{-6} = -\frac{50}{3}$$

$$V_{out}(s) = \frac{50}{3} (e^{-2t} - e^{-8t}) u(t) \text{ mV}$$

(c) with $i_w(t) = 10e^{-4t} u(t) \text{ mA}$

$$I_w(s) = \frac{10}{s+4}$$

$$V_{out}(s) = \frac{100s}{(s+2)(s+4)(s+8)} = \frac{K_1}{s+2} + \frac{K_2}{s+4} + \frac{K_3}{s+8}$$

18/20 Cont'd

(2)

$$K_1 = \frac{100s}{(s+4)(s+8)} \Big|_{s=-2} = \frac{-200}{2(6)} = -\frac{50}{3}$$


$$K_2 = \frac{100s}{(s+2)(s+8)} \Big|_{s=-4} = \frac{-400}{(-2)(4)} = \frac{150}{3}$$

$$K_3 = \frac{100s}{(s+2)(s+4)} \Big|_{s=-8} = \frac{-800}{(-6)(-4)} = -\frac{100}{3}$$

$$V_{out}(s) = \frac{50}{3} \left(3e^{-4t} - e^{-2t} - 2e^{-8t} \right) u(t) \text{ mV}$$

Chapter 10/Problem 21

(a) With the dot in position - A

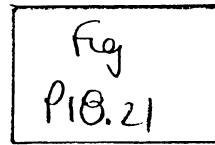

$$L_{eq} = L_1 + L_2 - 2M \\ = 2 + 2 - 2 = 2H$$

$$Z(s) = 8 + 2s$$

$$Z(j\omega) = 8 + j2\omega$$

$$Z(j2) = 8 + j4$$

With

$$V_s = 4 \cos 2tV, \quad \hat{V}_s = 4 \angle 0^\circ$$

$$\hat{I} = \frac{\hat{V}_s}{8 + j4} = \frac{4 \angle 0^\circ}{8.94 \angle 26.57^\circ} = 1.789 \angle -26.57^\circ A$$

$$i(t) = 1.789 \cos(2t - 26.57^\circ) A$$

and

$$p_R(t) = Ri(t)^2 = 8(1.789)^2 \cos^2(2t)$$

$$p_R(t) = 25.6 \cos^2(2t) W$$

(b) With the dot in position - B

$$L_{eq} = L_1 + L_2 + 2M = 2 + 2 + 2 = 6H$$

$$Z(s) = 8 + 6s$$

$$Z(j\omega) = 8 + j6\omega$$

$$Z(j2) = 8 + j12$$

$$\hat{I} = \frac{4 \angle 0^\circ}{14.42 \angle 56.31^\circ} = 0.277 \angle -56.31^\circ$$

$$i(t) = 0.277 \cos(2t - 56.31^\circ) A$$

and

$$p_R(t) = Ri(t)^2 = 8(0.277)^2 \cos^2(2t)$$

$$p_R(t) = 0.615 \cos^2(2t) W$$

Chapter 18 / Problem 22

(a) The dots are opposing

$$L_{eq} = L_1 + L_2 - 2M$$

$$= 3 + 2 - 2(2) = 1 \text{ H}$$

Fig
P18.22

(b) The step response with all LC 's equal to zero

$$Z(s) = s + 2 + \frac{1}{s} = \frac{s^2 + 2s + 1}{s}$$

For $v_{in}(t) = u(t)$

$$V_{in}(s) = \frac{1}{s}$$

$$I_{out}(s) = \frac{V_{in}(s)}{Z(s)} = \frac{1}{s^2 + 2s + 1} = \frac{1}{(s+1)^2}$$

$$i_{out}(t) = te^{-t} u(t) \text{ A}$$

(c) This is a simple RLC series circuit with

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1}} = 1 \text{ rad/s}$$

(d)

$$Q = \frac{\omega_0 L}{R} = \frac{1(1)}{2} = \frac{1}{2} \text{ rad/s}$$

$$B\omega = \frac{\omega_0}{Q} = \frac{1}{1/2} = 2 \text{ rad/s}$$

Check Q

$$Q = \frac{1}{RC\omega_0} = \frac{1}{2(1)(1)} = \frac{1}{2} \checkmark$$