

## CHAPTER 18 PROBLEM SOLUTIONS

**SOLUTION PROBLEM 18.34.** There is a correction to this problem: set  $M = 3$  H.

(a) The stored energy at  $t = 0$  is:

$$W(0) = 0.5L_1i_1^2(0) + 0.5L_2i_2^2(0) + Mi_1(0)i_2(0) = 8 \text{ J}$$

»  $L_1 = 10$ ;  $L_2 = 2$ ;  $M = 3$ ;  $i_1(0) = 1$ ;  $i_2(0) = -3$ ;

»  $W_0 = 0.5 * L_1 * i_1(0)^2 + 0.5 * L_2 * i_2(0)^2 + M * i_1(0) * i_2(0)$

$W_0 = 5$

(b) Writing two differential mesh equations we obtain

$$L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} + R_1 i_1 = 10 \frac{di_1}{dt} + 3 \frac{di_2}{dt} + i_1 = 0$$

and

$$L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} + R_2 i_2 = 2 \frac{di_2}{dt} + 3 \frac{di_1}{dt} + i_2 = 0$$

Taking the Laplace transform of these equations yields

$$10sI_1 - 10i_1(0) + 3sI_2 - 3i_2(0) + I_1 = (10s + 1)I_1 + 3sI_2 - 10i_1(0) - 3i_2(0) = 0$$

and

$$2sI_2 - 2i_2(0) + 3sI_1 - 3i_1(0) + I_2 = (2s + 1)I_2 + 3sI_1 - 3i_1(0) - 2i_2(0) = 0$$

Putting these equations in matrix form yields

$$\begin{pmatrix} 10s + 1 & 3s \\ 3s & 2s + 1 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 10i_1(0) + 3i_2(0) \\ 3i_1(0) + 2i_2(0) \end{pmatrix} = \begin{pmatrix} 1 \\ -3 \end{pmatrix}$$

Solving yields

$$\begin{aligned} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} &= \begin{pmatrix} 10s + 1 & 3s \\ 3s & 2s + 1 \end{pmatrix}^{-1} \begin{pmatrix} 1 \\ -3 \end{pmatrix} = \frac{1}{11s^2 + 12s + 1} \begin{pmatrix} 2s + 1 & -3s \\ -3s & 10s + 1 \end{pmatrix} \begin{pmatrix} 1 \\ -3 \end{pmatrix} \\ &= \frac{1}{(11s + 1)(s + 1)} \begin{pmatrix} 11s + 1 \\ -33s - 3 \end{pmatrix} = \frac{1}{s + 1} \begin{pmatrix} 1 \\ -3 \end{pmatrix} \end{aligned}$$

Therefore, by inspection,

$$i_1(t) = e^{-t}u(t) \text{ A} \quad \text{and} \quad i_2(t) = -3e^{-t}u(t) \text{ A}$$

**Remark:** normally,  $i_1(t)$  and  $i_2(t)$  would have two exponential terms present. Because of the special choice of initial conditions, a pole cancelled out.

(c) From equation 18.24 with the lower limit changed to zero and the upper limit changed to  $\infty$ , we have

$$W(0, \infty) = \int_0^{\infty} (v_1 i_1 + v_2 i_2) dt = 0.5 L_1 i_1^2(\infty) + 0.5 L_2 i_2^2(\infty) + M i_1(\infty) i_2(\infty) \\ - 0.5 L_1 i_1^2(0) + 0.5 L_2 i_2^2(0) + M i_1(0) i_2(0)$$

From part (b) all currents at  $t = \infty$  are zero, hence

$$W(0, \infty) = -0.5 L_1 i_1^2(0) + 0.5 L_2 i_2^2(0) + M i_1(0) i_2(0) = -5 \text{ J}$$

The result of part (a) indicates that the initial store energy is 5 J. The result of part (c) indicates that the energy returned to the circuit is also 5 J, i.e., the total energy accumulated in the inductors over  $[0, \infty)$  is -5 J. Hence 5 J is dissipated in the resistors.

**Remark:** the interested student might compute the integral  $\int_0^{\infty} (R_1 i_1^2(t) + R_2 i_2^2(t)) dt$ , the actual energy dissipated in the resistors over  $[0, \infty)$ , and show that this is 5 J.

### SOLUTION PROBLEM 18.35.

(a)

$$\gg L_1 = 4; L_2 = 9; M = 3;$$

$$\gg I_1 = 2; I_2 = -3;$$

$$\gg W = 0.5 * L_1 * I_1^2 + 0.5 * L_2 * I_2^2 - M * I_1 * I_2$$

$$W =$$

$$6.6500e+01$$

(b)

$$\gg K = 0.5 * L_1 * I_1^2$$

$$K = 8$$

$$\gg \% \text{ Minimize (over } I_2) K + 0.5 * 9 * I_2^2 - 3 * 2 * I_2$$

$$\gg \% \text{ Take Derivative and set to zero; then solve for } I_2.$$

$$\gg \% \text{ Derivative is: } 9 * I_2 - 6 = 0$$


$$\gg \% \text{ The result is } I_2 = 2/3 \text{ A.}$$

$$\gg I_2 = 2/3;$$

$$\gg W_{\min} = 0.5 * L_1 * I_1^2 + 0.5 * L_2 * I_2^2 - M * I_1 * I_2$$

$$W_{\min} = 6$$

(c)

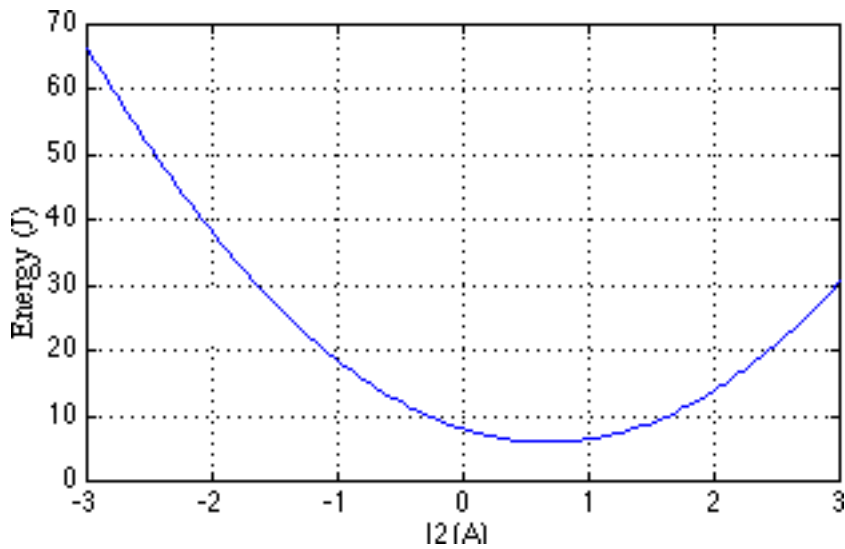**(d)**

$$\gg L1 = 4; L2 = 9; M = 3;$$

$$\gg k = M/\sqrt{L1*L2}$$

$$k = 5.0e-01$$

**SOLUTION PROBLEM 18.37.**

$$\gg k = 0.5;$$

$$\gg L1 = 9; L2 = 4; L3 = 1;$$

$$\gg M = 0.5*\sqrt{L1*L2}$$

$$M = 3$$

$$\gg Lcpld = L1 + L2 + 2*M$$

$$Lcpld = 19$$

$$\gg Leq = Lcpld + L3$$

$$Leq = 20$$

$$\gg I_{max} = 2;$$

$$\gg W_{max} = 0.5*Leq*I_{max}^2$$

$$W_{max} = 40 \text{ J}$$

**SOLUTION PROBLEM 18.41.**

$$\gg R_L = 100; R_s = 300e3; R = 10e3;$$

$$\gg m = 20; n = 5;$$

**(a)**

$$\gg Z_2 = R_L * m^2$$

$$Z_2 = 40000$$

$$\gg Req1 = Z_2 * R / (Z_2 + R)$$

$$Req1 = 8000$$

$$\gg Z_1 = Req1 * n^2$$

$$Z_1 = 200000$$

**(b)**

$$\gg \% Gv1 = v1/vin$$

$$\gg \% v1 = [Z1/(Rs + Z1)]vin$$

$$\gg Gv1 = Z1/(Rs+Z1)$$

$$Gv1 = 4.0000e-01$$

$$\gg \% Gv2 = v2/vin$$

$$\gg \% Gv2 = v2/v1 * v1/vin = (1/n) * G1$$

$$\gg Gv2 = G1/n$$

$$Gv2 = 8.0000e-02$$

$$\gg \% Gv3 = v3/vin$$

$$\gg Gv3 = -Gv2/m$$

$$Gv3 = -4.0000e-03$$

**(c)**

$$\gg \% Gi2 = i2/iin$$

$$\gg Gi2 = n*R/(R+Z2)$$

$$Gi2 = 1$$

$$\gg \% Gi3 = i3/iin = i3/i2 * i2/iin = -m*Gi2$$

$$\gg Gi3 = -m*Gi2$$

$$Gi3 = -20$$

**SOLUTION PROBLEM 18.55.** (a) The parameters in the circuit of figure P18.55b are given by equations in figure 18.22b. Specifically, since  $k = M/\sqrt{L_1 L_2} = 0.16/\sqrt{3.5 \times 0.008} = 0.95618$

$$\gg M = 0.16; L1 = 3.5; L2 = 0.008;$$

$$\gg k = M/\text{sqrt}(L1*L2)$$

$$k =$$

$$9.5618e-01$$

$$\gg La = (1 - k^2)*L1$$

$$La =$$

$$3.0000e-01$$

$$\gg Lb = k^2 * L1$$

$$Lb =$$

$$3.2000e+00$$

$$\gg N = M/L2$$

$$N =$$

$$20$$

**(b)**

$$\gg R = 500;$$

$$\gg w = 2*\text{pi}*60;$$

$$\gg V\text{seff} = 110;$$

$$\gg Zin = R + j*La*w + j*Lb*w$$

$$Zin =$$

$$5.0000e+02 + 1.3195e+03i$$

$$\gg I\text{seff} = V\text{seff}/Zin$$

$$I\text{seff} =$$

$$2.7624e-02 - 7.2899e-02i$$

$$\gg P\text{ave} = R*\text{abs}(I\text{seff})^2$$

Pave =  
3.0387e+00

(c)

»Zin2 = R + j\*La\*w

Zin2 =

5.0000e+02 + 1.1310e+02i

»Iseff2 = Vseff/Zin2

Iseff2 =

2.0929e-01 - 4.7341e-02i

»Is2mag = abs(Iseff2)

Is2mag =

2.1458e-01

» % The current in the secondary is (in A):

»Isecmag = Ismag\*N

Isecmag =

4.2916e+00

(d)

»% Our first step is to compute the reflected impedance:

»Zrefl = 100\*N^2

Zrefl =

40000

»% We now compute the impedance of the parallel combination

»% of Lb and Zrefl denoted Zpar

»Zpar = 1/(1/Zrefl + 1/(j\*w\*Lb))

Zpar =

3.6350e+01 + 1.2053e+03i

»% We now compute the input impedance:

»Zin = R+j\*w\*La + Zpar

Zin =

5.3635e+02 + 1.3184e+03i

»% Now we compute the voltage across the primary of the

»% ideal transformer, by voltage division:

»Vpar = Vseff\*Zpar/Zin

Vpar =

8.7342e+01 + 3.2500e+01i

»% Now we compute the voltage across the load:

»Vload = Vpar/N

Vload =

4.3671e+00 + 1.6250e+00i

»Vloadmag = abs(Vload)

Vloadmag =


4.6596e+00

»Iloadmag = Vloadmag/100

Iloadmag =

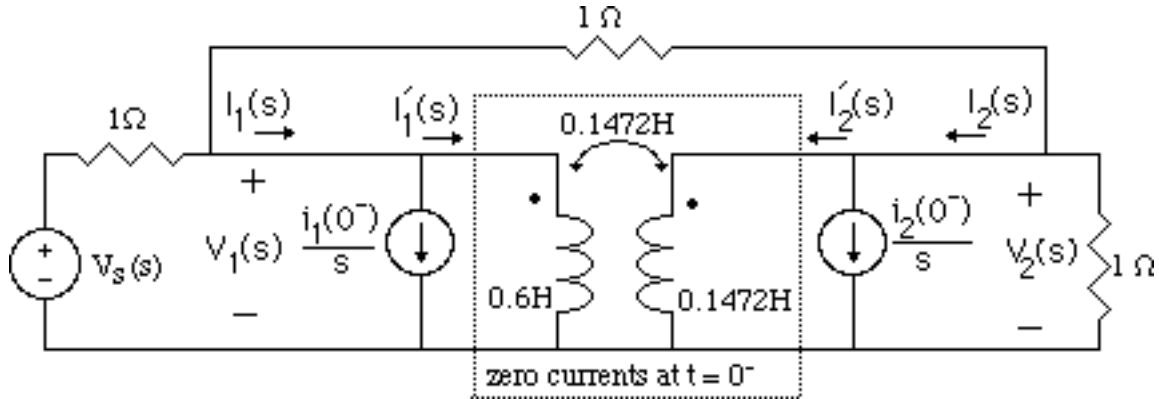4.6596e-02

**SOLUTION PROBLEM 18.65.** (a) The equivalent circuit accounting for initial conditions is given below:



(b) From the definition of coupled inductors

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0.6s & 0.1472s \\ 0.1472s & 0.1472s \end{bmatrix} \begin{bmatrix} I_1' \\ I_2' \end{bmatrix}$$

(c) Hence

$$\begin{bmatrix} I_1' \\ I_2' \end{bmatrix} = \begin{bmatrix} 0.6s & 0.1472s \\ 0.1472s & 0.1472s \end{bmatrix}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{1}{s} \begin{bmatrix} 15 & 0.1472 \\ -0.1472 & 0.6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

(d) Writing nodal equations we obtain,

$$\begin{bmatrix} V_s \\ 0 \end{bmatrix} = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \frac{1}{s} \begin{bmatrix} i_1(0^-) \\ i_2(0^-) \end{bmatrix} + \begin{bmatrix} I_1' \\ I_2' \end{bmatrix}$$

(e) Now we substitute our result of part (c):

$$\begin{bmatrix} V_s \\ 0 \end{bmatrix} = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \frac{1}{s} \begin{bmatrix} -2 \\ -2 \end{bmatrix} + \frac{1}{s} \begin{bmatrix} 2.208 & -2.208 \\ -2.208 & 9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

which simplifies to

$$\begin{bmatrix} V_s \\ 0 \end{bmatrix} = \frac{1}{s} \begin{bmatrix} 2s + 2.208 & -(s + 2.208) \\ -(s + 2.208) & 2s + 9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

or equivalently

$$\begin{bmatrix} 2s + 2.208 & -(s + 2.208) \\ -(s + 2.208) & 2s + 9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} sV_s + 2 \\ 2 \end{bmatrix}$$

(f) Solving these equations we obtain:

$$\begin{aligned} \begin{matrix} V_1 \\ V_2 \end{matrix} &= \begin{matrix} 2s + 2.208 & -(s + 2.208) \\ -(s + 2.208) & 2s + 9 \end{matrix}^{-1} \begin{matrix} sV_s + 2 \\ 2 \end{matrix} \\ &= \frac{1}{3s^2 + 18s + 15} \begin{matrix} 2s + 9 & (s + 2.208) \\ (s + 2.208) & 2s + 2.208 \end{matrix} \begin{matrix} sV_s + 2 \\ 2 \end{matrix} \end{aligned}$$

(g) If  $v_s(t) = 10u(t)$  V, then

$$\begin{matrix} V_1 \\ V_2 \end{matrix} = \frac{1}{3s^2 + 18s + 15} \begin{matrix} 2s + 9 & (s + 2.208) \\ (s + 2.208) & 2s + 2.208 \end{matrix} \begin{matrix} 12 \\ 2 \end{matrix} = \frac{1}{3s^2 + 18s + 15} \begin{matrix} 26s + 112.42 \\ 16s + 30.912 \end{matrix}$$

From MATLAB

```
»[r,p,k]=residue([16 30.912],[3 18 15])
```

r =

4.0907e+00

1.2427e+00

p =

-5

-1

k =

[]

Therefore,

$$v_2(t) = \left(4.0907e^{-5t} + 1.2427e^{-t}\right)u(t) \text{ V}$$

**SOLUTION PROBLEM 18.67.** The solution to this problem is based upon the following: (i)  $L_{eq} = L_1 + L_2 + 2M$  for series aiding connection (see example 18.4) and (ii)  $k = M/\sqrt{L_1 L_2}$  (a definition), and (iii)  $k = 1$  (an assumption).

(a) Given  $L_1 = L_2 = L$  and  $k = 1$ ,  $L_{eq} = L_1 + L_2 + 2M = L + L + 2k\sqrt{L^2} = 4L$ . Hence, when the number of turns is doubled, the inductance is quadrupled.

(b) For this part, let us first consider  $L_2$  which has  $2N$  turns. We can view  $L_2$  as two coils of  $N$  turns each connected in series aiding with coupling coefficient  $k = 1$ . Hence, according to part (a), the inductance of  $L_2$  is four times that of  $L_1$  which only has  $N$  turns. Hence,

$$L_{eq} = L_1 + L_2 + 2M = L + 4L + 2k\sqrt{4L^2} = 9L$$

Observe that the coil has  $3N$  turns yielding an inductance of  $9L = 3^2L$ .

(c) Suppose coil 1 and coil 2 consist of one turn each. Here the total number of turns is  $2N$  where  $N = 1$  turn. Suppose further that  $L_1 = L$ . From part (a),  $L_{eq} = 4L = (2)^2L$ . Now suppose coil one consists of one turn and coil 2 consists of  $M$  turns. We assume here as an induction hypothesis that

$$L_{eq} = (M + 1)^2 L$$

We must show that if coil 2 has  $(M+1)N$  turns then,

$$L_{eq} = (M + 2)^2 L$$

Our first step is to compute the equivalent inductance of coil 2. However, coil 2 consists of a single turn coupled to an  $M$ -turn coil, which by the induction hypothesis means that

$$L_2 = (M + 1)^2 L$$

Thus coil 1 in a series aiding connection with  $L_2$  leads to

$$\begin{aligned} L_{eq} &= L_1 + L_2 + 2M = L + (M + 1)^2 L + 2\sqrt{(M + 1)^2 L^2} = L + (M + 1)^2 L + 2(M + 1)L \\ &= L[(M + 1)^2 + 2(M + 1) + 1] = L[(M + 1) + 1]^2 = (M + 2)^2 L \end{aligned}$$

Given this relationship, if coil 1 consists of  $N_1$  turns, and one turn has an inductance  $L$ , then  $L_1 = (N_1)^2 L$ . Similarly,  $L_2 = (N_2)^2 L$ , and  $M = k\sqrt{L_1 L_2} = \sqrt{L_1 L_2} = \sqrt{(N_1)^2 (N_2)^2 L^2} = N_1 N_2 L$ . It immediately follows that

$$L_1 : L_2 : M = N_1^2 : N_2^2 : (N_1 N_2)$$


**SOLUTION PROBLEM 18.70.** (a)  $k = M / \sqrt{L_1 L_2}$

»  $M = 1.5$ ;  $L_1 = 1.5$ ;  $L_2 = 6$ ;

»  $k = M / \sqrt{L_1 L_2}$

$k = 5.0000e-01$

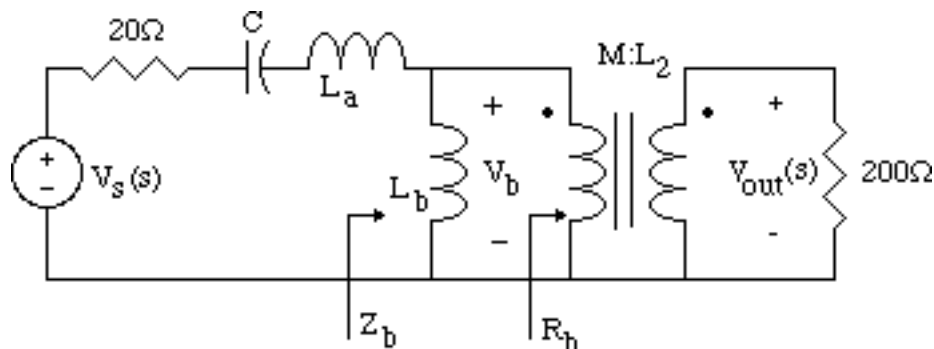(b) For this part and the remaining parts consider the following equivalent circuit where the coupled coils have been replaced by the model of figure 18.22(b).



»  $L_a = (1 - k^2) * L_1$

$L_a =$

1.1250e+00

»  $L_b = k^2 * L_1$

$L_b =$

3.7500e-01

»% The turns ratio is M:L2, i.e.,

»1.5/6

ans = 2.5000e-01

»% Therefore the turns ratio is 1:4. It follows that

»Rb = 200\*(1/4)^2

Rb =

1.2500e+01

To compute Z(s) we have,

$$Z(s) = 20 + \frac{1}{Cs} + L_a s + \frac{R_b L_b s}{L_b s + R_b} = 1.125s + 20 + \frac{12.5s}{s + \frac{100}{3}} + \frac{1}{Cs}$$

Hence,

$$Z(j\omega) = j1.125\omega + 20 + \frac{j12.5\omega}{j\omega + \frac{100}{3}} - \frac{j}{C} = 20 + \frac{12.5\omega^2}{\omega^2 + \frac{10^4}{9}} + j1.125\omega - \frac{1}{C} + \frac{416.67}{\omega^2 + \frac{10^4}{9}}$$

(c) For this part we need to make the imaginary part of Z(jw) real. To this end:

»K1 = 12.5\*100/3

K1 = 4.1667e+02

»w = 1333;

»K2 = 1.125\*w + K1\*w/(w^2 + 1e4/9)

K2 = 1.4999e+03

»C = 1/(K2\*w)

C = 5.0015e-07

Hence, we take C = 5 μF.

(d) At resonance, we have

$$Z(j\omega_r) = Z(j1333) = 20 + \frac{12.5\omega_r^2}{\omega_r^2 + \frac{10^4}{9}} = 32.5$$

and

$$Z_b(j\omega_r) = \frac{j12.5\omega_r}{j\omega_r + \frac{100}{3}} = \frac{j16,662}{33.33 + j1333} = 12.492 + j0.31238$$

By voltage division

$$\frac{V_{out}(j\omega_r)}{V_s(j\omega_r)} = \frac{V_{out}}{V_b} \times \frac{V_b}{V_s} = \frac{4}{1} \times \frac{Z_b(j\omega_r)}{Z(j\omega_r)} = 1.5379 + j0.038456$$

»Zb = j\*12.5\*w/(j\*w + 100/3)

Zb =

1.2492e+01 + 3.1238e-01i

»Zwr=20 + 12.5\*w^2/(w^2 + 1e4/9)

Zwr =

$$3.2492e+01$$

$$\gg G_v = 4 * Z_b / Z_{wr}$$

$$G_v =$$

$$1.5379e+00 + 3.8456e-02i$$

$$\gg \text{Mag}G_v = \text{abs}(G_v)$$

$$\text{Mag}G_v =$$

$$1.5384e+00$$


$$\gg \text{Ang}G_v = \text{angle}(G_v) * 180 / \pi$$

$$\text{Ang}G_v =$$

$$1.4325e+00$$

### SOLUTION PROBLEM 18.71.

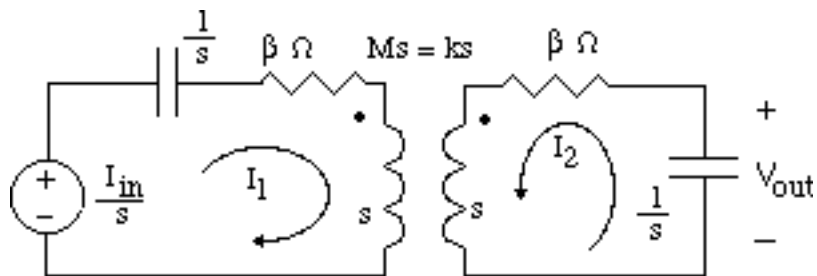(a) Following the hint we apply a source transformation to obtain



Writing two mesh equations we obtain the following matrix form of the mesh equations:

$$\begin{bmatrix} s + 1/s & ks \\ ks & s + 1/s \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{in}/s \\ 0 \end{bmatrix}$$

Solving for  $I_2$  yields

$$I_2 = \frac{\det \begin{bmatrix} s + 1/s & I_{in}/s \\ ks & 0 \end{bmatrix}}{\det \begin{bmatrix} s + 1/s & ks \\ ks & s + 1/s \end{bmatrix}} = \frac{-kI_{in}}{(s + 1/s)^2 - (ks)^2}$$

To find  $H(s)$  we have

$$\begin{aligned} H(s) &= \frac{V_{out}}{I_{in}} = \frac{-I_2/s}{I_{in}} = \frac{k/s}{(s + 1/s)^2 - (ks)^2} = \frac{k/s}{(s + ks + 1/s)(s - ks + 1/s)} \\ &= \frac{ks}{\left[ (1+k)s^2 + s + 1 \right] \left[ (1-k)s^2 + s + 1 \right]} \end{aligned}$$

(b)  $R = 0.02$  ,  $b = R = 0.02$  ,  $Q = 50$ , and  $k = 0.01, 0.02$ , and  $0.04$ .

```
»beta = 0.02; k1 = 0.01; k2 = 0.02; k3 = 0.04;
```

```
»p11 = roots([(1+k1) beta 1]);
```

```
»p12 = roots([(1-k1) beta 1]);
```

```
»p1 = [p11;p12]
```

```
p1 =
```

```
-9.9010e-03 + 9.9499e-01i
```

```
-9.9010e-03 - 9.9499e-01i
```

```
-1.0101e-02 + 1.0050e+00i
```

```
-1.0101e-02 - 1.0050e+00i
```

```
»p21 = roots([(1+k2) beta 1]);
```

```
»p22 = roots([(1-k2) beta 1]);
```

```
»p2 = [p21;p22]
```

```
p2 =
```

```
-9.8039e-03 + 9.9010e-01i
```

```
-9.8039e-03 - 9.9010e-01i
```

```
-1.0204e-02 + 1.0101e+00i
```

```
-1.0204e-02 - 1.0101e+00i
```

```
»p31 = roots([(1+k3) beta 1]);
```

```
»p32 = roots([(1-k3) beta 1]);
```

```
»p3 = [p31;p32]
```

```
p3 =
```

```
-9.6154e-03 + 9.8053e-01i
```

```
-9.6154e-03 - 9.8053e-01i
```

```
-1.0417e-02 + 1.0206e+00i
```

```
-1.0417e-02 - 1.0206e+00i
```

(c)

```
»f = 0.14:.0001:.18;
```

```
»n1 = [k1/(1-k1)^2 0];
```

```
n2 = [k2/(1-k2)^2 0];
```

```
n3 = [k3/(1-k3)^2 0];
```


```
»h1 = freqs(n1, poly(p1), 2*pi*f);
```

```
»h2 = freqs(n2, poly(p2), 2*pi*f);
```

```
»h3 = freqs(n3, poly(p3), 2*pi*f);
```

```
»plot(f, abs(h1), f, abs(h2), f, abs(h3))
```

```
»grid
```

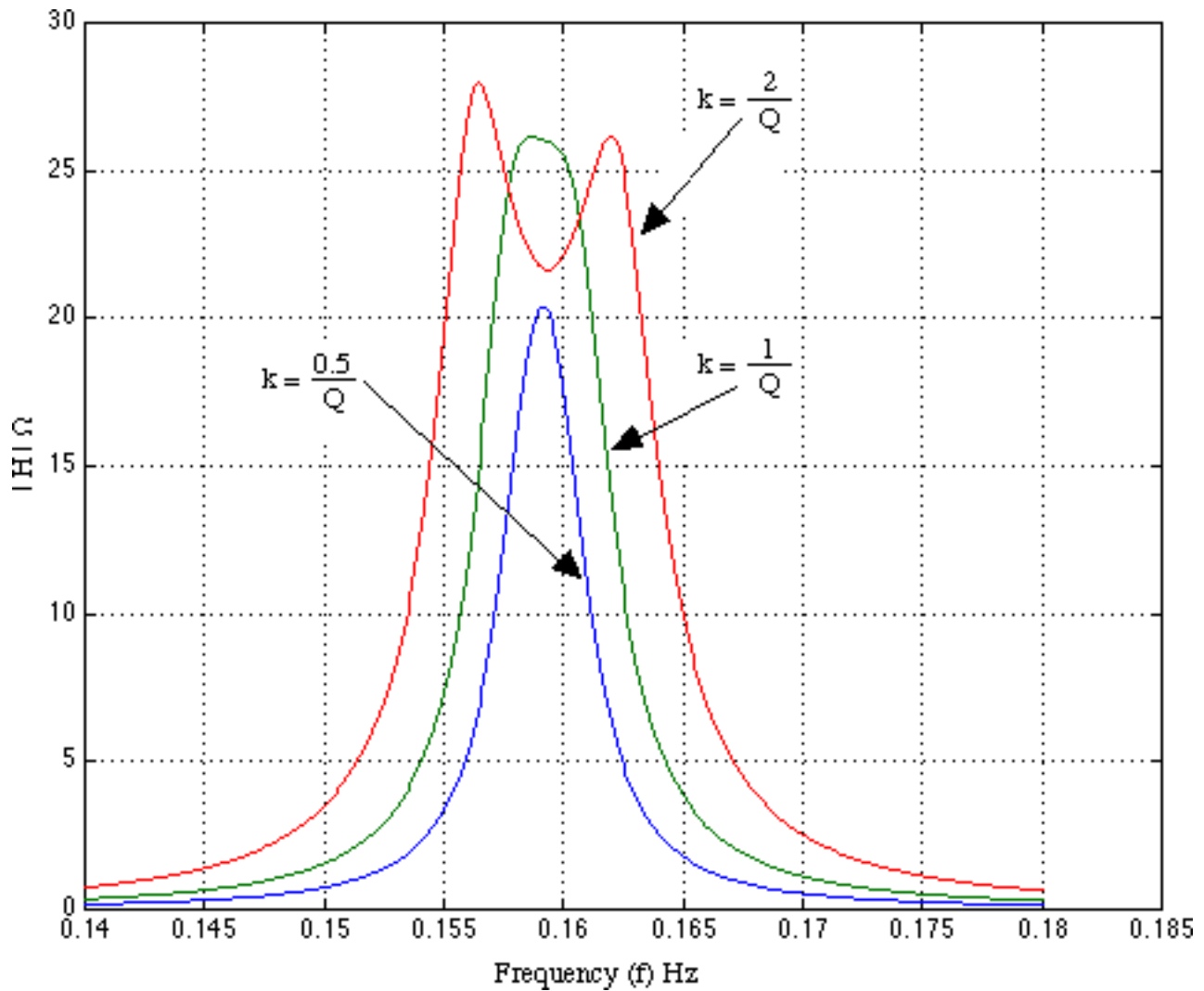

(d) An inspection of  $[f, \text{abs}(h_2)]$  (i.e., a tabulation of the values) in part (c) indicates that  $f_{\text{peak}} = 0.15865$  Hz and  $H_{\text{peak}} = 26.148$ . The frequency scale factor  $K_f$  is defined according to:  
 $\gg K_f = 455e3/f_{\text{peak}}$   
 $K_f = 2.8679e+06$

Further,

$\gg K_m = K_f * 2.35e-3$   
 $K_m = 6.7397e+03$

$\gg L_{\text{new}} = K_m * 1/K_f$   
 $L_{\text{new}} =$   
 $2.3500e-03$   
 $\gg C_{\text{new}} = 1/(K_m * K_f)$   
 $C_{\text{new}} =$   
 $5.1736e-11$   
 $\gg R_{\text{new}} = K_m * 0.02$   
 $R_{\text{new}} =$   
 $1.3479e+02$

The 3 dB down value of  $h_2$  is  $H_{\text{peak}}/\sqrt{2}$ . Hence

$$\gg H_{\max} = \max(\text{abs}(h_2))$$

$$H_{\max} =$$

$$2.6148\text{e}+01$$

$$\gg H_{3\text{db}} = H_{\max}/\sqrt{2}$$

$$H_{3\text{db}} =$$

$$1.8490\text{e}+01$$

Again, inspecting the tabulated values indicates that the 3 dB frequencies are:  $f_1 = 0.1569$  Hz and  $f_2 = 0.1614$  Hz. Finally

$$\gg B_f = f_2 - f_1$$

$$B_f = 4.5000\text{e}-03 \text{ Hz}$$

$$\gg B_{f_{\text{new}}} = K_f \cdot B_f$$

$$B_{f_{\text{new}}} = 1.2906\text{e}+04 \text{ Hz}$$

(e) For this part we redo part (a) with R, L, and C as literals.

Writing two mesh equations we obtain the following matrix form of the mesh equations:

$$\begin{array}{ccc} Ls + R + 1/Cs & kLs & I_1 \\ kLs & Ls + R + 1/Cs & I_2 \end{array} = \begin{array}{c} I_{in}/Cs \\ 0 \end{array}$$

Solving for  $I_2$  yields

$$I_2 = \frac{\det \begin{array}{cc} Ls + R + 1/Cs & I_{in}/Cs \\ kLs & 0 \end{array}}{\det \begin{array}{cc} Ls + R + 1/Cs & kLs \\ kLs & Ls + R + 1/Cs \end{array}} = \frac{-kL/C}{(Ls + R + 1/Cs)^2 - (kLs)^2} I_{in}$$

To find  $H(s)$  we have

$$\begin{aligned} H(s) &= \frac{V_{out}}{I_{in}} = \frac{-I_2/Cs}{I_{in}} = \frac{kL/C^2s}{(Ls + R + 1/Cs)^2 - (kLs)^2} = \frac{kL/C^2s}{(Ls + kLs + R + 1/Cs)(Ls - kLs + R + 1/Cs)} \\ &= \frac{kLs}{(LC(1+k)s^2 + CRs + 1)(LC(1-k)s^2 + CRs + 1)} = \frac{k s / LC^2}{(1+k)s^2 + \frac{R}{L}s + \frac{1}{LC}} \frac{1}{(1-k)s^2 + \frac{R}{L}s + \frac{1}{LC}} \\ &= \frac{k \frac{s}{C}}{(1+k)s^2 + \frac{0}{Q}s + \frac{2}{0}} \frac{1}{(1-k)s^2 + \frac{0}{Q}s + \frac{2}{0}} \end{aligned}$$

Evaluating this expression at  $s = j \omega$ , yields

$$H(j\omega) = \frac{jk \frac{3}{C_0}}{-(1+k) \frac{2}{C_0} + \frac{j\omega}{Q} + \frac{2}{C_0} \quad -(1-k) \frac{2}{C_0} + \frac{j\omega}{Q} + \frac{2}{C_0}}$$

$$= \frac{-jk/C_0}{k - \frac{j\omega}{Q} \quad k + \frac{j\omega}{Q}} = \frac{-jk/C_0}{k^2 + \frac{1}{Q^2}}$$

Therefore

$$|H(j\omega)| = \frac{1}{C_0} \times \frac{k}{k^2 + \frac{1}{Q^2}}$$

(f) To solve this part we differentiate and set equal to zero as follows:

$$\frac{d|H(j\omega)|}{dk} = \frac{1}{C_0} \times \frac{d}{dk} \frac{k}{k^2 + \frac{1}{Q^2}} = \frac{1}{C_0} \times \frac{1}{k^2 + \frac{1}{Q^2}} - \frac{2k^2}{k^2 + \frac{1}{Q^2}}^2 = 0$$

It follows that

$$\frac{2k^2}{k^2 + \frac{1}{Q^2}} = 1$$

Hence

$$k^2 = \frac{1}{Q^2}$$

or  $k = 1/Q$ . With this value of  $k$ ,

$$|H(j\omega)|_{\max} = \frac{1}{C_0} \times \frac{1/Q}{\frac{2}{Q^2}} = \frac{Q}{2C_0}$$

At  $\omega_0$ , the magnitude of the transfer function increases with increasing  $k$ , reaching a peak at  $k = 1/Q$  and then decreases with a further increase in  $k$  as born out in the plots of part (c).