

## CHAPTER 19 PROBLEM SOLUTIONS

**SOLUTION PROBLEM 19.40.** (a) Let  $Z_1 = R$  and  $Z_2 = 1/Cs$  or  $Y_2 = Cs$ . From problem 38,

$$h = \begin{array}{c|c} Z_1 & 1 \\ \hline -1 & Y_2 \end{array} = \begin{array}{c|c} R & 1 \\ \hline -1 & Cs \end{array}$$

(b) This part is a cascade of an ideal transformer and part (a). Label the voltage and current at the port 1 of  $N_1$  as  $\hat{V}_1$  and  $\hat{I}_1$ . From the properties of the ideal transformer,  $V_1 = -b\hat{V}_1$  and  $I_1 = -\hat{I}_1/b$ . Hence

$$\begin{array}{c|c} \hat{V}_1 & R & 1 & \hat{I}_1 \\ \hline I_2 & -1 & Cs & V_2 \end{array} \quad \begin{array}{c|c} -V_1/b & R & 1 & -bI_1 \\ \hline I_2 & -1 & Cs & V_2 \end{array}$$

Therefore

$$\begin{array}{c|c} V_1 & b^2R & -b & I_1 \\ \hline I_2 & b & Cs & V_2 \end{array}$$

From table 19.1, if  $h_{22} = Cs \neq 0$ , then the z-parameters exist and if  $h_{11} = b^2R \neq 0$ , the y-parameters exist, i.e., if  $C \neq 0$  and  $R \neq 0$  (assuming reasonably that  $b \neq 0$ ) respectively.

**SOLUTION PROBLEM 19.41.** For this solution we apply the definition of h-parameters: by inspection

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{1}{2+2s}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \left. \frac{2V_1 - 2sV_1}{I_1} \right|_{V_2=0} = \frac{(2-2s)V_1}{(2+2s)V_1} \bigg|_{V_2=0} = \frac{1-s}{s+1}$$

When  $I_1 = 0$ , then  $I_2 = 2V_1 + 2V_1 = 4V_1$  and  $V_2 = 0.5(2V_1) + \frac{1}{2s}(2V_1) = \frac{s+1}{s}V_1$ .

$$\text{Therefore, } h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{s}{s+1} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{4V_1}{V_2} \bigg|_{I_1=0} = \frac{4s}{s+1}.$$

**SOLUTION PROBLEM 19.42.** (a) In MATLAB

```
»h11 = 250; h12 = 0.025; h21 = 12.5; h22 = 2.25e-3;
```

```
»Zs = 1e3; ZL = 500;
```

```
»YL = 1/ZL
```

```
YL = 2.0000e-03
```

```
»Zin = h11 - h12*h21/(h22 + (1/ZL))
```

```
Zin = 1.7647e+02
```

```
»Yout = h22 - h12*h21/(h11 + Zs)
```

```
Yout = 2.0000e-03
```

```
»Zout = 1/Yout
```

```
Zout = 500
```

(b)

```
»% Gv1 = V1/Vs
```

```
»Gv1 = Zin/(Zin + Zs)
```

```
Gv1 = 1.5000e-01
```

```
»% Gv2 = V2/V1
```

```
»Gv2 = -h21/(Zin*(h22 + YL))
```

```
Gv2 = -1.6667e+01
```

```
»Gv = Gv1*Gv2
```

```
Gv = -2.5000e+00
```

(c) Given the above, the Thevenin equivalent seen by the capacitor is  $\mathbf{V_{oc}} = -2.5\mathbf{V_{in}}$  and

$$R_{th} = 500 \quad .$$

In MATLAB

```
»Zth = ZL*Zout/(ZL + Zout)
```

```
Zth = 250
```

```
»Vin = 10;
```

```
»Voc = -2.5*Vin;
```

```
»w = 400;
```

$$\gg Z_c = 1/(j * w * 10e-6)$$

$$Z_c = 0 - 2.5000e+02i$$

$$\gg V_c = V_{oc} * Z_c / (Z_{th} + Z_c)$$

$$V_c = -1.2500e+01 + 1.2500e+01i \gg V_{2mag} = \text{abs}(V_c)$$

$$\gg V_{2mag} = \text{abs}(V_c)$$

$$V_{2mag} =$$

$$1.7678e+01$$

$$\gg V_{2ang} = \text{angle}(V_c) * 180/\pi$$

$$V_{2ang} =$$

$$135$$

From above,

$$v_2(t) = 17.678\sqrt{2} \cos(400t + 135^\circ) \text{ V}$$

Therefore

$$\gg P_{ave} = V_{2mag}^2 / 500$$

$$P_{ave} =$$

$$6.2500e-01$$

### SOLUTION PROBLEM 19.43.

(a) Using the h-parameters of stage 2

$$Z_{in2} = h_{11} - \frac{h_{12}h_{21}}{h_{22} + Y_L} = 1000 + \frac{0.966 \times 51}{0.0008 + 1/64} = 4000$$

The load for stage 1 is the parallel combination of  $Z_{in2}$  and the 3 k resistance. However, because  $h_{12} = 0$ , the input impedance is unaffected by the load, and hence for stage 1,

$$Z_{in1} = h_{11} = 2000$$

(b) For stage 1, because  $h_{12} = 0$ , the output impedance is unaffected by the source impedance. Thus,

$$Y_{out1} = h_{22} = 0.05 \times 10^{-3} \text{ S},$$

$$Z_{out1} = 1/Y_{out1} = 20 \times 10^3$$

For stage 2, the source impedance is the parallel combination of  $Z_{out1}$  and the 3 k resistance.

$$\text{Thus} \\ Z_{s2} = \frac{20000 \times 3000}{20000 + 3000} = 2608.7$$

and

$$Y_{out2} = h_{22} - \frac{h_{12}h_{21}}{h_{11} + Z_{s2}} = 0.0008 + \frac{0.966 \times 51}{1000 + 2608.7} = 0.0145 \text{ S}$$

$$Z_{out2} = 1/Y_{out2} = 69.19$$

(c)

$$\frac{V_1}{V_s} = \frac{Z_{in1}}{Z_{in1} + Z_s} = \frac{2000}{2000 + 2000} = 0.5$$

The load of stage 1 is the parallel combination of  $Z_{in2}$  and  $Z_m$ . Thus

$$Y_{L1} = Y_{in2} + 1/3000 = 5.834 \times 10^{-4} \text{ S}$$

Hence

$$Z_{L1} = 1/ Y_{L1} = 1714$$

and

$$\left(\frac{V_2}{V_1}\right)_{\text{stage 1}} = \frac{1}{Z_{in1}} \times \frac{-h_{21}}{h_{22} + Y_{L1}} = \frac{1}{2000} \times \frac{-50}{(0.05 + 0.5834) \times 10^{-3}} = -39.46$$

For stage 2, the load is 64 . Hence

$$\left(\frac{V_2}{V_1}\right)_{\text{stage 2}} = \frac{1}{Z_{in2}} \times \frac{-h_{21}}{h_{22} + Y_{L2}} = \frac{1}{4000} \times \frac{51}{(0.8 + 1000/64) \times 10^{-3}} = 0.7762$$

Finally, the overall voltage gain is the product of the three gains calculated above

$$\frac{V_{out}}{V_s} = 0.5 \times (-39.46) \times (0.7762) = -15.32$$

(d) The input circuit consists of a series connection of  $V_s$ ,  $Z_s$ ,  $C$  and  $Z_{in1}$ . The remainder of the circuit is resistive and has no effect on the frequency response. The magnitude response is of the high pass type with

$$f_{3dB} = \frac{1}{2 (R_s + R_{in1})C} = \frac{1}{2 (2000 + 2000)10^{-6}} = 39.789 \text{ Hz}$$

**SOLUTION PROBLEM 19.44.** To meet the required matching, we must have

$$Z_{\text{out}} = Z_{\text{out}2} = Z_L = 64 = \frac{1}{Y_{\text{out}2}}$$

This requires that

$$Y_{\text{out}2} = h_{22} - \frac{h_{12}h_{21}}{h_{11} + Z_{s2}} = 0.0008 + \frac{0.966 \times 51}{1000 + Z_{s2}} = \frac{1}{64}$$

Solving for  $Z_{s2}$ , we obtain  $Z_{s2} = 2323.2$ . Now for stage 2,  $Z_{s2}$  is the parallel combination of  $Z_{\text{out}1} = 20 \text{ k}$  and  $Z_m$ :

$$Z_{s2} = \frac{20000 \times Z_m}{20000 + Z_m} = 2323.2$$

from which  $Z_m = 2628.5$ . With this new value of  $Z_m$ , we repeat the calculations of problem 19.43 to obtain  $Z_{\text{in}} = 2000$  and  $V_{\text{out}}/V_s = -14.26$ . Details follow.

Using the h parameters of stage 2

$$Z_{\text{in}2} = h_{11} - \frac{h_{12}h_{21}}{h_{22} + Y_L} = 1000 + \frac{0.966 \times 51}{0.0008 + 1/64} = 4000$$

For stage 1, because  $h_{12} = 0$ , the input impedance is not affected by the load and

$Z_{\text{in}1} = h_{11} = 2000$ . The voltage gains of the various stages are:

$$\frac{V_1}{V_s} = \frac{Z_{\text{in}1}}{Z_{\text{in}1} + Z_s} = \frac{2000}{2000 + 2000} = 0.5$$

The load of stage 1 is the parallel combination of  $Z_{\text{in}2}$  and  $Z_m$ . Thus

$$Y_{L1} = Y_{\text{in}2} + 1/2628.5 = 6.3044 \times 10^{-4} \text{ S}$$

Hence

$$\left(\frac{V_2}{V_1}\right)_{\text{stage 1}} = \frac{1}{Z_{\text{in}1}} \times \frac{-h_{21}}{h_{22} + Y_{L1}} = \frac{1}{2000} \times \frac{-50}{(0.05 + 0.63044) \times 10^{-3}} = -36.74$$

For stage 2, the load is 64. Hence

$$\left(\frac{V_2}{V_1}\right)_{\text{stage 2}} = \frac{1}{Z_{\text{in}2}} \times \frac{-h_{21}}{h_{22} + Y_{L2}} = \frac{1}{4000} \times \frac{51}{(0.8 + 1000/64) \times 10^{-3}} = 0.7762$$

Finally, the overall voltage gain is the product of the three gains calculated above

$$\frac{V_{\text{out}}}{V_s} = 0.5 \times (-36.74) \times (0.7762) = -14.26$$

**SOLUTION PROBLEM 19.45.**

(a) Using the h-parameters of stage 2

$$Z_{in2} = h_{11} - \frac{h_{12}h_{21}}{h_{22} + Y_L} = 500 + \frac{0.966 \times 51}{0.0016 + 1/32} = 2000$$

The load for stage 1 is the parallel combination of  $Z_{in2}$  and the 1.5 k resistance. However, because  $h_{12} = 0$ , the input impedance is unaffected by the load, and  $Z_{in1} = h_{11} = 1000$ .

(b) For stage 1, because  $h_{12} = 0$ , the output impedance is unaffected by the source impedance, and

$$Y_{out1} = h_{22} = 0.1 \times 10^{-3} \text{ S},$$

$$Z_{out1} = 1/Y_{out1} = 10^4$$

For stage 2, the source impedance is the parallel combination of  $Z_{out1}$  and the 1.5 k resistor

$$Z_{s2} = \frac{10^4 \times 1.5 \times 10^3}{10^4 + 1.5 \times 10^3} = 1304.3$$

and

$$Y_{out2} = h_{22} - \frac{h_{12}h_{21}}{h_{11} + Z_{s2}} = 0.0016 + \frac{0.966 \times 51}{500 + 1304.3} = 0.0289 \text{ S}$$

$$Z_{out2} = 1/Y_{out2} = 34.6$$

(c)

$$\frac{V_1}{V_s} = \frac{Z_{in1}}{Z_{in1} + Z_s} = \frac{1000}{1000 + 1000} = 0.5$$

The load of stage 1 is the parallel combination of  $Z_{in2}$  and  $Z_m$ . Thus

$$Y_{L1} = Y_{in2} + 1/1500 = 1.1667 \times 10^{-3} \text{ S}$$

Hence

$$Z_{L1} = 1/Y_{L1} = 857.1$$

$$\left(\frac{V_2}{V_1}\right)_{\text{stage 1}} = \frac{1}{Z_{in1}} \times \frac{-h_{21}}{h_{22} + Y_{L1}} = \frac{1}{1000} \times \frac{-50}{(0.1 + 1.1667) \times 10^{-3}} = -39.47$$

For stage 2, the load is 32 . Hence

$$\left(\frac{V_2}{V_1}\right)_{\text{stage 2}} = \frac{1}{Z_{in2}} \times \frac{-h_{21}}{h_{22} + Y_{L2}} = \frac{1}{2000} \times \frac{51}{0.0016 + 1/32} = 0.7762$$

Finally, the overall voltage gain is the product of the three gains calculated above

$$\frac{V_{\text{out}}}{V_s} = 0.5 \times (-39.47) \times (0.7762) = -15.32$$

(d) The input circuit consists of a series connection of  $V_s$ ,  $Z_s$ ,  $C$  and  $Z_{in1}$ . The remainder of the circuit is resistive and has no effect on the frequency response. The magnitude response is of the highpass type with

$$f_{3dB} = \frac{1}{2(R_s + R_{in1})C} = \frac{1}{2(1000 + 1000)10^{-6}} = 79.58 \text{ Hz}$$

**SOLUTION PROBLEM 19.46.** (a) Since the currents through  $Y_L$  and  $h_{22}$  are the same,  $h_{22} = Y_L$ .

(b) From current division,  $I_2 = \frac{Y_L}{Y_L + h_{22}} h_{21} I_1$        $\frac{I_2}{I_1} = \frac{Y_L h_{21}}{Y_L + h_{22}}$ .

(c)  $150 = \frac{I_2}{I_1} = \frac{Y_L h_{21}}{Y_L + h_{22}} = 0.5 h_{21}$        $h_{21} = 300$ .

(d)  $h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{-1}{2} = -0.5$ .

(e)  $\frac{I_1}{I_s} = \frac{Z_s}{Z_s + Z_{in}} = \frac{9 \times 10^3}{9 \times 10^3 + Z_{in}} = 0.9$        $Z_{in} = 1000$  . Given this quantity,

$$h_{11} = Z_{in} + \frac{h_{12} h_{21}}{h_{22} + Y_L} = 1000 - \frac{150}{0.25} = 400 \text{ .}$$

**SOLUTION PROBLEM 19.47.** Recall that

$$\begin{matrix} V_1 \\ I_2 \end{matrix} = \begin{matrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{matrix} \begin{matrix} I_1 \\ V_2 \end{matrix}$$

(a) From this expression and specification 1,  $h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = 0$ .

(b) From the formula for  $Y_{out}$  (equation 19.50), specification 2, and the result of part (a), we have

$$Y_{out} = \frac{1}{Z_{out}} = \frac{1}{800} = h_{22} - \frac{h_{12}h_{21}}{h_{11} + Z_s} = h_{22}$$

Hence,  $h_{22} = \frac{1}{800} = 1.25 \text{ mS}$ .

For maximum power transfer from amplifier to the load,

$$Z_{out} = 800 = b^2 Z_L = 8b^2$$

Therefore,  $b = 10$ .

(c) and (d) Observe that

$$Z_{in} = h_{11} - \frac{h_{12}h_{21}}{h_{22} + Y_L/b^2} = h_{11}$$

From specification 3 and voltage division,

$$\frac{V_1}{V_s} = \frac{24}{25} = \frac{Z_{in}}{Z_{in} + 40}$$

Equivalently,

$$\frac{V_s}{V_1} = \frac{25}{24} = 1 + \frac{40}{Z_{in}}$$

Hence  $h_{11} = Z_{in} = 40 \times 24 = 960$ .

(e) From equation 19.51,

$$G_{v2} = \frac{V_2}{V_1} = -100 = \frac{-h_{21}}{Z_{in}(h_{22} + Y_L/b^2)} = \frac{-h_{21}}{960(1.25 \times 10^{-3} + 1.25 \times 10^{-3})} = \frac{-h_{21}}{2.4}$$

Hence,  $h_{21} = 240$ .

(f) The power delivered to the load is  $P_L = \frac{V_2^2}{800}$  and the power delivered to the amplifier is

$P_{amp} = \frac{V_1^2}{Z_{in}} = \frac{V_1^2}{960}$ . Therefore the power gain is

$$\frac{P_L}{P_{amp}} = \frac{96}{80} \frac{V_2}{V_1}^2 = 1.2 \times 10^4$$

**SOLUTION PROBLEM 19.48.** Recall that

$$\begin{array}{r} V_1 \\ I_2 \end{array} = \begin{array}{cc} h_{11} & h_{12} \\ h_{21} & h_{22} \end{array} \begin{array}{r} I_1 \\ V_2 \end{array}$$

(a) From this expression and specification 1,  $h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = 0.01$ .

(b) For maximum power transfer from amplifier to the load,

$$Z_{out} = 800 = b^2 Z_L = 8b^2$$

Therefore,  $b = 10$ .

Now we find  $Z_{in}$ . From specification 3 and voltage division,

$$\frac{V_1}{V_s} = \frac{24}{25} = \frac{Z_{in}}{Z_{in} + 40} \quad (1)$$

Equivalently,

$$\frac{V_s}{V_1} = \frac{25}{24} = 1 + \frac{40}{Z_{in}} \quad Z_{in} = 40 \times 24 = 960$$

Using the formula for  $Z_{in}$  we have the following equation

$$Z_{in} = 960 = h_{11} - \frac{0.01h_{21}}{h_{22} + 1.25 \times 10^{-3}} \quad h_{11} = 960 + 0.01 \frac{h_{21}}{h_{22} + 1.25 \times 10^{-3}} \quad (2)$$

But from the given specs,

$$\frac{V_2}{V_1} = -100 = \frac{-h_{21}}{Z_{in}(h_{22} + Y_L/b^2)} = \frac{-h_{21}}{960(h_{22} + 1.25 \times 10^{-3})}$$

which implies that

$$\frac{h_{21}}{(h_{22} + 1.25 \times 10^{-3})} = 960 \times 10^2 \quad (3)$$

Substituting (3) into (2) allows us to solve for  $h_{11}$ :

$$h_{11} = 960 + 0.01 \times 960 \times 10^2 = 1920$$

Now let us rewrite equation (3) as:

$$h_{21} - 960 \times 10^2 h_{22} = 960 \times 10^2 \times 1.25 \times 10^{-3} = 120 \quad (4)$$

Also

$$Y_{out} = 1.25 \times 10^{-3} = h_{22} - \frac{h_{12}h_{21}}{h_{11} + Z_s} = h_{22} - \frac{0.01h_{21}}{1960}$$

Equivalently,

$$1960 \times 1.25 \times 10^{-3} = 2.45 = 1960h_{22} - 0.01h_{21} \quad (5)$$

Solving equations (4) and (5) simultaneously in MATLAB yields

```
»A = [1 -960e2;-0.01 1960]
```

```
A =
```

```
1.0000e+00 -9.6000e+04
```

```
-1.0000e-02 1.9600e+03
```

```
»b = [120; 2.45]
```

```
b =
```

```
1.2000e+02
```

```
2.4500e+00
```

```
»x = A\b
```

```
x =
```

```

4.7040e+02
3.6500e-03
»h21 = x(1); h22 = x(2);
h = [1920 0.01;h21 h22]
h =
1.9200e+03 1.0000e-02
4.7040e+02 3.6500e-03

```

We can verify these results as well as compute the overall amplifier gain using the following m-file:

```

% two-port analysis in terms of h-parameters
function [zin, zout] =twoport(h, zL, zs)
['twoport analysis using h-parameters']
h11= h(1,1); h12=h(1,2); h21=h(2,1); h22=h(2,2);
zin = h11 - h12*h21/(h22+ 1/zL)

yout= h22 - h12*h21/(h11+zs);
zout= 1/yout
v1tovs= zin/(zin+zs)
v2tov1= -h21/(zin*(h22+1/zL))
v2tovs= v1tovs*v2tov1

»twoport(h,ZL,Zs)
ans =
twoport analysis using h-parameters
zin =
960
zout =
8.0000e+02
v1tovs =
9.6000e-01
v2tov1 =
-100
v2tovs =
-96

```

Hence the overall voltage gain is  $V_L/V_s = -96/10 = -9.6$  because of the transformer.

Finally to compute power gains,

$$\gg V_s = 1; \quad V_{in} = 24/25;$$

$$\gg V_L = -9.6;$$

$$\gg P_{in} = V_{in}^2/960$$

$$P_{in} =$$

$$9.6000e-04$$

$$\gg P_{load} = V_L^2/8$$

$$P_{load} =$$

$$1.1520e+01$$

$$\gg P_{gain} = P_{load}/P_{in}$$

$$P_{gain} =$$

$$12000$$

### SOLUTION PROBLEM 19.49.

$$(a) \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{-C_\mu s V + g_m V}{\frac{1}{R} + (C + C_\mu)s} = \frac{-C_\mu s + g_m}{(C + C_\mu)s + \frac{1}{R}}$$

$$(b) \quad h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{R_x + \frac{1}{\frac{1}{R} + (C + C_\mu)s}}{I_1} = R_x + \frac{1}{\frac{1}{R} + (C + C_\mu)s}$$

(c) Under the condition that  $I_1 = 0$ ,  $V_1 = V$ . Using voltage division from  $V_2$  to  $V$  :

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{V}{V_2} = \frac{\frac{1}{\frac{1}{R} + C s}}{\frac{1}{C_\mu s} + \frac{1}{\frac{1}{R} + C s}} = \frac{C_\mu s}{\frac{1}{R} + C s + C_\mu s} = \frac{C_\mu s}{(C + C_\mu)s + \frac{1}{R}}$$

$$(d) \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{\frac{g_m V + \frac{1}{R} + C s V}{C_\mu s}}{\frac{(C + C_\mu)s + \frac{1}{R}}{C_\mu s}} = \frac{C_\mu s C s + g_m + \frac{1}{R}}{(C + C_\mu)s + \frac{1}{R}}$$

**SOLUTION PROBLEM 19.50:** (a) Recall t-parameter relationship:

$$\begin{array}{cccc} V_1 & & t_{11} & t_{12} & V_2 \\ I_1 & = & t_{21} & t_{22} & -I_2 \end{array}$$

For the given network,  $V_2 = Z_L(-I_2)$  and

$$V_1 = t_{11}V_2 + t_{12}(-I_2) = t_{11}Z_L(-I_2) + t_{12}(-I_2) = (t_{11}Z_L + t_{12})(-I_2)$$

Further,

$$I_1 = t_{21}V_2 + t_{22}(-I_2) = (t_{21}Z_L + t_{22})(-I_2)$$

Hence,

$$Z_{in} = \frac{V_1}{I_1} = \frac{(t_{11}Z_L + t_{12})(-I_2)}{(t_{21}Z_L + t_{22})(-I_2)} = \frac{t_{11}Z_L + t_{12}}{t_{21}Z_L + t_{22}}$$

(b) For the output impedance relationship, from the t-parameter relationships

$$V_1 = Z_s(-I_1) = t_{11}V_2 + t_{12}(-I_2) = -Z_s(t_{21}V_2 + t_{22}(-I_2))$$

Grouping  $V_2$  and  $I_2$  terms together on separate sides of the equation implies

$$(t_{21}Z_s + t_{11})V_2 = (t_{22}Z_s + t_{12})I_2$$

Thus

$$Z_{out} = \frac{V_2}{I_2} = \frac{t_{22}Z_s + t_{12}}{t_{21}Z_s + t_{11}}$$

**SOLUTION PROBLEM 19.51:**

45. From the z-parameter relationships

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad V_1 - z_{11}I_1 = z_{12}I_2 = -z_{12}(-I_2)$$

and

$$V_2 = z_{21}I_1 + z_{22}I_2 \quad z_{21}I_1 = V_2 + z_{22}(-I_2)$$

These two equations in matrix form are:

$$\begin{bmatrix} 1 & -z_{11} \\ 0 & z_{21} \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 0 & -z_{12} \\ 1 & z_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Solving for  $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix}^T$  yields

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \frac{1}{z_{21}} \begin{bmatrix} z_{21} & z_{11} & 0 & -z_{12} \\ 0 & 1 & 1 & z_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \frac{1}{z_{21}} \begin{bmatrix} z_{21} & z_{11} & z_{21} & -z_{12} \\ 1 & z_{22} & 1 & -I_2 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

**SOLUTION PROBLEM 19.52:** For figure 19.52a, by inspection

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Therefore T is as indicated in the problem.

For figure 19.52b, by inspection

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Therefore T is as indicated in the problem.

**SOLUTION PROBLEM 19.53:** Here we use the results of problem 19.52:

(a) For figure (a)

$$T_{new} = \begin{bmatrix} 1 & Z_1 & 1 & 0 \\ 0 & 1 & Y_2 & 1 \end{bmatrix} = \begin{bmatrix} 1 + Z_1 Y_2 & Z_1 \\ Y_2 & 1 \end{bmatrix}$$

(b) For figure (b)

$$T_{new} = \begin{matrix} 1 & 0 & 1 & Z_1 \\ Y_2 & 1 & 0 & 1 \end{matrix} = \begin{matrix} 1 & Z_1 \\ Y_2 & 1 + Z_1 Y_2 \end{matrix}$$

**SOLUTION PROBLEM 19.54:** By the properties of an ideal transformer,

$$V_1 = nV_2 \quad I_1 = \frac{-1}{n} I_2 = \frac{1}{n} (-I_2)$$

Therefore

$$\begin{matrix} V_1 & n & 0 & V_2 \\ I_1 & 0 & 1/n & -I_2 \end{matrix}$$

with the t-parameters given by the 2x2 matrix.

**SOLUTION PROBLEM 19.55:** This problem uses the results of the previous two problems.

(a)

$$T = \begin{matrix} 1 + Z_1 Y_2 & Z_1 & n & 0 \\ Y_2 & 1 & 0 & 1/n \end{matrix} = \begin{matrix} n(1 + Z_1 Y_2) & Z_1/n \\ nY_2 & 1/n \end{matrix}$$

(b)

$$T = \begin{matrix} n & 0 & 1 + Z_1 Y_2 & Z_1 \\ 0 & 1/n & Y_2 & 1 \end{matrix} = \begin{matrix} n(1 + Z_1 Y_2) & nZ_1 \\ Y_2/n & 1/n \end{matrix}$$

**SOLUTION PROBLEM 19.56:**

(a)

$$T = \begin{matrix} 0.25 & 0 & 8 & 4 \\ 0 & 4 & 2 & 5 \end{matrix} = \begin{matrix} 2 & 1 \\ 8 & 20 \end{matrix}$$

(b)

$$T = \begin{matrix} 1 & 0 & 8 & 4 \\ 1/R & 1 & 2 & 5 \end{matrix} = \begin{matrix} 8 & 4 \\ 2 + 8/R & 5 + 4/R \end{matrix}$$

(c)

$$T = \begin{matrix} 1 + Z_1 Y_2 & Z_1 & 8 & 4 \\ Y_2 & 1 & 2 & 5 \end{matrix} = \begin{matrix} 1 + 0.25s & 0.5s & 8 & 4 \\ 0.5 & 1 & 2 & 5 \end{matrix} = \begin{matrix} 8 + 3s & 4 + 3.5s \\ 6 & 7 \end{matrix}$$

**SOLUTION PROBLEM 19.57:** For each 2-port of the form of figure P19.53a, we have that the t-parameters are given by

$$T = \begin{array}{cc} 1 + Z_1 Y_2 & Z_1 \\ Y_2 & 1 \end{array}$$

The given network consists of three such sections in cascade whose t-parameters are respectively,

$$T_1 = \begin{array}{cc} 1 + s^2 & s \\ s & 1 \end{array}, \quad T_2 = \begin{array}{cc} 1 + 1 \times 0.5s & 1 \\ 0.5s & 1 \end{array} = \begin{array}{cc} 1 + 0.5s & 1 \\ 0.5s & 1 \end{array}, \text{ and}$$

$$T_3 = \begin{array}{cc} 1 + 2s \times \frac{1}{4}s & 2s \\ \frac{1}{4}s & 1 \end{array} = \begin{array}{cc} 1 + \frac{1}{2}s^2 & 2s \\ \frac{1}{4}s & 1 \end{array}$$

Observe that

$$T_1 T_2 = \begin{array}{cc} \frac{1}{2}s^3 + \frac{3}{2}s^2 + \frac{1}{2}s + 1 & s^2 + s + 1 \\ \frac{1}{2}s^2 + \frac{3}{2}s & s + 1 \end{array}$$

and the overall t-parameters are

$$T = T_1 T_2 T_3 = \begin{array}{cc} \frac{1}{4}s^5 + \frac{3}{4}s^4 + s^3 + \frac{9}{4}s^2 + \frac{3}{4}s + 1 & s^4 + 3s^3 + 2s^2 + 3s + 1 \\ \frac{1}{4}s^4 + \frac{3}{4}s^3 + \frac{3}{4}s^2 + \frac{7}{4}s & s^3 + 3s^2 + s + 1 \end{array}$$

**SOLUTION PROBLEM 19.58:** This problem is done primarily in MATLAB.

**Part (a)**

% The following code solves part (a) of the problem.

% Parameter Specification

t11= 0.895+j\*0.022;

t22= t11;

t12= 40 + j\*180;

% t21= (t11\*t22 -1)/t12;

% The above formula follows because it is a reciprocal network.

% The actual value is specified.

t21= -2.6175e-05+j\*1.1023e-03;

t=[t11 t12; t21 t22]

% Part (a) calculations

vr= 115200

ir = 361

vs= t11\*vr +t12\*ir

magvs=abs(vs)

angvs= angle(vs)\*180/pi

```

is=t21*vr+t22*ir
magis= abs(is)
angis= angle(is)*180/pi
pscomp=vs*conj(is)
ps=real(pscomp)
pr=real(vr*conj(ir))
eff= pr/ps
pf= ps/abs(pscomp)
ploss= ps- pr

```

The MATLAB output is as follows:

```

T =
 8.9500e-01 + 2.2000e-02i 4.0000e+01 + 1.8000e+02i
-2.6175e-05 + 1.1023e-03i 8.9500e-01 + 2.2000e-02i
vr = 115200
ir = 361

vs = 1.1754e+05 + 6.7514e+04i
magvs = 1.3555e+05
angvs = 2.9872e+01

is = 3.2008e+02 + 1.3493e+02i
magis = 3.4736e+02
angis = 2.2857e+01

pscomp = 4.6733e+07 + 5.7501e+06i
ps = 4.6733e+07
pr = 41587200

eff = 8.8989e-01
pf = 9.9252e-01
ploss = 5.1458e+06

```

### Part (b)

% The following code solves part (b) of the problem.

```

zL=500;
zin=(t11*zL + t12)/(t21*zL + t22)
yin = 1/zin
vsnew=134000;
iin= yin*vsnew
psnew= vsnew^2*real(yin)
m= inv(t)
v2=m(1,1)*vsnew +m(1,2) *iin
magv2=abs(v2)
iload= m(2,1) *vsnew + m(2,2)* iin
magild = abs(iload)
% Check value of rload
rload=abs(v2)/abs(iload)

```

The MATLAB output for part (b) is:

```

zin = 4.8759e+02 - 1.0031e+02i
yin = 1.9676e-03 + 4.0478e-04i
iin = 2.6366e+02 + 5.4241e+01i
psnew = 3.5331e+07

```

% m is the inverse of T-matrix.

```

m =
 8.9500e-01 + 2.2000e-02i -4.0000e+01 - 1.8000e+02i
 2.6175e-05 - 1.1023e-03i 8.9500e-01 + 2.2000e-02i

```

```

v2 = 1.1915e+05 - 4.6681e+04i
magv2 = 1.2796e+05
iloat = 2.3829e+02 - 9.3362e+01i
magild = 2.5593e+02
rload = 5.0000e+02

```

**SOLUTION PROBLEM 19.59.** From the given information, the circuit is linear and reciprocal. (a) Here  $i_2(t)$  is the integral of  $i_1(t)$ . Therefore, the new  $v_1(t)$  is the integral of the old  $v_2(t)$ . The result for  $t > 0$  is:

$$\begin{aligned}
 v_1(t) &= 3.005 - 3e^{-t} + e^{-t}[0.00865\sin(500t) - 0.005\cos(500t)] \\
 &= 3.005 - 3e^{-t} + e^{-t}\left[-2 \cdot 10^{-5}\cos(500t - \pi/6) + 0.01\sin(500t - \pi/6)\right]
 \end{aligned}$$

(b) From the problem statement

$$z_{21}(s) = \frac{3}{s+1} + 5 \frac{\cos \frac{\pi}{6} (s+1) + 250}{(s+1)^2 + (500)^2}$$

From reciprocity,  $z_{12}(s) = z_{21}(s)$ . For steady state analysis, we use phasors to obtain

$$\mathbf{V}_1 = z_{12}(j500)\mathbf{I}_2 = \frac{3}{1+j500} + 5 \frac{\cos \frac{\pi}{6} (1+j500) + 250}{(1+j500)^2 + (500)^2}$$

$$v_{1ss}(t) = 2.505\cos(500t - 30.15^\circ) \text{ V}$$

**SOLUTION PROBLEM 19.60.** Writing loop equations we have:

(i) For the left loop,

$$V_1 - aV_2 - 3(I_1 + I_3) = 0 \quad V_1 - aV_2 = 3I_1 + 3I_3$$

(ii) For the right loop,

$$V_2 + bI_1 - (I_2 - I_3) = 0 \quad V_2 = -bI_1 + I_2 - I_3$$

(iii) For the middle loop,

$$bI_1 + (I_3 - I_2) + I_3 + 3(I_1 + I_3) = 0 \quad 0 = (b + 3)I_1 - I_2 + 5I_3$$

Writing the first two equations in matrix form yields

$$\begin{array}{ccc|ccc} 1 & -a & V_1 & 3 & 0 & 3 & I_1 \\ 0 & 1 & V_2 & -b & 1 & -1 & I_2 \\ & & & & & & I_3 \end{array}$$

whose solution is

$$\begin{array}{l} V_1 \\ V_2 \end{array} = \begin{array}{ccc|ccc} 1 & a & 3 & 0 & 3 \\ 0 & 1 & -b & 1 & -1 \end{array} \begin{array}{l} I_1 \\ I_2 \\ I_3 \end{array} = \begin{array}{ccc|ccc} 3-ab & a & 3-a \\ -b & 1 & -1 \end{array} \begin{array}{l} I_1 \\ I_2 \\ I_3 \end{array}$$

Hence

$$\begin{array}{l} V_1 \\ V_2 \end{array} = \begin{array}{cc|c} 3-ab & a & I_1 \\ -b & 1 & I_2 \end{array} + \begin{array}{c} 3-a \\ -1 \end{array} I_3$$

From the third equation

$$I_3 = \begin{bmatrix} -0.2b - 0.6 & 0.2 \end{bmatrix} \begin{array}{l} I_1 \\ I_2 \end{array}$$

Thus

$$\begin{array}{l} V_1 \\ V_2 \end{array} = \begin{array}{cc|c} 3-ab & a \\ -b & 1 \end{array} + \begin{array}{c} 3-a \\ -1 \end{array} \begin{bmatrix} -0.2b - 0.6 & 0.2 \end{bmatrix} \begin{array}{l} I_1 \\ I_2 \end{array}$$

$$\begin{array}{l} V_1 \\ V_2 \end{array} = \begin{array}{cc|c} -0.6b - 0.8ab + 0.6a + 1.2 & 0.6 + 0.8a \\ -0.8b + 0.6 & 0.8 \end{array} \begin{array}{l} I_1 \\ I_2 \end{array}$$

For reciprocity,

$$z_{12} = z_{21} \quad a = -b$$

**SOLUTION PROBLEM 19.61.** (a) and (b) together: Observe that

$$V_1 - 0.5V_1 - I_1 = V_2 \quad I_1 = 0.5V_1 - V_2 \quad V_1 = 2I_1 + 2V_2$$

and

$$I_1 + I_2 = 0.5(V_2 - aI_1) \quad I_2 = -(0.5a + 1)I_1 + 0.5V_2$$

The h-parameters are

$$H = \begin{array}{cc} 2 & 2 \\ -(0.5a + 1) & 0.5 \end{array}$$

Reciprocity requires that

$$h_{12} = -h_{21} \quad 2 = 0.5a + 1 \quad a = 2$$

Thus

$$H = \begin{bmatrix} 2 & 2 \\ -2 & 0.5 \end{bmatrix}$$

**SOLUTION PROBLEM 19.62.** There are 2 corrections in the problem statement concerning the second set of expressions:

$$(1) \quad v_1(t) = 2e^{-t} - 1.5e^{-1.5t} \text{ V}$$

$$(2) \quad i_2(t) = 0.5 e^{-1.5t} \text{ A}$$

For both parts, recall, the y-parameters:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

(a) Part-1: From the first set of given data ( $V_2 = 0$ )

$$I_1 = \frac{1}{s}, \quad I_2 = \frac{0.5}{s+1}, \quad V_1 = \frac{0.5}{s+1} + \frac{0.5}{(s+1)^2} = \frac{0.5(s+2)}{(s+1)^2}$$

Hence,

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{2(s+1)^2}{s(s+2)}, \quad y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{s+1}{s+2}$$

(a) Part-2: From the second set of given data ( $Z_L = 1$ ,  $I_1 = 1/s$ , etc.), we have

$$I_2 = \frac{0.5}{s+1.5}, \quad V_1 = \frac{2}{s+1} - \frac{1.5}{s+1.5} = \frac{0.5(s+3)}{(s+1)(s+1.5)}$$

For a terminated 2-port,

$$I_2 = \frac{-V_2}{Z_L} = -V_2 = \frac{y_{21}}{y_{22} + Y_L} V_1 = \frac{y_{21}}{y_{22} + 1} V_1$$

Therefore

$$y_{22} = y_{21} \frac{V_1}{I_2} - 1 = \frac{s+1}{s+2} \times \frac{0.5(s+3)}{(s+1)(s+1.5)} \times \frac{s+1.5}{0.5} - 1 = \frac{(s+3)}{(s+2)} - 1 = \frac{1}{s+2}$$

Also,  $I_1 = y_{11}V_1 + y_{12}V_2$   $y_{12} = \frac{I_1 - y_{11}V_1}{V_2} = \frac{I_1 - y_{11}V_1}{-I_2}$ . Hence

$$y_{12} = -\frac{s+1.5}{0.5} \times \frac{1}{s} - \frac{2(s+1)^2}{s(s+2)} \frac{0.5(s+3)}{(s+1)(s+1.5)} = -\frac{(2s+3)(s+2)}{s(s+2)} + \frac{2(s+1)(s+3)}{s(s+2)}$$

$$= \frac{1}{(s+2)}$$

In conclusion

$$\begin{array}{l} y_{11} \ y_{12} \\ y_{21} \ y_{22} \end{array} = \begin{array}{l} \frac{2(s+1)^2}{s(s+2)} \quad \frac{1}{(s+2)} \\ \frac{s+1}{s+2} \quad \frac{1}{(s+2)} \end{array} = \frac{1}{(s+2)} \begin{array}{l} \frac{2(s+1)^2}{s} \quad 1 \\ \frac{s}{s+1} \quad 1 \end{array}$$

(b) This is a straightforward application of the conversion table 19.1.

**SOLUTION PROBLEM 19.63.** (a) Consider figure (a). Write two mesh equations:

$$V_1 = 16I_1 + \frac{2}{s}(I_1 + I_2) + 4I_1 = 20 + \frac{2}{s} I_1 + \frac{2}{s} I_2$$

$$V_2 = sI_2 + \frac{2}{s}(I_1 + I_2) + 4I_1 = 4 + \frac{2}{s} I_1 + s + \frac{2}{s} I_2$$

Therefore

$$Z = \frac{1}{s} \begin{array}{cc} 20s+2 & 2 \\ 4s+2 & s^2+2 \end{array}$$

Taking the inverse yields the y-parameters

$$Y = \frac{1}{Z} \begin{array}{cc} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{array} = \frac{1}{20s^2 + 2s + 32} \begin{array}{cc} s^2 + 2 & -2 \\ -(4s + 2) & 20s + 2 \end{array}$$

where

$$Z = \frac{(20s+2)(s^2+2) - 2(4s+2)}{s} = \frac{20s^3 + 2s^2 + 32s}{s} = 20s^2 + 2s + 32$$

Finally, the h-parameters are given as

$$H = \begin{array}{cc} 1/y_{11} & z_{12}/z_{22} \\ -z_{21}/z_{22} & 1/z_{22} \end{array} = \frac{1}{s^2+2} \begin{array}{cc} 20s^2 + 2s + 32 & 2 \\ -(4s+2) & s \end{array}$$

(b) Now consider figure (b).  $z_{11}$  is  $V_1$  when  $I_2 = 0$ . But if  $I_2 = 0$ , then because of the ideal transformer  $I_1 = 0$ , meaning that the ratio is not defined. Hence the z-parameters do not exist.

To find the h-parameters, observe that because of the ideal transformer,  $I_2 = -0.5I_1$ ,  $I_1 = -2I_2$ , and  $V_{pri} = 0.5V_{sec}$ . Writing a mesh equation at the right mesh first we obtain

$$V_2 = RI_2 + V_{sec} + (I_1 + I_2)R = V_{sec}$$

Now writing a mesh equation on the left we have

$$V_1 = RI_1 + V_{pri} + (I_1 + I_2)R = 1.5RI_1 + V_{pri} = 1.5RI_1 + 0.5V_2$$

Therefore

$$H = \begin{bmatrix} 1.5R & 0.5 \\ -0.5 & 0 \end{bmatrix}$$

To obtain the y-parameters we use table 19.1:

$$Y = \begin{bmatrix} \frac{1}{h_{11}} & \frac{1}{h_{21}} & -\frac{h_{12}}{h} \\ \frac{1}{h_{11}} & \frac{1}{h_{21}} & -\frac{h_{12}}{h} \end{bmatrix} = \begin{bmatrix} \frac{1}{6R} & \frac{4}{-2} & \frac{-2}{1} \end{bmatrix}$$

Note: the  $\det[Y] = 0$  implying again that the z-parameters do not exist.

(c) For this network we consider it as a cascade (left to right) of an ideal transformer, the middle network of a transformer and an inductor across the top, and finally another ideal transformer. The t-parameters of these two ports are respectively:

$$T_1 = \begin{bmatrix} a & 0 \\ 0 & 1/a \end{bmatrix}, T_2 = \begin{bmatrix} A & B \\ C & D \end{bmatrix}, T_3 = \begin{bmatrix} 1/b & 0 \\ 0 & b \end{bmatrix}$$

To find  $T_2$ , we replace the mutually coupled inductors by the pi-equivalent circuit of figure

18.25c where  $L_1 = 4$  H,  $L_2 = 9$  H,  $M = k\sqrt{L_1L_2} = 3$  H, and  $k = 0.75$ . Thus  $L_{left} = \frac{L_1M}{L_2 - M} = 4.5$

H,  $L_{right} = \frac{L_2M}{L_1 - M} = 27$  H, and  $L_{top} = \frac{M^2}{M} = 9$  H. Notice that the external 9 H inductor is in parallel with  $L_{top}$  leading to  $L_{par} = 4.5$  H. The y-matrix of this new pi-network is by inspection:

$$Y_{mid} = \begin{bmatrix} \frac{1}{s} & 2/4.5 & -1/4.5 \\ \frac{1}{s} & -1/4.5 & 1/27 + 1/4.5 \end{bmatrix} = \begin{bmatrix} \frac{1}{27s} & 12 & -6 \\ \frac{1}{27s} & -6 & 7 \end{bmatrix}$$

To compute the t-parameters we have

$$T_2 = \begin{bmatrix} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{-y_{12}}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{bmatrix} = \begin{bmatrix} 7/6 & 4.5s \\ 8/27s & 2 \end{bmatrix}$$

Therefore

$$T = T_1 T_2 T_3 = \begin{bmatrix} a & 0 & 7/6 & 4.5s & 1/b & 0 & 7a/6b & 4.5abs \\ 0 & 1/a & 8/27s & 2 & 0 & b & 8/27abs & 2b/a \end{bmatrix}$$

From table 19.1, we obtain

$$H = \begin{matrix} a^2 2.25s & 0.5a/b \\ -0.5a/b & 4/27b^2 \end{matrix}, \quad Z = s \begin{matrix} \frac{63a^2}{16} & \frac{27ab}{8} \\ \frac{27ab}{8} & \frac{27b^2}{4} \end{matrix}, \quad Y = \frac{1}{27a^2b^2s} \begin{matrix} 12b^2 & -6ab \\ -6ab & 7a^2 \end{matrix}$$

**SOLUTION PROBLEM 19.64.**

(a) The defining equation for the g-parameters is:

$$\begin{matrix} I_1 \\ V_2 \end{matrix} = \begin{matrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{matrix} \begin{matrix} V_1 \\ I_2 \end{matrix}$$

Because of the load impedance  $Z_L$ , we have  $V_2 = -Z_L I_2$ . Hence substituting for  $V_2$  in the second equation yields

$$V_2 = g_{21}V_1 + g_{22}I_2 = -Z_L I_2 \quad I_2 = \frac{-g_{21}V_1}{g_{22} + Z_L}$$

Substituting this equation into  $I_1 = g_{11}V_1 + g_{12}I_2$  we obtain

$$I_1 = g_{11}V_1 - g_{12} \frac{g_{21}V_1}{g_{22} + Z_L} = g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L} V_1$$

Therefore,

$$Y_{in} = g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L}$$

(b) Because of the source impedance  $Z_s$ , we have  $V_1 = -Z_s I_1$  or  $I_1 = -Y_s V_1$ . Hence substituting for  $V_1$  in the first equation yields

$$I_1 = g_{11}V_1 + g_{12}I_2 = -Y_s V_1 \quad V_1 = \frac{-g_{12}I_2}{g_{11} + Y_s}$$

Substituting this equation into  $V_2 = g_{21}V_1 + g_{22}I_2$  we obtain

$$V_2 = g_{21} \frac{-g_{12}I_2}{g_{11} + Y_s} + g_{22}I_2 = g_{22} - \frac{g_{12}g_{21}}{g_{11} + Y_s} I_2 \quad Z_{out} = g_{22} - \frac{g_{12}g_{21}}{g_{11} + Y_s}$$

(c)

$$G_1 = \frac{V_1}{V_s} = \frac{Z_{in}}{Z_s + Z_{in}} = \frac{Y_s}{Y_s + Y_{in}} = \frac{Y_s}{Y_s + g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L}} = \frac{Y_s(g_{22} + Z_L)}{(g_{22} + Z_L)(g_{11} + Y_s) - g_{12}g_{21}}$$

(d) Refer to figure P19.64, where  $V_2 = \frac{Z_L}{g_{22} + Z_L} g_{21}V_1$   $G_2 = \frac{V_2}{V_1} = \frac{g_{21}Z_L}{g_{22} + Z_L}$ .

$$(e) G_v = G_1 G_2 = \frac{Y_s (g_{22} + Z_L)}{(g_{22} + Z_L)(g_{11} + Y_s) - g_{12} g_{21}} \times \frac{g_{21} Z_L}{g_{22} + Z_L} = \frac{g_{21} Y_s Z_L}{(g_{22} + Z_L)(g_{11} + Y_s) - g_{12} g_{21}}$$

**SOLUTION PROBLEM 19.65.** Recall

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

For the given circuit

$$V_2 = \frac{1}{4}(I_2 - 4V_2) + V_1 \quad V_2 = \frac{1}{2}V_1 + \frac{1}{8}I_2$$

Also

$$V_2 = V_1 - \frac{1}{4}(I_1 - sV_1)$$

This implies that

$$I_1 = (4 + s)V_1 - 4V_2 = (4 + s)V_1 - 4\left(\frac{1}{2}V_1 + \frac{1}{8}I_2\right) = (2 + s)V_1 - \frac{1}{2}I_2$$

Thus the g-parameter matrix is:

$$G = \begin{bmatrix} 2 + s & -\frac{1}{2} \\ \frac{1}{2} & \frac{1}{8} \end{bmatrix}$$

**SOLUTION PROBLEM 19.66.** We first convert the y-parameters to t-parameters using table 19.1:

$$Y_{N1} \quad T_{N1} = \begin{bmatrix} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{-y_{12}}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{bmatrix} = \begin{bmatrix} -0.1 & -0.5 \\ -3.82 & -25.1 \end{bmatrix}$$

where  $y = 50.2 \times 0.2 - 2 \times 1.2 = 7.64$ . Now we convert the h-parameters to t-parameters using table 19.1:

$$H_{N2} \quad T_{N2} = \begin{bmatrix} \frac{-h}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{-h_{21}}{h_{21}} & \frac{-1}{h_{21}} \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 56 & 13 \\ 2 & 1 \end{bmatrix} = \begin{bmatrix} 11.2 & 2.6 \\ 0.4 & 0.2 \end{bmatrix}$$

where  $h = 13 \times 2 + 6 \times 5 = 56$ . To obtain the cascaded t-parameters we compute

$$T_{cas} = T_{N1}T_{N2} = \frac{1}{5} \begin{bmatrix} -6.6 & -1.8 \\ -264.12 & -74.76 \end{bmatrix} = \begin{bmatrix} -1.32 & -0.36 \\ -52.824 & -14.952 \end{bmatrix}$$

Thus,

$$Y_{in} = \frac{1}{Z_{in}} = \frac{t_{21}Z_L + t_{22}}{t_{11}Z_L + t_{12}} = \frac{\frac{603}{5}}{\frac{15}{5}} = 40.2 \text{ S}$$

To obtain the voltage gain, we first convert the t-parameters back to y-parameters (table 19.1) and then use the derived voltage gain formula:

$$T_{cas} = \begin{bmatrix} -1.32 & -0.36 \\ -52.824 & -14.952 \end{bmatrix} \quad Y_{cas} = \begin{bmatrix} 41.533 & 2 \\ 2.7778 & 3.6667 \end{bmatrix} \text{ S}$$

Hence,

$$G_v = \frac{V_L}{V_1} = \frac{-y_{21}}{y_{22} + Y_L} = \frac{-2.7778}{3.6667 + 0.5} = -0.66667$$

Alternately, one could consider the load as a 2-port, compute its t-parameters, construct the overall t-parameters as a cascade of three networks, and then use  $G_v = \frac{1}{t_{11}}$ .

### SOLUTION PROBLEM 19.67.

(a) Since only one  $C$  or  $L$ , we have in general:  $H(s) = \frac{as + b}{cs + d}$ . Since  $H(\infty) = 0 = \frac{a}{c}$ , we have that  $a = 0$ . Therefore,

$$H(s) = \frac{\frac{b}{c}}{s + \frac{d}{c}} = \frac{K}{s + \omega_c}$$

(b) To prove that  $\omega_c = \frac{1}{R_{th}C}$  or  $\frac{R_{th}}{L}$  where  $R_{th}$  is the Thevenin resistance seen by the energy storage element, we refer the reader to problem 19.69 which provides a general derivation with  $H(\infty)$  arbitrary; hence this problem is the special case of  $H(\infty) = 0$ .

(c) Here  $R_{th} = 2000 / (50 + 1000 / 200) = 195.49 \text{ } \Omega$ . Hence

$$\omega_c = \frac{1}{R_{th}C} = 25.58 \times 10^6 \text{ rad/s}$$

**SOLUTION PROBLEM 19.68.**

(a) Because there is only one energy storage element, it follows that the most general form of the transfer function is:  $H(s) = \frac{as + b}{cs + d}$ . Since  $H(0) = 0 = \frac{b}{d}$ , we have  $b = 0$ . Further, since the transfer function is high pass,  $c \neq 0$ , and

$$H(s) = \frac{as}{cs + d} = \frac{\frac{a}{c}s}{s + \frac{d}{c}} = \frac{Ks}{s + \omega_c}$$

(b) To prove that  $\omega_c = \frac{1}{R_{th}C}$  or  $\frac{R_{th}}{L}$  where  $R_{th}$  is the Thevenin resistance seen by the energy storage element, we refer the reader to problem 19.69 which provides a general derivation with  $H(0)$  arbitrary; hence this problem is the special case of  $H(0) = 0$ .

(c) Let us apply the result of example 19.1 to that part of the circuit to the right of the 1 k resistor and call the associated resistance  $Z_{in}$ . Here  $Z_1 = 1 \text{ k}$ ,  $Z_2 = 2 \text{ k}$ ,  $Z_L = 100 \text{ } \Omega$ , and  $\beta = 50$ . Hence

$$Z_{in} = (\beta + 1)Z_L = 5.1 \text{ k}$$

Thus


$$R_{th} = 200 + 1000 \parallel (2000 + 5100) = 1076.5$$

Hence,

$$\omega_c = \frac{1}{R_{th}C} = \frac{1}{1076.54 \times 2 \times 10^{-6}} = 464.45 \text{ rad/s}$$

**SOLUTION PROBLEM 19.69.** In this problem we assume (i) a single input single output system and that linear circuit seen by the energy storage element has a Thevenin equivalent or a Norton equivalent. For simplicity we will presume the existence of a Thevenin equivalent.

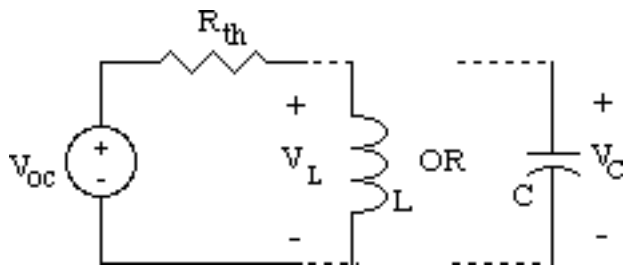(a) The Thevenin equivalent seen by the dynamic element L or C consists of  $Z_{th}(s)$  in series with  $V_{oc}(s)$ . Since the remainder network seen by L or C is non-dynamic (resistive, resistive with dependent sources and ideal op amps, etc), we have  $Z_{th}(s) = R_{th}$  and  $V_{oc}(s) = K_O \times \text{Input}(s)$ ,  $R_{th}$  and  $K_O$  being real constants.



By voltage division,

$$V_L = \frac{Ls}{Ls + R_{th}} V_{oc} = \frac{K_0 s}{s + \frac{R_{th}}{L}} \times Input(s) \quad (1)$$

and

$$V_C = \frac{\frac{1}{Cs}}{\frac{1}{Cs} + R_{th}} V_{oc} = \frac{\frac{K_0}{R_{th}C}}{s + \frac{1}{R_{th}C}} \times Input(s) \quad (2)$$

After  $V_L(s)$  or  $V_C(s)$  has been determined, we can find the Laplace transform of any other output (voltage or current) using the voltage source substitution theorem (chapter 6) and linearity (chapter 5):

$$Output(s) = K_1 \times Input(s) + K_2 (V_L(s) \text{ or } V_C(s)) \quad (3)$$

For the case of  $V_L(s)$ ,

$$Output(s) = K_1 + K_2 \frac{K_0 s}{s + \frac{R_{th}}{L}} \times Input(s) \quad (4)$$

and for the case of  $V_C(s)$ ,

$$Output(s) = K_1 + K_2 \frac{\frac{K_0}{R_{th}C}}{s + \frac{1}{R_{th}C}} \times Input(s) \quad (5)$$

For either case, the transfer function  $H(s)$  has the form

$$H(s) = \frac{Output(s)}{Input(s)} = \frac{K_3 s + K_4}{s + c} \quad (6)$$

where  $\tau_c = \frac{R_{th}}{L}$  or  $\frac{1}{R_{th}C}$  with  $K_3$  and  $K_4$  real constants.

It remains to give  $K_3$  and  $K_4$  some physical interpretations. In (6), let  $s = \infty$ , we have

$$H(\infty) = \frac{K_3s + K_4}{s + \tau_c} \Big|_{s=\infty} = K_3$$

On the other hand, letting  $s = 0$  in (6) produces

$$H(0) = \frac{K_3s + K_4}{s + \tau_c} \Big|_{s=0} = \frac{K_4}{\tau_c}$$

Substituting  $K_3$  and  $K_4$  into (6), we obtain the desired result

$$H(s) = \frac{Output(s)}{Input(s)} = \frac{H(\infty)s + \tau_c H(0)}{s + \tau_c} \quad (7)$$

(b) When  $s = \infty$ , the impedance of C is

$$Z_C(\infty) = \frac{1}{Cs} \Big|_{s=\infty} = 0$$

and the impedance of L is

$$Z_L(\infty) = Ls \Big|_{s=\infty} = \infty$$

Therefore in calculating  $H(\infty)$ , we may replace C by a short circuit and L by an open circuit. On the other hand, when  $s = 0$ , the impedance of C is

$$Z_C(0) = \frac{1}{Cs} \Big|_{s=0} = \infty$$

and the impedance of L is

$$Z_L(0) = Ls \Big|_{s=0} = 0$$

Therefore in calculating  $H(0)$ , we may replace C by an open circuit and L by a short circuit.

(c) For figure P19.69a, by inspection

$$R_{th} = 3 // (2 + 4) = 3 // 6 = 2$$

$$c = 1 / (R_{th} C) = 1 / (2 \times 0.5) = 1$$

$$H(\infty) = 4 / (2 + 4) = 2/3$$

$$H(0) = 4 / (2 + 3 + 4) = 4/9$$

Therefore

$$H(s) = \frac{H(\infty)s + cH(0)}{s + c} = \frac{\frac{2}{3}s + \frac{4}{9}}{s + 1} = \frac{\frac{2}{3}s + \frac{2}{3}}{s + 1}$$

For figure P19.69b

$$R_{th} = 3 // (2 + 4) = 3 // 6 = 2$$

$$c = R_{th} / L = 2 / 2 = 1$$

$$H(\infty) = 4 / (2 + 4) = 2/3$$

$$H(0) = 4 / (2 + 3 + 4) = 4/9$$

Therefore

$$H(s) = \frac{H(\infty)s + cH(0)}{s + c} = \frac{\frac{4}{9}s + \frac{2}{3}}{s + 1} = \frac{\frac{4}{9}(s + 1.5)}{s + 1}$$

**SOLUTION PROBLEM 19.70.** According to problem 19.68, the transfer function of the circuit is

$$H(s) = \frac{Ks}{s + \omega_c}$$

where  $\omega_c = \frac{1}{R_{th}C}$  and  $R_{th}$  is the Thevenin resistance seen by the storage element C. To find  $R_{th}$

we make use of figure 19.4 and the associated formula. The details are in the MATLAB code below:

```
»R1 = 200*1e3/1200
```

```
R1 =
```

```
1.6667e+02
```

```
»Z1 = R1+2e3
```

```
Z1 =
```

```
2.1667e+03
```

```
»Z3 = 100;
```

»beta = -50;  
 »Zout = Z1/(1+beta)  
 Zout =  
 -4.4218e+01  
 »Rth = 2000 + Zout  
 Rth =  
 1.9558e+03  
 »wc = 1/(Rth\*2e-6)  
 wc =  
 2.5565e+02


Hence

$$\omega_c = \frac{1}{1955.8 \times 2 \times 10^{-6}} = 255.65 \text{ rad/s}$$

**SOLUTION PROBLEM 19.71.** (a) Except for the terminating resistor, let the other element branches of the circuit be given by

$$Y_1 = \frac{1}{3s}, \quad Y_2 = \frac{1}{2s + \frac{1}{2s}} = \frac{2s}{4s^2 + 1}, \quad \text{and} \quad Z_3 = \frac{1}{s}$$

Consider the circuit

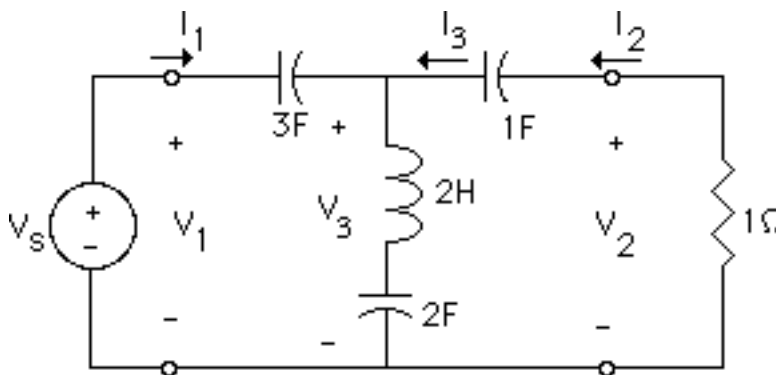

Here from problem 19.53a and from 19.52 a we obtain

$$\begin{array}{l} V_1 \\ I_1 \end{array} = \begin{array}{c} 1 + \frac{\frac{2}{3}}{4s^2 + 1} \\ \frac{2s}{4s^2 + 1} \end{array} \begin{array}{c} \frac{1}{3s} \\ 1 \end{array} \begin{array}{c} V_3 \\ -I_3 \end{array} \quad \text{and} \quad \begin{array}{c} V_3 \\ -I_3 \end{array} = \begin{array}{c} 1 \\ 0 \end{array} \begin{array}{c} \frac{1}{s} \\ 1 \end{array} \begin{array}{c} V_2 \\ -I_2 \end{array}$$

which implies that

$$\begin{array}{l} V_1 \\ I_1 \end{array} = \begin{array}{c} \frac{1}{4s^2 + 1} \\ \frac{2s}{4s^2 + 1} \end{array} \begin{array}{c} 4s^2 + 5/3 \\ 2s \end{array} \begin{array}{c} \frac{(16s^2 + 6)}{3s} \\ 4s^2 + 3 \end{array} \begin{array}{c} V_2 \\ -I_2 \end{array}$$

(b)

$$G_V(s) = \frac{-y_{21}}{y_{22} + y_L}$$


(c)

$$y_{21} = -\frac{1}{t_{12}} = -\frac{3s(4s^2 + 1)}{16s^2 + 6}, \quad y_{22} = \frac{t_{11}}{t_{12}} = \frac{3s \cdot 4s^2 + \frac{5}{3}}{16s^2 + 6} = \frac{s(12s^2 + 5)}{16s^2 + 6}, \quad \text{and } Y_L = 1$$

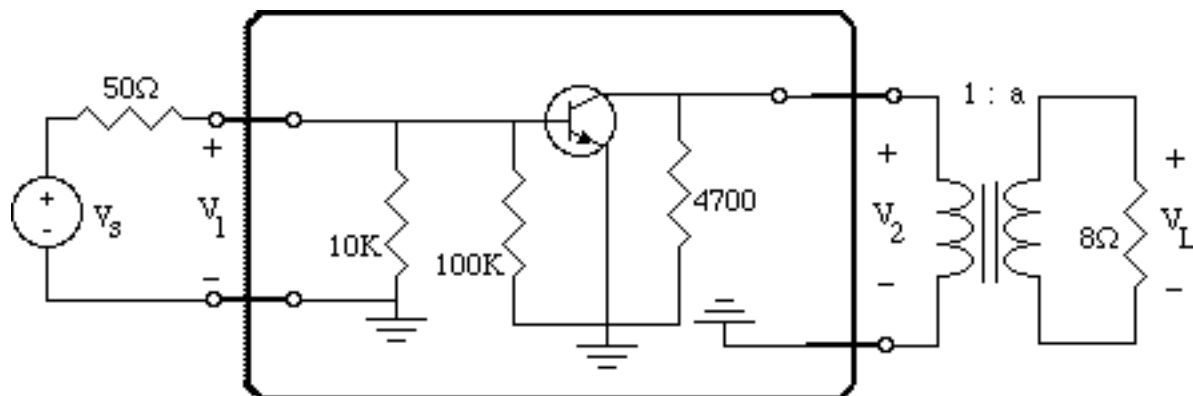(d) Hence,

$$G_V(s) = \frac{-y_{21}}{y_{22} + y_L} = \frac{\frac{3s(4s^2 + 1)}{16s^2 + 6}}{\frac{s(12s^2 + 5)}{16s^2 + 6} + 1} = \frac{3s(4s^2 + 1)}{12s^3 + 16s^2 + 5s + 6}$$

**SOLUTION PROBLEM 19.72.** For part (a), treating each capacitor as a short circuit yields the equivalent circuit below.



$$\gg h_{11T} = 4.2e3; \quad h_{12T} = 0; \quad h_{21T} = 150; \quad h_{22T} = 0.1e-3;$$

$$\gg hT = [h_{11T}, h_{12T}; h_{21T}, h_{22T}];$$

$$\gg yT = \text{htoy}(hT)$$

$$yT =$$

$$\begin{array}{cc} 2.3810e-04 & 0 \\ 3.5714e-02 & 1.0000e-04 \end{array}$$

By inspection, the  $y_{11}$  parameter of the overall two-port consists of the sum of  $y_{11T}$  plus the conductances of the two front end resistors. Also, the  $y_{22}$  parameter of the overall two port is  $y_{22T}$  plus the conductance of the 4.7k resistor. Hence,

$$\gg y = yT + [1/1e4 + 1/1e5 \quad 0; 0 \quad 1/4700]$$

$$y =$$

$$\begin{array}{cc} 3.4810e-04 & 0 \\ 3.5714e-02 & 3.1277e-04 \end{array}$$

Hence, the overall h-parameters are:

$$\gg h = \text{ytoh}(y)$$

$$h =$$

$$\begin{array}{cc} 2.8728e+03 & 0 \\ 1.0260e+02 & 3.1277e-04 \end{array}$$

(b)

$$\gg \text{yout} = h(2,2) - (h(1,2) * h(2,1) / (h(1,1) + 50))$$

$$\text{yout} =$$

$$3.1277e-04$$

$$\gg Z_{out} = 1/y_{out}$$

$$Z_{out} =$$

$$3.1973e+03$$

$$\gg a = \sqrt{8/Z_{out}}$$

$$a =$$

$$5.0021e-02$$

(c) To compute the gain we first need  $Z_{in}$ . From equation 19.49, since  $h_{12} = 0$ ,  $Z_{in} = h_{11}$ .

$$\gg Z_{in} = h(1,1)$$

$$Z_{in} =$$

$$2.8728e+03$$

From equation 19.51,

$$\gg G_{v2} = -h(2,1)/(Z_{in}*(h(2,2)+h(2,2)))$$

$$G_{v2} =$$

$$-5.7094e+01$$

From equation 19.52,

$$\gg G_{v1} = Z_{in}/(Z_{in} + 50)$$

$$G_{v1} =$$

$$9.8289e-01$$

To compute  $V_L/V_s$  we use:

$$\gg G_v = G_{v1}*G_{v2}*a$$

$$G_v =$$

$$-2.8071e+00$$

To compute  $V_L/V_1$  we use:

$$\gg G_{vv} = G_{v2}*a$$

$$G_{vv} =$$

$$-2.8559e+00$$

(d) For these calculations, we assume  $V_s$  is normalized to 1 V. Since we are computing gains, we may do this without loss of generality.

$$\gg V_s = 1;$$

$$\gg I_s = 1/(50 + Z_{in})$$

$$I_s =$$

$$3.4214e-04$$

Now we compute the normalized power delivered by the voltage source.

$$\gg P_{s\text{norm}} = V_s * I_s$$

$$P_{s\text{norm}} =$$

$$3.4214e-04$$

Next we compute the normalized power absorbed by the load.

$$\gg V_L = G_v * 1$$

$$V_L =$$

$$-2.8071e+00$$

$$\gg P_{L\text{norm}} = V_L^2 / 8$$

$$P_{L\text{norm}} =$$

$$9.8496e-01$$

Next, the power gain from source to load is:

$$\gg G_{pLs} = P_{L\text{norm}} / P_{s\text{norm}}$$

$$G_{pLs} =$$

$$2.8788e+03$$

Further, we compute the power gain from input to the two port to the load as follows:

$$\gg V_1 = V_s * Z_{in} / (Z_{in} + 50)$$

$$V_1 =$$

9.8289e-01

»P1 = V1\*Is

P1 =


3.3629e-04


»GpL1 = PLnorm/P1

GpL1 =

2.9289e+03

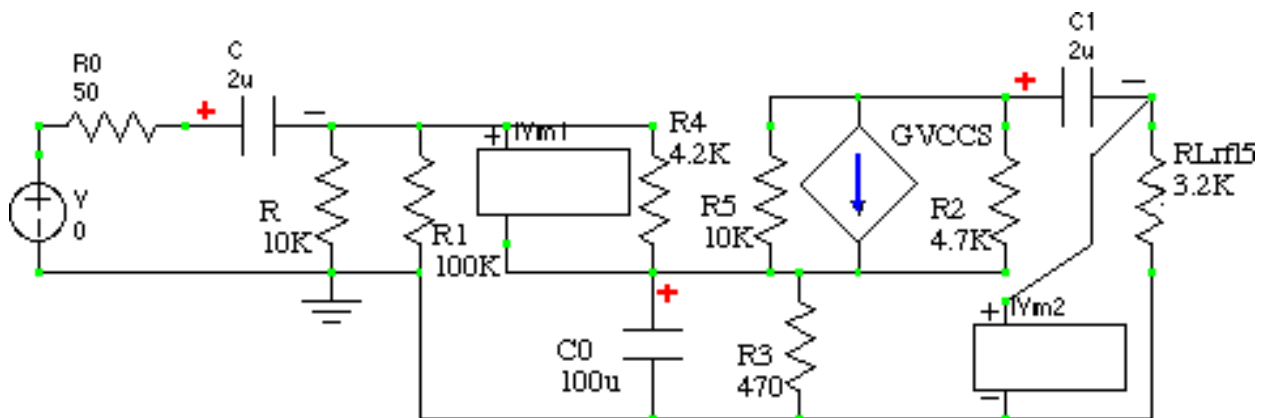- (e) SPICE Simulation Because the frequency response is flat for frequency above 800 Hz, we only plotted up to 1.6k Hz. The circuit diagram reflects the load back to the primary of the ideal transformer. In general, this is not possible. Hence for a SPICE simulation, it is necessary to use one of the models given in Figure 18.15 consisting of two controlled sources. For this example, this is not necessary. Note however that the actual output voltage is 0.05 times the values on the graph given below. This simulation assumes a 1 V source voltage and the parameter of GVCCS is 0.035714. Notice that in this problem



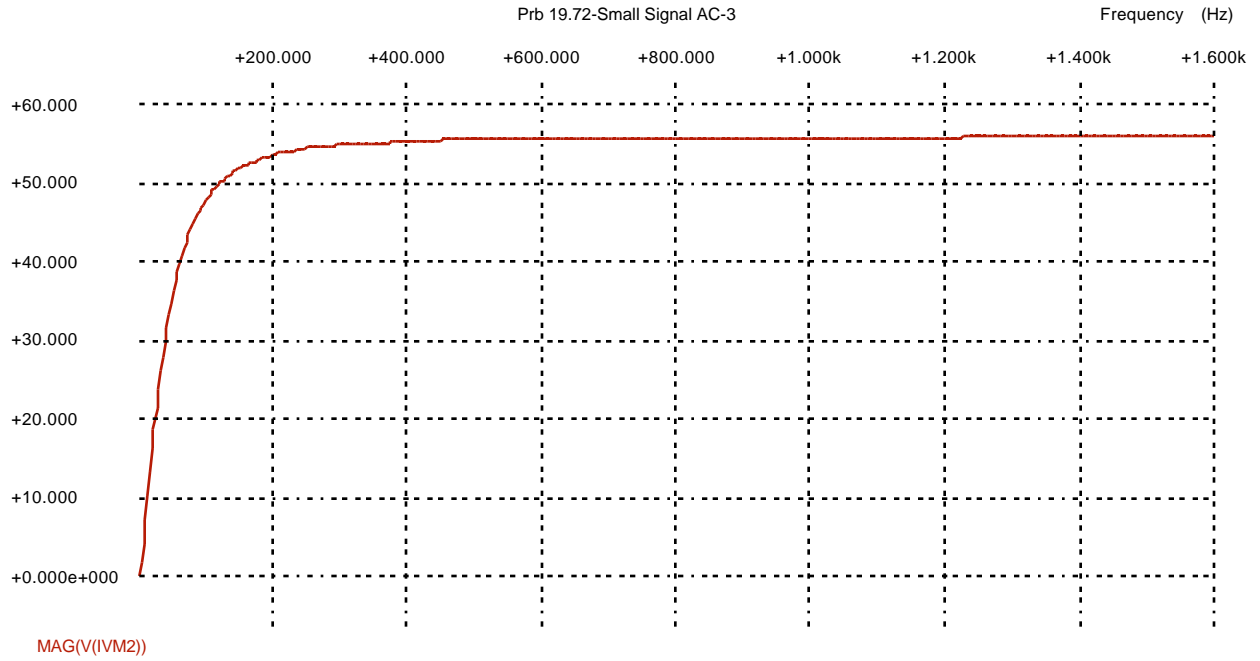

(f) For this part, we change  $100\ \mu\text{F}$  to  $10\ \mu\text{F}$ . The resulting plot shows degradation of the low end frequency response.

