

SOLUTIONS PROBLEMS CHAPTER 20

USEFUL MATLAB M-FILES FOR USE IN THE SOLUTION TO PROBLEMS IN THIS CHAPTER.

Program 1: converts y-parameters to t-parameters

```
% convert y parameters to t parameters
function [t,t11,t12,t21,t22] = ytot(y)
y11=y(1,1);
y12=y(1,2);
y21=y(2,1);
y22=y(2,2);
deltay= y11*y22-y12*y21;
t11=-y22/y21;
t12 = -1/y21;
t21= -deltay/y21;
t22= -y11/y21;
t= [ t11 t12; t21 t22];
```

Program 2: Computes Zin, Zout, and gains using two port h-parameters.

```
»% two-port analysis in terms of h-parameters
»function [zin, zout] =twoport(h, zL, zs)
»['twoport analysis using h-parameters']
»h11= h(1,1); h12=h(1,2); h21=h(2,1); h22=h(2,2);
»zin = h11 - h12*h21/(h22+ 1/zL)
»yout= h22 - h12*h21/(h11+zs);
»zout= 1/yout
»v1tovs= zin/(zin+zs)
»v2tov1= -h21/(zin*(h22+1/zL))
»v2tovs= v1tovs*v2tov1
```

Program 3: Computes Zin, Zout, and gains using two port y-parameters.

```
% two-port analysis in terms of y-parameters
function [zin, zout] =twoporty(y, zL, zs)
['twoport analysis using y-parameters']
y11= y(1,1); y12=y(1,2); y21=y(2,1); y22=y(2,2);
yin = y11 - y12*y21/(y22+ 1/zL)
zin= 1/yin
yout= y22 - y12*y21/(y11+1/zs)
zout= 1/yout
v1tovs= zin/(zin+zs)
v2tov1= -y21/(y22+1/zL)
v2tovs= v1tovs*v2tov1
```

Program 4: Computes Zin, Zout, and gains using two port t-parameters.

```
% two-port analysis in terms of t-parameters
function [zin, zout] =twoportt(t, zL, zs)
```

```

['analysis of terminated twoport using t-parameters']
t11= t(1,1); t12=t(1,2); t21=t(2,1); t22=t(2,2);
zin= (t11*zL + t12)/(t21*zL + t22)
zout= (t22*zs + t12)/(t21*zs + t11)
v2tov1= zL/(t11*zL + t12)
v1tovs= zin/(zin+zs)
v2tovs= v2tov1*v1tovs

```

Program 5: converts z-parameters to t-parameters

```

%converting z to t paramters (same sormulas as
%converting t to z parameters)

```

```

function [t,t11,t12,t21,t22] = ztot(z)
z11=z(1,1); z12=z(1,2); z21=z(2,1); z22=z(2,2);
deltaz= z11*z22 - z12*z21;
t11= z11/z21;
t12= deltaz/z21;
t21= 1/z21;
t22= z22/z21;
t= [ t11 t12; t21 t22];

```

SOLUTION 20.1.

For network a, the z-parameters are by inspection

$$Z_a = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix}$$

Similarly, for network b, the z-parameters are the same:

$$Z_b = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix}$$

The interconnection of networks a and b conforms to figure 20.2b, which is a series interconnection. Hence, the new overall z-parameters are

$$Z_{new} = Z_a + Z_b = 2 \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix}$$

SOLUTION 20.2. For networks a and b, the y-parameters are by inspection

$$Y_a = Y_b = \begin{bmatrix} 3 & -2 \\ -2 & 4 \end{bmatrix} \text{ S}$$

Hence, their z-parameters are the inverse of the y-parameter matrix:

$$Z_a = Z_b = \frac{1}{8} \begin{bmatrix} 4 & 2 \\ 2 & 3 \end{bmatrix}$$

The interconnection of networks a and b conforms to figure 20.2b, which is a series interconnection. Hence, the new overall z-parameters are

$$Z_{new} = Z_a + Z_b = \frac{1}{4} \begin{bmatrix} 4 & 2 \\ 2 & 3 \end{bmatrix}$$

SOLUTION 20.3. For network a consisting of the single inductor,

$$Z_a = \begin{bmatrix} s & s \\ s & s \end{bmatrix}$$

For network b, we have

$$Z_b = [Y_b]^{-1} = \frac{1}{2} \begin{bmatrix} 1 & 1 \\ 1 & 4 \end{bmatrix} = \begin{bmatrix} 0.5 & 0.5 \\ 0.5 & 2 \end{bmatrix}$$

The interconnection of networks a and b conforms to figure 20.2b, which is a series interconnection. Hence, the new overall z-parameters are

$$Z_{new} = Z_a + Z_b = \begin{bmatrix} s + 0.5 & s + 0.5 \\ s + 1 & s + 2 \end{bmatrix}$$

SOLUTION 20.4. For network a consisting of the single capacitor,

$$Z_a = \frac{1}{s} \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$

The interconnection of networks a and b conforms to figure 20.2b, which is a series interconnection. Hence, the new overall z-parameters are

$$Z_{new} = Z_a + Z_b = \frac{1}{s} \begin{bmatrix} 1 + 0.5s & 1 + 0.5s \\ 1 + s & 1 + 2s \end{bmatrix}$$

SOLUTION 20.5. For network a, the y-parameters are by inspection

$$Y_a = \begin{bmatrix} 3 & -2 \\ -2 & 3 \end{bmatrix} \text{ S}$$

Hence, their z-parameters are the inverse of the y-parameter matrix:

$$Z_a = \frac{1}{5} \begin{bmatrix} 3 & 2 \\ 2 & 3 \end{bmatrix} = \begin{bmatrix} 0.6 & 0.4 \\ 0.4 & 0.6 \end{bmatrix}$$

The interconnection of networks a and b conforms to figure 20.2b, which is a series interconnection. Hence, the new overall z-parameters are

$$Z_{new} = Z_a + Z_b = \begin{bmatrix} 1.6 & 0.9 \\ 0.4 & -0.4 \end{bmatrix}$$

SOLUTION 20.6. For networks Na and Nb, the y-parameters are:

$$Y_{Na} = Y_{Nb} = \begin{bmatrix} 0.7 & -0.2 \\ -0.2 & 0.7 \end{bmatrix} \text{ S}$$

Hence, their z-parameters are the inverse of the y-parameter matrix:

$$Z_{Na} = Z_{Nb} = \frac{20}{9} \begin{bmatrix} 0.7 & 0.2 \\ 0.2 & 0.7 \end{bmatrix} = \frac{1}{9} \begin{bmatrix} 14 & 4 \\ 4 & 14 \end{bmatrix}$$

The network Na* has the same z-parameters as Na and continues to act as a two when series interconnected to another 2-port because of the transformer. Hence, the interconnection of networks Na* and Nb forms a valid series interconnection in which cas

$$Z_{new} = Z_{Na^*} + Z_{Nb} = \frac{2}{9} \begin{bmatrix} 14 & 4 \\ 4 & 14 \end{bmatrix}$$

SOLUTION 20.7. For network Nb, the y-parameters are the same as in problem 20.6, i.e.,

$$Y_{Nb} = \begin{bmatrix} 0.7 & -0.2 \\ -0.2 & 0.7 \end{bmatrix} \text{ S and } Z_{Nb} = \frac{1}{9} \begin{bmatrix} 14 & 4 \\ 4 & 14 \end{bmatrix}$$

For network Na, consider the purely resistive part without the transformer. The y-parameters of this part are half the y-parameters of Nb, i.e.,

$$Y_R = \begin{bmatrix} 0.35 & -0.1 \\ -0.1 & 0.35 \end{bmatrix} \text{ S}$$

In MATLAB we use the m-file which converts y-parameters to t-parameters:

```

»y = [0.35 -0.1;-0.1 0.35];
»t = ytot(y)
t =
  3.5000e+00  1.0000e+01
  1.1250e+00  3.5000e+00

```

From figure 19.34, the transformer has to parameters with a = 2 given by

$$t_{trans} = \begin{bmatrix} 1/a & 0 \\ 0 & a \end{bmatrix} = \begin{bmatrix} 0.5 & 0 \\ 0 & 2 \end{bmatrix}$$

```


»ttrans = [0.5 0;0 2];
»tNa = ttrans*t
tNa =
  1.7500e+00  5.0000e+00
  2.2500e+00  7.0000e+00
»
»zNa = ttoz(tNa)
zNa =
  7.7778e-01  4.4444e-01
  4.4444e-01  3.1111e+00
»
»zNb = [14 4;4 14]/9;
»znew = zNa + zNb
znew =
  2.3333e+00  8.8889e-01
  8.8889e-01  4.6667e+00
»

```

SOLUTION 20.8. This problem is identical numerically to problem 20.6. Here however the isolation transformer is on the right hand side which makes no difference to the interconnection. Therefore,

$$Z_{new} = Z_{Na} + Z_{Nb} = \frac{2}{9} \begin{bmatrix} 14 & 4 \\ 4 & 14 \end{bmatrix}$$

SOLUTION 20.9. Figure 20.4 is

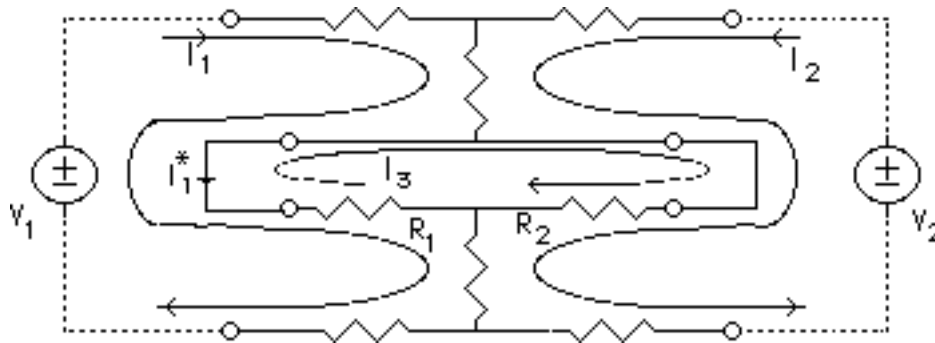

Using the values in figure 20.3, we obtain the following mesh equation matrix

$$\begin{matrix} V_1 & 4 + R_1 & 2 & -R_1 & I_1 \\ V_2 & = & 2 & 4 + R_2 & R_2 & I_2 \\ 0 & -R_1 & R_2 & R_1 + R_2 & I_3 \end{matrix}$$

For I_3 to be zero, the third equation implies that $R_1 I_1 = R_2 I_2$. Therefore,

$$V_1 = (4 + R_1)I_1 + 2 \frac{R_1}{R_2} I_1 = 4 + R_1 + \frac{2R_1}{R_2} I_1$$

Similarly

$$V_2 = 2I_1 + (4 + R_2) \frac{R_1}{R_2} I_1 = 2 + \frac{(4 + R_2)R_1}{R_2} I_1$$

Therefore

$$\frac{V_1}{V_2} = \frac{4 + R_1 + \frac{2R_1}{R_2}}{2 + \frac{(4 + R_2)R_1}{R_2}} = \frac{(4R_2 + R_1R_2 + 2R_1)}{(2R_2 + R_1R_2 + 4R_1)} = \frac{42}{48} = \frac{7}{8}$$

as was to be shown.

Now suppose, $\frac{V_1}{V_2} = \frac{7}{8}$ or equivalently $V_1 = \frac{7}{8} V_2$. With specific values

$$\begin{matrix} V_1 & 7/8 & 10 & 2 & -6 & I_1 \\ V_2 & = V_2 & 1 & = & 2 & 7 & 3 & I_2 \\ 0 & 0 & -6 & 3 & 9 & I_3 \end{matrix}$$

In MATLAB

```
»Z = [10 2 -6; 2 7 3; -6 3 9];
```

```
»b = [7/8 1 0]';
```

```
»I = inv(Z)*b
```

```
I =
```

```
6.2500e-02
```

```
1.2500e-01
```

2.7756e-17

Thus

$$\begin{aligned} I_1 &= 0.0625 \\ I_2 = V_2 &= 0.124 \\ I_3 &= 0 \end{aligned}$$

SOLUTION 20.10

(a) Write two loop equations assuming I_1 and I_2 are the usual port currents. Here

$$V_1 = Z_1 I_1 + V_{13} + Z_3 (I_1 + I_2)$$

and

$$V_2 = Z_2 I_2 + V_{23} + Z_3 (I_1 + I_2)$$

which in matrix form are

$$\begin{aligned} V_1 &= \begin{matrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{matrix} \begin{matrix} I_1 \\ I_2 \end{matrix} + \begin{matrix} V_{13} \\ V_{23} \end{matrix} \end{aligned}$$

However,

$$\begin{aligned} V_{13} \\ V_{23} \end{aligned} = Z_A \begin{aligned} I_1 \\ I_2 \end{aligned}$$

Therefore

$$\begin{aligned} V_1 \\ V_2 \end{aligned} = \begin{matrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{matrix} \begin{matrix} I_1 \\ I_2 \end{matrix} + Z_A \begin{matrix} I_1 \\ I_2 \end{matrix} = \begin{matrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{matrix} + Z_A \begin{matrix} I_1 \\ I_2 \end{matrix}$$

(b) The procedure of part (a) is repeated to produce the same result.

REMARK: this problem states that the two networks are equivalent two ports. Thus the configurations can be used interchangeably.

SOLUTION 20.11. Because of the isolation transformers, the overall Z-parameters are the sum of the three component Z-parameters. For N_a ,

$$Z_a = \begin{matrix} 2 & 1 \\ 1 & 2 \end{matrix}$$

For N_b ,

$$Z_b = \begin{matrix} 8 & 1 \\ 1 & 5 \end{matrix}$$

For N_c ,

$$Z_c = Z_a = \begin{matrix} 2 & 1 \\ 1 & 2 \end{matrix}$$

Therefore

$$Z = Z_a + Z_b + Z_c = \begin{bmatrix} 12 & 3 \\ 3 & 9 \end{bmatrix}$$

SOLUTION 20.12. (a) Given the Z-parameters of N, then

$$Y_N = Z_N^{-1} = \begin{bmatrix} 7 & 2 \\ 10 & 3 \end{bmatrix}^{-1} = \begin{bmatrix} 3 & -2 \\ -10 & 7 \end{bmatrix} \text{ S}$$

The 1-F capacitor considered as a two port has y-parameters

$$Y_C = \begin{bmatrix} s & -s \\ -s & s \end{bmatrix} \text{ S}$$

Therefore, the parallel connection of the two ports has y-parameters

$$Y = Y_N + Y_C = \begin{bmatrix} s & -s \\ -s & s \end{bmatrix} + \begin{bmatrix} 3 & -2 \\ -10 & 7 \end{bmatrix} = \begin{bmatrix} s+3 & -(s+2) \\ -(s+10) & s+7 \end{bmatrix} \text{ S}$$

(b) For this part, the same reasoning applies with s replaced by 1/s.

SOLUTION 20.13. The isolation transformer allows for the valid parallel connection of N_a^* and N_b in the sense that the overall y-parameters are the sum of the individual y-parameters. Further, because the ideal transformer is 1:1 with the standard dot locations, the y-parameters of N_a^* are those of N_a . Further, the y-parameters of N_b are the same as those of N_a as the circuits are simple vertical flips of each other. Therefore

$$Y_a^* = Y_a = \begin{bmatrix} 0.7 & -0.2 \\ -0.2 & 0.7 \end{bmatrix} = Y_b$$

Hence, the overall y-parameters are:

$$Y = 2 \times \begin{bmatrix} 0.7 & -0.2 \\ -0.2 & 0.7 \end{bmatrix} = \begin{bmatrix} 1.4 & -0.4 \\ -0.4 & 1.4 \end{bmatrix} \text{ S}$$

True-False: FALSE because the connection does not conform to figure 20.2a.

SOLUTION 20.14. From the previous example, the y-parameters of N_b are

$$Y_b = \begin{bmatrix} 0.7 & -0.2 \\ -0.2 & 0.7 \end{bmatrix} \text{ S}$$

The resistance values of the resistive part of N_a are twice those of N_b . Hence, the y-parameters of the resistive part are half those of N_b , i.e.,

$$\begin{matrix} I_1' \\ I_2' \end{matrix} = Y_{a,R} \begin{matrix} V_1' \\ V_2' \end{matrix} = \begin{bmatrix} 0.35 & -0.1 \\ -0.1 & 0.35 \end{bmatrix} \begin{matrix} V_1' \\ V_2' \end{matrix} \text{ S}$$

We obtain the y-parameters of N_a by considering the effect of the transformer on these y-parameters. Observe that

$$I_1 = 2I_1' \text{ and } V_1 = 0.5V_1'$$

Hence

$$\begin{matrix} I_1 \\ I_2 \end{matrix} = \begin{bmatrix} 0.7 & -0.2 \\ -0.1 & 0.35 \end{bmatrix} \begin{matrix} V_1' \\ V_2' \end{matrix} = \begin{bmatrix} 0.7 & -0.2 \\ -0.1 & 0.35 \end{bmatrix} \begin{matrix} 2V_1 \\ V_2 \end{matrix} = \begin{bmatrix} 1.4 & -0.2 \\ -0.2 & 0.35 \end{bmatrix} \begin{matrix} V_1 \\ V_2 \end{matrix}$$


Thus

$$Y_a = \begin{bmatrix} 1.4 & -0.2 \\ -0.2 & 0.35 \end{bmatrix} \text{ S}$$


It follows that


$$Y = Y_a + Y_b = \begin{bmatrix} 2.1 & -0.4 \\ -0.4 & 1.05 \end{bmatrix} \text{ S}$$

SOLUTION 20.15. (a)

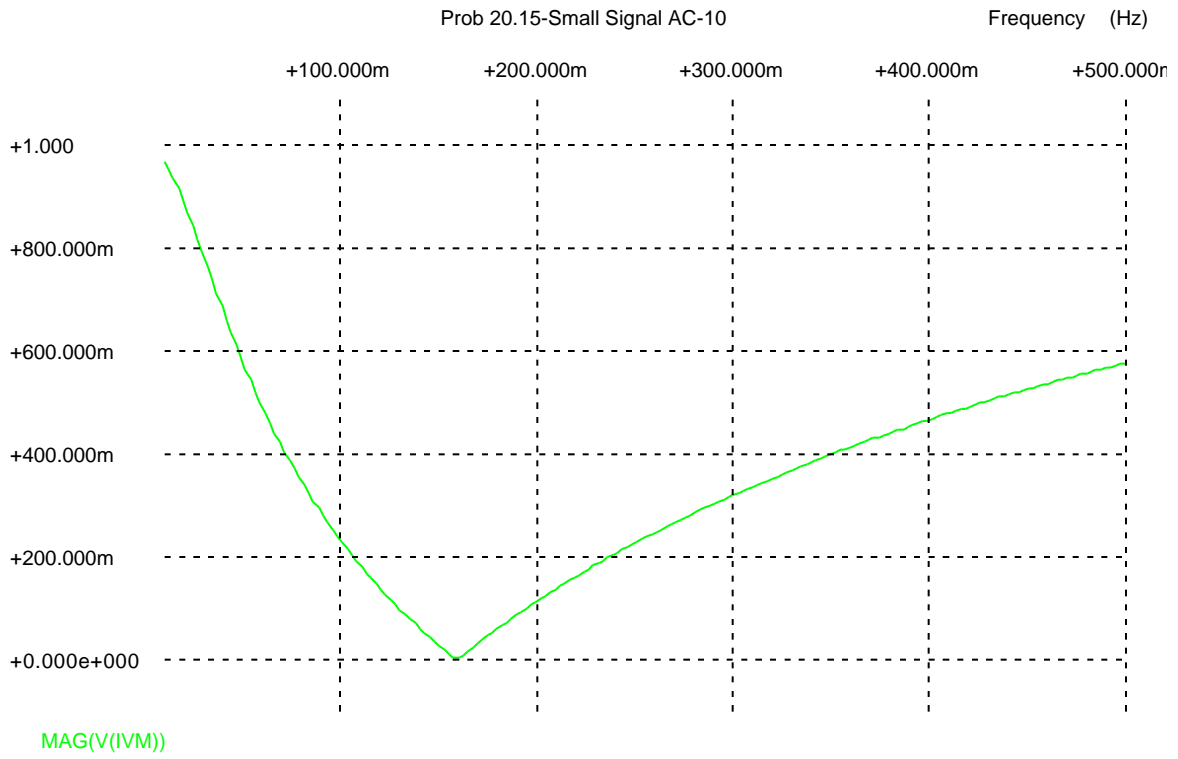

(b)

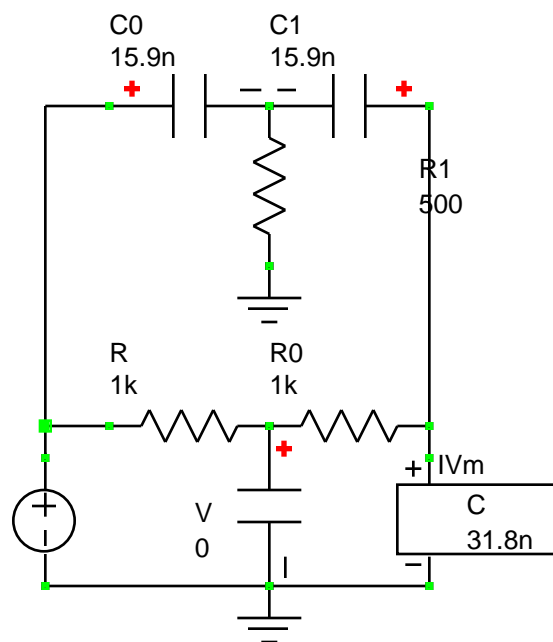

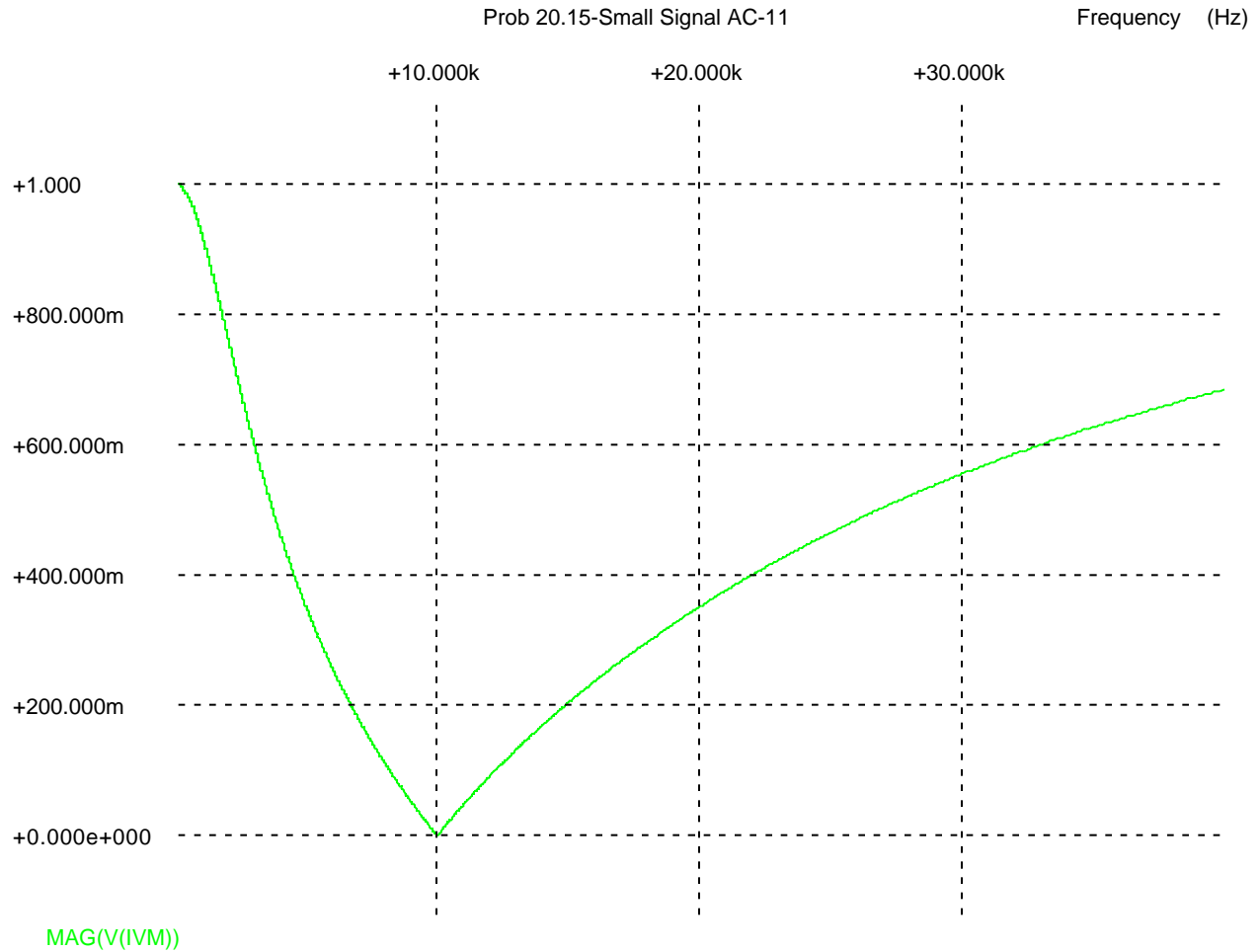

SOLUTION 20.16. (a) For network N_a , the y-parameters by inspection are:

$$Y_a = \begin{matrix} G_1 + j\omega C_1 & 0 \\ g_m & G_0 \end{matrix} = \begin{matrix} 2 + j10.21 & 0 \\ 95 & 0.07143 \end{matrix} \text{ mS}$$

For network N_b , the y-parameters by inspection are:

$$Y_b = \begin{pmatrix} G_f + j\omega C_2 & 1 \\ -1 & 1 \end{pmatrix} = \begin{pmatrix} 0.8333 + j1.021 & 1 \\ -1 & 1 \end{pmatrix} \text{ mS}$$

Therefore

$$Y = Y_a + Y_b = \begin{matrix} 2.8333 + j11.23 & -0.8333 - j1.021 \\ 94.167 - j1.021 & 0.9048 + j1.021 \end{matrix} \text{ mS}$$

(b), (c), and (d). Here we use the MATLAB m-file for two port analysis in terms of y-parameters:

```

»zs = 50; zL = 50;
»twoport(Y, zL, zs)
ans =
twoport analysis using y-parameters
yin =
 6.8501e-03 + 1.5594e-02i
zin =
 2.3614e+01 - 5.3756e+01i
yout =
 5.3617e-03 + 3.0023e-03i
zout =
 1.4199e+02 - 7.9506e+01i
v1tovs =
 5.5701e-01 - 3.2349e-01i
v2tov1 =
-4.4915e+00 + 2.6821e-01i
v2tovs =
-2.4150e+00 + 1.6023e+00i
»

```

SOLUTION 20.17. The t-parameters of the LR circuit follow from problem 19.53 with $Z_1 = Ls = s$ and $Z_2 = 0.5$:

$$T_{LR} = \begin{bmatrix} 1 + 2s & s \\ 2 & 1 \end{bmatrix}$$

Therefore

$$T_{cascade} = T^* T_{LR} = \begin{bmatrix} 5 + 2s & 2 + s \\ 5 + 2s & 2 + s \end{bmatrix}$$

SOLUTION 20.18. This problem can be solved in many ways. Here we emphasize the cascade nature of the two ports.

```

»% The y-parameters of Nb are:
»Yb = [8 2;20 6];
»% The z-parameters of Na are:
»Za = [0.75 -0.25;-2.5 1];
»% The t-parameters of Na are:
»Ta = ztot(Za)
Ta =
-3.0000e-01 -5.0000e-02
-4.0000e-01 -4.0000e-01
»% The t-parameters of Nb are:
»Tb = ytot(Yb)
Tb =

```

```

-3.0000e-01 -5.0000e-02
-4.0000e-01 -4.0000e-01
»% The t-parameters of the cascaded two port are:
»
»Tab = Ta*Tb
Tab =
  1.1000e-01  3.5000e-02
  2.8000e-01  1.8000e-01
»% Doing a t-parameter analysis we obtain:
»twoportt(Tab,0.25,0.5)
ans =
analysis of terminated twoport using t-parameters
zin =
  2.5000e-01
zout =
  5.0000e-01
v2tov1 =
  4
v1tovs =
  3.3333e-01
v2tovs =
  1.3333e+00
ans =
  2.5000e-01
»

```

SOLUTION 20.19. Use the h-parameter analysis m-file.

```

»H1 = [1e3 0.001;50 6e-5]; H2 = [1e3 0.99;-5 8e-4];
»zL = 100; zs = 2e3; zm = 10e3;
»% For part (a), the common collector stage:
»twoportH(H2,zL,0)
ans =
twoport analysis using h-parameters
zin =
  1.4583e+03
zout =
  1.7391e+02
v1tovs =
  1
v2tov1 =
  3.1746e-01
v2tovs =
  3.1746e-01

```

Remark: in the above, v_2 is V_{out} and v_1 is v_m ; z_{out} has no significance.

```
»% We now compute the load on the first stage.
```

```
»zin2 = 1.4583e+03;
```

```
»zLm = zm*zin2/(zin2 + zm)
```

```
zLm =
```

```
1.2727e+03
```

```
»% zLm is the load impedance on stage 1.
```

```
»% For part (a), the common emitter stage:
```

```
»twoport(H1,zLm,zs)
```

```
ans =
```

```
twoport analysis using h-parameters
```

```
zin =
```

```
9.4088e+02
```

```
zout =
```

```
2.3077e+04
```

```
v1tovs =
```

```
3.1993e-01
```

```
v2tov1 =
```

```
-6.2835e+01
```

```
v2tovs =
```

```
-2.0103e+01
```

Remark: in the above, v_2 is v_m and v_1 is V_{in} ; z_{out} is the output impedance of stage 1.

Conclusion: the input impedance to stage 1 is 940.88 and the input impedance to stage 2 is 1.4583 k .

(b) From the above output and remark, $V_m/V_{in} = -62.835$. Further $V_{out}/V_m = 0.31746$.

(c) From above $V_m/V_s = -20.103$. Therefore $V_{out}/V_s = V_{out}/V_m * V_m/V_s = -6.38$.

(d)

```
»zout1 = 2.3077e+04;
```

```
»zs2 = zm*zout1/(zm + zout1)
```

```
zs2 =
```

```
6.9768e+03
```

```
»twoport(H2,zL,zs2)
```

```
ans =
```

```
twoport analysis using h-parameters
```

```
zin =
```

```
1.4583e+03
```

```
zout =
```

```
7.0395e+02
```

```
v1tovs =
```

$1.7289e-01$
 $v_{2tov1} =$
 $3.1746e-01$
 $v_{2tovs} =$
 $5.4885e-02$

Conclusion: Z_{out} of amplifier is 704Ω .

SOLUTION 20.20

(a) Using MATLAB

```

»na = 1.1514;
»nb = 3.4012;
»Zlprime = nb^2*75 + j*1042.94
ZLprime =
  8.6761e+02 + 1.0429e+03i

```

```

»Zsprime = 75/na^2 + j*30
Zsprime =
  5.6573e+01 + 3.0000e+01i

```

(b) Since the h-parameters of the transistors are given, we can again use MATLAB and the m-file `twoporth` defined earlier. Hence:

```

»h = [ 60-j*50  0.01; -j*2  0.0005+j*0.0004];
»[Zin, Zout] = twoporth(h,ZLprime, Zsprime)
Zin =
  5.6569e+01 - 3.0000e+01i
Zout =
  8.6763e+02 - 1.0429e+03i

```

(c) Observe that $Z_{in} = 5.6569e+01 - 3.0000e+01i$ and $Z_{sprime} = 5.6573e+01 + 3.0000e+01i$, which are clearly conjugates of each other. Further, $Z_{out} = 8.6763e+02 - 1.0429e+03i$ and $Z_{Lprime} = 8.6761e+02 + 1.0429e+03i$, which are also conjugates of each other. Hence maximum power is transferred into and out of the transistor.

(d) For this part, we change all cascaded two ports to t-parameters. Specifically,

```

t0 = [1  75; 0  1];
t1 = [na  0; 0  1/na];
t2 = [ 1  j*30; 0  1];
t3 = htot(h);
t4 = [ 1  j*1042.9; 0  1];
t5 = [nb  0; 0  1/nb];
t6 = [1  0; 1/75  1];
t = t0*t1*t2*t3*t4*t5*t6

```

```

t =
  2.2176e-01 - 2.5959e-01i  8.3160e+00 - 9.7351e+00i
  1.4785e-03 - 1.7307e-03i  6.6577e-02 - 7.4415e-02i
»gain = 1/t(1,1)
gain = 1.9024e+00 + 2.2270e+00i

»gainmag = abs(gain)
gainmag = 2.9289e+00

»gainangle = angle(gain)*180/pi
gainangle = 4.9494e+01

```

In this case, $V_{out}/V_s = \text{gain} = 1.9024e+00 + 2.2270e+00i = 2.9289 \angle 49.494^\circ$

SOLUTION 20.21.

(a)

```
»Y2N = [1 0;20.1 0]*1e-3;
```

```
»Y10k = [1 -1;-1 1]*1e-4;
```

```
»Yshade = Y2N + Y10k
```

```
Yshade =
```

```
 1.1000e-03 -1.0000e-04
```

```
 2.0000e-02  1.0000e-04
```

```
»
```

(b) This is a series connection of two 2-ports. Hence we first convert the answer of part (a) to z-parameters.

```
»Y2N = [1 0;20.1 0]*1e-3;
```

```
»Y10k = [1 -1;-1 1]*1e-4;
```

```
»Yshade = Y2N + Y10k
```

```
Yshade =
```

```
 1.1000e-03 -1.0000e-04
```

```
 2.0000e-02  1.0000e-04
```

```
»Zshade = inv(Yshade)
```

```
Zshade =
```

```
 4.7393e+01  4.7393e+01
```

```
 -9.4787e+03  5.2133e+02
```

```
»Z1k = [1 1;1 1]*1e3;
```

```
»Zdashed = Zshade + Z1k
```

```
Zdashed =
```

```
 1.0474e+03  1.0474e+03
```

```
 -8.4787e+03  1.5213e+03
```

```
»
```

(c)

```
»twoportz(Zdashed,1e12,1e3)
```

```

ans =
twoport analysis using z-parameters
zin =
    1.0474e+03
zout =
    5.8588e+03
v1tovs =
    5.1157e-01
v2tov1 =
   -8.0950e+00
v2tovs =
   -4.1412e+00

```

Conclusion: $V_{out}/V_s = -4.1412$.

SOLUTION 20.22.

```

»Z = [3 1;5 2]*1e3;
»Y = inv(Z)
Y =
    2.0000e-03 -1.0000e-03
   -5.0000e-03  3.0000e-03
»% Consider the parallel connection of Y with the 1 k resistor
»Y1 = Y + [1 -1;-1 1]*1e-3
Y1 =
    3.0000e-03 -2.0000e-03
   -6.0000e-03  4.0000e-03
»
»% Now consider Y/Z in parallel with 1 k connected between B and C
»Y2 = Y + [0 0;0 1]*1e-3
Y2 =
    2.0000e-03 -1.0000e-03
   -5.0000e-03  4.0000e-03
»
»% This combination is in series with another 1 k resistor
»% Hence we need to compute Z2 first
»Z2 = inv(Y2)
Z2 =
    1.3333e+03  3.3333e+02
    1.6667e+03  6.6667e+02
»% Now we compute the series combo of Z2 and the 1 k resistor
»Z3 = Z2 + [1 1;1 1]*1e3
Z3 =
    2.3333e+03  1.3333e+03
    2.6667e+03  1.6667e+03
»

```

```

»
»% We now convert Y1 and Z3 to t-parameters and then multiply
»% together to obtain the overall t-parameters
»
»T1 = ytot(Y1)
T1 =
    6.6667e-01  1.6667e+02
           0  5.0000e-01
»T3 = ztot(Z3)
T3 =
    8.7500e-01  1.2500e+02
    3.7500e-04  6.2500e-01
»T = T1*T3
T =
    6.4583e-01  1.8750e+02
    1.8750e-04  3.1250e-01
»Y = ttoy(T)
Y =
    1.6667e-03  -8.8889e-04
   -5.3333e-03  3.4444e-03
»

```

SOLUTION 20.23. Refer to figure 20.13 for all problems.

(a) By inspection,

$$\begin{array}{rcccl}
 I_1 & 6 & -4 & -2 & V_1 \\
 I_2 & = & -4 & 4 + 5s & -5s & V_2 \\
 I_3 & & -2 & -5s & 2 + 5s & V_3
 \end{array}$$

The 3x3 coefficient matrix is the desired $Y_{\text{ind}}(s)$.

(b) Writing the nodal equation by inspection yields

$$\begin{array}{rcccl}
 I_1 & 0.5 & 0 & -0.25 & -0.25 & V_1 \\
 I_2 & & 0 & 1 & -0.5 & -0.5 & V_2 \\
 I_3 & = & -0.25 & -0.5 & 1.25 & -0.5 & V_3 \\
 \hline
 0 & & -0.25 & -0.5 & -0.5 & 1.25 & V_4
 \end{array}$$

Using MATLAB,

```

»W11=[0.5, 0 -0.25;0 1 -0.5;-0.25 -0.5 1.25]
W11 =
    5.0000e-01     0 -2.5000e-01
           0  1.0000e+00 -5.0000e-01
   -2.5000e-01 -5.0000e-01  1.2500e+00
»W12 = [-0.25 -0.5 -0.5]'

```

```

W12 =
-2.5000e-01
-5.0000e-01
-5.0000e-01
»W21 = [-0.25 -0.5 -0.5]
W21 =
-2.5000e-01 -5.0000e-01 -5.0000e-01
»W22 = 1.25
W22 =
1.2500e+00
»Yind = W11 - W12*inv(W22)*W21
Yind =
4.5000e-01 -1.0000e-01 -3.5000e-01
-1.0000e-01 8.0000e-01 -7.0000e-01
-3.5000e-01 -7.0000e-01 1.0500e+00
»

```

(c) Again, writing the nodal equation by inspection yields

$$\begin{array}{cccc|cc}
 I_1 & 5 & 0 & 0 & -5 & V_1 \\
 I_2 & 0 & 6 & -7 & 1 & V_2 \\
 I_3 & 0 & -4 & 8 & -4 & V_3 \\
 \hline
 0 & -5 & -2 & -1 & 8 & V_4
 \end{array}$$

Again, using MATLAB,

```

»W11 = [5 0 0;0 6 -7;0 -4 8]
W11 =
5 0 0
0 6 -7
0 -4 8
»W12 = [-5 1 -4]'
W12 =
-5
1
-4
»W21 = [-5 -2 -1]
W21 =
-5 -2 -1
»W22 = 8;
»Yind = W11 - W12*inv(W22)*W21
Yind =
1.8750e+00 -1.2500e+00 -6.2500e-01
6.2500e-01 6.2500e+00 -6.8750e+00
-2.5000e+00 -5.0000e+00 7.5000e+00
»

```

(d) This part is similar to part (a) as it does not require the method of matrix partitioning. By inspection,

$$\begin{array}{rcccl} I_G & (C_{GD} + C_{GS})s & -C_{GD}s & -C_{GS}s & V_G \\ I_D = & -C_{GD}s + g_m & C_{GD}s & -g_m & V_D \\ I_S & -C_{GS}s - g_m & 0 & C_{GS}s + g_m & V_S \end{array}$$

The 3x3 coefficient matrix is the desired $Y_{ind}(s)$.

SOLUTION 20.24. (a) With regard to the given information, the associated indefinite admittance matrix is the coefficient matrix in the following nodal equation given reference to figure 20.13:

$$\begin{array}{rcccl} I_G & 0 & 0 & 0 & V_G \\ I_D = & g_m & 0 & -g_m & V_D \\ I_S & -g_m & 0 & g_m & V_S \end{array}$$

We use property 5 to compute the remaining answers:

(a)-(a): Y_{GD} is as given.

$$(a)-(b): Y_{SD} = \begin{array}{cc} g_m & 0 \\ -g_m & 0 \end{array} \text{ S}$$

$$(a)-(c): Y_{GS} = \begin{array}{cc} 0 & 0 \\ -g_m & g_m \end{array} \text{ S}$$

$$(a)-(d): Y_{DG} = \begin{array}{cc} 0 & g_m \\ 0 & 0 \end{array} \text{ S}$$

$$(a)-(e): Y_{DS} = \begin{array}{cc} 0 & -g_m \\ 0 & g_m \end{array} \text{ S}$$

$$(a)-(e): Y_{SG} = \begin{array}{cc} g_m & -g_m \\ 0 & 0 \end{array} \text{ S}$$

(b) Transmission from port-1 to port-2 occurs when the 2-1 entry of the 2-port y-matrix is nonzero. Hence, the following all have the desired transmission: Y_{GD} , Y_{SD} , Y_{GS} .

SOLUTION 20.25. Using the zero-sum properties of the rows and columns, we have by inspection:

$$Y_{ind} = \begin{array}{ccc} 40 & 2 & -42 \\ ? & ? & -50 \\ ? & -22 & 92 \end{array} = \begin{array}{ccc} 40 & 2 & -42 \\ 30 & 20 & -50 \\ -70 & -22 & 92 \end{array} \text{ S}$$

SOLUTION 20.26. (a) $Y_{ind} = \begin{matrix} 8 & ? & ? \\ -2 & 9 & -7 \\ -6 & ? & ? \end{matrix} = \begin{matrix} 8 & -2 & -6 \\ -2 & 9 & -7 \\ -6 & -7 & 13 \end{matrix}$ S, where the second equality arises

because a purely

resistive network has a symmetric indefinite admittance matrix.

(b) Construct a common ground 2-port with input terminal C, common terminal A, and output terminal B:

$$Y_{CB} = \begin{matrix} 13 & -7 \\ -7 & 9 \end{matrix} \text{ S}$$

Therefore, since the output terminal B is shorted, $Y_L = \infty$, i.e.,

$$Y_{in} = y_{11} - \frac{y_{12}y_{21}}{y_{22} + Y_L} = 13 \text{ S}$$

Hence

$$Z_{in} = \frac{1}{13}$$

(c) Construct a common ground 2-port with input terminal A, common terminal B, and output terminal C:

$$Y_{AC} = \begin{matrix} 8 & -6 \\ -6 & 13 \end{matrix} \text{ S}$$

Hence, the required voltage gain is

$$G_V = \frac{V_2}{V_1} = \frac{-y_{21}}{y_{22} + Y_L} = \frac{-y_{21}}{y_{22}} = \frac{6}{13}$$

Therefore, $V_2 = \frac{6}{13} V_1$.

SOLUTION 20.27.

(a) Using the zero-sum property of the rows and columns of an indefinite admittance matrix we can write down by inspection (in mS)

$$\begin{matrix} I_B & 1 & -1 & 0 & V_B \\ I_E & = & -100 & 100.1 & -0.1 & V_E \\ I_C & & 99 & 99.1 & 0.1 & V_C \end{matrix}$$

(b) The y-parameters (also in mS) of the common emitter configuration are easily computed as

$$\begin{matrix} I_B \\ I_C \end{matrix} = \begin{matrix} 1 & 0 \\ 99 & 0.1 \end{matrix} \begin{matrix} V_{BE} \\ V_{CE} \end{matrix}$$

Hence in MATLAB

»Y = [1 0;99 0.1];

»Z = inv(Y)

Z =

$$\begin{matrix} 1.0000\text{e}+00 & 0 \\ -9.9000\text{e}+02 & 1.0000\text{e}+01 \end{matrix}$$

where Z is in k Ω . It follows that $V_{CE} = -990I_B + 10I_C$ where I_B and I_C are in mA and V_{CE} is in volts.

SOLUTION 20.28. Expanding the given y-parameter matrix into an indefinite admittance matrix yields

$$\begin{matrix} I_G & V_G & 0.2 + j2.5 & -0.01 - j0.65 & -0.19 - j1.85 & V_G \\ I_D = Y_{ind} & V_D & 3.1 - j0.65 & 0.05 + j0.8 & -3.15 - j0.15 & V_D \\ I_S & V_S & -3.3 - j1.85 & -0.04 - j0.15 & 3.34 + j2 & V_S \end{matrix}$$

By inspection, with G as the common terminal, S as the input terminal, and D as the output terminal, we obtain,

$$Y_{new} = \begin{matrix} 3.34 + j2 & -0.04 - j0.15 \\ -3.15 - j0.15 & 0.05 + j0.8 \end{matrix} \text{ mS}$$

SOLUTION 20.29. Here we use the zero-sum properties of the columns and rows to complete the indefinite admittance matrix:

$$Y_{ind} = \begin{matrix} -s & ? & ? \\ s-1 & 2 & ? \\ 1 & 2s-1 & -2s \end{matrix} = \begin{matrix} -s & -2s-1 & 3s+1 \\ s-1 & 2 & -s-1 \\ 1 & 2s-1 & -2s \end{matrix} \text{ S}$$

In figure (b), the top 2-port has $y_{top} = \begin{bmatrix} -s & -2s-1 \\ s-1 & 2 \end{bmatrix}$ S and the bottom 2-port has y-parameters

$y_{bot} = \begin{bmatrix} -2s & 2s-1 \\ -s-1 & 2 \end{bmatrix}$ S. Since these 2-ports are connected in parallel, the overall 2-port y-parameters are

$$y = y_{top} + y_{bot} = \begin{bmatrix} -s & -2s-1 \\ s-1 & 2 \end{bmatrix} + \begin{bmatrix} -2s & 2s-1 \\ -s-1 & 2 \end{bmatrix} = \begin{bmatrix} -3s & -2 \\ -2 & 4 \end{bmatrix} \text{ S}$$

SOLUTION 20.30. From problem 28,

$$\begin{array}{rcccl} I_G & V_G & 0.2 + j2.5 & -0.01 - j0.65 & -0.19 - j1.85 & V_G \\ I_D = Y_{ind} & V_D & 3.1 - j0.65 & 0.05 + j0.8 & -3.15 - j0.15 & V_D \\ I_S & V_S & -3.3 - j1.85 & -0.04 - j0.15 & 3.34 + j2 & V_S \end{array}$$

Hence

$$y_{GS} = \begin{bmatrix} 0.2 + j2.5 & -0.19 - j1.85 \\ -3.3 - j1.85 & 3.34 + j2 \end{bmatrix} \text{ S}$$

SOLUTION 20.31. (a) Here, by inspection we can compute the indefinite admittance matrix as the coefficient matrix of the following nodal equations:

$$\begin{array}{rcccl} I_A & V_A & Y_1 + Y_2 + 2 & -Y_2 & -Y_1 - 2 & V_A \\ I_B = Y_{ind} & V_B & Y_2 - 2 & -Y_2 & 2 & V_B \\ I_C & V_C & -Y_1 - 2Y_2 & 2Y_2 & Y_1 & V_C \end{array}$$

(b)

$$y_{AB} = \begin{bmatrix} Y_1 + Y_2 + 2 & -Y_2 \\ Y_2 - 2 & -Y_2 \end{bmatrix}$$

(c)

$$y_{AC} = \begin{bmatrix} Y_1 + Y_2 + 2 & -Y_1 - 2 \\ -Y_1 - 2Y_2 & Y_1 \end{bmatrix}$$

SOLUTION 20.32. (a) Here, by inspection we can compute the indefinite admittance matrix as the coefficient matrix of the following nodal equations:

$$\begin{array}{r} I_A \\ I_B = Y_{ind} \\ I_C \end{array} \begin{array}{r} V_A \\ V_B \\ V_C \end{array} = \begin{array}{r} Y_1 + Y_2 \\ -Y_2 + g_m \\ -Y_1 - g_m \end{array} \begin{array}{r} -Y_2 \\ Y_2 + Y_3 \\ -Y_3 \end{array} \begin{array}{r} -Y_1 \\ -Y_3 - g_m \\ Y_1 + Y_3 + g_m \end{array} \begin{array}{r} V_A \\ V_B \\ V_C \end{array}$$

(b)

$$y_{AB} = \begin{array}{r} Y_1 + Y_2 \\ -Y_2 + g_m \end{array} \begin{array}{r} -Y_2 \\ Y_2 + Y_3 \end{array}$$

(c)

$$y_{AC} = \begin{array}{r} Y_1 + Y_2 \\ -Y_1 - g_m \end{array} \begin{array}{r} -Y_1 \\ Y_1 + Y_3 + g_m \end{array}$$

SOLUTION 20.33. (a) Here the nodal equation matrix is:

$$\begin{array}{r} I_A \\ I_B \\ I_C \\ 0 \end{array} = \begin{array}{r} W_{11} \\ W_{21} \\ W_{21} \\ 0 \end{array} \begin{array}{r} V_A \\ V_B \\ V_C \\ V_D \end{array} = \begin{array}{r} 8 \\ 0 \\ 0 \\ -8 \end{array} \begin{array}{r} 0 \\ 2 + 2s \\ -2s \\ -2 \end{array} \begin{array}{r} 0 \\ -2s - 10 \\ 16 + 2s \\ -6 \end{array} \left| \begin{array}{r} -8 \\ 8 \\ -16 \\ 16 \end{array} \right. \begin{array}{r} V_A \\ V_B \\ V_C \\ V_D \end{array}$$

where V_D is the internal node voltage. Using the method of matrix partitioning,

$$Y_{ind} = W_{11} - W_{12}W_{22}^{-1}W_{21} = \begin{array}{r} 8 \\ 0 \\ 0 \end{array} \begin{array}{r} 0 \\ 2 + 2s \\ -2s \end{array} \begin{array}{r} 0 \\ -2s - 10 \\ 16 + 2s \end{array} - \frac{1}{16} \begin{array}{r} -8 \\ 8 \\ -16 \end{array} \begin{array}{r} -8 \\ -2 \\ -6 \end{array}$$

$$= \begin{array}{r} 8 \\ 0 \\ 0 \end{array} \begin{array}{r} 0 \\ 2 + 2s \\ -2s \end{array} \begin{array}{r} 0 \\ -2s - 10 \\ 16 + 2s \end{array} - \begin{array}{r} 0.5 \\ 0.5 \\ -1 \end{array} \begin{array}{r} -8 \\ -2 \\ -6 \end{array} = \begin{array}{r} 4 \\ 4 \\ -8 \end{array} \begin{array}{r} -1 \\ 3 + 2s \\ -2s - 2 \end{array} \begin{array}{r} -3 \\ -2s - 7 \\ 10 + 2s \end{array} \text{ S}$$

(b) When C is grounded,

$$y_{AB} = \begin{array}{r} 4 \\ 4 \end{array} \begin{array}{r} -1 \\ 3 + 2s \end{array} \text{ S and } z_{AB} = \frac{1}{8s + 16} \begin{array}{r} 3 + 2s \\ -4 \\ 4 \end{array}$$

(c) When B is grounded

$$y_{AC} = \begin{array}{r} 4 \\ -8 \end{array} \begin{array}{r} -3 \\ 10 + 2s \end{array} \text{ S}$$

SOLUTION 20.34. (a) Writing the usual node equations we have,

$$\begin{array}{l} I_A \\ I_B \\ I_C \\ \hline 0 \end{array} = \begin{array}{cc} W_{11} & W_{12} \\ W_{21} & W_{22} \end{array} \begin{array}{l} V_A \\ V_B \\ V_C \\ \hline V_D \end{array} = \begin{array}{ccc|c} s+0.5 & -s & 0 & -0.5 \\ -s & s+0.5 & 0 & -0.5 \\ 0 & 0 & 0.5s & -0.5s \\ \hline -0.5 & -0.5 & -0.5s & 0.5s+1 \end{array} \begin{array}{l} V_A \\ V_B \\ V_C \\ V_D \end{array}$$


Using the method of matrix partitioning,

$$\begin{aligned} Y_{ind} &= W_{11} - W_{12}W_{22}^{-1}W_{21} = \begin{array}{ccc|c} s+0.5 & -s & 0 & 1 \\ -s & s+0.5 & 0 & -\frac{0.5}{s+2} \\ 0 & 0 & 0.5s & s \end{array} \begin{bmatrix} 1 & 1 & s \end{bmatrix} \\ &= \begin{array}{ccc|ccc} s+0.5 & -s & 0 & 1 & 1 & s \\ -s & s+0.5 & 0 & -\frac{0.5}{s+2} & 1 & s \\ 0 & 0 & 0.5s & s & s & s^2 \end{array} \\ &= \frac{1}{s+2} \begin{array}{ccc|ccc} s^2+2.5s+0.5 & -s^2-2s-0.5 & -0.5s & & & \\ -s^2-2s-0.5 & s^2+2.5s+0.5 & -0.5s & & & \\ -0.5s & -0.5s & s & & & \end{array} \text{ S} \end{aligned}$$

(b) Here

$$y_{AB} = \frac{1}{s+2} \begin{array}{ccc|ccc} s^2+2.5s+0.5 & -s^2-2s-0.5 & & & & \\ -s^2-2s-0.5 & s^2+2.5s+0.5 & & & & \\ & & & & & \end{array} \text{ S}$$

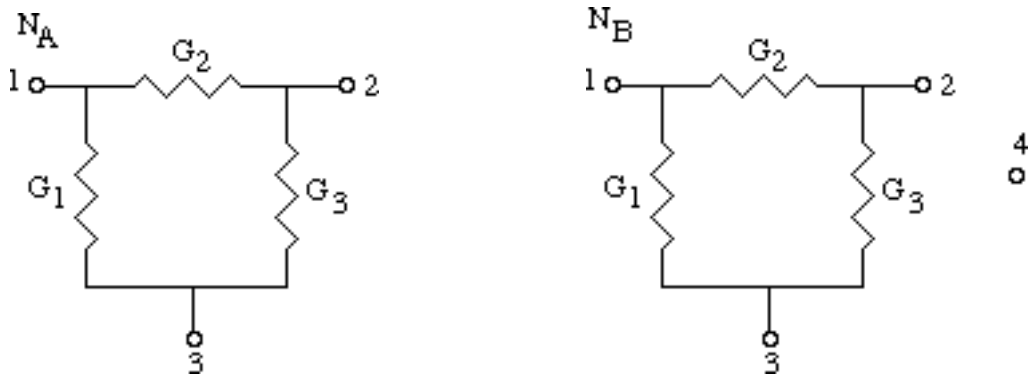SOLUTION 20.35. (a) Rule 1: Consider the two networks N_A (3 external nodes) and N_B (4 external nodes) given below:




The two indefinite admittance matrices are

$$Y_{indN_A} = \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 \\ -G_2 & G_2 + G_3 & -G_3 \\ -G_1 & -G_3 & G_1 + G_3 \end{bmatrix} \quad \text{and} \quad Y_{indN_B} = \begin{bmatrix} G_1 + G_2 & -G_2 & -G_1 & 0 \\ -G_2 & G_2 + G_3 & -G_3 & 0 \\ -G_1 & -G_3 & G_1 + G_3 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

Observe that Y_{indN_B} can be obtained from Y_{indN_A} by adding a column of zeros and a row of zeros to form a 4x4 matrix.

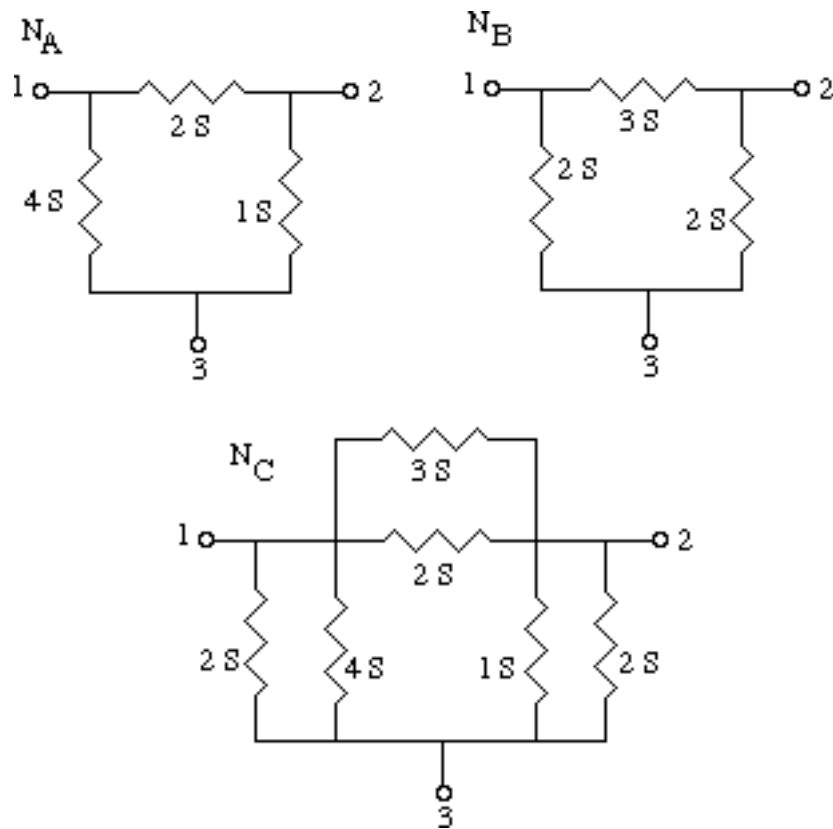(b) Rule 2: Consider two networks N_A and N_B and a third network N_C which combines elements of N_A and N_B as given below:




The corresponding indefinite admittance matrices are:

$$Y_{indN_A} = \begin{bmatrix} 6 & -2 & -4 \\ -2 & 3 & -1 \\ -4 & -1 & 5 \end{bmatrix}, \quad Y_{indN_B} = \begin{bmatrix} 5 & -3 & -2 \\ -3 & 5 & -2 \\ -2 & -2 & 4 \end{bmatrix}, \quad \text{and} \quad Y_{indN_C} = \begin{bmatrix} 11 & -5 & -6 \\ -5 & 8 & -3 \\ -6 & -3 & 9 \end{bmatrix}.$$

Clearly,

$$Y_{indN_C} = Y_{indN_A} + Y_{indN_B}$$

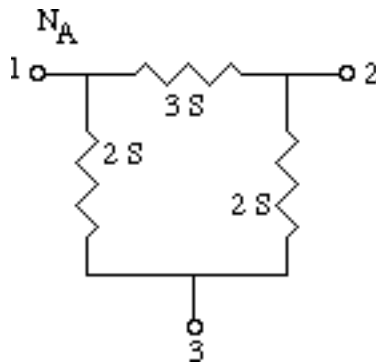
(c) Rule 3: Consider the 3-terminal network



with indefinite admittance matrix

$$Y_{indN_A} = \begin{bmatrix} 5 & -3 & -2 \\ -3 & 5 & -2 \\ -2 & -2 & 4 \end{bmatrix} \text{ S}$$

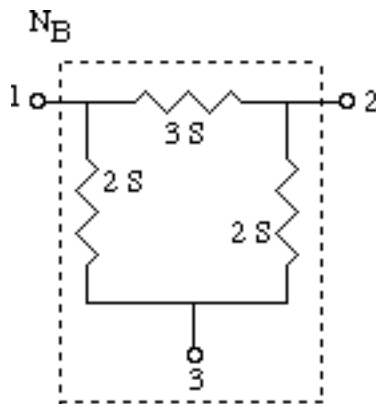If we move node 3 inside to form a 2-terminal network and labeled as N_B ,




then from nodal analysis we have

$$\begin{array}{ccc|cc} I_1 & 5 & -3 & -2 & V_1 \\ I_2 & -3 & 5 & -2 & V_2 \\ 0 & -2 & -2 & 4 & V_3 \end{array}$$

Using the method of matrix partitioning,

$$Y_{indN_B} = \begin{bmatrix} 5 & -3 \\ -3 & 5 \end{bmatrix} - \frac{1}{4} \begin{bmatrix} -2 & -2 \\ -2 & -2 \end{bmatrix} = \begin{bmatrix} 4 & -4 \\ -4 & 4 \end{bmatrix} \text{ S}$$

This computation is the one given by the formula in the problem. To see that this is correct, we observe that the internal simplification of N_B leads to the following:

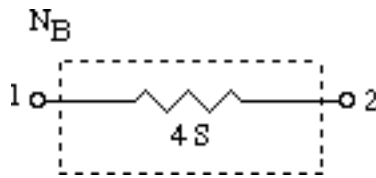

SOLUTION 20.36.

Part (a)

»Yinda= [1/2 -1/4 0 -1/4 0; -1/4 1/2 0 0 -1/4; ...
0 0 0 0 0; -1/4 0 0 1/2 -1/4; 0 -1/4 0 -1/4 1/2]

Yinda =

5.0000e-01	-2.5000e-01	0	-2.5000e-01	0
-2.5000e-01	5.0000e-01	0	0	-2.5000e-01
0	0	0	0	0
-2.5000e-01	0	0	5.0000e-01	-2.5000e-01
0	-2.5000e-01	0	-2.5000e-01	5.0000e-01

»Yindb= [0 0 0 0 0; 0 0 0 0 0; 0 0 3/4 -1/2 -1/4; ...
0 0 -1/2 5/8 -1/8; 0 0 -1/4 -1/8 3/8]

Yindb =

0	0	0	0	0
0	0	0	0	0
0	0	7.5000e-01	-5.0000e-01	-2.5000e-01
0	0	-5.0000e-01	6.2500e-01	-1.2500e-01
0	0	-2.5000e-01	-1.2500e-01	3.7500e-01

Part (b)

»Yind = Yinda + Yindb

Yind =

5.0000e-01	-2.5000e-01	0	-2.5000e-01	0
-2.5000e-01	5.0000e-01	0	0	-2.5000e-01
0	0	7.5000e-01	-5.0000e-01	-2.5000e-01
-2.5000e-01	0	-5.0000e-01	1.1250e+00	-3.7500e-01
0	-2.5000e-01	-2.5000e-01	-3.7500e-01	8.7500e-01

% To suppress nodes 4 and 5 we use the partitioned matrix formula as follows:

»W11= [Yind(1:3, 1:3)]

W11 =

```

5.0000e-01 -2.5000e-01    0
-2.5000e-01 5.0000e-01    0
    0        0 7.5000e-01

```

```

»W12=[Yind(1:3, 4:5)]

```

```

W12 =

```

```

-2.5000e-01    0
    0 -2.5000e-01
-5.0000e-01 -2.5000e-01

```

```

»W21= [Yind(4:5, 1:3)]

```

```

W21 =

```

```

-2.5000e-01    0 -5.0000e-01
    0 -2.5000e-01 -2.5000e-01

```

```

»W22= [Yind(4:5, 4:5)]

```

```

W22 =

```

```

1.1250e+00 -3.7500e-01
-3.7500e-01 8.7500e-01

```

```

»Yind123 = W11 - W12*inv(W22)*W21

```

```

Yind123 =

```

```

4.3519e-01 -2.7778e-01 -1.5741e-01
-2.7778e-01 4.1667e-01 -1.3889e-01
-1.5741e-01 -1.3889e-01 2.9630e-01

```

(d) For the required Y-matrix we delete row and column 3 to obtain

```

»Ysc = Yind123(1:2,1:2)

```

```

Ysc =

```

```

4.3519e-01 -2.7778e-01
-2.7778e-01 4.1667e-01

```

```

»Zoc = inv(Ysc)

```

```

Zoc =

```

```

4.0000e+00 2.6667e+00
2.6667e+00 4.1778e+00

```

SOLUTION 20.37. Since complex roots must occur in conjugate pairs, we will only check $j\omega_0$.

$$0 = p(j\omega_0) = -ja_3\omega_0^3 - a_2\omega_0^2 + ja_1\omega_0 + a_0 = a_0 - a_2\omega_0^2 + j(a_1\omega_0 - a_3\omega_0^3)$$

Both real and imaginary parts must be zero, i.e.,

$$a_0 - a_2\omega_0^2 = 0 \quad \text{and} \quad a_1\omega_0 - a_3\omega_0^3 = \omega_0(a_1 - a_3\omega_0^2) = 0$$

From the first equation, $a_2\omega_0^2 = a_0$. The second equation above must be true for arbitrary ω_0 which implies that $a_1 = a_3\omega_0^2$. Equivalently $a_1a_2 = a_3a_2\omega_0^2 = a_3a_0$. Conclusion: this condition leads to imaginary complex roots.

(b) Given the above condition, what are the resulting imaginary roots of the polynomial? Since the polynomial is cubic, we can assume $a_3 \neq 0$. In this case,

$$\begin{aligned} 0 = p(s) &= s^3 + \frac{a_2}{a_3}s^2 + \frac{a_1}{a_3}s + \frac{a_0}{a_3} = s^3 + \frac{a_1}{a_3}s^2 + \frac{a_2}{a_3}s^2 + \frac{a_1a_2}{a_3^2} = s^3 + \frac{a_1}{a_3}s^2 + \frac{a_2}{a_3}s^2 + \frac{a_1}{a_3} \\ &= s^3 + \frac{a_1}{a_3}s^2 + \frac{a_2}{a_3}s^2 + \frac{a_1}{a_3} \end{aligned}$$

Therefore, the roots are: $s = \pm j\sqrt{\frac{a_1}{a_3}}, -\frac{a_2}{a_3}$.

SOLUTION 20.38.

(a) The four 2-port equations arising from the interconnection are:

$$V_1 = V_{1a} - V_{1b} \quad I_1 = I_{1a} = -I_{1b} \quad V_2 = V_{2a} = V_{2b} \quad I_2 = I_{2a} + I_{2b}$$

Thus

$$V_1 = V_{1a} - V_{1b} = (h_{11a}I_{1a} + h_{12a}V_{2a}) - (h_{11b}I_{1b} + h_{12b}V_{2b}) = (h_{11a} + h_{11b})I_1 + (h_{12a} - h_{12b})V_2$$

and

$$I_2 = I_{2a} + I_{2b} = (h_{21a}I_{1a} + h_{22a}V_{2a}) + (h_{21b}I_{1b} + h_{22b}V_{2b}) = (h_{21a} - h_{21b})I_1 + (h_{22a} + h_{22b})V_2$$

This proves that the series-parallel connection has the required h-parameters.

(b) The four 2-port equations arising from the interconnection are:

$$V_2 = V_{2a} - V_{2b} \quad I_2 = I_{2a} = -I_{2b} \quad V_1 = V_{1a} = V_{1b} \quad I_1 = I_{1a} + I_{1b}$$

Thus,

$$I_1 = I_{1a} + I_{1b} = (g_{11a}V_{1a} + g_{12a}I_{2a}) + (g_{11b}V_{1b} + g_{12b}I_{2b}) = (g_{11a} + g_{11b})V_1 + (g_{12a} - g_{12b})I_2$$

and

$$V_2 = V_{2a} - V_{2b} = (g_{21a}V_{1a} + g_{22a}I_{2a}) - (g_{21b}V_{1b} + g_{22b}I_{2b}) = (g_{21a} - g_{21b})V_1 + (g_{22a} + g_{22b})I_2$$

This proves that the parallel-series connection has the required g-parameters.

SOLUTION 20.39.

(a) Refer here to N_a in figure P20.39b. With reference to figure 19.28b, $h_{11} = 11 \text{ k}$, $h_{12} = 0$, $h_{21} = 95.9$, and $h_{22} = 1/10^5 = 10^{-5} \text{ S}$. Similarly, by inspection with reference to equation 19.33, $h_{11} = 90 \parallel 10 = 9 \text{ k}$, $h_{12} = 0.1$ (reverse voltage division), $h_{21} = -0.1$, and $h_{22} = 10^{-5} \text{ S}$.

(b) By problem 20.38, part (a),

$$h_{11} = h_{11a} + h_{11b} = 20 \text{ k}$$

$$h_{12} = h_{12a} - h_{12b} = -0.1$$

$$h_{21} = h_{21a} - h_{21b} = 96$$

$$h_{22} = h_{22a} + h_{22b} = 2 \times 10^{-5} \text{ S}$$

(c) Recall from chapter 19 that $Z_{in} = \frac{V_1}{I_1} = h_{11} - \frac{h_{12}h_{21}}{h_{22} + Y_L}$ and $Y_{out} = \frac{I_2}{V_2} = h_{22} - \frac{h_{12}h_{21}}{h_{11} + Z_s}$ in

which case Z_{out} is the reciprocal. Using our MATLAB script, we have

```
h = [20e3 -0.1; 96 0.02e-3 ];
zL= 1e8;
zs= 5e3;
»twoport(h,zL,zs)
ans =
twoport analysis using h-parameters
zin =
 4.9976e+05
zout =
 2.4752e+03
v1tovs =
 9.9009e-01
v2tov1 =
 -9.5998e+00
v2tovs =
 -9.5047e+00
```

REMARK: We have used the following m-file code for "twoport":

```
»% two-port analysis in terms of h-parameters
»function [zin, zout] =twoport(h, zL, zs)
»['twoport analysis using h-parameters']
»h11= h(1,1); h12=h(1,2); h21=h(2,1); h22=h(2,2);
»zin = h11 - h12*h21/(h22+ 1/zL)
»yout= h22 - h12*h21/(h11+zs);
```

»zout= 1/yout
 »v1tovs= zin/(zin+zs)
 »v2tov1= -h21/(zin*(h22+1/zL))
 »v2tovs= v1tovs*v2tov1

SOLUTION 20.40.

(a) The y-parameters for N_a are:

$$y_{AB} = \begin{matrix} 7 & 4 \\ 4 & 7 \end{matrix}^{-1} = \frac{1}{33} \begin{matrix} 7 & -4 \\ -4 & 7 \end{matrix} \text{ S}$$

Hence the indefinite admittance matrix for N_a is:

$$Y_{indN_a} = \frac{1}{33} \begin{matrix} 7 & -4 & -3 \\ -4 & 7 & -3 \\ -3 & -3 & 6 \end{matrix} \text{ S}$$

Let us consider the associate 2-port with port A grounded and B as the new port 1 input. The problem is then solved by computing the input impedance with port 2 open circuited. Hence, the new y-parameters are:

$$y_{BC} = \frac{1}{33} \begin{matrix} 7 & -3 \\ -3 & 6 \end{matrix} \text{ S}$$

Thus $Y_{in} = y_{11} - \frac{y_{12}y_{21}}{y_{22}} = \frac{1}{33} \left(7 - \frac{9}{6} \right) = \frac{5.5}{33} = \frac{1}{6} \text{ S}$. Hence, $Z_{in} = 6 \Omega$ is the unique reading.

(b) The answer is not unique as demonstrated in part (c).

(c) The following two networks have the given Z-parameters, but the meter reading for N_1 is 4 Ω but for N_2 it is 2 Ω .

