

### PROBLEM SOLUTIONS CHAPTER 3.

**Solution 3.1.** Select the bottom node as the reference node, and write a node equation at the positive terminal of the  $V_1$  resistor:

$$\begin{aligned}\frac{V_1 - V_0}{3R} + \frac{V_1}{6R} + \frac{V_1 - 4V_0}{6R} &= 0 \\ 2V_1 - 2V_0 + V_1 + V_1 - 4V_0 &= 0 \\ 4V_1 &= 6V_0 \\ V_1 &= 1.5V_0\end{aligned}$$

**Solution 3.2** Write a node equation at the top node:

$$\begin{aligned}0.6 - \frac{V_x}{100} - \frac{2V_x}{100} - \frac{V_x}{50} &= 0 \\ -V_x - 2V_x - 2V_x &= -60 \\ -5V_x &= -60 \\ V_x &= 12V\end{aligned}$$

**Solution 3.3**

$$\begin{aligned}0.6 - \frac{V_x}{100} + \frac{25V_x}{100} - \frac{V_x}{50} - \frac{V_x - 0.2V_x}{40} &= 0 \\ -\frac{3V_x}{100} + \frac{25V_x}{100} - \frac{8V_x}{400} &= -0.6 \\ V_x &= -\frac{0.6 \times 400}{80} \\ V_x &= -3V\end{aligned}$$

**Solution 3.4 (a)**

It is evident from the figure that  $V_c = 20$ . We need to write two equations in  $V_a$  and  $V_b$  and put them in matrix form. In this case, we can write the matrix equation by inspection. Note that the resistors are identified by conductance values.

$$\begin{bmatrix} 15m & -5m \\ -5m & 35m \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 0.5 \\ 0.5 \end{bmatrix}$$

(b) Solve the matrix equation by inverting the left-most matrix:

$$\begin{aligned} \begin{matrix} V_a \\ V_b \end{matrix} &= \frac{1}{525\mu - 25\mu} \begin{matrix} 35m & 5m & 0.5 \\ 5m & 15m & 0.5 \end{matrix} \\ &= \frac{1}{0.5} \begin{matrix} 35 & 5 & 0.5 \\ 5 & 15 & 0.5 \end{matrix} \\ &= \begin{matrix} 40 \\ 20 \end{matrix} \end{aligned}$$

(c)  $V_x = V_{ab} = V_a - V_b = 20V$ ,  $V_{da} = -V_a = -40$ ,  $V_{db} = -V_b = -20$ .

(d)  $P_i = 0.5 \times 40 = 20W$ ,  $P_v = 20 \times (20 - 20) = 0$ .  $P_{diss} = 40 \times 40 \times 10m + 20 \times 20 \times 5m + 20 \times 20 \times 5m = 20W$ .

Power delivered equals dissipated power.

**Solution 3.6** Write two nodal equations:

$$\begin{aligned} \frac{V_{s1} - V_1}{3000} &= I_{s3} + \frac{V_1 - V_2}{6000} \\ \frac{V_2}{30000} &= \frac{V_{s2} - V_2}{12000} + \frac{V_1 - V_2}{6000} \end{aligned}$$

Rewrite equations as:

$$\begin{aligned} 2V_{s1} - 2V_1 &= 6000I_{s3} + V_1 - V_2 \\ 2V_2 &= 5V_{s2} - 5V_2 + 10V_1 - 10V_2 \end{aligned}$$

Cast into a matrix equation

$$\begin{matrix} -3 & 1 & V_1 \\ -10 & 17 & V_2 \end{matrix} = \begin{matrix} 6000I_{s3} - 2V_{s1} \\ 5V_{s2} \end{matrix}$$

Solving the matrix equation yields:

$$\begin{matrix} V_1 & 181.46 \\ V_2 & 124.39 \end{matrix}$$

Power absorbed by the 6k resistor is  $(V_1 - V_2)^2 / R = 0.5429W$ .

Similarly,  $P_{s1} = (V_{s1} - V_1) / 3000 \times V_{s1} = 4.7W$ ,  $P_{s2} = (V_{s2} - V_2) / 12000 \times V_{s2} = -0.32W$

$P_{s3} = I_{s3} \times (V_{s2} - V_1) = -1.21W$

**Solution 3.7** (a) Again, the matrix equation can be written by inspection:

$$\begin{matrix} G_1 + G_2 + G_4 & -G_4 & V_B \\ -G_4 & G_3 + G_4 + G_s & V_C \end{matrix} = \begin{matrix} 50G_1 \\ 50G_3 \end{matrix}$$

(b) Substituting the values of conductances and inverting the above matrix equation yields:

$$V_B = 34.0132V$$

$$V_C = 33.6842V$$


(c) Power delivered is  $80.7566W$ . Using the Principle of Conservation of Power:

$$P_{del} = P_1 + P_2 + P_3 + P_4 + P_5$$

or,

$$P_{del} = 50 \times \frac{V_A - V_B}{20} + \frac{V_A - V_C}{20} = 80.7566W$$

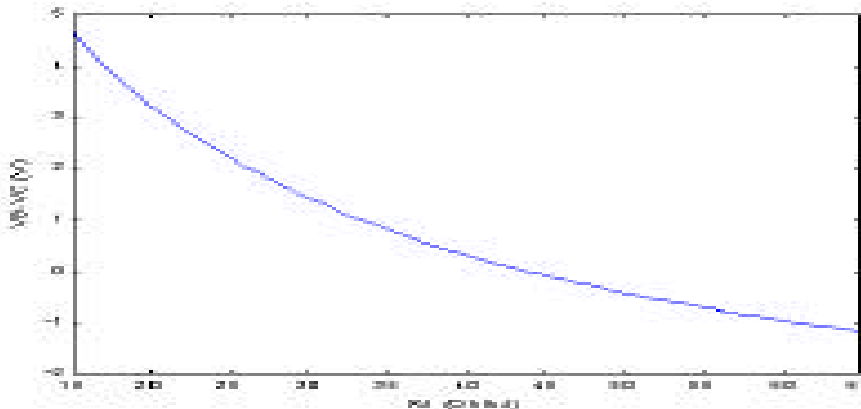(d) In this part, we take the above matrix equation and solve it for each value of  $G_s$ . If we do this, we can get a feel for the behavior of  $V_B$  and  $V_C$  w.r.t. changes in  $G_s$ . The following plot is the voltage difference between the two nodes as a function of  $G_s$ , and hence as a function of temperature.



As can be seen, in this figure, the voltage difference between B and C does not change linearly with  $R_s$ . Since this resistance itself changes linearly with temperature, this means that  $V_B - V_C$  does not change proportionally to temperature.

**Solution 3.8** The answer is:

$$\begin{array}{cccccc}
G_1 + G_2 & -G_1 & -G_2 & 0 & V_1 & -I_{s1} \\
-G_1 & G_1 + G_3 + G_4 + G_7 & -G_4 & -G_7 & V_2 & 0 \\
-G_2 & -G_4 & G_4 + G_5 + G_6 + G_2 & -G_6 & V_3 & 0 \\
0 & -G_7 & -G_6 & G_6 + G_8 + G_7 & V_4 & I_{s2}
\end{array} =$$

**Solution 3.9** Write the matrix equation by inspection:

$$\begin{array}{cccc}
4/100 & -1/100 & -1/100 & V_1 \\
-1/100 & 4/100 & -1/100 & V_2 \\
-1/100 & -1/100 & 4/100 & V_3
\end{array} = \begin{array}{c} \frac{V_{s1}}{100} \\ \frac{V_{s1}}{100} \\ I_{s2} \end{array}$$

Solving the equation in MATLAB, we get:  $V_1 = 7$ ,  $V_2 = 7$ ,  $V_3 = 11$ , and  $P = 0.6$ .

$$P = V_{s1} \times \frac{V_{s1} - V_1}{100} + \frac{V_{s1} - V_2}{100} = 10 \times \frac{3}{10} + \frac{3}{10} = 0.6W$$

**Solution 3.10 (a)**

Nodal equation for A:

$$\frac{V_A - V_{s1}}{10} + \frac{V_A - V_B}{10} + \frac{V_A - V_C}{10} = 0$$

(b) At node B:

$$\frac{V_B}{10} + \frac{V_B - V_A}{10} - I_{s2} = 0$$

(c) At node C:

$$I_{s2} - I_{s3} + \frac{V_C - V_A}{10} = 0$$

(d) Manipulate algebraically to cast as the following matrix equation:

$$\begin{array}{cccc}
3 & -1 & -1 & V_A \\
-1 & 2 & 0 & V_B \\
-1 & 0 & 1 & V_C
\end{array} = \begin{array}{c} V_{s1} \\ 10I_{s2} \\ 10(I_{s3} - I_{s2}) \end{array}$$

$$\begin{array}{cc}
V_A & -13\frac{1}{3} \\
V_B & = 13\frac{1}{3} \\
V_C & -43\frac{1}{3}
\end{array}$$

(e)  $P = (-10-13.333)/10 \times (-10) = 23.33W$ .

**Solution 3.12**

We are required to write the equations in matrix form. First, write a node equation at  $V_A$  and  $V_{out}$ :

$$V_A - 5 + \frac{V_A}{5} + \frac{V_A - V_{out}}{10} = 0$$

$$\frac{V_{out} - V_A}{10} - 7.5V_A + \frac{V_{out}}{10} = 0$$

Now group the coefficients for  $V_A$  and  $V_{out}$ , and write the matrix equation:

$$\begin{matrix} 1 + 1/5 + 1/10 & -1/10 & V_A & = & 5 \\ -1/10 + 7.5 & 2/10 & V_{out} & = & 0 \end{matrix}$$

$$\begin{matrix} V_A & = & 1 \\ V_{out} & = & -37 \end{matrix}$$

where the matrix inversion was performed in MATLAB. The ratio of the output voltage to the input voltage is  $-37/5$ .

**Solution 3.13 (a)** Nodes A and B are already labeled:

$$(V_A - 9)0.1 + (V_A - 0.5V_B)0.2 + (V_A - V_B)0.3 = 0$$

$$(V_B - V_A)0.3 + (V_B - 9)0.5 + 0.4V_B = 0$$

This can be rearranged into:

$$(0.1 + 0.2 + 0.3)V_A - 0.3V_B - (0.2 \times 0.5)V_B = 0.9$$

$$-0.3V_A + (0.3 + 0.5 + 0.4)V_B = 4.5$$

The matrix equation can now be easily obtained:

$$\begin{matrix} 0.6 & -(0.5)(0.2) - 0.3 & V_A & = & 0.9 \\ -0.3 & 1.2 & V_B & = & 4.5 \end{matrix}$$

$$\begin{matrix} V_A & = & 4.8 \\ V_B & = & 4.95 \end{matrix}$$

(b)  $I_{in} = -(V_A - V_s)0.1 - (V_B - V_s)0.5 = 2.445A$

$$(c) P_s = V_S I_{in} = 22.005W, P_{dep} = 0.5 \times V_{out} \times (0.5V_{out} - V_A) \times 0.2 = -1.151W.$$

$$(d) P = V^2/R = (4.95) \times (4.95) \times 0.4 = 9.801W.$$

**Solution 3.14** (a) We write node equations at  $V_A$  and  $V_B$ :

$$-I_{s1} + \frac{V_A}{20k} + gm_1 V_A + \frac{V_A - V_B}{10k} = 0$$

$$\frac{V_B - V_A}{10k} - gm_2 (V_A - V_B) + \frac{V_B}{2.5k} + I_{s2} - gm_1 V_A = 0$$

Rearranging, we have:

$$\frac{1}{20k} + gm_1 + \frac{1}{10k} V_A - \frac{V_B}{10k} = I_{s1}$$

$$\frac{-1}{10k} - gm_2 - gm_1 V_A + \frac{1}{10k} + gm_2 + \frac{1}{2.5k} V_B = -I_{s2}$$

(b)

$$\begin{matrix} 1/20k + gm_1 + 1/10k & -1/10k & V_A & = & I_{s1} \\ -1/10k - gm_2 - gm_1 & 1/10k + gm_2 + 1/2.5k & V_B & = & -I_{s2} \end{matrix}$$

(c) The above matrix is inserted into MATLAB, with all the values substituted, to obtain:

$$\begin{matrix} V_A & = & 9.722 \\ V_B & = & 5.972 \end{matrix}$$

$$(d) V_o = V_A - V_B = 3.75V$$

$$(e) P_1 = V_A I_{s1} = 0.0292W, P_{gm1} = -V_o gm_1 V_A = -0.008W, P_{gm2} = V_B gm_2 V_o = 0.0112W, P_2 = -V_B I_{s2} = -0.0119W.$$

**Solution 3.15**  $I_1 = 0.4$ . Write nodal equations at A and B

$$\frac{V_A}{100} + \frac{V_A - V_B}{20} + 0.03(V_A - V_B) = 0.4$$

$$\frac{V_B - V_A}{20} + \frac{V_B}{40} + \frac{V_B - 80}{40} = 0$$

Rearranging and casting into matrix form:

$$\begin{array}{rcl}
 1/100 + 1/20 + 0.03 & -1/20 - 0.03 & V_A = 0.4 \\
 -1/20 & 1/20 + 1/40 - 1/40 & V_B = 0 \\
 & & V_A = 40 \\
 & & V_B = 40
 \end{array}$$

It is obvious then, that  $V_x$ , the voltage between A and B, is zero.

### Solution 3.16

$$1) \quad V_A = 3000i_x = 3000 \times \frac{V_A - V_B}{9000} = \frac{V_A - V_B}{3}$$

Equation at node B:

$$\frac{V_B - V_A}{9000} + \frac{V_B}{6000} + \frac{V_B - V_D}{18000} = 0 \text{ is equivalent to:}$$

$$2) \quad -2V_A + 6V_B - V_D = 0$$

Equation at node D:

$$\frac{V_D - V_B}{18000} + \frac{V_D}{9000} + I_S = 0 \text{ which can be rewritten as:}$$

$$3) \quad 3V_D - V_B = -360 \text{ Solving the system formed by equations (1), (2) and (3) we obtain:}$$

$$V_A = 9V, \quad V_B = -18V, \quad V_D = -126V.$$

### Solution 3.17 (a) Choose E as the reference node

$$V_A = 2i_x$$

At node B

$$6 = (V_B - V_C)/3 + (V_B - V_A)/2$$

Or

$$6 = 5/6V_B - 1/3V_C - V_A/2$$

At node C,

$$V_C = 2i_y$$

At node D,

$$V_D = -12V$$

$$i_y = (V_D - V_A)/2 = V_D/2 - i_x$$

From here on, the solution involves algebraic manipulations to solve the system of equations. MATLAB or hand analysis can be performed to obtain:

$$V_A = 48V, \quad V_B = 12V, \quad V_C = -60V.$$

$$(b) \quad P_{6A} = 6(12) = 72W$$

$$I_{12V} = 30 - 8 = 22A \quad (P_{12V} = 264W).$$

$$P_{2i_x} = 2i_x \times (-i_z - i_y) = 2 \times 24 \times (+18 + 30) = 2304W$$

$$P_{2i_y} = 2i_y \times (-i_x + \frac{v_c - v_D}{6}) = 2 \times (-30) \times (-24 - 8) = 1920W$$

$$(c) P_3 = i_x \times (V_B - V_C) = 1728W = 1728W$$

$$P_6 = 6 \times 8 \times 8 = 384W$$

$$P_{2y} = 2 \times i_y \times i_y = 1800W$$

$$P_2 = (V_B - 2i_x)(V_B - 2i_x)/2 = 648W.$$

$$(c) V_D = -12V, V_A = 2i_x, V_C = 2i_z.$$

Substitute the above  $V_A$  and  $V_C$  into the node equation for node B:

$$i_z = (V_B - 2i_x)/2 = V_B/2 - i_x \text{ and}$$

$$i_x = (V_B - 2i_z)/3 = V_B/3 - 2/3i_z$$

Substitute  $i_z$  into  $i_x$  to obtain:  $i_x = 0, V_A = 0$ . Then,  $V_B$  can be deduced to be 12.

Finally,  $V_C = 12V$ .

Now, compute the powers.

$$P_{6A} = 72W, P_3 = 0, P_6 = (V_C - V_D)^2/6 = 96W, P_{2y} = 72W, P_{2z} = 72W.$$

$$P_{12V} = 12 \times \left( \frac{V_A - V_D}{2} + \frac{V_C - V_D}{6} \right) = 12 \times (6 + 4) = 120W,$$

$$P_{2ix} = 0W, P_{2iy} = 12 \times 4 = 48W$$

**Solution 3.18** The three node equations at A, C, and D are:

$$-0.8 - 0.3 = 0.015V_A + 0.02V_A - 0.02V_C$$

$$V_C = 440$$

$$-0.8 + 2.5 = -0.005V_D + 0.025V_C - 0.025V_D$$

As can be seen, these really reduce to only two equations in two unknowns. These can be solved rather easily either by hand or by MATLAB to obtain:  $V_A = 220V, V_D = 310V$ . Note that all of these voltages are already referenced to node B (i.e.  $V_A = V_{AB}$ , etc).

**Solution 3.19 (a)** Supernode is BC (50 V source).

**(b)** Only one node equation needs to be written:

$$\frac{V_B}{90} - \frac{V_A}{90} + \frac{V_B}{10} + \frac{V_C}{10} - \frac{V_A}{10} + \frac{V_C}{90} = 0$$

with the constraint that  $V_C - V_B = 50$ .

(c) The constraint equation can be substituted into the B node equation to obtain

$$V_B = 125V. \text{ Thus, } V_C = 175V, \text{ and } i_x = (V_C - V_A)/10 = -12.5A.$$

(d)  $(V_A - V_B)/90 = 1.94A \rightarrow P_{300} = 300 \times (1.94 + 12.5) = 4332W$ .

$V_C/90 = 1.94 \rightarrow P_{50} = -528W$ .

$$P_{50} = 50 \times (i_x + \frac{V_C}{90}) = -528W$$

**Solution 3.20 (a)**  $V_B = V_A - 440$  and  $V_C = V_A - 460$ .

(b) Supernode is one including A, B, and C.

(c)  $(V_C - 40)0.15 + 0.05V_B + 0.25V_A - 25 + 0.2(V_A - 40) = 0$

This can easily be rearranged to get  $V_A = 200V$ .

(d) power  $P_s = V_A \times I = 200 \times 25 = 5000W = 5KW$

**Solution 3.22 (a)**  $V_C = V_{s2} = 6V$

(b)  $I_x = 0.01V_A$

(c) Supernode at A,B, encompassing the controlled source. So, we have one equation:

$$I_{s1} = 0.01V_A + 0.0125V_B + 0.1V_B - 0.1V_C$$

(d) Substitute the constraint equations,  $V_A - V_B = 20I_x = 0.2V_A$ , (equivalently:  $V_A = \frac{V_B}{0.8}$ ) into the above

equation:  $V_A = \frac{V_B}{0.8}$

$$I_{s1} = 0.01 \frac{V_B}{0.8} + 0.0125V_B + 0.1V_B - 0.1V_C$$

$$V_B = 6.4V$$

$$V_A = 8V$$

(e)  $I_x = 0.08A$ .

(f)  $P_{0.0125} = V_B^2 / R = 0.512W$

(g)  $P = I_{s1} \times V_A = 0.2 \times 8 = 1.6W$

**Solution 3.23 (a)**  $V_C = V_{s2} = 50V$ .

(b)  $i_x = V_A/100$ .

(c) Supernode A,B:

$$I_{s1} = 0.01V_A + 0.05V_B + 0.05V_B - 0.05V_{s2} + 0.09V_A - 0.09V_{s2}$$

$$V_A = V_B + 300i_x = V_B + 3V_A$$

(d) Solving the above two equations yields:  $V_A = -90V$ ,  $V_B = 180V$ .

(e)  $i_x = \frac{V_A}{100} = \frac{-90}{100} = -0.9A$

(f)  $(V_B - V_C)(V_B - V_C)/R = 845W$ .

(g)  $P_{S1} = I_{S1} \times V_A = 2 \times (-90) = -180W$

**Solution 3.24 (a)**  $V_B - V_C = 3V_x = 3V_B$ ;  $V_C = -2V_B$

(b) Supernode at B and C, encompassing controlled source.

(c)

$$I_{s2} = \left(\frac{V_B}{10} - \frac{V_A}{10}\right) + \frac{V_B}{10} + \frac{V_C}{10} + \left(\frac{V_C}{10} - \frac{V_A}{10}\right); V_C = -2V_B; 10I_{s2} = -2(V_B + V_A)$$

equivalently:  $2V_A + 2V_B = -10$

(d)

$$(0.1V_A - 0.1V_{s1}) + (0.1V_A - 0.1V_B) + (0.1V_A - 0.1V_C) = 0; 0.3V_A + 0.1V_B = 0.1V_{s1}; \text{equivalently:}$$

$$3V_A - V_B = -10$$

(e) Again, any method can be used to simplify and solve the system of two equations. The solution is:

$$V_A = -2.5V, V_B = -2.5V.$$

**Solution 3.25 (a)**  $V_A = V_{s1} = 16V$ .

(b) Supernode at C and D, encompassing controlled voltage source.

(c)  $I_{s2} = (0.75mV_D - 0.75mV_B) + (1mV_C - 1mV_A)$

(d)  $V_C = 4V_B + V_D$

(e)

$$0.75mV_D + (0.75mV_B - 0.75mV_D) + (0.25mV_B - 0.25mV_A) = 0$$

$$\text{or } 1mV_B - 0.25mV_A = 0$$

(f) We now have three equations in  $V_B$ ,  $V_C$ , and  $V_D$ . These can be solved using any method. By inspection, we can immediately deduce  $V_B$  from  $V_A$  using the last equation:  $V_B = 4V$ .

The remaining two equations can be solved to obtain:  $V_C = 20V$  and  $V_D = 4V$ .

**Solution 3.26 (a)** The supernode is the combination of A, C, and the controlled voltage source.

(b) Write node equations starting at the supernode:

$$(G_2V_A - G_2V_{in}) + (G_3V_A) + (G_4V_A - G_4V_B) + (G_6V_C) + (G_5V_C - G_5V_B) = 0$$

$$(G_2 + G_3 + G_4)V_A + (-G_4 - G_5)V_B + (G_6 + G_5)V_C = G_2V_{in}$$

and

$$(2G_6V_C) + (G_4V_B - G_4V_A) + (G_5V_B - G_5V_C) + (G_1V_B - G_1V_{in}) = 0$$

$$(-G_4)V_A + (G_1 + G_4 + G_5)V_B + (2G_6 - G_5)V_C = G_1V_{in}$$

and

$$V_A - V_C = 3V_x, \quad V_A - V_C = 3(V_{in} - V_A), \quad 4V_A - V_C = 3V_{in}$$

In matrix form:

$$\begin{array}{cccccc} 0.8 & -0.5 & 0.2 & V_A & & 6 \\ -0.4 & 0.6 & 0.1 & V_B & = & 6 \\ 4 & 0 & -1 & V_C & & 180 \end{array}$$

(c) The above system of equations can be solved to obtain:  $V_A = 38.75V$ ,  $V_B = 40V$ ,  $V_C = -25V$ .

(d)  $I_{in} = (G_7V_{in}) + (G_2V_{in} - G_2V_A) + (G_1V_{in} - G_1V_B) = 5A$ .

→  $R_{eq} = 12$  and  $P = 300W$ .

$P = V_{in} \times I_{in} = 60 \times 5 = 300W$

(e)  $I_{out} = V_C G_6 = -2.5A$  →  $P = 62.5W$ .

**Solution 3.27 (a)** Supernode is A,B encompassing controlled voltage source.

(b)

$$(V_A - V_{s1}) + 0.4V_B + (0.2V_B - 0.2V_C) = 0$$

$$\rightarrow V_A + 0.6V_B - 0.2V_C = V_{s1}$$

(c)  $V_A - V_B = I_B = 0.4V_B$  →  $V_A = 1.4V_B$ .

(d)  $I_{s2} = 0.2V_B + (0.2V_C - 0.2V_B) = 0.2V_C$ .

(e)

In matrix form:

$$\begin{array}{cccccc} 1 & 0.6 & -0.2 & V_A & & 8 \\ 1 & -1.4 & 0 & V_B & = & 0 \\ 0 & 0 & 0.2 & V_C & & 2 \end{array}$$

The solution is:  $V_C = 10V$ ,  $V_A = 7V$ ,  $V_B = 5V$ .

$$(f) \quad i = (V_A - V_{s1})1S = -1 \rightarrow P_{ccvs} = (V_A - V_B) \times (V_A - V_{s1}) \times 1S = -2W$$

$$P_{vccs} = (V_{s1} - V_C)(0.2V_B) = -2W.$$

**Solution 3.28 (a)** Supernode at A,C, CCVS.

(b) Node equation at supernode:

$$I_s + 0.25mV_A = G_1V_A + (G_2V_A - G_2V_B) + (G_5V_C) + (G_4V_C - G_4V_B)$$

$$\rightarrow I_s = (G_1 + G_2 - 0.25m)V_A + (-G_2 - G_4)V_B + (G_4 + G_5)V_C$$

Constraint:

$$V_A - V_C = 10^4 i_x = 10^4 G_3 V_B$$

$$\rightarrow 0 = V_A - 10^4 G_3 V_B - V_C$$

At node B:

$$G_3V_B + (G_2V_B - G_2V_A) + (G_4V_B - G_4V_C) = 0$$

$$\rightarrow -G_2V_A + (G_3 + G_2 + G_4)V_B - G_4V_C = 0$$

(c) Matrix equation:

$$\begin{array}{cccccccccc} G_1 + G_2 - 0.25m & -G_2 - G_4 & G_4 + G_5 & V_A & I_s & 0 & -1 & 1 & V_A & 2 \\ 1 & -10^4 G_3 & -1 & V_B & = 0 & ; & 1000 & -1000 & -1000 & V_B = 0 \\ -G_2 & G_3 + G_2 + G_4 & -G_4 & V_C & 0 & -0.2 & 1.1 & -0.8 & V_C & 0 \end{array}$$

(d) Substitute the values of conductances and solve the above matrix equation in MATLAB to obtain:

$$V_A = -38V, V_B = -20V, V_C = -18V.$$

$$(e) P = V \times I = (10^4 G_3 V_B) \times [-I_s + V_A G_1 + G_2(V_A - V_B)] = (-20) \times [-2m - 1.9m - 3.6m] = 0.15W$$

**Solution 3.29**

Loop equation:  $V_{in} = 2kI_1 + 500(I_1 + 20m)$

$$\rightarrow V_{in} = 2500I_1 + 10 \rightarrow I_1 = 20mA.$$

$$P_{vin} = 20m \times 60 = 1.2W.$$

$$P_1 = 20m \times (500I_1 + 500 \times 20m) = 0.4W.$$

$$P_{2k} = I_1 \times I_1 \times R = 0.8W.$$

$$P_{500} = (I_1 + 20m)^2 R = 0.8W.$$

total power absorbed by resistors:  $P_R = 0.8 + 0.8 = 1.6$

total power delivered by sources:  $P_s = 1.2 + 0.4 W = 1.6W$

Conservation of power is verified.

### Solution 3.30

$$\text{Loop equation: } 100(I_1 - 0.5) + 200I_1 + 500 \times (I_1 + 20m) = 0$$

$$\rightarrow I_1 = 0.05A.$$

$$P_{0.5A} = I \times V_{100} ; V_{100} = 100 \times (0.5 - 0.05); \text{ where } V_{100} \text{ is the voltage on the } 100 \text{ resistor.}$$

$$P_{0.5A} = 0.5(0.5 \times 100 - 0.05 \times 100) = 22.5W.$$

$$P_{20m} = 20m(I_1 + 20m)500 = 0.7W.$$

### Solution 3.31

$$\text{Loop equation: } 3.3 = 50I_1 + (50m + I_1)100 + (I_1 - 30m)40 + (I_1 - 50m)60$$

$$\rightarrow I_1 = 0.01A.$$

The power delivered by the independent voltage source:

$$P = I_1 \times 3.3 = 0.033W.$$

### Solution 3.32

$$\text{Loop equation: } 50 = 300I_1 + (I_1 - 0.4I_1)500$$

$$50 = (300 + 500 - 200)I_1 \rightarrow I_1 = 0.0833A.$$

Power absorbed by the 500 resistor.

$$P_{500} = (I_1 - 0.4I_1)^2 500 = 1.25W.$$

### Solution 3.33

$$\text{Loop equation: } 1000(I_1 - I_s) + 4000I_1 + 5000(I_1 - g_m V_x) = 0 \quad 10000I_1 - 2V_x = 50$$

and

$$V_x = 1000(I_s - I_1) \quad 1000I_1 + V_x = 50.$$

Solve the above two equations in  $I_1$  and  $V_x$  to obtain:  $I_1 = 12.5mA$ ,  $V_x = 37.5V$ .

$$\text{Thus, } R_{eq} = V_x / I_s = 750\Omega,$$

$$P = I_{vccs} \times V_{vccs} = g_m \times V_x \times 5000 \times (g_m V_x - I_1) = 0.1875W$$

### Solution 3.34

Loop equation:  $V_{in} = 2I_{in} + 14I_{in} - 10V_1$

$$V_1 = 2I_{in}$$

After replacing  $V_1$  in the loop equation we obtain:

$$\rightarrow V_{in} = -4I_{in} \rightarrow$$

$$R_{leg} = \frac{V_{in}}{I_{in}} = -4$$

### Solution 3.35

Loop equation:  $V_s = 500I_1 + 100(I_1 + 0.5) + 400(I_1 - 0.001V_x) + 100(I_1 + 0.005V_y)$

$$V_x = 500I_1, V_y = 400I_1 - 400 \times 0.001 V_x = 400I_1 - 200I_1 = 200I_1$$

After replacing  $V_x$  and  $V_y$  in the loop equation we obtain:

$$V_s - 50 = 1000I_1 \rightarrow I_1 = 0.1A$$

$$V_y = 200I_1 = 20V \rightarrow P_{400ohm} = V_y^2 / 400 = 1W$$

$$R_{eq} = V_s / I_1 = 150 / 0.1 = 1500 \ .$$

### Solution 3.36

Select clockwise loop current  $I_1$  in the left loop. Select anti clockwise loop current  $I_2$  in the right loop.

The two mesh equations are:

$$12 = I_1 + 10(I_1 + I_2)$$

and  $10(I_2 + I_1) + 2I_2 + 12 = 0$

The two simultaneous equations can be solved easily to obtain:  $I_1 = 0.75A$ ,  $I_2 = +0.375A$ .

$$P_{10ohm} = (I_1 + I_2)^2 / 10 = 0.127W.$$

Battery 1 supplies more current. ( $I_1 > I_2$ )

### Solution 3.37

(a) The equation for the left loop is:

$$660 = I_1R + 1.296(I_1 + I_2) + 590 + I_1R$$

The equation for the right loop is:

$$660 = (0.3 - R) I_2 + 1.296 (I_1 + I_2) + 590 + (0.3 - R) I_2$$

Simplifying the two equations:

$$70 = 1.596I_1 + 1.296I_2$$

$$70 = 1.296I_1 + 1.596I_2$$

The solution of these two equations is:  $I_1 = I_2 = 24.2\text{A}$ .

(b)  $I_1 + I_2 = 48.4$ , voltage across locomotive =  $590 + 48.4 \times 1.296 \rightarrow$  power =  $31592\text{W}$ .

(c) Because the locomotive is  $1/3$  distance from either station it follows that

$R = 1/3 \times 0.3 = 0.1$ . The two equations become:

$$70 = I_1(2R + 1.296) + 1.296I_2$$

$$70 = 1.296I_1 + (1.296 + 0.6 - 2R)I_2$$

The solution of these two equations is:  $I_1 = 32.64\text{A}$ ,  $I_2 = 16.32\text{A}$ .

Current in locomotive motor  $I_1 + I_2 = 48.96\text{A}$ .


Voltage across locomotive  $590 + (I_1 + I_2) \times 1.296$

It follows that:

$$\rightarrow P = (I_1 + I_2)(590 + 49 \times 1.296) = 31993\text{W}.$$

### Solution 3.38

(a)

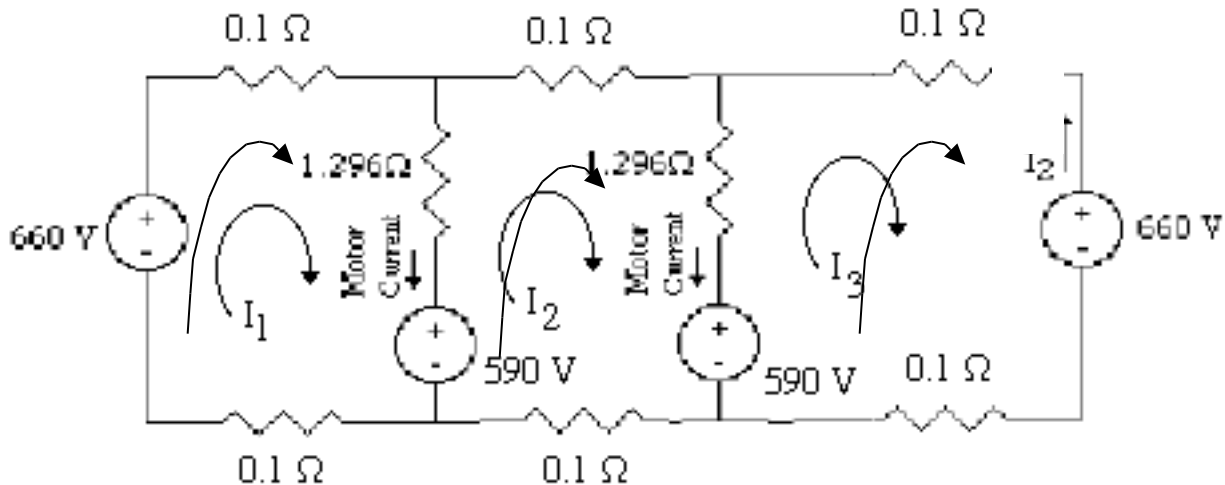

(b) The three loop equations are:

$$660 - 590 = 0.1I_1 + 1.296(I_1 - I_2) + 0.1I_1$$

$$0 = 1.296(I_2 - I_1) + 0.2I_2 + 1.296(I_2 - I_3)$$

$$-70 = 1.296(I_3 - I_2) + 0.2I_3$$


These three equations can be solved using any method to obtain:

$$I_1 = 46.8\text{A}, I_2 = 0, I_3 = -46.8\text{A}.$$

(c) Motor currents are 46.8A each.

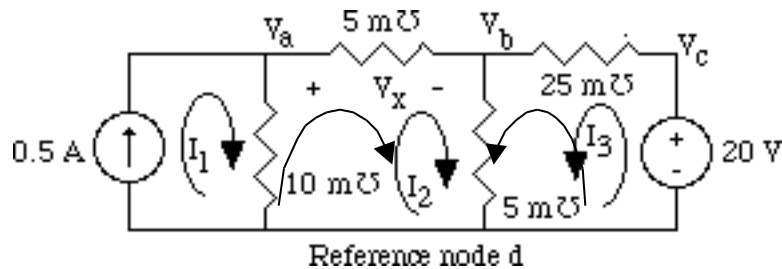(d)  $P_s = VI = 660 \times 46.8 = 30.9\text{kW}$ . Each source supplies 30.9kW.

**Solution 3.39 (a)** Define three meshes with three mesh currents. The first,  $I_1$ , is a clockwise current around the first mesh. The second,  $I_2$ , is a clockwise current around the middle loop of the circuit (through the 10mS, 5ms, and 5ms conductances). The third,  $I_3$ , is a *counterclockwise* current through the right-most loop containing the voltage source.



\*current names shown above.

(b)  $I_1 = 0.5\text{A}$

$$\left(\frac{I_2}{10\text{m}} - \frac{I_1}{10\text{m}}\right) + \frac{I_2}{5\text{m}} + \left(\frac{I_2}{5\text{m}} + \frac{I_3}{5\text{m}}\right) = 0.$$

$$\left(\frac{I_3}{25\text{m}} + \frac{I_3}{5\text{m}}\right) + \frac{I_2}{5\text{m}} = 20$$

These are two equations in two unknown currents. After grouping the terms, it can be verified that:

$$I_2 = 0.1\text{A}, I_3 = 0.$$

(c)  $V_x = 20\text{V}$

$$V_{\text{ad}} = (0.5 - I_2)/10\text{m} = 40\text{V}$$

$$V_{\text{bd}} = 20\text{V}$$

(d)  $P_{0.5} = V_a \times 0.5 = 40 \times 0.5 = 20\text{W}$

$$P_{20\text{V}} = 0\text{W}$$

$$P_{\text{resistors}} = 2 \times I_2^2/5\text{m} + (0.5 - I_2)^2/10\text{m} = 20\text{W}$$

The conservation of power is verified.

**Solution 3.40 (a)** We can either write down the equations or evaluate the matrix by inspection:

$$90 \times (I_2 - 4.8m) + 10kI_2 + 50 = 0$$

$$90kI_3 + 10 \times (I_3 - 4.8m) = 50$$

OR

$$\begin{array}{cccc} 100k & 0 & I_2 & 90k \times 4.8m - 50 \\ 0 & 100k & I_3 & 10k \times 4.8m + 50 \end{array} =$$

(b) The solution of the above equation is:  $I_2 = 3.82mA$ ,  $I_3 = 0.98mA$ .

(c) Current source:  $P = 4.8m \times [(4.8m - I_2)90k + (4.8m - I_3)10k] = 0.61W$ .

Voltage source:  $P = 50(I_3 - I_2) = -142mW$ .

**Solution 3.41 (a)** By inspection:

$$\begin{array}{cccc} 112k & -90k & -10k & I_1 & 180 \\ -90k & 100k & 0 & I_2 & -60 \\ -10k & 0 & 100k & I_3 & 60 \end{array} =$$

(b) Using MATLAB:

$$I_1 = 4.4mA, I_2 = 3.36mA, I_3 = 1.04mA$$

$$i_x = -I_2 = -3.36mA$$

(c)  $P_{180} = 180 \times 4.4m = 0.792W$ ,  $P_{60} = 60(I_3 - I_2) = -0.139W$ .

**Solution 3.42** The matrix equation is:

$$\begin{array}{cccc} 8 & -6 & 3 & I_1 & 14 \\ -6 & 8 & -2 & I_2 & 0 \\ 3 & -2 & 4 & I_3 & 6 \end{array} =$$

whose solution is:  $I_1 = 4A$ ,  $I_2 = 3A$ ,  $I_3 = 0A$

$$v = (I_1 + I_3 + I_2) \times 2 = 2V$$

**Solution 3.43 (a)** First, note that two mesh currents are needed. Two clockwise currents are defined:  $I_1$  in the middle loop, and  $I_2$  in the right-most loop:

Middle loop equation:

$$100I_1 - 100I_{s1} + 20I_x + 80I_1 - 80I_2 = 0, \text{ where } I_x = I_{s1} - I_1$$

and

Right-most loop equation:

$$80I_2 - 80I_1 + 10I_2 + V_{s2} = 0$$

These can easily be cast into the following matrix equation:

$$\begin{matrix} 160 & -80 & I_1 & = & 16 \\ -80 & 90 & I_2 & = & -6 \end{matrix}$$

(b) The solution of this equation is:  $I_1 = 0.12\text{A}$ ,  $I_2 = 0.04\text{A}$ .

(c)  $V_A = 100(I_{s1} - I_1) = 8\text{V}$  and  $V_B = 80x(I_1 - I_2) = 6.4\text{V}$ .

(d)  $P_{s1} = I_{s1} V_A = 1.6\text{W}$ .

(e)  $P_{0.0125S} = (I_1 - I_2)^2 / 0.0125 = 0.512\text{W}$ .

**Solution 3.44 (a)** Create two clockwise mesh currents in the top loop ( $I_2$ ) and the bottom-left loop ( $I_1$ ).

The bottom-right loop has an independent current source. Writing the loop equations:

$$V_{s1} = 200 (I_1 - I_2) + 200 (I_1 + I_{s2})$$

$$200 (I_2 - I_1) + 100I_2 + 300I_x + 200 (I_2 + I_{s2}) = 0, \text{ where } I_x = I_1 - I_2$$

(b) Solving, we get:  $I_1 = -0.1\text{A}$ ,  $I_2 = -0.7\text{A}$ ,  $I_x = 0.6\text{A}$ .

(c)  $V_B = (I_1 + I_{s2})200 = 130\text{V}$ .

(d)  $P_{vs1} = I_1 V_{s1} = -25\text{W}$ ,  $P_{is2} = (V_B + (I_{s2} + I_2)200)I_{s2} = 105\text{W}$ ,  $P_{300ix} = (-I_2)(300I_x) = 126\text{W}$ .

**Solution 3.45 (a)** Create two clockwise mesh currents in the top loop ( $I_1$ ) and the middle loop ( $I_2$ ) (all resistor loop):

Top loop equation:

$$0.5v_x = 500 (I_1 - I_2) + 500I_1 \text{ where } v_x = -500I_1$$

and

Middle loop equation:

$$600 (I_2 - I_{s1}) + 500 (I_2 - I_1) + 900 (I_2 + I_{s2}) = 0$$

(b) Solving, we get:  $I_1 = 0.015\text{A}$ ,  $I_2 = 0.0375\text{A}$ ,  $v_x = -7.5\text{V}$ .

(c)  $P_{is1} = I_{s1} [0.5v_x + (I_{s1} - I_2)600] = 109.7\text{W}$

$P_{0.5vx} = 0.5v_x(I_1 - I_{s1}) = 1.63\text{W}$

$P_{is2} = (I_2 + I_{s2}) \times 900 \times I_{s2} = 53.2\text{W}$

**Solution 3.46** Write the mesh equations in terms of R's and then substitute the values from the matrix:

Mesh 1 equation:

$$v_1 = R_1 (i_1 - i_3) + R_2 (i_1 - i_2) - 25i_2$$

From this equation, and the first row of the matrix equation, we can deduce that

$$R_1 = 5$$

and

$$R_2 + 25 = 40 \quad R_2 = 15 \quad .$$

Similarly:

Mesh 3 equation:  $R_1(i_3 - i_1) + i_3 R_4 + R_3(i_3 - i_2) = 0$

From which we can deduce:

$$R_3 = 25 \quad \text{and} \quad R_4 = 5 \quad .$$

**Solution 3.47**

Modified loop 1 equation:

$$V_{s1} = 3MI_1 + v + 2MI_1$$

Constraint equation:

$$-I_1 + I_2 = I_{s3}$$

Modified loop 2 equation:

$$v = 2MI_2 + V_{s2} + 8MI_2$$

Or in matrix form:

$$\begin{matrix} 5M & 0 & 1 & I_1 & V_{s1} \\ -1 & 1 & 0 & I_2 & = I_{s3} \\ 0 & -10M & 1 & v & V_{s2} \end{matrix}$$

Solving:  $I_1 = -1.1 \mu A, I_2 = -0.95 \mu A.$

The power  $P_{s3} = I_{s3} \times v = 7.58 \mu W$

**Solution 3.50**  $I_2 = 2A, I_3 = -7A$


Loop 1 equation:

$$V_s = 3I_1 + 3(I_1 - I_2) + 6(I_1 + I_3 - I_2) + 2v_y + 2(I_1 + I_3) = 14I_1 + 2v_y - 74 \quad 14I_1 + 2V_Y = 88$$

$$v_y = 3(I_1 - I_2) = 3I_1 - 6$$

Solving the above system, we obtain:  $I_1 = 5A \rightarrow v_y = 9$ ,  $v$  can be found from the loop 3 equation  $v + (I_1 + I_3 - I_2).6 + 2v_y + 2(I_3 + I_1) = 0$ . Solving, we obtain  $v = 10V$   
 Finally,  $P_{v_s} = V_s \times I_1 = 70W$ .

**Solution 3.51**

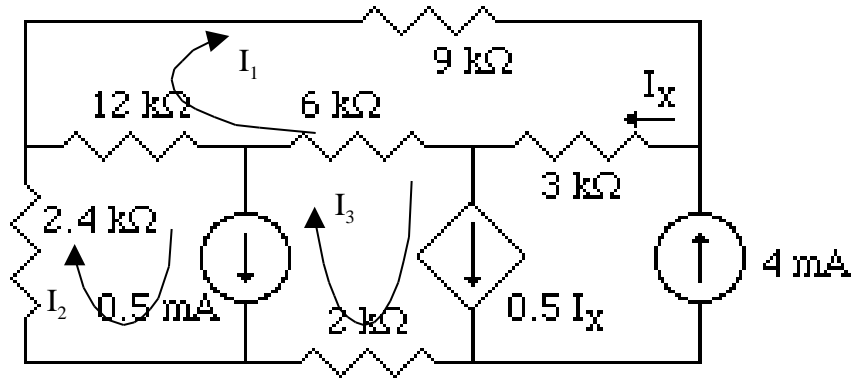

Mesh 1 equation:

$$9kI_1 + 3k(I_1 - I_4) + 6k(I_1 - I_3) + 12k(I_1 - I_2) = 0$$

where we have used the fact that  $I_x = I_1 - I_4$  (and  $I_4 = -4mA$ )

Mesh 3 equation:

$$6k(I_3 - I_1) - v_2 + 2kI_3 + v = 0$$

Mesh 2 equation:

$$2.4kI_2 + 12k(I_2 - I_1) - v = 0$$

Constraint equations:

$$I_2 - I_3 = 0.5mA$$

$$I_3 - I_4 = 0.5I_x = 0.5I_1 - -0.5I_4 = 0.5I_1 + 2mA ; 0.5I_1 - I_3 = -2mA$$

The above five equations need to be put into matrix form:

$$\begin{matrix} 30k & -12k & -6k & 0 & 0 & I_1 & -12 \\ -6k & 0 & 8k & 1 & -1 & I_2 & 0 \\ -12k & 14.4k & 0 & -1 & 0 & I_3 & = & 0 \\ 0 & 1 & -1 & 0 & 0 & v & 0.5m \\ 0.5 & 0 & -1 & 0 & 0 & v_2 & 2m \end{matrix}$$

The solution is:

$$\begin{aligned}
 I_1 &= -0.002A \\
 I_2 &= -0.0025A \\
 I_3 &= -0.003A \\
 v &= -12V \\
 v_2 &= -24V
 \end{aligned}$$


$$I_x = I_1 - I_4 = 2mA$$

Power delivered by 0.5mA current source:  $P_1 = 0.5mv = -6mW$

Power delivered by the dependent current source:  $P_2 = 0.5I_x \cdot v_2 = 1m \times (-24) = -24mW$

Power delivered by 4mA current source:  $P_3 = 4m \times (3k I_x - V_2) = 120mW$

**Solution 3.52**

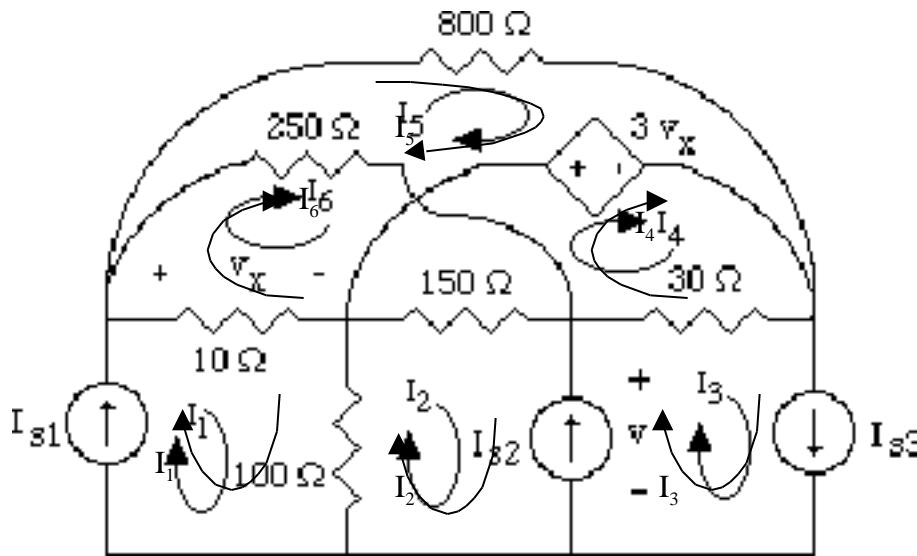

Write the following equations:

Mesh 2 equation:

$$100(I_2 - I_1) + 150(I_2 - I_4 - I_6) + v = 0$$

Mesh 4 equation:

$$3v_x + 30(I_4 - I_3) + 150(I_4 - I_2 + I_6) = 0$$

Mesh 5 equation:

$$800I_5 - 3v_x + 10(I_5 - I_1 + I_6) = 0$$

Mesh 6 equation:

$$250I_6 + 150(I_6 + I_4 - I_2) + 10(I_6 + I_5 - I_1) = 0$$

Constraint equation:

$$I_{s2} = -I_2 + I_3$$

Substituting the values of  $I_1 = I_{s1} = 1.15$  and  $I_3 = I_{s3} = 0.95$ , and noting that

$$v_x = (I_1 - I_6 - I_5)10$$

we can write:

$$\begin{array}{cccccc} 250 & -150 & 0 & -150 & 1 & I_2 & 100I_1 \\ -150 & 180 & -30 & 120 & 0 & I_4 & 30I_3 - 30I_1 \\ 0 & 0 & 840 & 40 & 0 & I_5 & = 40I_1 \\ -150 & 150 & 10 & 410 & 0 & I_6 & 10I_1 \\ 1 & 0 & 0 & 0 & 0 & v & I_3 - I_{s2} \end{array}$$

$$\begin{array}{ll} I_2 & 0.65 \\ I_4 & 0.45 \\ I_5 & = 0.05 \\ I_6 & 0.1 \\ v & 35 \end{array}$$

Finally,  $v_x = 10V$  and  $v$  is as given above.

### Solution 3.53 (a)

Replace the voltage source by current sources:

At node 1

$$i_{s1} = (V_2 - V_1) / 12k$$

At node 2

$$(V_2 - V_1) / 12k + (V_2 - V_3) / 90k + (V_2 - V_4) / 10k = 0$$

At node 3

$$i_{s2} = (V_3 - V_2) / 90k + V_3 / 10k$$

At node 4

$$i_{s2} + (V_4 - V_2) / 10k + V_4 / 90k = 0$$

$$V_1 = 180$$

$$V_4 - V_3 = 60$$

(b) In matrix form:

$$\begin{array}{cccccccc}
-1/12k & 1/12k & 0 & 0 & -1 & 0 & V_1 & 0 \\
-1/12k & 1/12k + 1/90k + 1/10k & -1/90k & -1/10k & 0 & 0 & V_2 & 0 \\
0 & -1/90k & 1/90k + 1/10k & 0 & 0 & -1 & V_3 & 0 \\
0 & -1/10k & 0 & 1/90k + 1/10k & 0 & 1 & V_4 & = 0 \\
1 & 0 & 0 & 0 & 0 & 0 & i_{s1} & 180 \\
0 & 0 & -1 & 1 & 0 & 0 & i_{s2} & 60
\end{array}$$

The solution from MATLAB is

180.0000  
127.2000  
33.6000  
93.6000  
-0.0044  
0.00232

(c) Power delivered by  $S_1$  is:

$$P_{s1} = V_{s1} \times (-I_{s1}) = 0.792W$$

Power delivered by  $S_2$  is:

$$P_{s2} = V_{s2} \times (-I_{s2}) = -0.139W$$

**Solution 3.54 (a)** Replace the 100 ohm resistor, the controlled voltage source, and  $v_{s2}$  by current source.

Then write the node equations:

$$\begin{aligned}
I_{s1} &= i_x + I_1 + 0.09(V_1 - V_3) \\
I_1 &= V_2/20 + 0.05(V_2 - V_3) \\
-I_2 &= 0.05(V_3 - V_2) + 0.09(V_3 - V_1) \\
V_3 &= V_{s2} \\
V_1 - V_2 &= 300i_x = 300V_1/100
\end{aligned}$$

In matrix form:

$$\begin{array}{ccccccc}
0.1 & 0 & -0.09 & 1 & 0 & V_1 & 2 \\
0 & 0.1 & -0.05 & -1 & 0 & V_2 & 0 \\
-0.09 & -0.05 & 0.14 & 0 & 1 & V_3 & = 0 \\
0 & 0 & 1 & 0 & 0 & I_1 & 50 \\
2 & 1 & 0 & 0 & 0 & I_2 & 0
\end{array}$$

(b) Using MATLAB to solve the above system the solution is:

$$\begin{aligned}
V_1 &= -90.0000V \\
V_2 &= 180.0000V
\end{aligned}$$

$$V_3 = 50.0000V$$

$$I_1 = 15.5000A$$

$$I_2 = -6.1000A$$


(c) Power delivered by the current source is

$$P_{s1} = I_{s1} \times V_1 = -180W$$

Power delivered by the voltage source is:

$$P_{s2} = V_{s2} \times (-I_2) = 305W$$

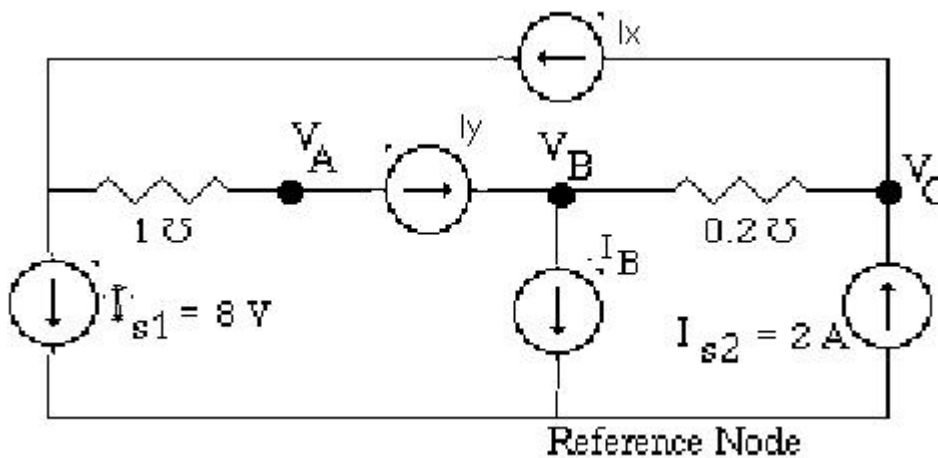**Solution 3.55** Modify the circuit so that it looks like the following:



The modified node equations are:

$$I_{s1} = -I_y + I_x$$

$$I_b = I_y + 0.2(V_C - V_B)$$

$$I_{s2} = 0.2(V_C - V_B) + I_x$$

The equations describing the constitutive relationships of elements in the original network are:

$$V_A - V_B = I_b$$

$$I_x = 0.2V_b$$

$$I_b = 0.4V_b$$

$$I_y = 8 - V_A$$


These can be cast into a matrix equation and solved easily to obtain the same result as previously arrived at.

In matrix form:

$$\begin{array}{cccccccc}
 0 & 0 & 0 & 1 & -1 & 0 & -1 & V_A & 0 \\
 0 & -0.2 & 0.2 & 0 & 1 & -1 & 0 & V_B & 0 \\
 0 & -0.2 & 0.2 & 1 & 0 & 0 & 0 & V_C & 2 \\
 1 & -1 & 0 & 0 & 0 & -1 & 0 & I_x & = 0 \\
 0 & 0.2 & 0 & -1 & 0 & 0 & 0 & I_y & 0 \\
 0 & 0.4 & 0 & 0 & 0 & -1 & 0 & I_b & 0 \\
 1 & 0 & 0 & 0 & 1 & 0 & 0 & I_{s1} & 8
 \end{array}$$

$$\begin{array}{ll}
 V_A & 7V \\
 V_B & 5V \\
 V_C & 10V \\
 I_x & = 1A \\
 I_y & 1A \\
 I_b & 2A \\
 I_{s1} & 0A
 \end{array}$$

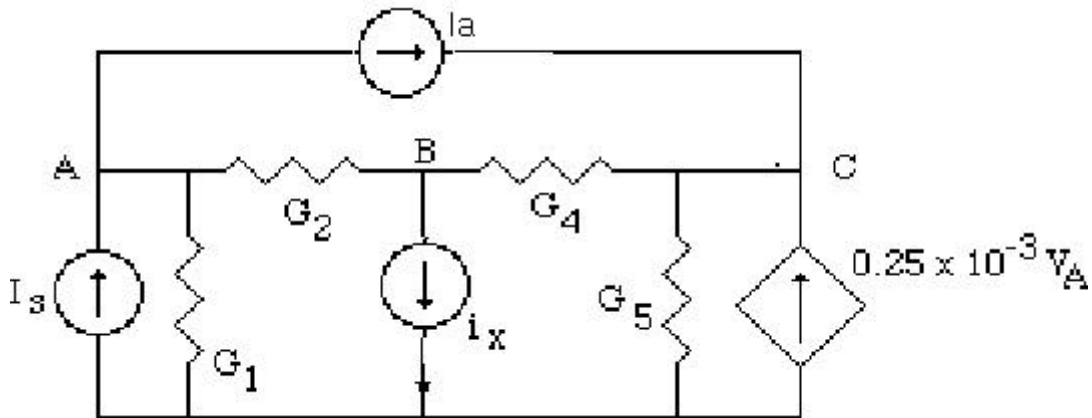**Solution 3.56** Modify the circuit as follows:



The modified node equations are:

$$\text{At node A:} \quad I_s = G_1 V_A + G_2 (V_A - V_B) + I_a$$

$$\text{At node B:} \quad G_2 (V_A - V_B) = I_x + G_4 (V_B - V_C)$$

$$\text{At node C:} \quad 0.25 \text{m} V_A + I_a = G_4 (V_C - V_B) + G_5 V_C$$

The equations describing the constitutive relationships of elements in the original network are:

$$I_x = G_3 V_B$$

$$V_A - V_C = 10^4 I_x$$

These can be cast into a matrix equation that can be solved in MATLAB.

In Matrix form:

$$\begin{array}{cccccc} 0.25m & -0.2m & 0 & 1 & 0 & V_A & 2m \\ -0.2m & 1m & -0.8m & 0 & 1 & V_B & 0 \\ -0.25m & -0.8m & 1m & -1 & 0 & V_C & = & 0 \\ 0 & -0.1m & 0 & 0 & 1 & I_a & 0 \\ 1 & 0 & -1 & 0 & -10^4 & I_x & 0 \end{array}$$

The solution is:

$$\begin{array}{ll} V_A & -38V \\ V_B & -20V \\ V_C & = -18V \\ I_a & 0.0075A \\ I_x & -0.002A \end{array}$$

We observe that we have obtained the same results as in problem 3.28.

**Solution 3.57** Replace dependent source by  $i_{35}$  (from 3 to 5). Also, replace voltage source by  $i_{10}$  (from 1 to 0). Now, write the modified node equations. The reference node is  $O:V_O = 0V$  :

At node 1:  $i_{10} = (V_6 - V_1) + (V_2 - V_1)$

At node 2:  $2 = (V_2 - V_1) + (V_2 - V_3)$

At node 3:  $i_{35} = (V_4 - V_3) + (V_2 - V_3)$

At node 4:  $2 = 2 + (V_4 - V_3) + V_4$

At node 5:  $i_{35} = (V_5 - V_6) + V_5$

At node 6:  $2 = (V_5 - V_6) - V_6$

Constraints:

$$V_3 - V_5 = 15V_x = 15V_4$$

$$V_1 = 5$$

The following matrix equation is obtained:

$$\begin{array}{cccccccccc}
-2 & 1 & 0 & 0 & 0 & 1 & -1 & 0 & V_1 & 0 \\
-1 & 2 & -1 & 0 & 0 & 0 & 0 & 0 & V_2 & 2 \\
0 & 1 & -2 & 1 & 0 & 0 & 0 & -1 & V_3 & 0 \\
0 & 0 & -1 & 2 & 0 & 0 & 0 & 0 & V_4 & 0 \\
0 & 0 & 0 & 0 & 2 & -1 & 0 & -1 & V_5 & = 0 \\
0 & 0 & 0 & 0 & 1 & -2 & 0 & 0 & V_6 & 2 \\
0 & 0 & 1 & -15 & -1 & 0 & 0 & 0 & i_{10} & 0 \\
1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & i_{35} & 5
\end{array}$$

The solution of this equation is obtained from MATLAB:

$$V_1 = 5.0000V$$

$$V_2 = 3.3571V$$

$$V_3 = 0.2857V$$

$$V_4 = -0.1429V$$

$$V_5 = 1.8571V$$

$$V_6 = -0.0714V$$

$$i_{10} = -6.7143A$$

$$i_{35} = 3.7857A$$

The power delivered by the dependent voltage source connected between nodes 3 and 5:

$$P_{35} = 15v_x(-i_{35}) = 15 \times V_4 \times (-i_{35}) = 8.115W$$

The power delivered by the current source connected between nodes 2 and 4:

$$P_{24} = (2A) \times (V_2 - V_4) = 7W$$

The power delivered by the current source connected between nodes 4 and 6:

$$P_{46} = (2A) \times (V_4 - V_6) = -0.143W$$


The power delivered by the voltage source connected between nodes 1 and 0:

$$P_{10} = 5V \times (I_{12} + I_{16}) = 5x[(V_1 - V_2) + (V_1 - V_6)] = 33.57W$$

**Solution 3.59** Using the appropriate element stamps for each element of the circuit, we obtain the following system:

$$\begin{array}{cccccc}
0.15 + 0.2 & -0.15 & -0.2 & 0 & V_A & -8 - 3 \\
-0.15 & 0.15 + 0.05 & 0 & -1 & V_B & 3 \\
-0.2 & 0 & 0.25 + 0.2 & 1 & V_C & = 25 \\
0 & -1 & 1 & 0 & I_x & 440
\end{array}$$

**Solution 3.60**

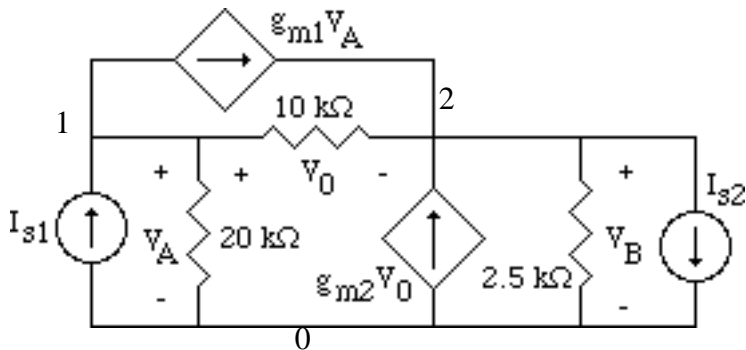

$$\begin{bmatrix} 1/20k + 1/10k + g_{m1} & -1/10k \\ -1/10k - g_{m1} - g_{m2} & g_{m2} + 1/10k + 1/2.5k \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_{s1} \\ -I_{s2} \end{bmatrix}$$

The solution is the same as that of problem 3.14.

**Solution 3.62 (a)** Because  $R_T(T)$  can be approximated by a straight line between  $(250, 0^\circ C)$  and  $(80, 50^\circ C)$  it follows that:

$$R_T(T) = -3.4T + 250$$

(b) For  $T = 25^\circ C$ ,  $R_T = 165$

(c) The voltage across the  $R_T + R_L$  series combination can be obtained from voltage division:

$$V_{T,L} = \frac{R_T + R_L}{R_T + 2R_L + R} 12 = 4.7857V$$

This is the same as the voltage across  $R_x$  because the meter is at zero deflection. Thus,

$$\frac{R_x}{R_x + R} 12 = 4.7857. \text{ It follows that } R_x = 165.84 \Omega.$$

(d) We first denote the nodes:

- A - the node common to  $R, R_x$  and the voltmeter;
- B - the node common to  $R, R$  and the voltage source;
- C - the node common to  $R_L, R_T$  and  $R_L$ ;
- D - the node common to  $R_x, R_L$  and the voltage source.

The reference node is D:  $V_D = 0$ . It follows that  $V_B = 12V$ .

We also have:  $v_{out} = V_A - V_C$

The node equations are:

At node A:  $\frac{V_A - V_C}{R_m} + \frac{V_A - 12}{R} + \frac{V_A}{R_x} = 0$

Equivalently:  $V_A(RR_x + R_mR_x + R_mR) - V_C RR_x = 12R_mR_x$   
 $V_A \times 4199.86 - V_C \times 41.46 = 19900.8$  (1)

At node C:  $\frac{V_C - 12}{R + R_L} + \frac{V_C}{R_T + R_L} + \frac{V_C - V_A}{R_m} = 0$

Equivalently:  $(V_C - 12) \times 0.004 + \frac{V_C}{R_T + 2.5} + (V_C - V_A) 10^{-4} = 0$

$$V_C(0.004 R_T + 0.01 + 1 + 0.00025 + R_T \times 10^{-4}) -$$

$$-V_A(R_T \times 10^{-4} + 0.00025) = 0.48 \times (R_T + 2.5)$$

The last equation can be rewritten as:

$$V_C(0.0041R_T + 1.01025) - V_A(R_T \times 10^{-4} + 0.00025) = 0.48(R_T + 2.5)$$
 (2)

From (1) and (2), we obtain:

$$(0.0041R_T + 1.01025) \times \frac{-19900.8 + V_A \times 4199.86}{41.46} -$$

$$-V_A \times (R_T \times 10^{-4} + 0.00025) = 0.48(R_T + 2.5)$$

Equivalently:  $V_A \times (R_T \times 0.415 + 102.337) = 2.448 \times R_T + 486.12$

It follows that  $V_A = \frac{2.448 \times R_T + 486.12}{0.415 \times R_T + 102.337}$

From the equation at node A:

$$v_{out} = V_A - V_C = -R_m \times \frac{V_A - 12}{R} + \frac{V_A}{R_x} = \frac{2.448 \times R_T + 486.12}{0.415 \times R_T + 102.337} \times (-100.3) + 480$$

At  $T = 0^\circ C$ :  $R_T = 250$  . It follows that  $v_{out} = -54.4415V$

At  $T = 50^\circ c$ :  $R_T = 80$  . It follows that  $v_{out} = 80V$

(e): The formula has been derived at part d):

$T$	$R_T$	$v_{out}$
$0^\circ C$	250	-54.4415V
$5^\circ C$	233	-52.4136V
$10^\circ C$	216	-50.2368V
$15^\circ C$	199	-47.8938V
$20^\circ C$	182	-45.3650V
$25^\circ C$	165	-42.6273V


30°C

148

-39.6537V

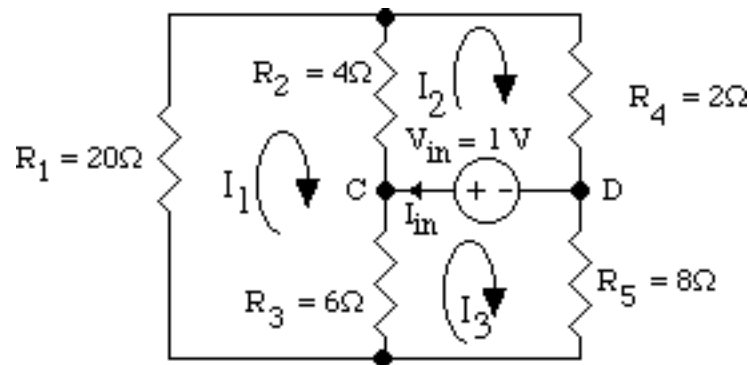**Solution 3.63**

Place a source  $V_{in}$  between C and D, and calculate the current drawn from the source as below:



Loop 1 equation:

$$I_1 R_1 + (I_1 - I_2) R_2 + (I_1 - I_3) R_3 = 0$$

Equivalently:

$$I_1 (R_1 + R_2 + R_3) - I_2 R_2 - I_3 R_3 = 0$$

Loop 2 equation:

$$(I_2 - I_1) R_2 + I_2 R_4 - 1 = 0$$

Equivalently:

$$-I_1 R_2 + I_2 (R_2 + R_4) = 1$$

Loop 3 equation:

$$1 + I_3 R_5 + (I_3 - I_1) R_3 = 0$$

Equivalently:

$$-R_3 I_1 + I_3 (R_3 + R_5) = -1$$

We obtain the following system of equations:

$$30I_1 - 4I_2 - 6I_3 = 0$$

$$-4I_1 + 6I_2 = 1$$

$$-6I_1 + 14I_3 = -1$$

$$I_1 = 0.0096A, I_2 = 0.1731A, I_3 = -0.0673A;$$

$$I_{in} = I_2 - I_3 = 0.2404A$$

$$R_{eg,CD} = \frac{V_{in}}{I_{in}} = \frac{1}{0.2404} = 4.16$$

### Solution 3.64

The node equation at node A is:

$$V_A G_1 + (V_A - V_B)G_2 + (V_A - V_C)G_3 = 0$$

Equivalently:

$$(G_1 + G_2 + G_3)V_A - V_B G_2 - V_C G_3 = 0$$

The supernode is identified by a Gaussian surface enclosing the controlled voltage source. The supernode equation is:

$$G_2(-V_A + V_B) - 6 + G_4 V_C + G_3(V_C - V_A) = 0$$

Equivalently, we have:

$$-V_A(G_2 + G_3) + G_2 V_B + V_C(G_3 + G_4) = 6$$

One way of obtaining the solution to the problem is:

We multiply the above two equations by 30.

$$-30(G_2 + G_3)V_A + 30G_2 V_B + 30(G_3 + G_4)V_C = 180$$

and

$$30(G_1 + G_2 + G_3)V_A - 30G_2 V_B - 30G_3 V_C = 0$$

By equating the coefficient of the above two equations with the coefficients of the first and second given equations, we obtain:

$$30G_2 = 30 \quad G_2 = 0.1S$$

$$30G_3 = 2 \quad G_3 = 0.067S$$

$$30(G_1 + G_2 + G_3) = 11 \quad G_1 = 0.2S$$

$$30(G_3 + G_4) = 32 \quad G_4 = 0.87S$$

$\beta$  can be obtained as follows:

$$V_C - V_B = \beta V_X = \beta(V_C - V_A)$$

Equivalently:

$$\beta V_A - V_B + (1 - \beta)V_C = 0$$

By comparing with the third given equation  $\beta = 3$ .

### Solution of 3.66

(a)

At node A:  $(V_A - V_C)/2 + (V_A - V_B)/2 + (V_A - V_D)/2 = 14$

At node B:  $(V_B - V_A)/2 + (V_B - V_C)/2 + (V_B - V_D)/2 = 7$


At node C:  $(V_C - V_A)/2 + (V_C - V_B)/2 + (V_C - V_D)/2 + 2V_C = 0$

At node D:  $(V_D - V_A)/2 + (V_D - V_B)/2 + (V_D - V_C)/2 + 0.5V_D = 0$

These can be solved in MATLAB to obtain:

- 22.0000
- 18.5000
- 7.5000
- 12.0000

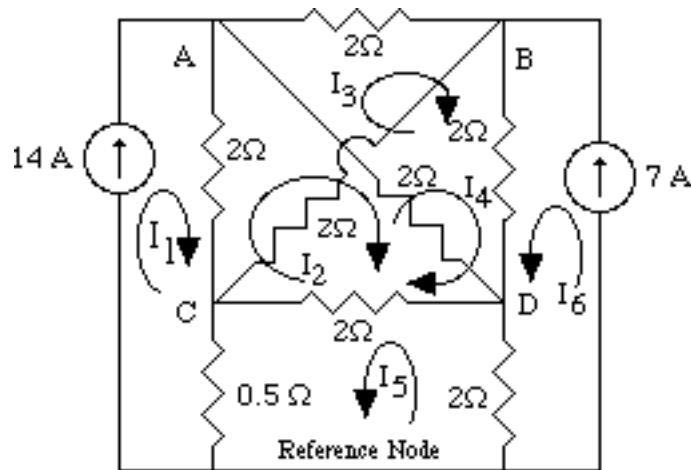(b) Mesh analysis would result in the same voltages



The loops and their current loops are:

$$A,C,14A:I_1$$

$$A,C,D:I_2$$

$$A,B,D:I_3$$

$$B,C,D:I_4$$

$$C,D,\text{reference node}:I_5$$

$$B,D,7A:I_6$$

$$I_1 = 14A, I_6 = 7A$$

$$\text{Loop } ACDE \text{ equation: } 2(I_2 - I_1) + 2(I_2 - I_3) + 2(I_2 + I_4 + I_5) = 0$$

$$\text{Loop } BCD \text{ equation: } 2(I_3 + I_6 + I_4) + 2(I_2 + I_4 + I_5) + 2I_4 = 0$$

$$\text{Loop } ABD \text{ equation: } 2(I_3 + I_4 + I_6) + 2(I_3 - I_2) + 2I_3 = 0$$

$$\text{Loop } CD_{ref} \text{ node equation: } 2(I_5 + I_2 + I_4) + 2(I_5 - I_6) + 0.5(I_5 + I_1) = 0$$

In matrix form:

$$\begin{array}{cccccc}
 6 & -2 & 2 & 2 & I_2 & 28 & I_2 & 6.75 \\
 2 & 2 & 6 & 2 & I_3 & -14 & I_3 & 1.75 \\
 -2 & 6 & 2 & 0 & I_4 & = -14 & ; & I_4 = -5.5 \\
 2 & 0 & 2 & 4.5 & I_5 & 7 & I_5 & 1
 \end{array}$$

$$V_A = 2(I_1 - I_2) + 0.5(I_1 + I_5) = 22V$$

$$V_B = 2(I_4 + I_3 + I_6) + 2(I_6 - I_5) = 18.5V$$

$$V_C = 0.5(I_1 + I_5) = 7.5V$$

$$V_D = 2(I_6 - I_5) = 12V$$

(c) Mesh analysis requires more work.

(d) The removal of the top resistor will result in more node equations than loop equations. The addition of a resistor between node A and reference node will result in more loop equations than node equations.