

## PROBLEM SOLUTIONS CHAPTER 5.

**Solution 5.1.** (a)  $V_s = 10$  V,  $P = 20$  W and  $P = V_s \times I_s$  implies  $I_s = 2$  A.

(b)  $R_{in} = V_s/I_s = 10/2 = 5$

(c) By the linearity/proportionality property:  $\frac{V_s^{new}}{V_s^{old}} = \frac{I_s^{new}}{I_s^{old}}$  which implies  $\frac{2}{10} = \frac{I_s^{new}}{2}$  implies

$$I_s^{new} = 0.4 \text{ A.}$$

(d)  $P^{new} = V_s^{new} \times I_s^{new} = 2 \times 0.4 = 0.8$  watts. Observe that

$$\frac{P^{new}}{P^{old}} = \frac{0.8}{20} \quad \frac{V_s^{new}}{V_s^{old}} = \frac{2}{10}$$

It follows that the proportionality property does not hold for power calculations.

**Solution 5.2** First note that the ratio  $I_R/V_s$  is constant. With the given values of voltage and current, this ratio is:

$$I_R/V_s = 0.25/25 = 0.01$$

Power dissipated in the resistor is

$$P = I_R^2 R = 2.5 \rightarrow I_R^2 = 2.5/R = 0.25 \rightarrow I_R = 0.5$$

Since  $I_R$  is always  $0.01 \times V_s$ , it follows that  $V_s = 50$ V.

**Solution 5.3** Label the resistances  $R_1, R_2,$  and so on in the manner shown in Example 5.11. In this problem, we have  $R_1$  to  $R_{10}$  (the last being the 2 Ohm resistance at the voltage source). First, assume that  $V_1$  (the voltage across  $R_1$ ) is 1V. Then evaluate the rest of the currents and voltages until you deduce the

resulting  $V_s$ . It should be noted that the equivalent resistance looking into  $R_3, R_5, R_7,$  and  $R_9$  is always

2 .

$$V_1 = 1 \quad I_1 = \frac{V_1}{4} = 0.25 \quad I_2 = 0.25 \quad V_2 = I_2 \times 2 = 0.5 \text{ V}$$

$$V_3 = V_1 + V_2 = 1.5 \rightarrow I_3 = \frac{V_3}{3} = 0.5 \rightarrow I_4 = I_3 + I_2 = 0.75 \rightarrow V_4 = I_4 \times 4 = 3$$

$$V_5 = V_3 + V_4 = 4.5 \rightarrow I_5 = \frac{V_5}{3} = 1.5 \rightarrow I_6 = I_5 + I_4 = 2.25 \rightarrow V_6 = I_5 \times 4 = 9$$

$$V_7 = V_6 + V_5 = 13.5 \rightarrow I_7 = \frac{V_7}{3} = 4.5 \rightarrow I_8 = I_7 + I_6 = 6.75 \rightarrow V_8 = I_8 \times 4 = 27$$

$$V_9 = V_8 + V_7 = 40.5 \rightarrow I_9 = \frac{V_9}{3} = 13.5 \rightarrow I_{10} = I_9 + I_8 = 20.25 \rightarrow V_{10} = I_{10} \times 2 = 40.5$$

$$V_s = V_9 + V_{10} = 40.5 + 40.5 = 81 \text{ V}$$

Thus, an 81 V input produces a 1 V output  $\rightarrow V_{\text{out}} = (1/81) \times V_s = 2 \text{ V}$ .

**Solution 5.4** Label the resistances  $R_1$  to  $R_{10}$  progressively from right to left just like in the previous problem. Then, assume  $I_{\text{out}} = 1$  and proceed as follows:

$$I_{\text{out}} = 1 \rightarrow V_1 = I_{\text{out}} \times 4 = 4 \rightarrow I_2 = \frac{V_1}{4} = 1$$

$$I_3 = I_1 + I_2 = 2 \rightarrow V_3 = I_3 \times 4 = 8 \rightarrow V_4 = V_3 + V_1 = 12 \rightarrow I_4 = \frac{V_4}{3} = 4$$

$$I_5 = I_4 + I_3 = 6 \rightarrow V_5 = I_5 \times 4 = 24 \rightarrow V_6 = V_5 + V_4 = 36 \rightarrow I_6 = \frac{V_6}{3} = 12$$

$$I_7 = I_6 + I_5 = 18 \rightarrow V_7 = I_7 \times 4 = 72 \rightarrow V_8 = V_7 + V_6 = 108 \rightarrow I_8 = \frac{V_8}{3} = 36$$

$$I_9 = I_8 + I_7 = 54 \rightarrow V_9 = I_9 \times 4 = 216 \rightarrow V_{10} = V_9 + V_8 = 324 \rightarrow I_{10} = \frac{V_{10}}{3} = 108$$

$$I_s = I_{10} + I_9 = 162$$

$$\rightarrow I_{out}/I_s = 1/162 \rightarrow I_{out} = (1/162) \times 40.5 = 0.25A.$$

**Solution 5.5** (a) MATLAB code given in problem.

(b) Substitute to obtain  $V_1 = 10V$ .

(c)  $R_{eq} = V_s/I_s = 11.6667$  .


(d) First, define  $r1 = 1:0.25:10$ ;

then create an outermost loop around the code of part (a) as: `for j=1:length(r1)`

then, in the statement defining R, do `R = [R1(j), R2, R3, R4, R5, R6, R7, R8]'`;

Finally, replace the last statement with `Vs(j) = V(n) + V(n-1); end;`

The following is the resulting plot:

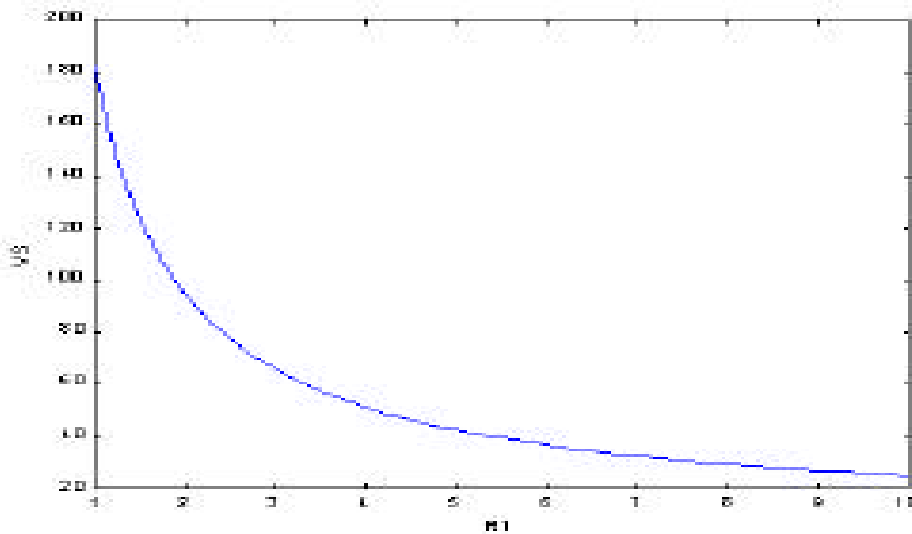

**Solution 5.6 (a)**

The following code can be used:

`n = 9;`

```

v = zeros(n,1);
i = zeros(n,1);
r = [r1 r2 r3 r4 r5 r6 r7 r8 r9]';
i(1) = 1;
v(1) = i(1)*r(1);
i(2) = i(1);
for k=2:2:n-2
    v(k) = r(k)*i(k);
    v(k+1) = v(k)+v(k-1);
    i(k+1) = v(k+1)/r(k+1);
    i(k+2) = i(k+1) + i(k);
end;
v(8) = i(8)*r(8);
v(9) = v(8) + v(7);
i(9) = v(9)/r(9);
Is = i(9) + i(8);

```

It follows that  $I_s = 16.9877A$ .

(b) By the proportionality property:  $\frac{I_1^{new}}{I_1^{old}} = \frac{I_s^{new}}{I_s^{old}}$   $I_1^{new} = \frac{1}{16.9877} \times 200mA = 11.77mA$

(c)  $R_{eq} = v(9)/I_s = 38.15 \text{ } .$

**Solution 5.7**  $V_a = 12V, i_b = 60m$


By inspection:

$$V_{out\_a} = 300/900 \times 12 = 4V$$

$$V_{out\_b} = (300||600) \times 60m = 12$$

–  $V_{\text{out}} = 4 + 12 = 16\text{V}.$

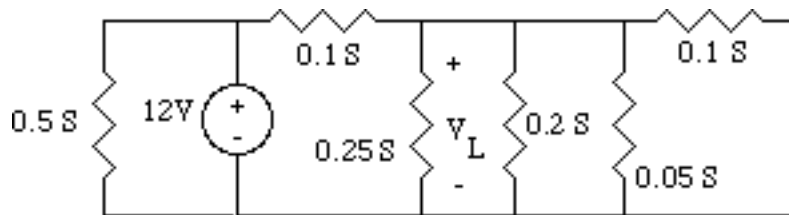
**\*SOLUTION 5.8. Part 1:** Set the 3 A current source to zero. This generates an open circuit in place of the current source eliminating the effect of the series 0.1 S resistor. The equivalent circuit is:



By voltage division,

$$V_L^{12V} = \frac{\frac{1}{0.25 + 0.2 + 0.05}}{\frac{1}{0.25 + 0.2 + 0.05} + \frac{1}{0.1}} \times 12 = \frac{2}{2 + 10} \times 12 = 2\text{ V}$$

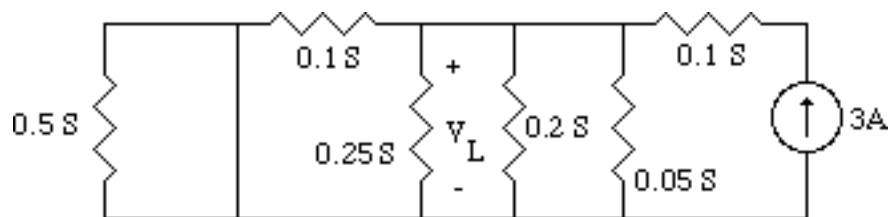**Part 2:** Set the 12 V source to zero. This generates a short circuit in place of the voltage source which shorts out the effect of the 0.5 S resistor. The equivalent circuit is:




Note that the 0.1 S resistor in series with the 3 A source is redundant to the calculation of VL. Hence, by Ohm's law,

$$V_L^{3A} = \frac{1}{0.25 + 0.2 + 0.05 + 0.1} \times 3 = \frac{3}{0.6} = 5\text{ V}$$

Therefore by superposition,

$$V_L = V_L^{12V} + V_L^{3A} = 2 + 5 = 7 \text{ V}$$

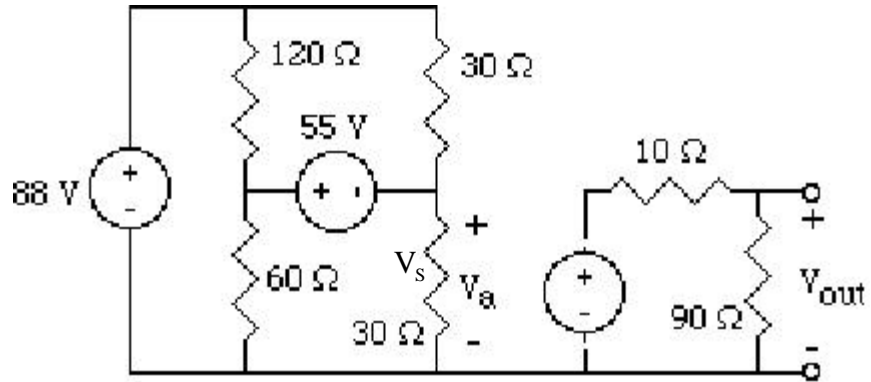**Solution 5.9** Replace the dependent source by an independent voltage source  $V_s$ :




In the following analysis, we have to always compute  $V_a$  because It defines the constraint on  $V_s$ . So, when only the 88V source is active,  $V_a$  is the result of voltage division between the  $60\parallel 30$  resistor and the  $120\parallel 30$  resistor. So,

$$V_{a_1} = 40\text{V}$$

And, since deactivated  $V_s$ ,  $V_{out_1} = 0$ .

Now, due to the 55V source, we have

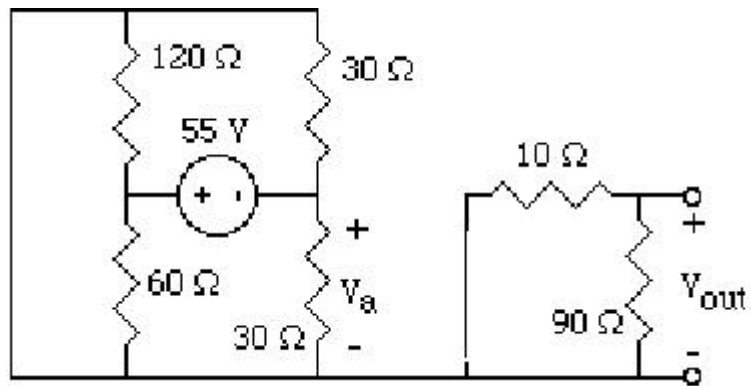

Now, the 120 and 60 resistors are in parallel, and the same can be said about the 30 and 30 resistors.

Thus, another voltage divider gives:

$$V_{a_2} = -15V \text{ and } V_{out_2} = 0V.$$

Finally, when  $V_{S1}$  is active, the left part of the circuit consists only of resistances, so  $V_{a_3} = 0$ .  $V_{out}$  is given by another divider formula:

$$V_{out_3} = 90/100 \times V_S$$

Now add all contributions:

$$V_a = 40 - 15 + 0 = 25V$$


$$V_{out} = 0 + 0 + 0.9V_S, \text{ where } V_S = 2V_a.$$

$$V_{out} = 0.9 \times 2 \times 25 = 45V.$$

Finally,  $P = V^2/R = 22.5W$ .


### Solution 5.10

Due to 3A source:

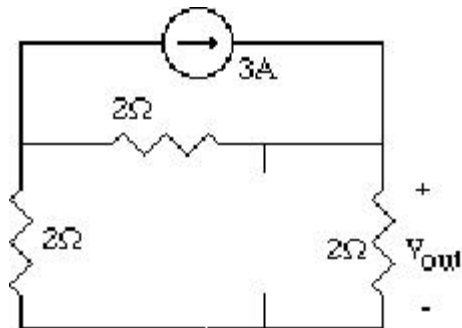


$i_{out} = 1A$  by current division between the two paths. So,  $v_{out_1} = 2V$ .

Due to 1A source:

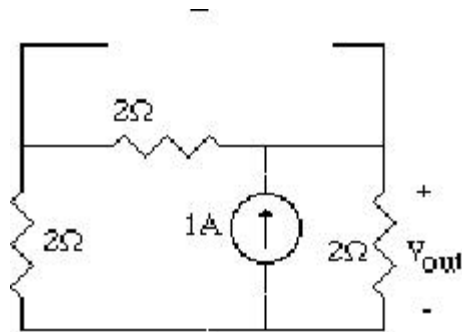

$i_{\text{out}} = 2/3\text{A}$  again by current division. So,  $v_{\text{out}_2} = 4/3\text{V}$ .

Due to 1V source:

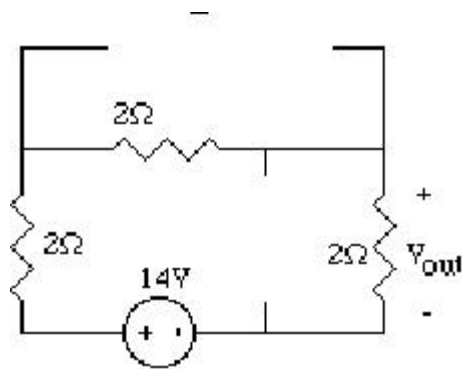


$i_{\text{out}} = 14/6 = 7/3\text{A}$  (by Ohm's Law). So,  $v_{\text{out}_3} = 14/3\text{V}$ .

Finally,  $v_{\text{out}} = 6/3 + 4/3 + 14/3 = 8\text{V}$ , and the power delivered by the source is  $8 \times 1 = 8\text{ W}$ .

### Solution 5.11


Due to 22 V source:

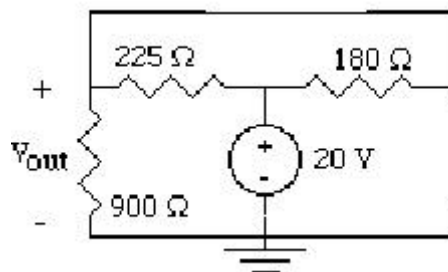

$R_{\text{eq}} = 900 \parallel 225 = 180$ . Now, by voltage divider:

$$V_{\text{out}_1} = 0.5 \times 22 = 11 \text{ V.}$$


Due to the 20 V source:

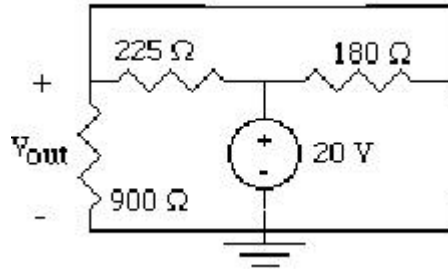

$R_{\text{eq}} = 180 \parallel 225 = 100$  . So, again, by voltage division:

$$V_{\text{out}_2} = 900 / (900 + 100) \times 20 = 18 \text{ V.}$$

Finally, due to current source:

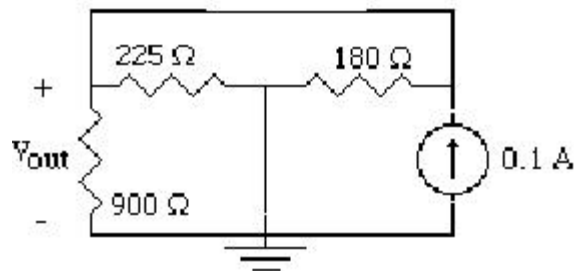


We have three resistances in parallel with a resistance equal to 90 . So,  $V_{\text{out}_3} = 0.1 \times 90 = 9 \text{ V.}$

$$V_{\text{out}} = 11 + 18 + 9 = 38 \text{ V and } P = 38 \times 38 / 900 = 1.6 \text{ W.}$$
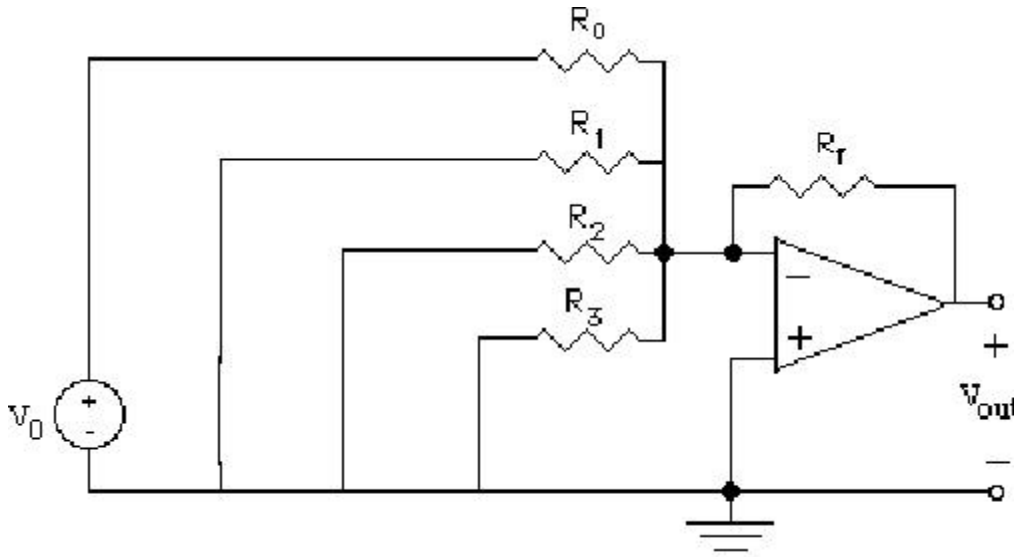
### Solution 5.12

Find contribution to  $V_{\text{out}}$  :



First, note that no current flows through  $R_1 - R_3$  because of the virtual ground property of the op-amp. Thus, this circuit is identical to the inverting amplifier studied in Chapter 4. So,


$$V_{out\_0} = -\frac{R_f}{R_0} V_0$$

Similarly, when each of the other sources is activated, the circuit will be an inverting amplifier. So,

$$V_{out\_1} = -\frac{R_f}{R_1} V_1, \quad V_{out\_2} = -\frac{R_f}{R_2} V_2, \quad V_{out\_3} = -\frac{R_f}{R_3} V_3$$

$$V_{out} = -R_f \left( \frac{V_0}{R_0} + \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

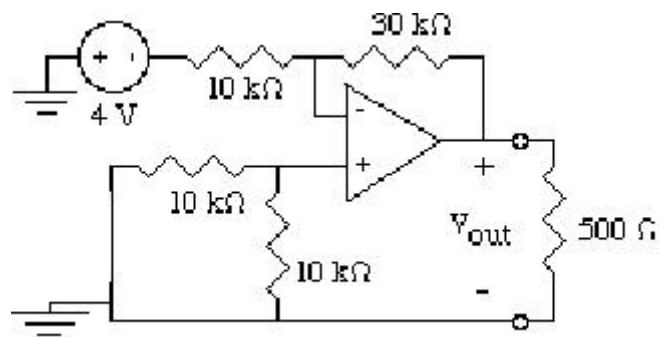
**Solution 5.13** Due to the 4 V source, the circuit looks like an inverting amplifier:



So,  $V_{\text{out}_1} = -30/10 \times (-4) = 12$  (from the results of Chapter 4).

Again, note here that no current flows through the two resistances connected to the + terminal of the op amp. Since no current flows through them, then no voltage develops across them. So, the + terminal can be assumed to be connected to ground, and this is why we say that the circuit looks like that of the inverting amplifier.

Now, due to the 6 V source:

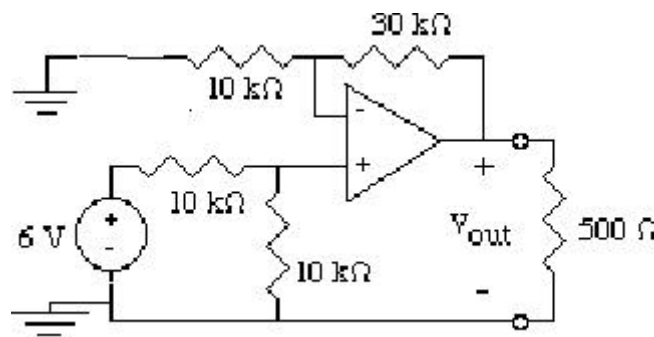

The voltage at the + terminal is established by a resistive divider between the two 10K resistors. So, this voltage is 3V. Thus, the voltage at the negative terminal is also 3V. We can now use KVL on the inverting side of the op-amp to get:

$$V_{\text{out}_2} = 3 + 30\text{k} \times 0.3\text{m} = 12\text{V}$$

So,  $V_{\text{out}} = 12 + 12 = 24\text{V}$ , and  $P = (24) \times (24) / 500 = 1.15\text{W}$ .

### Solution 5.14

(a) When  $V_{S2}$  is deactivated. The circuit looks like two inverting amplifiers in cascade.

Thus, by inspection,  $V_1 = -2V_{S1}$  and  $V_{\text{out}_1} = -3V_1 = 6V_{S1} = 3\text{V}$ .

(b) Similarly, when  $V_{S1}$  is zero,  $V_1$  is zero because the first inverting amplifier has zero input. Thus, the circuit consists just of the second inverting amplifier:

$$V_{out\_2} = -3/2V_{s2} = -4.5$$

(c)  $V_{out} = 3 - 4.5 = -1.5V.$

**\*SOLUTION 5.15.** For  $V_{s1}$  and  $V_{s2}$ , the situation reduces to the analysis of two inverting amplifiers in cascade. For  $V_{s3}$ , the situation is simply a single stage inverting amplifier. Note that because of the virtual ground at the inverting terminal of the op amp, when  $V_{s1}$  and  $V_{s2}$  are zero, they have no contribution to the input of the second stage.

(a) With  $V_{s2}$  and  $V_{s3}$  set to zero,

$$V_{out}^{s1} = \frac{-R}{R} \frac{-2R}{2R} V_{s1} = V_{s1} = 5 \text{ V}$$

(b) With  $V_{s1}$  and  $V_{s3}$  set to zero,

$$V_{out}^{s2} = \frac{-R}{R} \frac{-2R}{R} V_{s2} = 2V_{s2} = 2 \times (-2.5) = -5 \text{ V}$$

(c) With  $V_{s1}$  and  $V_{s2}$  set to zero,

$$V_{out}^{s3} = \frac{-R}{R} V_{s3} = -V_{s3} = -2 \text{ V}$$

(d) By superposition,

$$V_{out} = V_{out}^{s1} + V_{out}^{s2} + V_{out}^{s3} = -2 \text{ V}$$

### Solution 5.16

If the op-amp were ideal, we would get:

$$V_{out} = -4V_{s1} - 2V_{s2} = -26$$

This is clearly beyond the linear range of operation of the op-amp. In other words, the amplifier responds in a non-linear manner to this level of input. Hence, superposition, which relies on linearity, cannot be used.

**Solution 5.17**

We know by linearity that

$$V_{\text{out}} = aI_{s1} + bV_{s2}$$

Substitute the first measurement to obtain:

$$5 = 0 + b \times 10 \rightarrow b = 0.5$$

Now, take the second measurement:

$$1 = a \times 10 + 0 \rightarrow a = 0.1$$

So,

$$V_{\text{out}} = 0.1I_{s1} + 0.5V_{s2}$$

At 20A, 20V:  $V_{\text{out}} = 12\text{V}$

**Solution 5.18**

Again  $V_{\text{out}} = aI_{s1} + bV_{s2}$

Substitute the two measurements to obtain:

$$5a + 10b = 15$$

$$2a + 5b = 10$$

These two simultaneous equations in a and b can easily be solved to obtain:

$$a = -5 \quad \text{and} \quad b = 4$$

Therefore, at 1A and 5V,

$$V_{\text{out}} = -5 + 20 = 15\text{V}$$

**Solution 5.19 (a)**

Again,

$$V_{\text{out}} = aI_{s1} + bV_{s2}$$

Substituting the result of the first measurement into this equation yields:

$$a \times 4 \times \cos(2t) + 0 = -2\cos(2t) \rightarrow a = -0.5$$

Now, substitute the second measurement:

$$0 + 10b = 55 \rightarrow b = 5.5$$

Therefore, for the given input current and voltage:

$$V_{\text{out}} = -\cos(2t) - 55\cos(2t) = -56\cos(2t) \text{ V}$$

(b) 
$$V_{\text{out}} = 2\cos(5t) + 110\cos(5t) = 112\cos(5t) \text{ V}$$

### **Solution 5.20 (a)**

First of all,

$$I_{\text{load}} = aV_a + bI_b$$

Now, substitute the two measurements into this equation:

$$7a + 3b = 1$$

$$9a + b = 3$$

Solving these two equations for the unknowns a and b, we get

$$a = 0.4 \quad \text{and} \quad b = -0.6$$

(b) 
$$I_{\text{load}} = 0.4 \times 15 - 0.6 \times 9 = 0.6 \text{ A}$$

### **Solution 5.21 (a)**

We know that the output is going to be a linear combination of the three inputs:

$$V_{\text{out}} = aI_{s1} + bV_{s2} + cV_{s3}$$

Now, substitute the three measurements into this relationship:

$$50ma - 2b + 5c = -13$$

$$0 + 3b + 5c = 2$$

$$0 + 2b + 4c = 0$$

These equations can be written in matrix form and solved as follows:

$$\begin{array}{cccccc} 0.05 & -2 & 5 & a & -13 & a & 100 \\ 0 & 3 & 5 & b & = & 2 & b = 4 \\ 0 & 2 & 4 & c & 0 & c & -2 \end{array}$$

(b) Substitute the given values of the input sources to obtain:

$$V_{\text{out}} = 100 \times 1 - 4 \times 40 + 2 \times 10 = -40\text{V}$$

### Solution 5.22

$$V_{\text{out}} = AI_{s1} + BV_{s2} + CV_{s3}$$

Substituting the measurements into this equation results in a system of three equations and three unknowns. This system can be written in matrix form by inspection:

$$\begin{array}{cccccc} 30 \times 10^{-3} & 2 & -1 & A & 11.5 & A & 150 \\ -20 \times 10^{-3} & 4 & 2 & B & = & 27 & B = 5.5 \\ -10 \times 10^{-3} & -3 & 1 & C & -14 & C & 4 \end{array}$$

This can be solved to obtain:

### Solution 5.23 (a)

The coefficient matrix is inverted, and both sides of the nodal equation are multiplied by it to obtain:

$$\begin{array}{l} V_a \\ V_b \end{array} = \begin{array}{ccc} 43.0108 & 0.233 & 0.02V_{s1} - 0.00125V_{s2} \\ 43.0108 & -1.4337 & V_{s2} \end{array}$$

Expanding the first row of the above equation gives:

$$V_a = 0.8602V_{s1} - 0.0538V_{s2} + 0.233V_{s2}$$

This is exactly in the form required, where  $A = 0.8602$  and  $B = 0.1792$

(b) For this part, we expand the second row of the equation:

$$V_b = 0.8602V_{s1} - 0.0538V_{s2} - 1.4337V_{s2}$$

Again, this is in the desired form, where  $A = 0.8602$  and  $B = -1.4875$

(c)  $V_{ab} = V_a - V_b = 0 + 1.667 V_{s2}$

Thus,  $A = 0$  and  $B = 1.667$

**Solution 5.24 (a)**

Again, we invert the coefficient matrix to obtain

$I_1$	0.0022	0.0022	0.0022	0.6296	-0.0741	$V_{s1}$
$I_2$	0.0022	0.0022	0.0022	-0.7037	0.2593	0
$I_3 =$	0.0022	0.0022	0.0022	-0.3704	-0.0741	0
$v_1$	-0.2222	0.7778	-0.2222	137.037	-92.5926	$I_{s2}$
$v_2$	-0.3333	-0.3333	0.6667	-11.1111	77.7778	0

Expanding the first row of this equation:

$$I_1 = 0.0022V_{s1} + 0.6296I_{s2}$$

So,  $A = 0.0022$ ,  $B = 0.6296$

(b) Similarly, expanding the third row:

$$I_3 = 0.0022V_{s1} + -0.3704I_{s2}$$

So,  $A = 0.0022$ ,  $B = -0.3704$

(c) By the same procedure,  $A = -0.3333$  and  $B = -11.1111$

**Solution 5.25**


Invert the coefficient matrix and multiply both sides of the equation in the problem by this inverse matrix to obtain

$$\begin{array}{rcccccccc}
 V_1 & 0 & 0 & 0 & -3 & 2 & -1 & -4 & I_{s1} \\
 V_2 & 0 & 0 & 0 & -3 & 1 & -1 & -4 & 0 \\
 V_3 & 0 & 0 & 0 & 12 & -3 & 3 & 16 & 0 \\
 I_a = & 0 & 0 & 0 & -4 & 1 & -1 & -5 & 0 \\
 I_b & 0 & -1 & 0 & -16.6 & 9.2 & -5.2 & -21.8 & V_{s2} \\
 I_c & 1 & 1 & 0 & -42.1 & -16.2 & 11.7 & 53.8 & 0 \\
 I_d & 1 & 1 & 1 & 26.1 & -12.2 & 7.7 & 32.8 & 0
 \end{array}$$

The second to last row can be expanded to get  $I_c = I_{s1} - 16.2V_{s2} \rightarrow A = 1, B = -16.2$
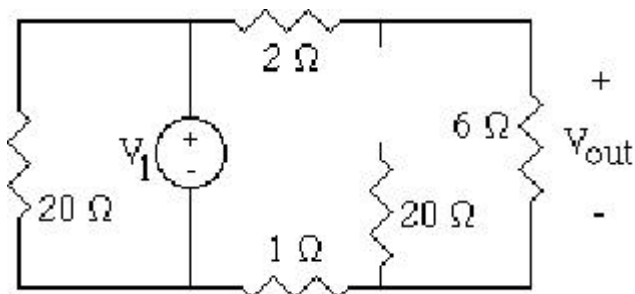
### Solution 3.26 (a)


First compute the response due to  $V_1$ :



By voltage divider:

$$V_{out_1} = 6/(2+6+1) \times V_1 = 2/3 V_1$$

Then, due to  $I_2$ :

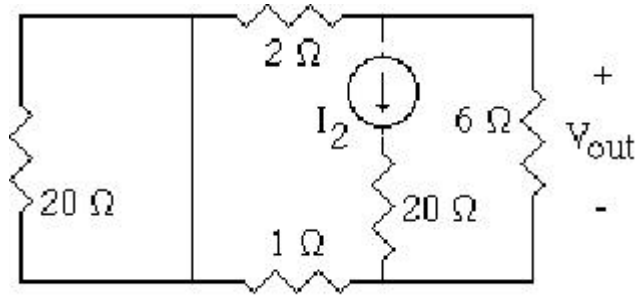

$I_2$  flows through the 20 ohm resistor in series with  $6 \parallel 20$ . Thus,


$$V_{out_2} = -2I_2$$

Therefore,  $V_{out} = 2/3V_1 - 2I_2$

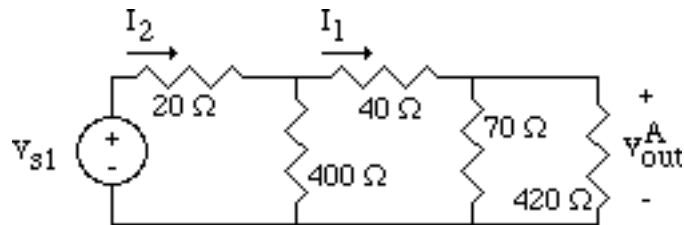(b)  $V_{out} = 8\cos(10t) - 4$

**\*SOLUTION 5.27.** (a) By linearity  $V_{out} = A V_{s1} + B I_{s2}$ .

To find A, let  $I_{s2} = 0$ . The circuit becomes a ladder network as follows.



Let  $V_{out}^A = 1$  V. Then

$$\gg I_1 = 1/420 + 1/70$$

$$I_1 = 1.6667e-02$$

$$\gg V_{400} = I_1 \cdot 40 + 1$$

$$V_{400} = 1.6667e+00$$

$$\gg I_{400} = V_{400}/400$$

$$I_{400} = 4.1667e-03$$

$$\gg I_2 = I_1 + I_{400}$$

$$I_2 = 2.0833e-02$$


$$\gg V_{s1} = I_2 * 20 + V_{400}$$

$$V_{s1} = 2.0833e+00$$

$$\gg A = 1/V_{s1}$$

$$A = 4.8000e-01$$

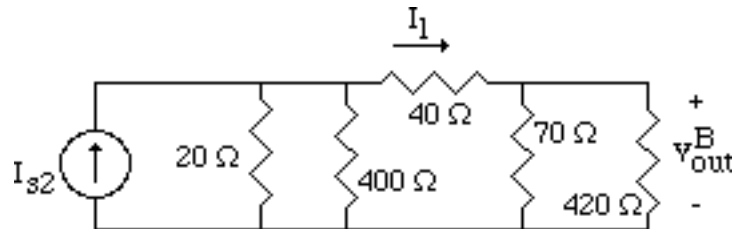To find B, let  $V_{s1} = 0$ . The circuit becomes a ladder network as follows.



Again assume that  $V_{out}^B = 1$  V. Then

$$\gg I_1 = 1/420 + 1/70$$

$$I_1 = 1.6667e-02$$

$$\gg V_{400} = I_1 * 40 + 1$$

$$V_{400} = 1.6667e+00$$

$$\gg I_{400} = V_{400}/400$$

$$I_{400} = 4.1667e-03$$

$$\gg I_{20} = V_{400}/20$$

$$I_{20} = 8.3333e-02$$

$$\gg I_{s2} = I_{20} + I_{400} + I_1$$

$$I_{s2} = 1.0417e-01$$

$$\gg B = 1/I_{s2}$$

$$B = 9.6000e+00$$

Hence by linearity  $V_{out} = 0.48 V_{s1} + 9.6 I_{s2}$ .

(b)

$$\gg V_{out} = A * 20 + B * 0.5$$


$$V_{out} = 1.4400e+01$$

(c) Doubling resistances does not change voltage ratios hence A is the same. However, the doubling also doubles the voltage to current ratio. Hence, B is doubled. It follows that if all resistances are doubled, then

$$V_{out} = 0.48 V_{s1} + 19.2 I_{s2}$$

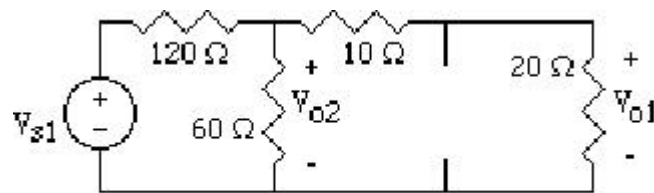**Solution 5.28 (a) (b)**

We solve parts (a) and (b) at the same time. First, we find the responses to  $V_{s1}$ :




Equivalent resistance across  $V_{o2}$ :  $60\parallel 30 = 20$

Now, by voltage divider:  $V_{o2_1} = 20/140V_{s1}$

This voltage now divides between  $V_{o1}$  and the 10 ohm resistance:

$$V_{o1_1} = 20/30V_{o2_1} = 2/3 \times 1/7V_{s1} = 2/21V_{s1}$$

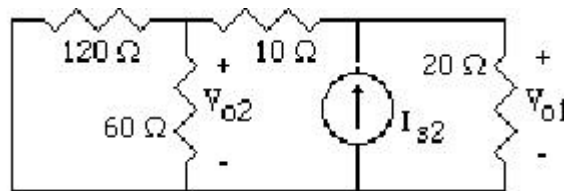Now, compute the responses due to  $I_{s2}$ :



Equivalent resistance across  $V_{o2}$ :  $60\parallel 120 = 40$

By voltage division:  $V_{o2_2} = 40/50V_{o1_2}$

Where  $V_{o1_2} = I_{s2} \times (50\parallel 20) = 14.286I_{s2}$


Now, add the contributions:

$$V_{o1} = 0.0952V_{s1} + 14.286I_{s2}$$

$$V_{o2} = 0.1429V_{s1} + 11.4288I_{s2}$$

**Solution 5.29 (a)**


Find contribution due to  $v_1$ :

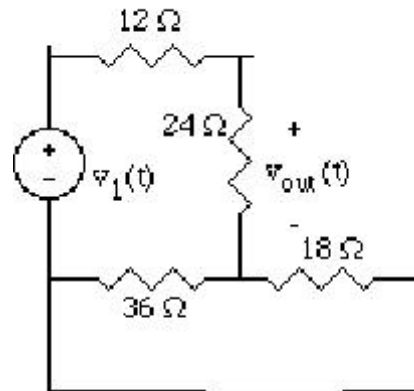

The parallel combination results in a 12 ohm resistance in series with the remaining two. Thus, by voltage division:

$$v_{out1} = 24/48v_1 = 0.5v_1$$

Now, due to  $v_2$

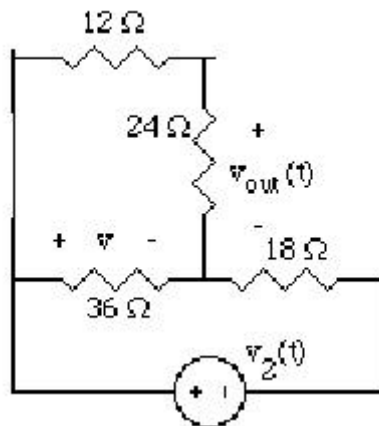


The equivalent resistance across  $v$  in this figure is  $36 \parallel (24+12) = 18$ , which means that by voltage divider:

$$v = 0.5v_2$$

Similarly, by another voltage division application

$$v_{out2} = 24 / 36 \times v = 0.66 \times 0.5v_2 = 0.333v_2$$


Now, due to  $i_3$

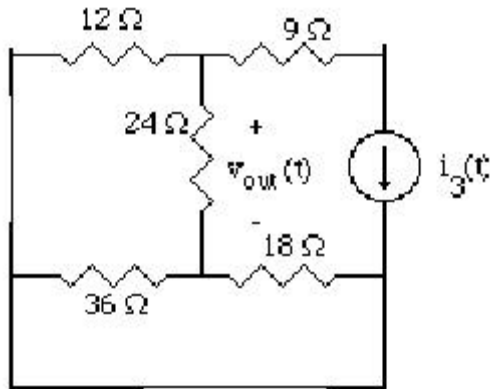

Define  $R_{eq1} = 24 + 36 \parallel 18 = 36 \Omega$ . This resistance is in parallel with the 12 ohm resistance to introduce an equivalent of  $9 \Omega$ . The total voltage that develops across this 9 ohm resistance is  $-9i_{s3}$ . This voltage divides between  $v_{out}$  and the  $36 \parallel 18$  resistance:

$$v_{out3} = \frac{24}{36} v_1 = -9 \times \frac{24}{36} i_{s3} = -6i_{s3}$$

Finally, due to  $i_4$ :

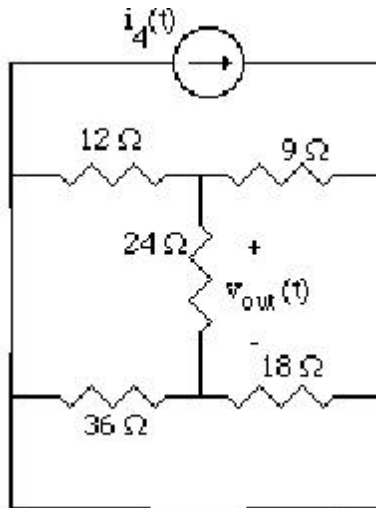

A similar analysis of this resistive network can reveal that  $v_{out4} = 6i_{s4}$ . Thus

$$v_{out} = 0.5v_1 + 0.333v_2 - 6i_{s3} + 6i_{s4}$$

(b) For this part, note that scaling resistance values does not affect voltage ratios. This can be evident from the application of any voltage divider formula. On the other hand, scaling resistances does affect current-

to-voltage or voltage-to-current ratios. This is by definition of a resistance! So, in the above equation, doubling the resistances does not affect the first two terms, but doubles the second two terms.

**Solution 5.30 (a)**

Define two clockwise mesh currents:  $I_1$  in the bottom left loop and  $I_2$  in the top loop. The bottom right loop has a current source, so it will not be considered:

$$V_a - (I_1 - I_2)3 - I_2 - (I_1 - i_b) = 0$$

and

$$6I_2 - I_2 + (I_2 - I_1)3 = 0$$

Solving these two equations for the two currents gives:

$$I_1 = 8 \text{ A} \quad \text{and} \quad I_2 = 3 \text{ A}$$

The power delivered by the dependent source is:  $P = i_x \times I_{ix}$  where  $I_{ix}$  is the current leaving the '+' terminal of the dependent voltage:  $P = i_x \times (I_2 - I_1) = I_2 \times (I_2 - I_1) = -15\text{W}$

$$\rightarrow v_{out} = I_1 + i_b = 8 + 26 = 34\text{V}$$

(b) Now, we express  $v_{out} = Av_a + Bi_b$

Turning off  $i_b$ , we still have two loops, in which we can define the same mesh currents as above to obtain:


$$v_a - 3(I_1 - I_2) - I_2 - I_1 = 0$$

$$I_2 - 3(I_2 - I_1) - 6I_2 = 0$$

Solving for the two currents, we get  $I_1 = 4/13v_a$  which sets up  $v_{out}$  across the 1 ohm resistor:

$$V_{out1} = 4/13v_a$$

Now, turn off the voltage source:

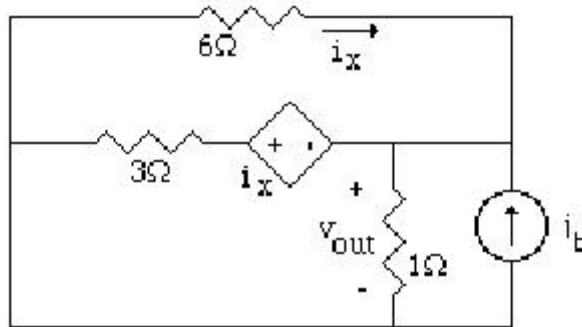

Write a node equation at  $v_{out}$ :


$$\frac{v_{out}}{6} + \frac{v_{out}}{1} + \frac{v_{out} - v_{out}/6}{3} - i_b = 0$$

$$? \quad v_{out} = \frac{9}{13} i_b$$



So,  $v_{out} = 4/13 v_a + 9/13 i_b$

(c) Substitute into the above equation:  $v_{out} = 35V$

**Solution 5.31** By inspection:

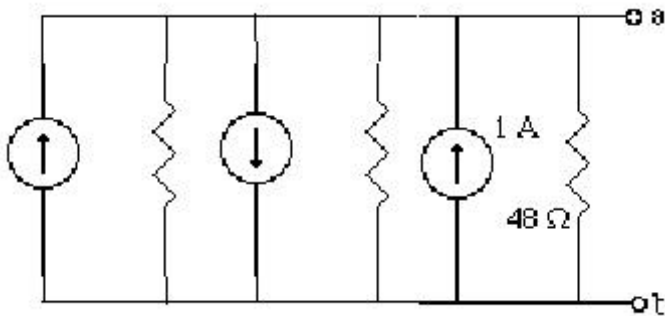


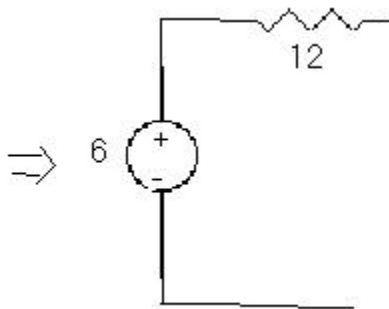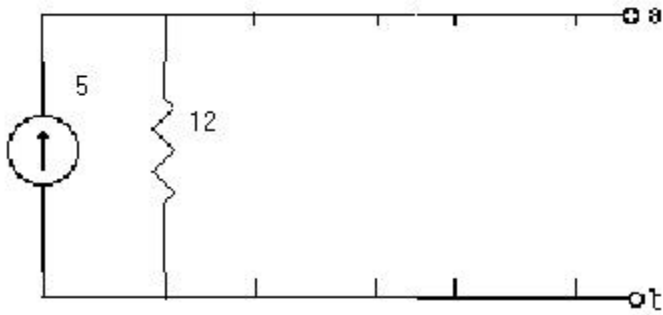where the leftmost current is 0.25 with a resistance of 32 . Similarly, the downward current is 0.75 and its resistance is 32 . This reduces to:


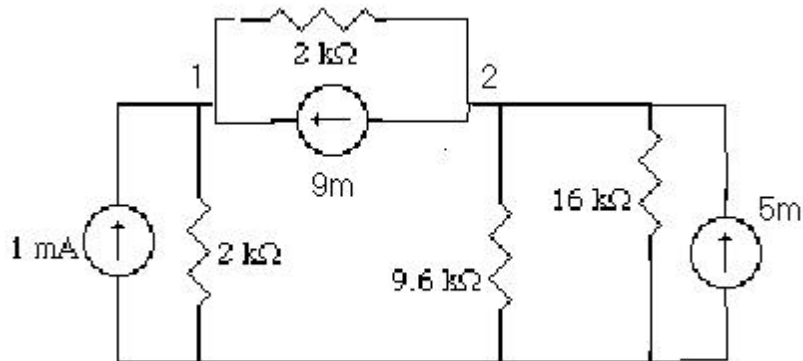
### Solution 5.32

The circuit can be transformed as follows:



Write two nodal equations at 1 and 2:

$$-1m + \frac{v_1}{2k} - 9m + \frac{v_1 - v_2}{2k} = 0$$

$$\frac{v_2 - v_1}{2k} + 9m + \frac{v_2}{9.6k} + \frac{v_2}{16k} - 5m = 0$$


These two equations can be solved using any method to obtain:

$$v_1 = 11.2\text{V} \quad \text{and} \quad v_2 = 2.4\text{V}$$


The power absorbed by the  $9.6\text{k}\Omega$  resistor is:


$$P = \frac{V_2^2}{9.6 \times 10^3} = 0.6\text{mW}$$

**Solution 5.33**

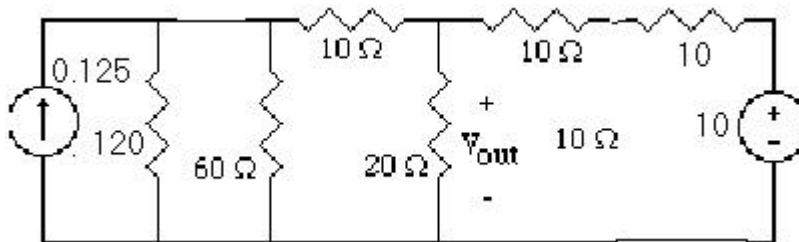

Then

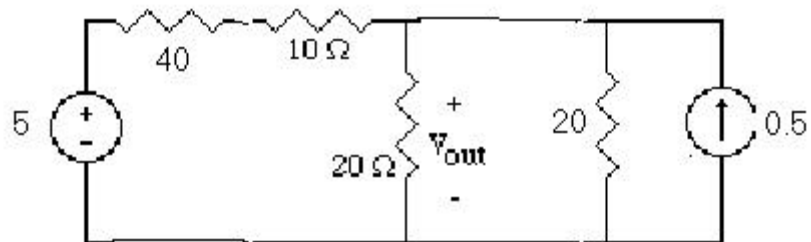

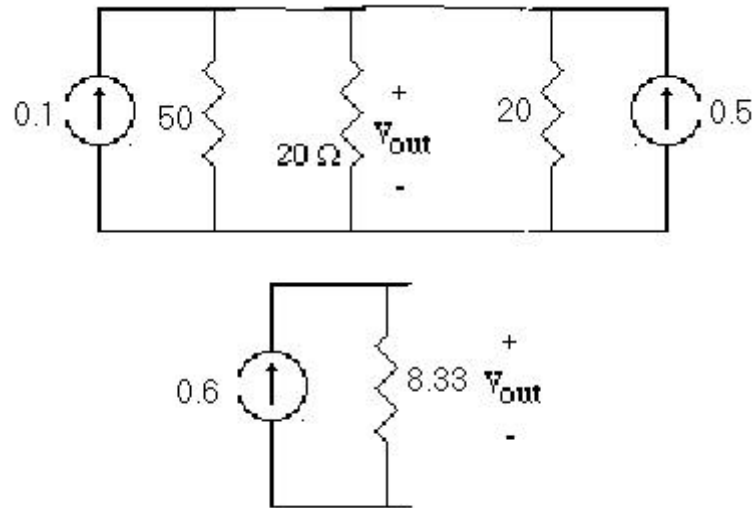




Output voltage is 5V

(b)  $P = 1.25\text{W}$

(c) For a given resistance, doubling the voltage increases the current by two times. So, the current is doubled. It follows that  $V_{\text{out}}^{\text{new}} = 2 \times V_{\text{out}}^{\text{old}} = 10\text{V}$


**Solution 5.34**

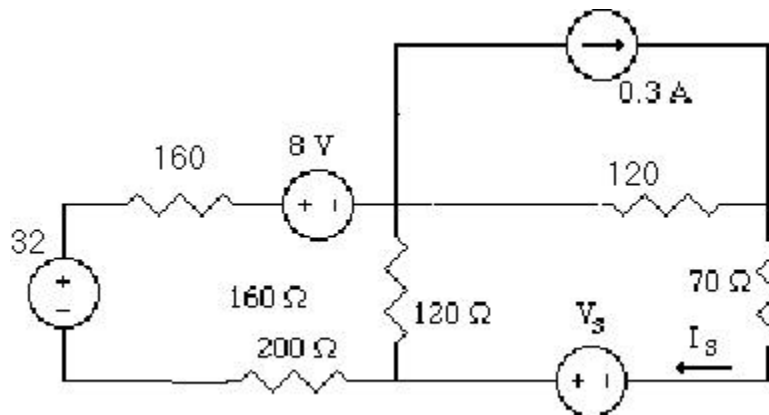

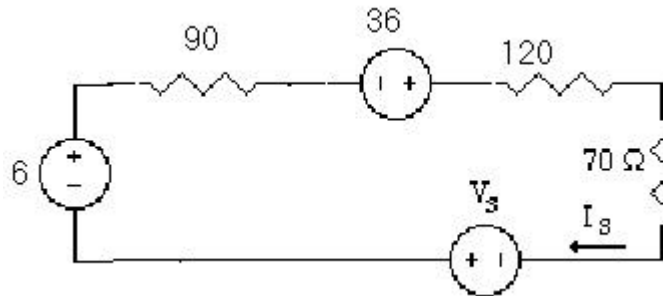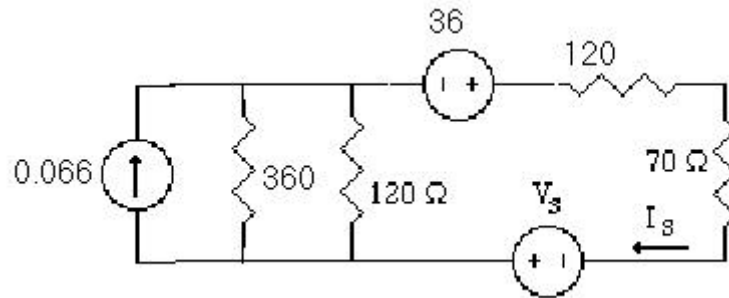

This circuit is easy enough to solve by inspection.  $V_s = 28\text{V}$ .

### Solution 5.35

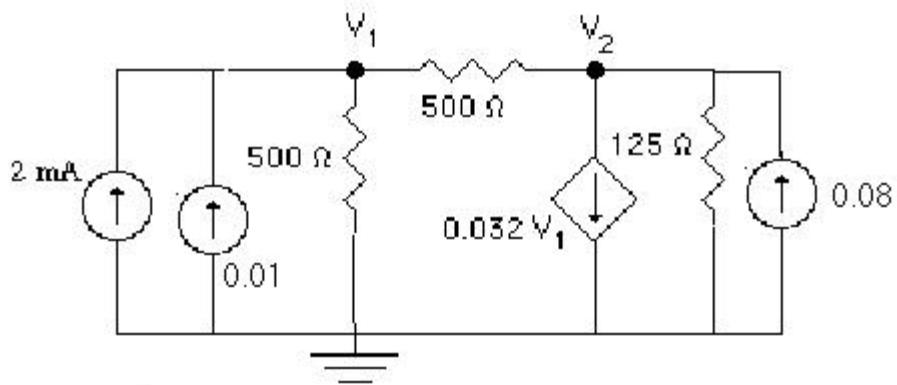


Now, write two node equations:

$$\frac{v_1}{500} - \frac{v_2}{500} + \frac{v_1}{500} = 12\text{m}$$

$$\frac{v_2}{500} - \frac{v_1}{500} + 0.032v_1 + \frac{v_2}{125} = 80\text{m}$$

These two equations can be solved to get  $v_1 = 2.8\text{V}$ ,  $v_2 = -0.4\text{V}$ .

Solution 5.36

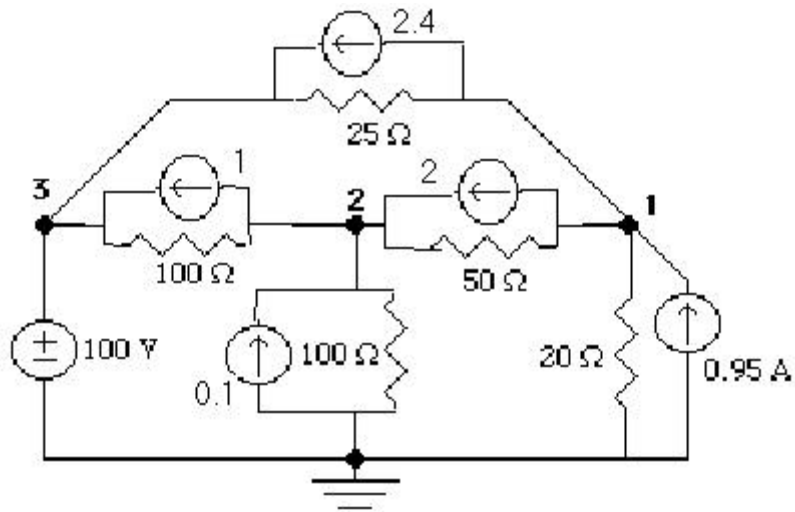

Now, we can write the node equations:


$$\frac{v_1}{50} - \frac{v_2}{50} + \frac{v_1}{25} - \frac{100}{25} + 0.2 + 0.4 + \frac{v_1}{20} - 0.95 = 0$$

$$\frac{v_2}{100} - \frac{100}{100} + \frac{v_2}{50} - \frac{v_1}{50} + \frac{v_2}{100} + 1 - 0.1 - 0.2 = 0$$


Solving these two equations yields:

$$v_1 = 25V \quad \text{and} \quad v_2 = 20V$$

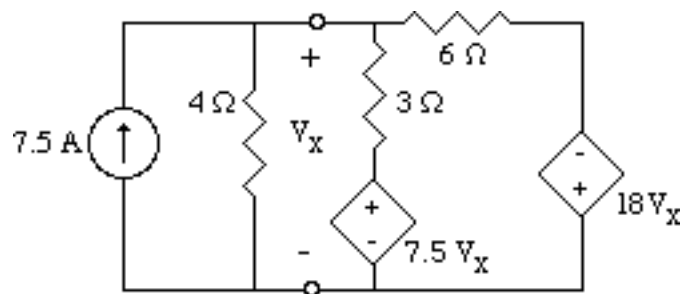**\*SOLUTION 5.37.** After a source transformation on the 30 V independent source and one on the  $9V_x$  dependent source we obtain the circuit below.



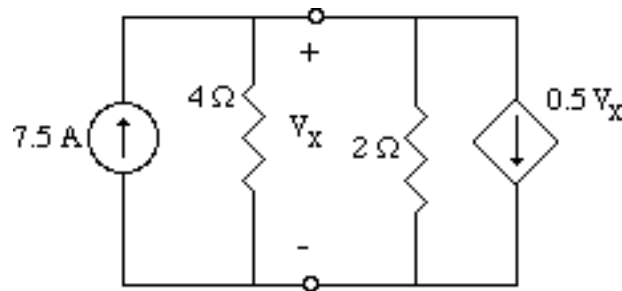Transforming the two dependent voltage sources and combining yields the following circuit.




Writing a single node equation for  $V_x$  yields

$$7.5 = \frac{V_x}{4} + \frac{V_x}{2} + \frac{V_x}{2} = 1.25V_x$$

Hence,  $V_x = 6 \text{ V}$ .
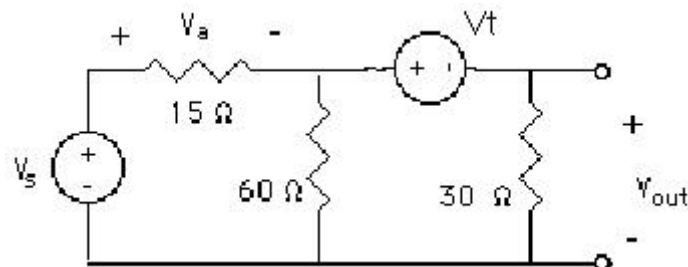
### Solution 5.38

Replace the dependent source with a temporary independent source. When doing the analysis, always compute  $V_a$  in order to keep track of the constraint on the dependent source.



When  $V_t$  is not active,  $v_{out1}$  is obtained from a voltage divider between the  $60\parallel 30$  combination and the 15 ohm resistor:

$$v_{out1} = 4/7V_s$$

Similarly  $v_{a1} = 3/7V_s$

Now, compute the response due to the temporary source.

Straightforward voltage division also applies here to get:

$$v_{a2} = -2/7Vt$$

and  $v_{out2} = -5/7Vt$

So,  $v_{out} = 4/7V_s - 5/7Vt$

$$v_a = 3/7V_s - 2/7Vt, \quad \text{where } Vt = \mu v_a \rightarrow v_a = 3/7V_s - 2\mu/7v_a$$

Rearranging,


$$v_a = \frac{3}{7 + 2\mu} V_s$$

Then,

$$v_{out} = \frac{4}{7} V_s - \frac{5\mu}{7} v_a$$

$$v_{out} = \frac{4 - \mu}{7 + 2\mu} V_s$$

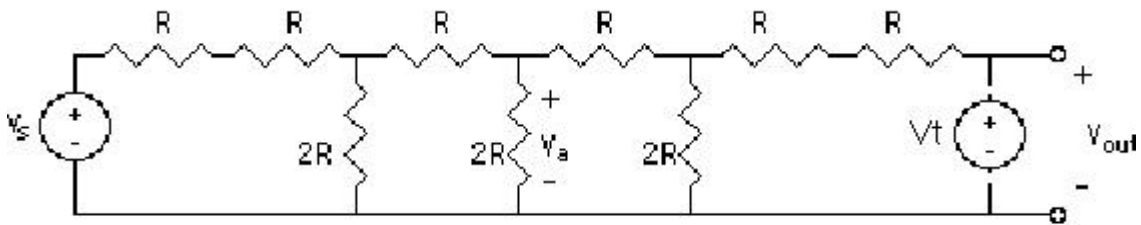**Solution 5.39** Replace the dependent source by a temporary independent source:



When  $Vt$  is shorted, the result is a ladder network. The input resistance looking each of the vertical branches is  $R$ . Label these vertical branches  $V_1, V_a, V_2$  from left to right. It follows that

$$V_1 = R/3RV_s$$

$$- \quad V_{a_1} = R/2R \times R/3RV_s = 1/6V_s$$

Also,  $V_{out_1} = 0$

Now, short  $V_s$  and turn on  $Vt$ .

Again, the result is a ladder network (note the symmetry in the above figure). Thus, we can write by inspection:

$$V_{a_2} = 1/6V_t$$

$$V_{out_2} = V_t$$

Adding the contributions:

$$V_{out} = 0 + V_t = V_t = \mu V_a \quad \text{where we have substituted the constraint on } V_t$$

and 
$$V_a = 1/6V_s + 1/6V_t = 1/6V_s + 1/6 \mu V_a$$


$$\rightarrow V_a = [1/(6 - \mu)]V_s$$

Substitute this  $V_a$  into the expression for  $V_{out}$ :

$$V_{out} = \frac{\mu}{6 - \mu} V_s$$
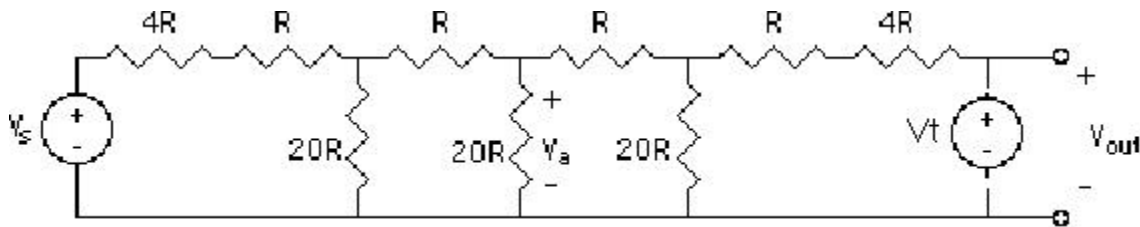
### Solution 5.40

The first step is to replace the dependent source with a temporary independent source. Then, superposition can proceed as usual.



Now, let's short the temporary source,  $V_t$ . Again, this network is a ladder network, like the one in the previous problem. However, now, the equivalent resistance looking into each of the vertical branches (from left to right) is different. Now, it is

$$R_{eq} = 20R || (R + 4R) = 20R \times 5R / 25R = 4R$$

Now, again, define the voltages across these three vertical branches (from left to right) as  $V_1, V_a, V_2$ . It follows by voltage division that

$$V_1 = 4/9 V_s$$

$$\rightarrow V_{a_1} = 4/5 \times 4/9 \times V_s$$

$$\rightarrow V_{a_1} = 16/45 V_s$$

It should be noted that  $V_{out} = 0$ .

Now, short the input source and find the response due to  $V_t$ . Again, in this case, the circuit is identical to the case when  $V_s$  was active (note the symmetry in the above figure). Therefore,

$$V_{a_2} = 16/45 V_t$$

$$V_{out_2} = V_t$$

Adding the two contributions:

$$V_a = \frac{16}{45} V_s + \frac{16}{45} \mu V_a$$

$$? V_a = \frac{1}{\left(\frac{45}{16} - \mu\right)} V_s$$


$$V_{out} = V_t = \mu V_a$$

and


$$V_{out} = \frac{16\mu}{45 - 16\mu} V_s$$
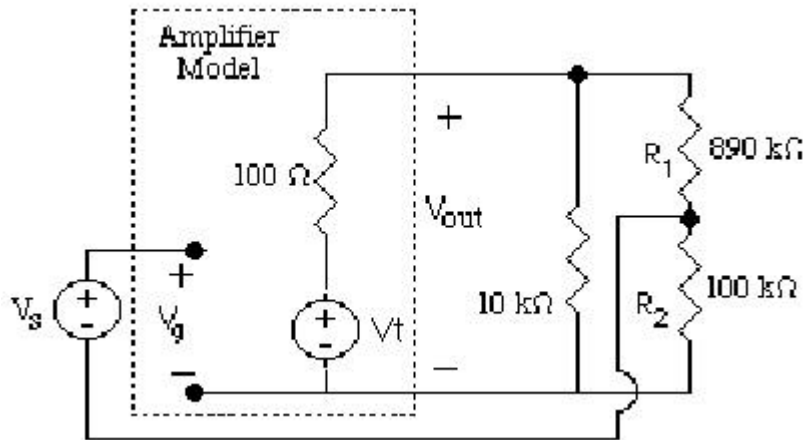
### Solution 5.41

First, replace the controlled source by a temporary independent source:



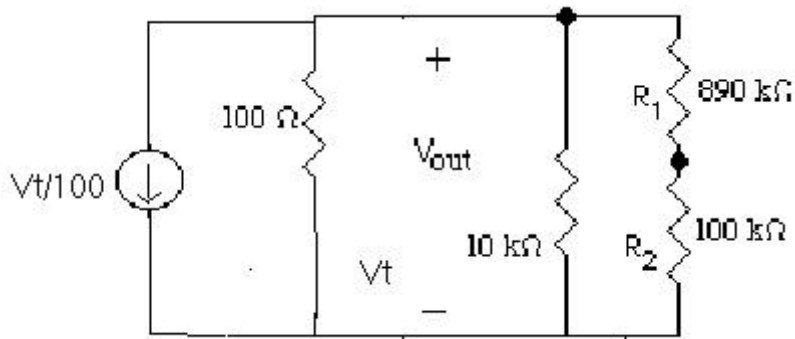Now, do a source transformation on the  $V_t$  source:



The equivalent resistance seen by the current source is  $99 \text{ k}\Omega$ . Therefore:

$$V_{\text{out}} = -99/100V_t = -0.99V_t$$

Now,  $V_t = \mu V_g$  and  $I_L = -0.99V_t/990\text{k}$  where  $I_L$  is the current through  $R_2$

$$\rightarrow V_{R_2} = I_L R_2 = (100\text{k}/990\text{k}) \times (-0.99V_t) = -0.1V_t$$

By KVL

$$V_g = V_{R_2} + V_s = -0.1V_t + V_s = -0.1\mu V_g + V_s$$

Rearranging

$$V_g = \frac{1}{0.1\mu + 1} V_s$$

Finally, and substituting:

$$\frac{V_{out}}{V_s} = -0.99\mu \frac{1}{1+0.1\mu}$$

$$\frac{V_{out}}{V_s} = -8.91$$

Solution 5.42

$$\frac{V_{out}}{V_{in}} = \frac{b_0 + b_1x}{a_0 + a_1x} = \frac{b_0 + b_1R}{1 + a_1R}$$

At  $R = 0$

$$\frac{V_{out}}{V_{in}} = \frac{b_0}{1} = 20$$

$$? \quad b_0 = 20$$

At infinite  $R$

$$\frac{V_{out}}{V_{in}} = \frac{b_1}{a_1} = 8$$

$$? \quad b_1 = 8a_1$$

Finally, at  $R = 10$

$$\frac{20 + 80a_1}{1 + 10a_1} = 10$$

$$? \quad a_1 = 0.5$$

$$? \quad b_1 = 4$$

Substituting these values for  $R = 2$  yields

$$\frac{V_{out}}{V_{in}} = \frac{20 + 4}{1 + 0.5} \frac{2}{2} = 14$$

**SOLUTION 5.43.** From the chapter

$$\frac{V_{out}}{V_{in}} = \frac{b_0 + b_1\mu}{a_0 + a_1\mu} = \frac{b_0 + b_1\mu}{1 + a_1\mu}$$

Equivalently,

$$-\mu \frac{V_{out}}{V_{in}} a_1 + b_0 + \mu b_1 = \frac{V_{out}}{V_{in}}$$

Plugging in the data yields three equations in three unknowns which in matrix form are:

$$\begin{array}{cccccc} 0 & 1 & 0 & a_1 & 264 & \\ -154 & 1 & 1 & b_0 & = & 154 \\ -168 & 1 & 2 & b_1 & & 84 \end{array}$$

»A=[0 1 0;-154 1 1;-168 1 2]

A =

$$\begin{array}{ccc} 0 & 1 & 0 \\ -154 & 1 & 1 \\ -168 & 1 & 2 \end{array}$$

»y = [264 154 84]'

y =

$$\begin{array}{c} 264 \\ 154 \\ 84 \end{array}$$

»Coefs = A\y

Coefs =

$$\begin{array}{c} 2.8571e-01 \\ 2.6400e+02 \\ -6.6000e+01 \end{array}$$

Therefore,  $a_1 = 0.28571$ ,  $b_0 = 264$ , and  $b_1 = -66$ . Making  $a_1 = 1$ , will yield a different set of answers.

When  $m = \mu$ ,  $V_{out}/V_{in} = b_1/a_1 = -231$ .