

## PROBLEM SOLUTIONS CHAPTER 14

### SOLUTION 14.1.

(a)

$$Z(s) = \frac{R(Ls + \frac{1}{Cs})}{R + Ls + \frac{1}{Cs}} = \frac{Cs(RLCs^2 + R)}{Cs(RCs + LCs^2 + 1)} = \frac{RLC(s^2 + 1/LC)}{LC(s^2 + \frac{R}{L}s + \frac{1}{LC})} = \frac{R(s^2 + 1/LC)}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

(b)

$$\begin{aligned} Z(s) &= R + \frac{(Ls)(\frac{1}{Cs})}{Ls + \frac{1}{Cs}} = R + \frac{LCs}{C(LCs^2 + 1)} = R + \frac{Ls}{LCs^2 + 1} \\ &= \frac{RLCs^2 + Ls + R}{LCs^2 + 1} = \frac{RLC(s^2 + \frac{1}{RC}s + \frac{1}{LC})}{LC(s^2 + \frac{1}{LC})} \end{aligned}$$

Hence,

$$Z(s) = \frac{R s^2 + \frac{1}{RC}s + \frac{1}{LC}}{s^2 + \frac{1}{LC}}$$

### SOLUTION 14.2.

(a)

$$Z_{in}(s) = \frac{V_s(s)}{I_s(s)} = \frac{(10 + 0.2s)(\frac{80}{s})}{10 + 0.2s + \frac{80}{s}} = \frac{s(800 + 16s)}{s(0.2s^2 + 10s + 80)} = \frac{800s + 4000}{s^2 + 50s + 400}$$

(b) If  $i_s(t) = 3e^{-20t}u(t)$  A then

$$I_s(s) = \frac{3}{s + 20}$$

and

$$\begin{aligned} V_s(s) &= Z_{in}(s)I_s(s) = \frac{800s + 4000}{s^2 + 50s + 400} - \frac{3}{s + 20} = \frac{2400s + 12,000}{(s + 10)(s + 20)(s + 40)} \\ &= \frac{K_1}{s + 10} + \frac{K_2}{s + 20} + \frac{K_3}{s + 40} \end{aligned}$$

Here

$$\begin{aligned} K_1 &= \left. \frac{2400s + 12,000}{(s + 20)(s + 40)} \right|_{s=-10} = \frac{+12,000 - 24,000}{(10)(30)} = -40 \\ K_2 &= \left. \frac{2400s + 12,000}{(s + 10)(s + 40)} \right|_{s=-20} = \frac{12,000 - 48,000}{(-10)(20)} = 180 \end{aligned}$$

$$K_3 = \left. \frac{2400s + 12,000}{(s+10)(s+20)} \right|_{s=-40} = \frac{12,000 - 96,000}{(-30)(-20)} = -140$$

$$V_s(s) = \frac{180}{s+20} - \frac{40}{s+10} - \frac{140}{s+40}$$

and for  $t > 0$ ,

$$v_s(t) = 180e^{-20t} - 40e^{-10t} - 140e^{-40t} \text{ V}$$

### SOLUTION 14.3.

(a)

$$Y_p(s) = Cs + \frac{1}{R} = 2 \times 10^{-3}s + \frac{1}{0.10} = 2 \times 10^{-3}(s + 50)$$

Then

$$Z_p(s) = \frac{500}{s+50}$$

and

$$Z_{in}(s) = 1.25s + \frac{500}{s+50} = \frac{1.25s^2 + 62.5s + 500}{s+50}$$

and

$$Y_{in}(s) = \frac{I_s(s)}{V_s(s)} = \frac{1}{Z_{in}(s)} = \frac{s+50}{1.25s^2 + 62.5s + 500} = \frac{0.80s + 40}{s^2 + 50s + 400}$$

With  $v_s(t) = 90e^{-40t}u(t)$ , then

$$V_s(s) = \frac{90}{s+40}$$

and

$$\begin{aligned} I_s(s) &= V_s(s)Y_{in}(s) = \frac{90}{s+40} \frac{0.80s + 40}{(s+10)(s+40)} \\ &= \frac{72s + 3600}{(s+10)(s+40)^2} = \frac{K_1}{s+10} + \frac{C_1}{s+40} + \frac{C_2}{(s+40)^2} \end{aligned}$$

Here

$$K_1 = \left. \frac{72s + 3600}{(s+40)^2} \right|_{s=-10} = \frac{3600 - 720}{(30)^2} = \frac{2880}{900} = 3.20$$

and with

$$\begin{aligned} p(s) &= \frac{72s + 3600}{s+10} & p(-40) &= \frac{720}{-30} = -24 \\ p(s) &= \frac{(s+10)(72) - (72s + 3600)}{(s+10)^2} \\ p(-40) &= \frac{-30(72) - (-2880 + 3600)}{(-30)^2} = \frac{-2160 - 720}{900} = -3.20 \end{aligned}$$

Then

$$C_2 = \frac{p(-40)}{0!} = -24, \quad C_1 = \frac{p(-40)}{1!} = -3.20,$$

$$I_s(s) = \frac{3.20}{s+10} - \frac{3.20}{s+40} + \frac{24}{(s+40)^2}$$

and for  $t > 0$

$$i_s(t) = 3.20e^{-10t} - 3.20e^{-40t} + 24te^{-40t} \text{ A}$$

#### SOLUTION 14.4.

(a) Find  $Z_{in}(s)$  vis  $Y_{in}(s)$

$$\begin{aligned} Y_{in}(s) &= Cs + \frac{1}{Ls+20} + \frac{1}{10} = \frac{200Cs + 10LCs^2 + 10 + 20 + Ls}{10(Ls+20)} \\ &= \frac{10LCs^2 + (200C+L)s + 30}{10Ls+200} \end{aligned}$$

and

$$Z_{in}(s) = \frac{1}{Y_{in}(s)} = \frac{10Ls+200}{10LCs^2 + (200C+L)s + 30}$$

With  $C = 10^{-3} F$  and  $L = 0.05 H$

$$Z_{in}(s) = \frac{0.50s + 200}{0.0005s^2 + 0.25s + 30} = \frac{1000s + 4 \times 10^5}{s^2 + 500s + 60,000}$$

(b) If  $i_s(t) = 0.3u(t)$  A, then

$$I_s(s) = \frac{0.30}{s}$$

and

$$\begin{aligned} V_{in}(s) &= Z_{in}(s)I_s(s) = 300 \frac{s+400}{s(s^2+500s+60,000)} = 300 \frac{s+400}{s(s+200)(s+300)} \\ &= 300 \left( \frac{K_1}{s} + \frac{K_2}{200} + \frac{K_3}{300} \right) \end{aligned}$$

It follows that

$$\begin{aligned} K_1 &= \left. \frac{s+400}{(s+200)(s+300)} \right|_{s=0} = \frac{400}{200(300)} = \frac{1}{150} \\ K_2 &= \left. \frac{s+400}{s(s+300)} \right|_{s=-200} = \frac{200}{(-200)(100)} = -\frac{1}{100} \end{aligned}$$

and

$$K_3 = \left. \frac{s+400}{s(s+200)} \right|_{s=-300} = \frac{100}{(-300)(-100)} = \frac{1}{300}$$

Thus

$$V_{in}(s) = 300 \frac{1}{s} - \frac{1}{s+200} + \frac{1}{s+300}$$

$$= \frac{2}{s} - \frac{3}{s+200} + \frac{1}{s+300}$$

and for  $t > 0$

$$v_{in}(t) = 2 - 3e^{-200t} + e^{-300t} \text{ V}$$

### SOLUTION 14.5.

$$Z(s) = \frac{s+20}{s+40}$$

and the network is “at rest”

(a) If

$$v_{in}(t) = 20u(t) \quad V_{in}(s) = \frac{20}{s}$$

then

$$I_{in}(s) = \frac{V_{in}(s)}{Z(s)} = \frac{20}{s} \frac{s+40}{s+20} = 20 \frac{s+40}{s(s+20)}$$

Using a partial function expansion

$$I_{in}(s) = 20 \frac{s+40}{s(s+20)} = 20 \frac{K_1}{s} + \frac{K_2}{s+20}$$

in which case

$$K_1 = \left. \frac{s+40}{s+20} \right|_{s=0} = \frac{40}{20} = 2, \quad K_2 = \left. \frac{s+40}{s} \right|_{s=-20} = \frac{20}{-20} = -1$$

Thus

$$I_{in}(s) = 20 \frac{2}{s} - \frac{1}{s+20}$$

and

$$i_{in}(t) = 20(2 - e^{-20t})u(t) \text{ A}$$

(b) Note that

$$v_{in}(t) = 20e^{-40t} \quad V_{in}(s) = \frac{20}{s+40}$$

Then

$$I_{in}(s) = \frac{V_{in}(s)}{Z(s)} = \frac{20}{s+40} \frac{s+40}{s+20} = \frac{20}{s+20}$$

in which case

$$i_{in}(t) = 20e^{-20t}u(t) \text{ A}$$

(c) Note that

$$v_{in}(t) = 20e^{-20t} \quad V_{in}(s) = \frac{20}{s+20}$$

Then

$$I_{in}(s) = \frac{V_{in}(s)}{Z(s)} = \frac{20}{s+20} \frac{s+40}{s+20} = 20 \frac{s+40}{(s+20)^2}$$

Using a partial fraction expansion

$$I_{in}(s) = 20 \frac{s+40}{(s+20)^2} = 20 \frac{C_1}{s+20} + \frac{C_2}{(s+20)^2}$$

Here

$$p(s) = s + 40 \quad p(-20) = 20$$

$$p'(s) = 1 \quad p'(-20) = 1$$

and

$$C_1 = \frac{p'(-20)}{1!} = 1, \quad C_2 = \frac{p(-20)}{0!} = \frac{20}{1} = 20$$

in which case

$$I_{in}(s) = 20 \frac{1}{s+20} + \frac{20}{(s+20)^2}$$

so that

$$i_{in}(t) = \left(20e^{-20t} + 400te^{-20t}\right)u(t) \text{ A}$$

### SOLUTION 14.6.

(a) Apply an arbitrary  $I_{in}(s)$  to the upper terminal of Fig. P14.6a. Assuming branch currents  $I_a(s)$  and  $I_b(s)$ , it follows by KCL that

$$\begin{aligned} I_{in}(s) &= I_a(s) + I_b(s) = 0.020sV_a(s) + 0.005s[V_a(s) - sV_a(s)] \\ &= (0.020 + 0.005 - 0.015)sV_a(s) = 0.010sV_a(s) \end{aligned}$$

Hence,

$$Z_{in}(s) = \frac{V_a(s)}{I_{in}(s)} = \frac{1}{0.010s} = \frac{100}{s}$$

(b) Similarly apply an arbitrary  $I_{in}(s)$  to Fig P14.6b to obtain, in the s-domain, by KCL

$$\begin{aligned} I_{in}(s) &= 10sV_{in}(s) + \frac{1}{50}V_{in}(s) + 0.10sV_{in}(s) - \frac{V_{in}(s)}{4} = 10s + \frac{1}{50} + \frac{30}{4s} V_{in}(s) \\ &= \frac{2000s^2 + 4s + 1500}{200s} V_{in}(s) \end{aligned}$$

Hence

$$Y_{in}(s) = \frac{I_{in}(s)}{V_{in}(s)} = \frac{10s^2 + 0.02s + 7.50}{s}$$

(c) Here we apply  $V_{in}(s)$  to the input terminals of figure P14.6c. By KCL

$$V_{in}(s) = 10I_{in}(s) + 0.2sI_{in}(s) + \frac{400}{s}I_{in}(s) - \frac{1}{2}I_{in}(s) = 10 + 0.2s + \frac{200}{s}I_{in}$$

in which case

$$Z_{in}(s) = \frac{V_{in}(s)}{I_{in}(s)} = \frac{0.2s^2 + 10s + 200}{s}$$

**SOLUTION 14.7.** Writing two loop equations we obtain:

$$V_{in}(s) = 100I_1(s) + 200I_2(s)$$

and

$$100I_1(s) + 100 + \frac{100}{s} I_2(s) = 0$$

In matrix form (dropping the s-dependence)

$$\begin{array}{cc} 100 & 200 \\ 100 & 100 + \frac{100}{s} \end{array} \begin{array}{l} I_1 \\ I_2 \end{array} = \begin{array}{l} V_{in} \\ 0 \end{array}$$

Using Cramer's rule,

$$I_1 = \frac{\det \begin{array}{cc} V_{in} & 200 \\ 0 & 100 + \frac{100}{s} \end{array}}{\det \begin{array}{cc} 100 & 200 \\ 100 & 100 + \frac{100}{s} \end{array}} = \frac{100s + 100}{s} \times \frac{1}{100 \frac{100s + 100}{s} - 200} V_{in}$$

Hence

$$Z_{in}(s) = \frac{V_{in}}{I_1} = -100 \frac{s-1}{s+1}$$

**SOLUTION 14.8.**

Working in the s-domain, apply KVL to the left side of the circuit to obtain

$$V_{in}(s) = \frac{100}{s} I_{in}(s) + \frac{s}{100} I_{in}(s) + V_2(s)$$

Now apply KCL to the right side to obtain

$$I_{in}(s) = \frac{s}{100} V_2(s) + \frac{100}{s} V_2(s)$$

Thus

$$V_{in}(s) = \frac{s^2 + 10^4}{100s} I_{in}(s) + V_2(s)$$

To find  $V_2(s)$  note that

$$I_{in}(s) = \frac{s^2 + 10^4}{100s} V_2(s)$$

implying that

$$V_2(s) = \frac{100s}{s^2 + 10^4} I_{in}(s)$$

Thus

$$V_{in}(s) = \frac{s^2 + 10^4}{100s} + \frac{100s}{s^2 + 10^4} I_{in}(s) = \frac{(s^2 + 10^4)^2 + 10^4 s^2}{100s(s^2 + 10^4)} I_{in}(s)$$

implying that

$$Z_{in}(s) = \frac{V_{in}(s)}{I_{in}(s)} = \frac{s^4 + 3 \times 10^4 s^2 + 10^8}{100s(s^2 + 10^4)}$$

and

$$Y_{in}(s) = \frac{1}{Z_{in}(s)} = \frac{100s(s^2 + 10^4)}{s^4 + 3 \times 10^4 s^2 + 10^8} \text{ S}$$

### SOLUTION 14.9.

Three mesh equations for the circuit

$$\begin{array}{cccccc} R + Z_2(s) & -Z_2(s) & -R & I_1(s) & V_{in}(s) & \\ -Z_2(s) & 2R + Z_2(s) & -R & I_2(s) & = & 0 \\ -R & -R & 2R + Z_1(s) & I_3(s) & & 0 \end{array}$$

Solve for  $I_1(s)$  via Cramer's rule

$$I_1 = \frac{\det \begin{array}{ccc} V_{in} & -Z_2(s) & -R \\ 0 & 2R + Z_2(s) & -R \\ 0 & -R & 2R + Z_1(s) \end{array}}{\det \begin{array}{ccc} R + Z_2(s) & -Z_2(s) & -R \\ -Z_2(s) & 2R + Z_2(s) & -R \\ -R & -R & 2R + Z_1(s) \end{array}} = \frac{V_{in} (3R^2 + 2R(Z_1 + Z_2) + Z_1 Z_2)}{d(s)}$$

where

$$\begin{aligned} d(s) &= (R + Z_2)(3R^2 + 2R(Z_1 + Z_2) + Z_1 Z_2) + Z_2(-Z_2(2R + Z_1) - R^2) - (2R^2 Z_2 + 2R^3) \\ &= R^3 + 2R^2 Z_1 + 2R^2 Z_2 + 3R Z_1 Z_2 \end{aligned}$$

Under the condition that  $Z_1(s)Z_2(s) = R_2$ , we have

$$Z_{in}(s) = \frac{V_{in}}{I_1} = \frac{R^3 + 2R^2 Z_1 + 2R^2 Z_2 + 3R Z_1 Z_2}{3R^2 + 2R(Z_1 + Z_2) + Z_1 Z_2} = \frac{4R^3 + 2R^2(Z_1 + Z_2)}{4R^2 + 2R(Z_1 + Z_2)} = R$$

### SOLUTION 14.10.

(a)  $Y_{in}(s) = Cs + \frac{1}{R}$  implies a parallel RC circuit with values R and C respectively.

(b)  $Y_{in}(s) = \frac{1}{Z_{in}(s)} = 2s + \frac{1}{4}$  which is a parallel RC circuit of values 4 and 2 F respectively.

(c)  $Z_{in}(s) = 1 + \frac{1}{2s + 0.25} = 1 + \frac{1}{Y_b(s)}$ . Using the result of part (b), this circuit is a 1 resistor in series with the parallel RC of part (b).

(d)  $Z_{in}(s) = \frac{2s + 8}{s + 2} = 2 + \frac{4}{s + 2} = 2 + \frac{1}{0.25s + \frac{1}{2}}$ . Using the results of parts (b) and (c), this circuit is a 2 resistor in series with a parallel combination of a 0.25 F capacitor and a 2 resistor.

(e)  $Z_{in}(s) = \frac{s + 3}{s + 1} + \frac{s + 6}{s + 4} = 2 + \frac{2}{s + 1} + \frac{2}{s + 4} = 2 + \frac{1}{0.5s + 1/2} + \frac{1}{0.5s + 1/0.5}$ . Using the above results, this circuit is a 2 resistor in series with a parallel combination of a 0.5 F capacitor and a 2 resistor which is in series with another parallel combination of a 0.5 F capacitor and a 0.5 resistor.

#### SOLUTION 14.11.

(a) Clearly this is an inductor of value L in series with a resistor of value R.

(b) Inverting the admittance we have  $Z_{in}(s)$  of the form of part (a). Hence the circuit is a 0.5 H inductor in series with a 10 resistor.

(c)  $Y_{in}(s) = 0.2 + \frac{1}{0.5s + 10} = 0.2 + \frac{1}{Z_b(s)}$ . Using the result of part (b), the circuit is 0.2 S resistor in parallel with a series connection of a 0.5 H inductor and a 10 resistor.

(d)  $Y_{in}(s) = \frac{10s + 50}{s + 1} = 10 + \frac{40}{s + 1} = 10 + \frac{1}{0.025s + 0.025}$ . This is similar to part (c). Hence the circuit is a 10 S resistor in parallel with a series connection of a 25 mH inductor and a 0.025 resistor.

(e)  $Y_{in}(s) = \frac{s + 3}{s + 1} + \frac{s + 6}{s + 4} = 2 + \frac{2}{s + 1} + \frac{2}{s + 4} = 2 + \frac{1}{0.5s + 0.5} + \frac{1}{0.5s + 2}$ . Hence, the circuit is a 2 S resistor in parallel with the series connection of a 0.5 H inductor and a 0.5 resistor which in turn is in parallel with a 0.5 H inductor and 2 resistor.

#### SOLUTION 14.12.

(a)  $Z_{in}(s) = Ls + \frac{1}{Cs}$  represents a series connection of an inductance L and a capacitance C.

(b)  $Y_{in}(s) = Cs + \frac{1}{Ls}$  represents a parallel connection of an inductance L and a capacitance C.

(c)  $Z_{in}(s) = \frac{0.125s^2 + 1}{0.25s} = 0.5s + \frac{1}{0.25s}$  which is a series connection of a 0.5 H inductor and a 0.25 F capacitor.

(d)  $Y_{in}(s) = \frac{0.125s^2 + 1}{0.25s} = 0.5s + \frac{1}{0.25s}$  which is a parallel connection of a 0.5 F capacitor and 0.25 H inductor.

(e)  $Z_{in}(s) = \frac{s^2 + 1}{s} + \frac{0.25s^2 + 1}{0.25s} = 2s + \frac{1}{s} + \frac{4}{s} = 2s + \frac{1}{0.25s}$  which is a 2 H inductor in series with a 0.2 F capacitor.

(f)  $Z_{in}(s) = \frac{s^2 + 1}{s} + \frac{0.25s}{0.25s^2 + 1} = s + \frac{1}{s} + \frac{1}{s + \frac{1}{0.25s}}$ . This circuit is a 1 H inductor in series with a 1 F capacitor which is in series with a parallel connection of a 1 F capacitor and a 0.25 H inductor.

(g)  $Y_{in}(s) = \frac{s^2 + 1}{s} + \frac{0.25s}{0.25s^2 + 1} = s + \frac{1}{s} + \frac{1}{s + \frac{1}{0.25s}}$ . This circuit is a 1 F capacitor in parallel with a 1 H inductor which is in parallel with a series connection of a 1 H inductor and a 0.25 F capacitor.

### SOLUTION 14.13.

With  $L[v_{out}(t)] = V_0(s)$  and  $L[v_{in}(t)] = V_i(s)$  and  $v_{out}(0^-) = 0$ ,

$$sV_0(s) + 25V_0(s) + \frac{100}{s}V_0(s) = 5V_i(s) - \frac{10}{s}V_i(s)$$

which implies that

$$\frac{s^2 + 25s + 100}{s} V_0(s) = \frac{5s - 10}{s} V_i(s)$$

The transfer function is

$$H(s) = \frac{V_0(s)}{V_i(s)} = \frac{5s - 10}{s^2 + 25s + 100} = \frac{5s - 10}{(s + 5)(s + 20)}$$

(a) If  $v_{in}(t) = te^{-5t}u(t)$  V, then

$$V_i(s) = \frac{1}{(s + 5)^2}$$

and

$$V_{out}(s) = \frac{5s - 10}{(s + 20)(s + 5)^3} = \frac{K_1}{s + 20} + \frac{C_1}{s + 5} + \frac{C_2}{(s + 5)^2} + \frac{C_3}{(s + 5)^3}$$

$$K_1 = \left. \frac{5s - 10}{(s + 5)^3} \right|_{s=-20} = \frac{-110}{(-15)^3} = \frac{-110}{-3375} = \frac{22}{675}$$

$$p(s) = \frac{5s - 10}{s + 20}$$

$$p(s) = \frac{(s + 20)(5) - (5s - 10)}{(s + 20)^2} = \frac{110}{(s + 20)^2} = 110(s + 20)^{-2}$$

$$p(s) = \frac{-220}{(s + 20)^3}$$

$$p(-5) = \frac{-25 - 10}{15} = \frac{-35}{15} = -\frac{7}{3} = -\frac{1575}{675}$$

$$p(-5) = \frac{110}{(-15)^2} = \frac{110}{225} = \frac{330}{675}$$

$$p(-5) = -\frac{220}{(-15)^3} = -\frac{220}{3375} = -\frac{44}{675}$$

Then

$$C_3 = \frac{p(-5)}{0!} = -\frac{1575}{675}, \quad C_2 = \frac{p(-5)}{1!} = \frac{330}{675}, \quad C_1 = \frac{p(-5)}{2!} = \frac{1}{2} - \frac{44}{675} = -\frac{22}{675}$$

and

$$V_{out}(s) = \frac{1}{675} \frac{22}{s+20} - \frac{22}{s+5} + \frac{330}{(s+5)^2} - \frac{1575}{(s+5)^3}$$

This yields

$$v_{out}(t) = \frac{1}{675} 22e^{-20t} - 22e^{-5t} + 330te^{-5t} - \frac{1575}{2} t^2 e^{-5t} u(t) \text{ V}$$

(b) If  $v_{in}(t) = u(t)$  V,

$$V_{in}(s) = \frac{1}{s}$$

and

$$V_{out}(s) = \frac{5s-10}{s(s+5)(s+20)} = \frac{K_1}{s} + \frac{K_2}{s+5} + \frac{K_3}{s+20}$$

$$K_1 = \left. \frac{5s-10}{(s+5)(s+20)} \right|_{s=0} = \frac{-10}{100} = -\frac{1}{10}$$

$$K_2 = \left. \frac{5s-10}{s(s+20)} \right|_{s=-5} = \frac{-25-10}{(-5)(+15)} = \frac{-35}{-75} = \frac{7}{15}$$

and

$$K_3 = \left. \frac{5s-10}{s(s+5)} \right|_{s=-20} = \frac{-100-10}{(-20)(-15)} = \frac{-110}{300} = -\frac{11}{30}$$

Thus

$$v_{out}(t) = \frac{7}{15} e^{-5t} - \frac{11}{30} e^{-20t} - \frac{1}{10} u(t) \text{ V}$$

By virtue of linearity and time invariance, if  $v_{in}(t) = [u(t) - u(t-0.5)]$  V,

$$\begin{aligned} v_{out}(t) &= \frac{7}{15} e^{-5t} - \frac{11}{30} e^{-20t} - \frac{1}{10} u(t) \\ &\quad - \frac{7}{15} e^{-5(t-0.5)} - \frac{11}{30} e^{-20(t-0.5)} - \frac{1}{10} u(t-0.5) \text{ V} \end{aligned}$$

### SOLUTION 14.14.

Here  $v_{in}(t) = \cos(t)u(t)$  V and  $i_{out}(t) = 2\sin(t)u(t)$  A, in which case

$$H(s) = \frac{I_{out}(s)}{V_{in}(s)} = \frac{\frac{2}{s^2+1}}{\frac{s}{s^2+1}} = \frac{2}{s}$$

**SOLUTION 14.15.**

Here  $v_{in}(t) = te^{-t}u(t)$  V which implies that  $V_{in}(s) = \frac{1}{(s+1)^2}$ . Further,

$v_{out}(t) = (1+t-0.5t^2)e^{-t}u(t) + \sin(t)u(t) - \cos(t)u(t)$  V in which case

$$V_{out}(s) = \frac{1}{s+1} + \frac{1}{(s+1)^2} + \frac{1}{(s+1)^3} + \frac{1}{s^2+1} - \frac{s}{s^2+1}$$

(a) Hence

$$\begin{aligned} H(s) &= \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{s+1} + \frac{1}{(s+1)^2} + \frac{1}{(s+1)^3} - \frac{s-1}{s^2+1} (s+1)^2 \\ &= (s+1) + 1 + \frac{1}{(s+1)} - \frac{(s-1)(s+1)^2}{s^2+1} \end{aligned}$$

Simplifying

$$H(s) = \frac{s^3 + 2s^2 + 5s + 2}{(s+1)(s^2+1)}$$

(b) If  $v_{in}(t) = (1+t)u(t)$  V, then  $V_{in}(s) = \frac{1}{s} + \frac{1}{s^2} = \frac{s+1}{s^2}$ . Hence

$$V_{out}(s) = H(s)V_{in}(s) = \frac{s^3 + 2s^2 + 5s + 2}{s^2(s^2+1)} = \frac{5}{s} + \frac{2}{s^2} - \frac{4s}{s^2+1}$$

implying that

$$v_{out}(t) = [5 + 2t - 4\cos(t)]u(t) \text{ V}$$

**SOLUTION 14.16.**

(a) By a voltage divider (Fig. P14.16a)

$$V_{out}(s) = \frac{Z_4(s)}{Z_3(s) + Z_4(s)} V_{in}(s)$$

and

$$H(s) = \frac{Z_4(s)}{Z_3(s) + Z_4(s)}$$

(b) In Fig. P14.16b,

$$Y_{in}(s) = Y_1(s) + Y_2(s)$$

and

$$V_{out}(s) = \frac{1}{Y_{in}(s)} I_{in}(s) = \frac{1}{Y_1(s) + Y_2(s)} I_{in}(s)$$

Hence

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} = \frac{1}{Y_1(s) + Y_2(s)}$$

(c) By current division,

$$I_{out}(s) = \frac{\frac{1}{Z_3(s) + Z_4(s)}}{Y_1(s) + Y_2(s) + \frac{1}{Z_3(s) + Z_4(s)}} I_{in}(s) = \frac{1}{[Y_1(s) + Y_2(s)][Z_3(s) + Z_4(s)] + 1} I_{in}(s)$$

Hence

$$V_{out}(s) = Z_4(s)I_{out}(s) = \frac{Z_4(s)}{[Y_1(s) + Y_2(s)][Z_3(s) + Z_4(s)] + 1} I_{in}(s).$$

and

$$H(s) = \frac{V_{out}}{I_{in}} = \frac{Z_4(s)}{[Y_1(s) + Y_2(s)][Z_3(s) + Z_4(s)] + 1}$$

**SOLUTION 14.17.** With  $V_{in}(s) = V_i$  and  $V_{out}(s) = V_0$ ,  $H(s) = \frac{V_0}{V_i}$ . By voltage division,

$$H(s) = \frac{V_0}{V_i} = \frac{\frac{1}{10^{-4}s + 10^{-3}}}{10^3 + \frac{1}{10^{-4}s + 10^{-3}}} = \frac{1}{0.1s + 2} = \frac{10}{s + 20}$$

(a)  $V_{out}(s) = \frac{400}{s(s + 20)} = \frac{20}{s} - \frac{20}{s + 20}$        $v_{out}(t) = (20 - 20e^{-20t})u(t)$  V. Plot omitted.

(b) If  $v_{in}(t) = 40[u(t) - u(t - 0.2)]$  V, then by linearity and time invariance

$$v_{out}(t) = 20(1 - e^{-20t})u(t) - 20[1 - e^{-20(t-0.2)}]u(t - 0.2)$$
 V

(c) If  $v_{in}(t) = 40[u(t) + u(t - 0.2)]$  V, then by linearity and time invariance

$$v_{out}(t) = 20(1 - e^{-20t})u(t) + 20[1 - e^{-20(t-0.2)}]u(t - 0.2)$$
 V

(d) If  $v_{in}(t) = 40e^{-20t}u(t)$  V,  $V_i(s) = \frac{40}{(s + 20)}$ . Hence,

$$V_0(s) = H(s)V_i(s) = \frac{400}{(s + 20)^2} \quad v_{out}(t) = 400te^{-20t}u(t)$$
 V

(e) If  $v_{in} = 40te^{-20t}u(t)$  V, then  $V_i(s) = \frac{40}{(s + 20)^2}$ . Hence,

$$V_0(s) = H(s)V_i(s) = \frac{400}{(s + 20)^3} \quad v_{out}(t) = 200t^2e^{-20t}u(t)$$
 V

**SOLUTION 14.18.**

(a) By voltage division

$$V_{out}(s) = \frac{\frac{2s+1}{s}}{2 + \frac{2}{s} + \frac{2s+1}{s}} V_{in}(s) = \frac{\frac{2s+1}{s}}{\frac{2s+2+2s+1}{s}} V_{in}(s) = \frac{2s+1}{4s+3} V_{in}(s)$$

Hence

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{2s+1}{4s+3}$$

(b) With  $v_{in}(t) = 8u(t)$  then

$$V_{out}(s) = H(s)V_{in}(s) = \frac{2s+1}{4s+3} \frac{8}{s} = \frac{16s+8}{s(4s+3)}$$

Using MATLAB

```
»n = [16 8]; d = [4 3 0];
```

```
»[r,p,k] = residue(n,d)
```

```
r =
```

```
1.3333e+00
```

```
2.6667e+00
```

```
p =
```

```
-7.5000e-01
```

```
0
```

```
k = []
```

Then

$$v_{out}(t) = \frac{8}{3} + \frac{4}{3} e^{-0.75t} u(t) \text{ V}$$

(c) If  $v_{in}(t) = 8\sin(2t)u(t)$ , then

$$V_{out}(s) = H(s)V_{in}(s) = \frac{2s+1}{4s+3} \frac{16}{s^2+4}$$

Using MATLAB,

```
»ilaplace((32*s+16)/((4*s+3)*(s^2+4)))
```

```
ans =
```

```
-32/73*exp(-3/4*t)+32/73*cos(2*t)+280/73*sin(2*t)
```

Hence,

$$v_{out}(t) = \left( -0.43836e^{-0.75t} + 0.43836\cos(2t) + 3.8356\sin(2t) \right) u(t) \text{ V}$$

(d) With  $v_{in}(t) = 8\sin(8t)u(t)$ 

$$\begin{aligned} V_{out}(s) &= H(s)V_{in}(s) = \frac{2s+1}{4s+3} \frac{64}{s^2+64} = \frac{128s+64}{(4s+3)(s^2+64)} \\ &= \frac{0.12391s + 31.907}{s^2+64} - \frac{0.12391}{s+0.75} \end{aligned}$$

Using MATLAB

```
»ilaplace((128*s + 64)/((4*s+3)*(s^2+64)))
```

```
ans =
```

```
-128/1033*exp(-3/4*t)+128/1033*cos(8*t)+4120/1033*sin(8*t)
```

```

»
»128/1033
ans =
  1.2391e-01
»4120/1033
ans =
  3.9884e+00

```

$$v_{out}(t) = \left(0.12391\cos(8t) + 3.9884\sin(8t) - 0.12391e^{-0.75t}\right)u(t) \text{ V}$$

### SOLUTION 14.19.

With a source transformation  $I_{in}(s) = \frac{V_{in}(s)}{R}$ .

(a) By current division,

$$I_C(s) = \frac{Cs}{\frac{1}{R} + Cs + \frac{1}{Ls}} \frac{V_{in}(s)}{R} = \frac{LCs^2}{LCs^2 + \frac{L}{R}s + 1} \frac{V_{in}(s)}{R} = \frac{s^2}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} \frac{V_{in}(s)}{R}$$

Here

$$H(s) = \frac{I_C(s)}{V_{in}(s)} = \frac{1}{R} \frac{s^2}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

(b) With  $R = \frac{2}{3}$ ,  $C = 0.5F$  and  $L = 1H$ ,

$$H(s) = \frac{3}{2} \frac{s^2}{s^2 + 3s + 2}$$

If  $v_{in}(t) = e^{-t}u(t)$  V, then  $V_{in}(s) = \frac{1}{s+1}$ . Hence

$$I_C(s) = H(s)I_{in}(s) = \frac{3}{2} \frac{s^2}{s^2 + 3s + 2} \frac{1}{s+1} = \frac{3s^2}{2(s+1)^2(s+2)} = \frac{K_1}{s+2} + \frac{C_1}{s+1} + \frac{C_2}{(s+1)^2}$$

Using MATLAB,

```

»n = [3 0 0]; d = conv([2 4],[1 2 1]);

```

```

»[r,p,k] = residue(n,d)

```

```

r =

```

```

  6.0000e+00

```

```

 -4.5000e+00

```

```

  1.5000e+00

```

```

p =

```

```

 -2.0000e+00

```

```

 -1.0000e+00

```

```

 -1.0000e+00

```

```

k =

```

```

 []

```

```

»

```

$$I_C(s) = \frac{6}{s+2} - \frac{4.5}{s+1} + \frac{1.5}{(s+1)^2}$$

and

$$i_C(t) = 6e^{-2t} - \frac{9}{2}e^{-t} + \frac{3}{2}te^{-t} u(t) \text{ A}$$

### SOLUTION 14.20.

(a) Make a source transformation:

$$V_{in}(s) = \frac{1}{C_S} I_{in}(s) = \frac{250}{s} I_{in}(s)$$

By voltage division

$$\begin{aligned} V_{out}(s) &= \frac{10}{\frac{250}{s} + \frac{250}{s} + \frac{1}{20}s + 10} \frac{250}{s} I_{in}(s) = \frac{2500}{s \left( \frac{1}{20}s^2 + 10s + 500 \right)} I_{in}(s) \\ &= \frac{50,000}{s(s^2 + 200s + 10,000)} I_{in}(s) \end{aligned}$$

and

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} = \frac{50,000}{s(s^2 + 200s + 10,000)}$$

(b) If  $i_{in}(t) = \delta(t)$  implies  $I_{in}(s) = 1$ . Using MATLAB

```
»n = 50e3; d = [1 200 10e3 0];
```

```
»[r,p,k] = residue(n,d)
```

```
r =
```

```
-5
```

```
-500
```

```
5
```

```
p =
```

```
-100
```

```
-100
```

```
0
```

```
k =
```

```
[]
```

Hence

$$V_{out}(s) = \frac{50,000}{s(s+100)^2} = \frac{5}{s} - \frac{5}{s+100} - \frac{500}{(s+100)^2}$$

and

$$v_{out}(t) = \left( 5 - 5e^{-100t} - 500te^{-100t} \right) u(t) \text{ V}$$

This is the impulse response

(c) If  $L_{in}(t) = 100u(t)$  mA so that  $I_{in}(s) = \frac{0.1}{s}$ . Therefore

$$V_{out}(s) = \frac{5000}{s^2(s+100)^2}$$

In MATLAB,

```

>>n = 5000; d = conv([1 0 0],[1 200 1e4])
d =
    1    200   10000    0    0
>>[r,p,k] = residue(n,d)
r =
  1.0000e-02
  5.0000e-01
 -1.0000e-02
  5.0000e-01
p =
 -100
 -100
  0
  0
k =
 []
Hence

```

$$V_{out}(s) = \frac{-0.01}{s} + \frac{0.5}{s^2} + \frac{0.01}{s+100} + \frac{0.5}{(s+100)^2}$$

and

$$v_{out}(t) = \left[ 0.01e^{-100t} + 0.5te^{-100t} - 0.01 + 0.5t \right] u(t)$$

(d) By superposition and time invariance, if

$$i_{in}(t) = 100[u(t) + u(t-1)] \text{ mA}$$

then the result of part (c) can be adjusted to

$$v_{out}(t) = \left[ 0.01e^{-100t} + 0.5te^{-100t} - 0.01 + 0.5t \right] u(t) \\ - \left[ 0.01e^{-100(t-1)} + 0.5te^{-100(t-1)} - 0.01 + 0.5(t-1) \right] u(t-1) \text{ V}$$

**SOLUTION 14.21.** For this problem change the 20 mH inductor to one of 0.3 H.

(a)

$$Y_{in} = \frac{1}{15} + \frac{1}{0.3s+90} + \frac{1}{0.1s+10} = \frac{(s+200)(s+400)}{15(s+100)(s+300)}$$

and

$$H(s) = \frac{I_{out}}{I_{in}} = \frac{1/15}{Y_{in}} = \frac{(s+100)(s+300)}{(s+200)(s+400)}$$

(b) If  $i_{in}(t) = (t) u(t)$ , then  $I_{in}(s) = 1/s$  and

$$I_{out}(s) = H(s) = \frac{(s+100)(s+300)}{(s+200)(s+400)} = 1 - \frac{50}{s+200} - \frac{150}{s+400}$$

Hence

$$i_{out}(t) = (t) u(t) + (-50e^{-200t} - 150e^{-400t}) u(t) \text{ A}$$

(c) We first find the response to  $i_{in}(t) = 16u(t)$  mA. Here  $I_{in}(s) = 0.016/s$  and

$$I_{\text{out}}(s) = H(s)I_{\text{in}}(s) = \frac{0.016(s + 100)(s + 300)}{s(s + 200)(s + 400)} = \frac{0.006}{s} + \frac{0.004}{s + 200} + \frac{0.006}{s + 400}$$

Hence


$$i_{\text{out}}(t) = (6 + 4e^{-200t} + 6e^{-400t})u(t) \text{ mA}$$

By linearity and time invariance, the response to  $i_{\text{in}}(t) = 16[u(t) - u(t - 0.01)]$  mA is

$$i_{\text{out}}(t) = (6 + 4e^{-200t} + 6e^{-400t})u(t) - (6 + 4e^{-200(t-0.01)} + 6e^{-400(t-0.01)})u(t - 0.01) \text{ mA}$$

A plot of  $i_{\text{out}}(t)$  using MATLAB is given below.
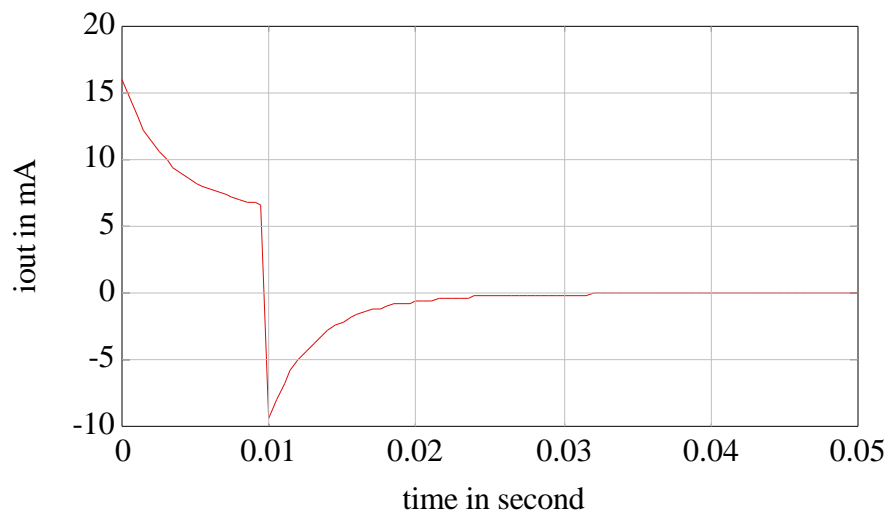
```
t= 0: 0.0005: 0.05;
f1= (6 + 4*exp(-200*t) + 6*exp(-400*t)).*u(t);
f2= (6 + 4*exp(-200*(t-0.01)) + 6*exp(-400*(t-0.01))).*u(t-0.01);
iout= f1 - f2;
plot(t, iout)
grid
ylabel('iout in mA')
xlabel(' time in second')
```



**REMARK:** Notice that the resistor current is not continuous.

**SOLUTION 14.22.** (a) First observe that the admittance of a parallel LC is

$$Y_{LC}(s) = Cs + \frac{1}{Ls}$$

Using voltage division,

$$V_{out}(s) = \frac{C_1 s + \frac{1}{Ls}}{C_1 s + \frac{1}{Ls} + C_2 s + \frac{1}{Ls}} V_{in}(s) = \frac{C_1 s + \frac{1}{Ls}}{(C_1 + C_2)s + \frac{2}{Ls}} V_{in}(s) = \frac{LC_1 s^2 + 1}{L(C_1 + C_2)s^2 + 2} V_{in}(s)$$

Finally

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{C_1}{(C_1 + C_2)} \frac{s^2 + \frac{1}{LC_1}}{s^2 + \frac{2}{L(C_1 + C_2)}} = 0.2 \frac{s^2 + 4 \times 10^6}{s^2 + 1.6 \times 10^6}$$

(b) Using MATLAB,

```

»syms s t
»ilaplace(0.2*(s^2+4e6)/(s^2+1.6e6))
ans =
1/5*Dirac(t)+120*10^(1/2)*sin(400*10^(1/2)*t)
»120*10^(1/2)
ans = 3.7947e+02

```

$$h(t) = 0.2L^{-1} \frac{s^2 + 4 \times 10^6}{s^2 + 1.6 \times 10^6} = 0.2\delta(t) + 379.47\sin(1264.9t)u(t) \text{ V}$$

### SOLUTION 14.23.

$$Y_1(s) = C_1 s + \frac{1}{R_1} = \frac{R_1 C_1 s + 1}{R_1}$$

$$Y_2(s) = C_2 s + \frac{1}{R_2} = \frac{R_2 C_2 s + 1}{R_2}$$

Then  $Z_1(s) = \frac{R_1}{R_1 C_1 s + 1}$  and  $Z_2(s) = \frac{R_2}{R_2 C_2 s + 1}$ . By voltage division,

$$\begin{aligned} V_{out}(s) &= \frac{\frac{R_2}{R_2 C_2 s + 1}}{\frac{R_1}{R_1 C_1 s + 1} + \frac{R_2}{R_2 C_2 s + 1}} V_{in}(s) = \frac{\frac{R_2}{R_2 C_2 s + 1} V_{in}(s)}{\frac{R_1 R_2 C_2 s + R_1 + R_1 R_2 C_1 s + R_2}{(R_1 C_1 s + 1)(R_2 C_2 s + 1)}} \\ &= \frac{R_2 (R_1 C_1 s + 1)}{(C_1 + C_2) R_1 R_2 s + R_1 + R_2} V_{in}(s) \end{aligned}$$

Thus the transfer function is:

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{R_2 (R_1 C_1 s + 1)}{(C_1 + C_2) R_1 R_2 s + R_1 + R_2}$$

(b) If  $C_1 = 0.5 \text{ F}$ ,  $C_2 = 1.0 \text{ F}$  and  $v_{in}(t) = 10 u(t) \text{ V}$ , then

$$V_{out}(s) = H(s)V_{in}(s) = \frac{0.5R_1R_2s + R_2}{1.5R_1R_2s + R_1 + R_2} \frac{10}{s}$$

Moreover, with  $\frac{R_1}{R_2} = 4$  so that  $R_1 = 4R_2$

$$V_{out}(s) = \frac{2R_2^2s + R_2}{6R_2^2s + 5R_2} \frac{10}{s} = \frac{20R_2^2(s + \frac{1}{2R_2})}{6R_2^2s(s + \frac{5}{6R_2})} = \frac{10}{3} \frac{s + \frac{1}{2R_2}}{s(s + \frac{5}{6R_2})}$$

The partial fraction expansion is

$$V_{out}(s) = \frac{10}{3} \frac{s + \frac{1}{2R_2}}{s(s + \frac{5}{6R_2})} = \frac{10}{3} \frac{K_1}{s} + \frac{K_2}{s + \frac{5}{6R_2}}$$

Observe that

$$\frac{K_2}{s + \frac{5}{6R_2}} \stackrel{L^{-1}}{\longrightarrow} K_2 e^{-\frac{5}{6R_2}t}$$

and that it is required that

$$-\frac{5}{6R_2} = -\frac{5}{3}$$

Thus

$$R_2 = 0.5, \quad R_1 = 4R_2 = 2$$

and

$$V_{out}(s) = \frac{10}{3} \frac{s+1}{s(s + \frac{5}{3})} = \frac{10}{3} \frac{0.6}{s} + \frac{0.4}{s + \frac{5}{3}} = \frac{2}{s} + \frac{4/3}{s + \frac{5}{3}}$$

Thus,

$$v_{out}(t) = 2 + \frac{4}{3} e^{-\frac{5}{3}t} u(t)$$

(c) If  $R_1C_1 = R_2C_2 = \tau$ , then the transfer function is

$$\begin{aligned} H(s) &= \frac{R_2(R_1C_1s + 1)}{R_1R_2C_1s + R_1R_2C_2s + R_1 + R_2} = \frac{R_2\tau s + R_2}{[R_2(R_1C_1) + R_1(R_2C_2)]s + R_1 + R_2} \\ &= \frac{R_2(\tau s + 1)}{(R_1R_2)(\tau s + 1)} = \frac{R_2}{R_2 + R_1} \end{aligned}$$

The zero-state response is

$$V_{out}(s) = \frac{R_2}{R_2 + R_1} 10u(t)$$

(d) Using  $H(s)$  from part (c) with the requirement that  $R_1 C_1 = R_2 C_2$ , then

$$H(s) = \frac{R_2}{R_1 + R_2} = \frac{1}{10}$$

With  $R_2 = 10^6$ , then  $10R_2 = R_1 + R_2$   $R_1 = 9R_2 = 9 \text{ M}$ . Since  $C_2 = 5 \times 10^{-12}$  F, then

$$C_1 = \frac{R_2 C_2}{R_1} = 0.556 \times 10^{-12} \text{ F}$$

### SOLUTION 14.24.

(a)  $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$ . Here  $I_b(s) = \frac{V_{in}(s)}{2000}$ . The parallel admittance at the right is

$$Y_R(s) = Cs + \frac{1}{R} = \frac{RCs + 1}{R}$$

so that

$$Z_R(s) = \frac{R}{RCs + 1}$$

Then

$$V_{out}(s) = -Z_R(s)\beta I_b(s) = -\frac{R\beta}{2000(RCs + 1)}$$

(b) With  $V_1(s) = V_{in}(s) - V_{out}(s)$ , then

$$Cs(V_{out}(s) - V_{in}(s)) + \frac{1}{s}V_{out}(s) + \frac{1}{2}[V_{out}(s) - 3V_{in}(s) + 3V_{out}(s)] = 0$$

Hence

$$Cs + \frac{3}{2} V_{in}(s) = Cs + \frac{1}{s} + 2 V_{out}(s)$$

and

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{s(Cs + 1.5)}{Cs^2 + 2s + 1} = \frac{s(s + 0.75)}{s^2 + s + 0.5}$$

(c) Transform the current source  $i_{in}(t)$  into a voltage source. In the s-domain with  $I_{in}(s) = 2V_{in}(s)$

Here  $Z_C(s) = \frac{1}{Cs} = \frac{1}{2s}$  which implies  $Y_C(s) = 2s$ . A single node equation yields

$$\frac{2}{3}[V_{out}(s) - V_{in}(s)] - \frac{2}{3}V_{out}(s) + 2sV_{out}(s) = -\frac{2}{3}V_{in}(s) + \frac{2}{3} - \frac{2}{3} + 2s V_{out}(s) = 0$$

$$\frac{2}{3}V_{in}(s) = 2sV_{out}(s) \text{ implies } V_{out}(s) = \frac{V_{in}(s)}{3s}$$

But  $V_{in}(s) = \frac{I_{in}(s)}{2}$  in which case

$$V_{out}(s) = \frac{I_{in}(s)}{6s}$$

and

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} = \frac{1}{6s}$$

**SOLUTION 14.25.** Here in the s-domain

$$I_{in}(s) = \frac{V_{in}(s) - V_C(s)}{0.5s + 10}$$

and with a node at  $V_C(s)$

$$-I_{in}(s) + \frac{sV_C(s)}{500} + \frac{1}{2}I_{in}(s) = 0 \text{ implies } \frac{sV_C(s)}{50} = \frac{1}{2}I_{in}(s) = \frac{V_{in}(s) - V_C(s)}{s + 20}$$

Hence,

$$\frac{s^2 + 20s + 500}{500} V_C(s) = V_{in}(s)$$

and the transfer function is

$$H(s) = \frac{V_C(s)}{V_{in}(s)} = \frac{500}{s^2 + 20s + 500}$$

With  $v_{in}(s) = 4\sqrt{5}u(t)$  V which implies  $V_{in}(s) = \frac{4\sqrt{5}}{s}$ , and

$$V_C(s) = \frac{2000\sqrt{5}}{s(s + 10 - j20)(s + 10 + j20)} = \frac{K_1}{s} + \frac{K}{s + 10 - j20} + \frac{K^*}{s + 10 + j20}$$

where  $K^*$  designates the complex conjugate of  $K$

$$K_1 = \left. \frac{2000\sqrt{5}}{s^2 + 20s + 500} \right|_{s=0} = \frac{2000\sqrt{5}}{500} = 8.944$$

$$\begin{aligned} K &= \left. \frac{2000\sqrt{5}}{s(s + 10 + j20)} \right|_{s=-(10-j20)} \\ &= \frac{2000\sqrt{5}}{(-10 + j20)(j40)} = \frac{2000\sqrt{5}}{-(800 + j400)} = -4.472 + j2.236 = Je^{j\phi} \end{aligned}$$

where  $\phi = 153.44^\circ$ . Then with

$$\begin{aligned} K^* &= -4.472 - j2.236 = 5e^{-j\phi} \\ V_C(s) &= \frac{8.944}{s} + \frac{A + jB}{s + 10 + j20} + \frac{A - jB}{s + 10 - j20} \end{aligned}$$

Here

$$A = -4.472, B = 2.236, \sqrt{A^2 + B^2} = 5$$

and

$$\text{arc tan} \frac{B}{A} = \text{arc tan} \frac{2.236}{-4.472} = \text{arc tan} \frac{1}{-2} = -153.44^\circ$$

With the help of Table 13.1.

$$v_C(t) = \left[ 8.944 + 10e^{-10t} \cos(20t + 153.44^\circ) \right] u(t) \text{ V}$$

**SOLUTION 14.26.** In the  $s$ -domain we first find  $V_x(s)$  in terms of  $V_{in}(s)$  via voltage division:

$$V_x(s) = \frac{Z_p(s)}{40 + Z_p(s)} V_{in}(s)$$

where

$$Z_p(s) = \frac{(0.40s)(40)}{0.40s + 40} = \frac{40s}{s + 100}$$

Hence

$$V_x(s) = \frac{\frac{40s}{s+100}}{40 + \frac{40s}{s+100}} V_{in}(s) = \frac{40s}{80s + 4000} = \frac{0.5s}{s + 50} V_{in}(s)$$

and

$$I_L(s) = \frac{V_x(s)}{0.4s} = \frac{2.5}{s} V_x(s)$$

Then from the right hand side by another voltage division

$$V_{out}(s) = \frac{10}{\frac{1000}{s} + 10} 0.25V_x(s) = \frac{10s}{10s + 1000} 0.25V_x(s) = \frac{0.25s}{s + 100} V_x(s)$$

(a) If  $v_{in}(s) = 20(1 - e^{-40t})u(t)$ , then  $V_{in}(s) = \frac{20}{s} - \frac{20}{s + 40}$ . Hence

$$V_x(s) = \frac{0.5s}{s + 50} \left( \frac{20}{s} - \frac{20}{s + 40} \right) = \frac{s}{s + 50} \left( \frac{10}{s} - \frac{10}{s + 40} \right)$$

and

$$I_L(s) = \frac{2.5}{s} V_x(s) = \frac{2.5}{s + 50} \left( \frac{1}{s} - \frac{1}{s + 40} \right) = \frac{0.05}{s} + \frac{-0.25}{s + 40} + \frac{0.2}{s + 50}$$

Hence

$$i_L(t) = \left[ 0.05 + 0.2e^{-50t} - 0.25e^{-40t} \right] u(t) \text{ A}$$

(b)  $V_{in}(s) = \frac{20}{s} - \frac{20}{s + 40}$ . From, part (a), it was found that

$$V_{out}(s) = \frac{0.25s}{s + 100} V_x(s) = \frac{0.25s}{s + 100} \times \frac{0.5s}{s + 50} V_{in}(s) = \frac{s}{s + 100} \times \frac{s}{s + 50} \times \left( \frac{2.5}{s} - \frac{2.5}{s + 40} \right)$$

$$= \frac{100s}{(s+40)(s+50)(s+100)} = \frac{-20/3}{(s+40)} + \frac{10}{(s+50)} + \frac{-10/3}{(s+100)}$$

Thus,

$$V_{out}(t) = 10e^{-50t} - \frac{10}{3}e^{-100t} - \frac{20}{3}e^{-40t} u(t) \text{ V}$$

**SOLUTION 14.27.** In both parts (a) and (b), the op-amp is ideal. It will not draw current and the virtual ground principle requires that

$$v^+ = v^- = 0$$

(a) For a node at the inverting terminal with node voltage  $v_1(t) = 0$ , KCL gives in the s-domain

$$\frac{V_{in}(s)}{R_1} = -CsV_{out}(s) - \frac{V_{out}(s)}{R_2} \text{ implies } \frac{V_{in}(s)}{R_1} = -Cs + \frac{1}{R_2} V_{out}(s)$$

in which case

$$\frac{V_{in}(s)}{R_1} = -\frac{R_2Cs + 1}{R_2} V_{out}(s)$$

Then,

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_2}{R_1} \frac{1}{R_2Cs + 1} = -\frac{1}{R_1C} \frac{1}{s + \frac{1}{R_2C}}$$

To make

$$H(s) = -\frac{20}{s+4}$$

make

$$\frac{1}{R_1C} = 20 \text{ and } \frac{1}{R_2C} = \frac{1}{4}$$

If

$$C = 1\mu\text{F} = 10^{-6}\text{F}$$

$$\frac{1}{R_2C} = 4 \text{ or } R_2 = \frac{1}{4C} = \frac{10^6}{4} = 250 \text{ k}$$

and

$$\frac{1}{R_1C} = 20 \text{ or } R_1 = \frac{2}{20C} = \frac{10^6}{20} = 50 \text{ k}$$

(b) With Fig. 14.27b in the s-domain and  $v_1(t)$  at the inverting terminal, KCL gives

$$C_1sV_{in}(s) + \frac{V_{in}(s)}{R_1} = -C_2sV_{out}(s) - \frac{V_{out}(s)}{R_2}$$

$$\frac{R_1C_1s + 1}{R_1} V_{in}(s) = -\frac{R_2C_2s + 1}{R_2} V_{out}(s)$$

Then

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_2}{R_1} \frac{R_1 C_1 s + 1}{R_2 C_2 s + 1} = -\frac{R_1 R_2 C_1}{R_1 R C_2} \frac{s + \frac{1}{R_1 C_1}}{s + \frac{1}{R_2 C_2}} = -\frac{C_1}{C_2} \frac{s + \frac{1}{R_1 C_1}}{s + \frac{1}{R_2 C_2}}$$

(c) If

$$H(s) = -5, \quad C_2 = 1\mu F \text{ and } R_2 = 1 M$$

then

$$\frac{C_1}{C_2} = 5 \text{ and } C_1 = 5\mu F$$

The bracketed term must cancel and with

$$R_2 C_2 = 10^6 (10^{-6}) = 1$$

Then with  $C_1 = 5\mu F$

$$R_1 C_1 = 1$$

$$R_1 = \frac{1}{C_1} = \frac{1}{5 \times 10^{-6}} = 200k$$

(d) Using  $H(s)$  in part (b)

$$H(s) = -\frac{C_1}{C_2} \frac{s + \frac{1}{R_1 C_1}}{s + \frac{1}{R_2 C_2}}$$

to obtain

$$H(s) = -5 \frac{s+1}{s+2}$$

with  $C_2 = 1\mu F$

$$C_1 = 5C_2 = 5 \times 10^{-6} F \quad (5\mu F)$$

$$\frac{1}{R_1 C_1} = 1 \text{ or } R_1 = \frac{1}{C_1} = \frac{10^6}{5} = 200k$$

$$\frac{1}{R_2 C_2} = 2 \text{ or } R_2 = \frac{1}{2C_2} = -\frac{10^6}{2} = 500k$$

**SOLUTION 14.28.** Here, the op-amp will not draw current at the non-inverting terminal and the principal of the virtual ground demand that

$$v_1 = v_2 = V_{in}(s)$$

For Fig. 14.28 in the s-domain with a node  $V_1(s)$  taken at the inverting terminal

$$\frac{V_{in}(s)}{R_1} + \frac{V_{in}(s) - V_{out}(s)}{Z_p(s)} = 0$$

Here

$$Z_p(s) = \frac{\frac{R_2}{Cs}}{\frac{1}{Cs} + R_2} = \frac{R_2}{R_2Cs + 1} = \frac{1}{C(s + \frac{1}{R_2C})}$$

and

$$\begin{aligned} \left(\frac{1}{R_1} + C\left(s + \frac{1}{R_2C}\right)\right) V_{in}(s) &= C\left(s + \frac{1}{R_2C}\right) V_{out}(s) \\ R_1C \left(s + \frac{1}{R_2C}\right) + 1 \ V_{in}(s) &= R_1C \left(s + \frac{1}{R_2C}\right) V_{out}(s) \end{aligned}$$

and

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{R_1C\left(s + \frac{1}{R_2C}\right) + 1}{R_1C\left(s + \frac{1}{R_2C}\right)} = \frac{s + \frac{1}{R_2C} + \frac{1}{R_1C}}{s + \frac{1}{R_1C}}$$

Here  $\frac{1}{R_2C} + \frac{1}{R_1C} = 4$

and

$$\frac{1}{R_1C} = 2$$

If  $C = 1\mu F$  then  $R_1 = \frac{1}{2C} = \frac{10^6}{2} = 500\ k$

and  $\frac{1}{R_2C} = 4 - 2 = 2$  implies  $R_2 = 500\ k$  .

**SOLUTION 14.29.** For the non-inverting configuration in the s-domain, each of the two op-amps in cascade have a transfer function

$$H(s) = -\frac{Z_f(s)}{Z_{in}(s)}$$

Then for the two op-amps

$$H_0(s) = -\frac{Z_{f1}(s)}{Z_{in1}(s)} \cdot -\frac{Z_{f2}(s)}{Z_{in,2}} = \frac{Z_{f,1}(s)Z_{f,2}(s)}{Z_{in,1}(s)Z_{in,2}(s)}$$

For Fig. P14.29a in the s-domain

$$Z_{in,1} = 25k \quad , \quad Z_{in,2} = 50k \quad , \quad Z_{f,1} = \frac{1}{C \left(s + \frac{1}{RC}\right)} = \frac{250,000}{s + 5} \quad , \quad \text{and} \quad Z_{f,2} = \frac{1}{C \left(s + \frac{1}{RC}\right)} = \frac{250,000}{s + 2.5}$$

Hence for Fig. P14.29a

$$H_a(s) = \frac{250,000}{s+2.5} \frac{250,000}{s+5.0} = \frac{50}{(s+2.5)(s+5)}$$

If  $v_{in}(t) = u(t)$ , then  $V_{in}(s) = \frac{1}{s}$  and

$$V_{out}(s) = \frac{50}{s(s+2.5)(s+5)} = \frac{4}{s} - \frac{8}{s+2.5} + \frac{4}{s+5}$$

Hence,

$$v_{out}(t) = \left[ 4 - 8e^{-2.5t} + 4e^{-5t} \right] u(t) \text{ V}$$

(b) For Fig. P14.29b in the s-domain,  $Z_{in,1}$ ,  $Z_{f1}$ , and  $Z_{f2}$  are in part (a). However,

$$Z_{in,2} = \frac{1}{Cs} = \frac{250,000}{s}$$

Thus

$$H_b(s) = \frac{250,000}{s+2.5} \frac{250,000}{\frac{s+5}{s}} = \frac{10}{s+2.5} \frac{s}{s+5} = \frac{10s}{s + \frac{5}{2}(s+5)}$$

With  $V_{in}(s) = \frac{1}{s}$ ,

$$V_{out}(s) = \frac{10s}{(s+2.5)(s+5)} \frac{1}{s} = \frac{20}{(s+2.5)(s+5)} = \frac{4}{s+2.5} - \frac{4}{s+5}$$

and

$$v_{out}(t) = \left( 4e^{-2.5t} - 4e^{-5t} \right) u(t) \text{ V}$$

### SOLUTION 14.30.

(a)-(b). The subcircuit is an integrator, with

$$\frac{V_{out}(t)}{V_1(s)} = -\frac{1}{s}$$

(c) This subcircuit is again an integrator, with

$$\frac{V_1(t)}{V_2(s)} = -\frac{1}{s}$$

(d) Applying KCL to the inverting input terminal of the top left op amp, we have

$$G_2 V_{out}(s) + V_3(s) + V_2(s) = 0$$

or

$$V_2(s) = -G_2 V_{out}(s) - V_3(s)$$

(e) Applying KCL to the inverting input terminal of the bottom op amp, we have

$$G_3 V_1(s) + G_1 V_{in}(s) + V_3(s) = 0$$

or

$$V_3(s) = -G_3 V_1(s) - G_1 V_{in}(s)$$

(f) The results of parts (b), (c) and (d) do not involve  $V_{in}$ . Therefore, we can solve for  $V_1$ ,  $V_2$  and  $V_3$  in terms of  $V_{out}$  from these three equations:

$$V_1(s) = -s V_{out}(s)$$

$$V_2(s) = -s V_1(s) = s^2 V_{out}(s)$$

and

$$V_3(s) = -V_2(s) - G_2 V_{out}(s) = -(s^2 + G_2) V_{out}(s)$$

Substituting these relationships into the result of part (e), we obtain

$$-s G_3 V_{out}(s) + G_1 V_{in}(s) - (s^2 + G_2) V_{out}(s) = 0$$

Therefore

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{G_1}{s^2 + G_3 s + G_2}$$

**SOLUTION 14.31.** Use the parallel equivalent circuit model for the capacitor with the standard directions for voltage and current as given in figure 14.16. For the single node with  $v_C(0^-) = 20$  V,

$$\frac{V_C(s)}{\frac{10}{s}} + \frac{V_C(s)}{40 + 10} - \frac{1}{10} v_C(0^-) = 0 \quad \text{implies} \quad \frac{s}{10} + \frac{1}{50} V_C(s) = \frac{1}{10} (20) = 2$$

Equivalently,  $(50s + 10)V_C(s) = (s + 0.2)V_C(s) = 20$  or  $V_C(s) = \frac{20}{s + 0.2}$ . Therefore,

$$v_C(t) = 20e^{-0.2t} u(t) \text{ V}$$

**SOLUTION 14.32.** Using the equivalent model for the inductor in figure 14.19, we can compute the total admittance as

$$Y(s) = \frac{5}{2s} + \frac{1}{40} + \frac{1}{10} = \frac{5}{2s} + \frac{1}{8} = \frac{2s + 40}{16s} = \frac{s + 20}{8s}$$

Using current division,

$$I_{out}(s) = \frac{0.1}{s+20} \times \frac{-i_L(0)}{s} = -\frac{0.8i_L(0^-)}{s+20} = -\frac{1.6}{s+20}$$

Thus

$$i_{out}(t) = -1.6e^{-20t} u(t) \text{ A}$$

**SOLUTION 14.33.** Using the equivalent model for the inductor in figure 14.19 and for the capacitor using figure 14.16, we may combine the current sources to form an equivalent source (with  $C = 0.1$  F) to obtain

$$I_{eq}(s) = \frac{1}{10} v_C(0^-) - \frac{i_L(0^-)}{s} = 0.2 - \frac{1}{s}$$

Note that

$$Y(s) = Cs + \frac{1}{Ls} = \frac{LCs^2 + 1}{Ls} = C \frac{s^2 + \frac{1}{LC}}{s}$$

With  $C = 0.1$  F and  $L = 0.4$  H,  $\frac{1}{LC} = 25$  and

$$Z(s) = \frac{1}{C} \frac{s}{s^2 + 25} = \frac{10s}{s^2 + 25}$$


Thus

$$V_C(s) = Z(s)I_{eq}(s) = \frac{10s}{s^2 + 25} \frac{s-5}{5s} = \frac{2(s-5)}{s^2 + 25} = \frac{2s}{s^2 + 25} - \frac{10}{s^2 + 25}$$

and

$$v_C(t) = (2\cos(5t) - 2\sin(5t)) u(t) \text{ V}$$

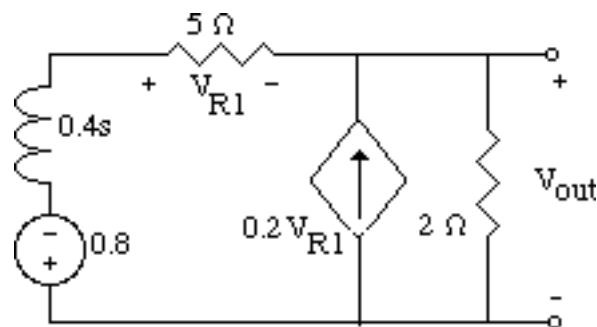**SOLUTION 14.34.** Consider the equivalent circuit below:



Writing a single node equation we have,

$$\begin{aligned}
 0 &= 0.5V_{out} - 0.2V_{R1} + \frac{1}{5 + 0.4s} (V_{out} + 0.8) \\
 &= 0.5V_{out} + 5 \times 0.2 \times \frac{1}{5 + 0.4s} (V_{out} + 0.8) + \frac{1}{5 + 0.4s} (V_{out} + 0.8) \\
 &= 0.5V_{out} + \frac{2}{5 + 0.4s} (V_{out} + 0.8)
 \end{aligned}$$

Therefore

$$V_{out} = \frac{-8}{s + 22.5}$$

and

$$v_{out}(t) = -8e^{-22.5t} u(t) \text{ V}$$

**SOLUTION 14.35.** Redraw the circuit in the s-domain and use an equivalent circuit for the capacitor (figure 14.16) that accounts for the initial condition. By KCL

$$\frac{V_C(s)}{R} + CsV_C(s) = Cv(0^-) + I_{in}(s)$$

With  $R = 50$  and  $C = 0.02$  F,

$$\frac{V_C(s)}{50} + 0.02sV_C(s) = 0.02v_C(0^-) + I_{in}(s)$$

or

$$V_C(s) + sV_C(s) = v_C(0^-) + 50I_{in}(s)$$

which is equivalent to

$$(s + 1)V_C(s) = v_C(0^-) + 50I_{in}(s)$$

(a) With  $v_C(0^-) = 8$  V and  $i_{in}(t) = 40\delta(t)$  mA so that  $I_{in}(s) = 0.04$ ,

$$(s + 1)V_C(s) = 8 + 2 \quad \text{implies} \quad V_C(s) = \frac{10}{s + 1}$$

and

$$v_C(t) = 10e^{-10t} u(t) \text{ V}$$

(b) With  $v_C(0^-) = 1$  V and  $i_{in}(t) = 200e^{-t}u(t)$  mA we have that  $I_{in}(s) = \frac{0.2}{s + 1}$ . Thus

$$V_C(s) = \frac{v_C(0^-)}{(s + 1)} + \frac{50}{(s + 1)} I_{in}(s) = \frac{1}{(s + 1)} + \frac{10}{(s + 1)^2}$$

and

$$v_C(t) = \left( e^{-t} + 10te^{-t} \right) u(t) \text{ V}$$

**SOLUTION 14.36.**

(a) By current division

$$H(s) = \frac{I_L(s)}{I_{in}(s)} = \frac{1}{Ls + 1}$$

(b) The given data in Laplace transforms are:

$$I_{in}(s) = \frac{I_0}{s^2} \quad \text{and} \quad I_L(s) = \frac{15}{s^2} - \frac{3}{s} + \frac{3}{s+5} = \frac{75}{s^2(s+5)}$$


Under the assumption of zero initial inductor current,

$$I_L(s) = H(s) I_{in}(s) = H(s) \frac{I_0}{s^2} = \frac{I_0}{(Ls + 1)s^2} = \frac{I_0/L}{(s + 1/L)s^2} = \frac{75}{s^2(s+5)}$$

Equating coefficients, we obtain the answers

$$L = 1/5 = 0.2 \text{ H and } I_0 = 75L = 15 \text{ A}$$

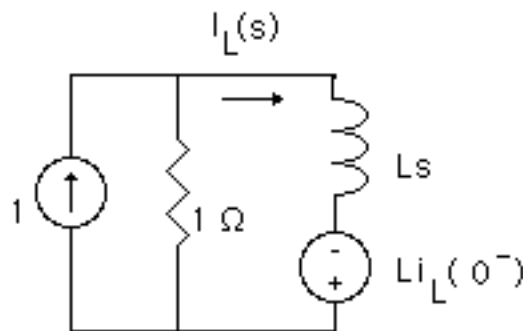(c) The s-domain equivalent is shown below.



Applying KVL to the right mesh, we have

$$LsI_L(s) - L i_L(0^-) + 1 \times [I_L(s) - 1] = 0$$

Solving for  $I_L(s)$  from this equation, and equating it to  $10/(s+5)$ , we have

$$I_L(s) = \frac{L i_L(0^-) + 1}{Ls + 1} = \frac{i_L(0^-) + 1/L}{s + 1/L} = \frac{10}{s + 5}$$

from which  $L = 0.2 \text{ H}$  and  $i_L(0^-) = 5 \text{ A}$ .

### SOLUTION 14.37.

(a) By inspection,

$$H(s) = \frac{I_L(s)}{V_{in}(s)} = \frac{1}{2s + 200} = \frac{0.5}{s + 100}$$

Given  $v_{in}(t) = 2u(t)$  V, then  $V_{in}(s) = 2/s$ , and

$$I_L(s) = \frac{1}{s(s + 100)} = \frac{0.01}{s} - \frac{0.01}{s + 100}$$

in which case


$$i_L(t) = 0.01 (1 - e^{-100t}) \text{ A}$$

Plots are omitted.

(b) By linearity and time invariance,

$$i_L(t) = 0.01 (1 - e^{-100t})u(t) - 0.01(1 - e^{-100(t-0.05)})u(t - 0.05) \text{ A}$$

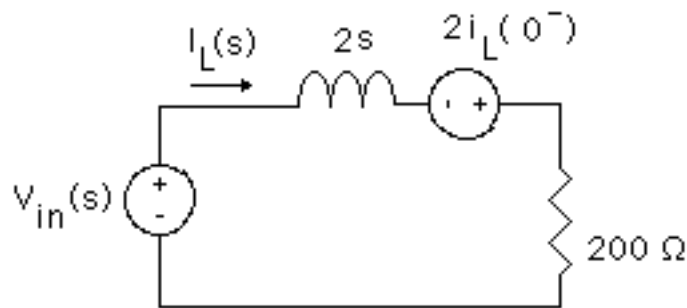(c) Correction: (a) should be (c). With nonzero initial inductor current, the s-domain equivalent becomes:



Given  $i_L(0^-) = 0.01$  A and  $v_{in}(t) = 2e^{-200t}u(t)$  V, then  $V_{in}(s) = 2/(s + 200)$  and

$$\begin{aligned} I_L(s) &= \frac{\frac{2}{s + 200} + 0.02}{(2s + 200)} = \frac{0.01s + 3}{(s + 100)(s + 200)} \\ &= \frac{0.02}{s + 100} - \frac{0.01}{s + 200} \end{aligned}$$

in which case

$$i_L(t) = (0.02e^{-100t} - 0.01e^{-200t}) u(t) \text{ A}$$

(d) Correction . (b) should be (d).

Given  $i_L(0^-) = 0.01$  A and  $v_{in}(t) = 2\cos(200t)u(t)$  V, then

$$V_{in}(s) = \frac{2s}{s^2 + 40000}$$

and

$$I_L(s) = \frac{\frac{2s}{s^2 + 40000} + 0.02}{(2s + 200)} = \frac{0.01s^2 + s + 400}{(s + 100)(s^2 + 40000)}$$

We use MATLAB to do the partial fraction expansion.

```
n = [ 0.01 1 400];
d = conv([ 1 100], [ 1 0 40000]);
[ r p k ] = residue (n,d)
r =
  0.0010 - 0.0020i
  0.0010 + 0.0020i
  0.0080
p =
  1.0e+02 *
  0.0000 + 2.0000i
  0.0000 - 2.0000i
 -1.0000
```

From the above MATLAB output,

$$I_L(s) = \frac{0.008}{s + 100} + \frac{0.001 - j0.002}{s - j200} + \frac{0.001 + j0.002}{s + j200} = \frac{0.008}{s + 100} + \frac{0.002s + 0.8}{s^2 + 200^2}$$

From table 13.1, item 18,

$$i_L(t) = (0.008e^{-100t} + 0.002 \cos(200t) + 0.004 \sin(200t)) u(t) \text{ A}$$