

INDEX

A

Acceptor atoms, **64**
 A.C. equivalent circuit, **248**
 A. C. load line, **251**
 Active region, **475**
 Alpha, **148**
 Amplitude modulation, **414**
 Amplification, **146**
 Amplifier:
 Class A power, **312**
 bandwidth, **284**
 Class B power, **312**
 Class C power, **313**
 Class C tuned, **402**
 direct coupled, **299**
 distortion in, **311**
 AND gate, **740**
 Anode, **33**
 Antenna, **413**
 Astable multivibrator, **478**
 Audio amplifier, **307**
 Avalanche breakdown, **72**

B

Band:
 conduction, **51**
 valence, **51**
 Bandwidth, **284**

Barrier potential, **67**
 Base, **143**
 Bel power gain, **283**
 Bel voltage gain, **284**
 Beta, **153**
 Binary system, **730**
 Bipolar transistor, **146**
 Bi-stable multivibrator, **482**
 Boolean algebra, **748**
 Breakdown:
 Avalanche, **72**
 Zener, **108**
 Bridge rectifier, **92**
 Bypass capacitor, **242**

C

Capacitor filter, **103**
 Cathode, **33**
 Cathode ray oscilloscope, **616**
 CE amplifier, **164**
 Chassis, **24**
 Chip, semiconductor, **628**
 Choke input filter, **104**
 Clampers, **495**
 Class A operation, **312**
 Class B operation, **312**
 Class C operation, **313**

Clippers, **487**
 Collector, **143**
 Collector feedback bias, **209**
 Colpitts oscillator, **372**
 CB amplifier, **148**
 Complementary-symmetry, **330**
 Conduction band, **51**
 Constant current source, **9**
 Constant voltage source, **8**
 Coupling capacitor, **242**
 Covalent bond, **56**
 Crystal oscillator, **383**
 Current feedback, **347**
 Current gain, **173**
 Cut-off frequency, **285**

D

D. C. amplifier, **299**
 D. C. equivalent circuit, **247**
 Decibel, **283**
 Depletion layer, **67**
 Diac, **586**
 Differential amplifier, **664-687**
 Diffusion, **67**
 Digital circuit, **730**
 Diode circuits, **76-124**
 Direct coupling, **299**
 Discrete circuit, **627**
 Distortion, **311**
 Donor atom, **63**
 Doping, **62**
 Double based diode, **590**
 Drain-source curve, **511**
 Driver stage, **325**
 Dynamic resistance, **79**
 Dual-in-line pack, **635**

E

Efficiency:
 Half-wave rectifier, **88**

Full-wave rectifier, **94**
 Electromagnetic deflection, **618**
 Electrons, **4**
 Electron emission, **28-37**
 Electron gun, **617**
 Electron-hole pair, **61**
 Emitter, **143**
 Emitter follower, **349**
 Encoder, **746**
 Energy band theory, **50**
 Equivalent circuit of amplifier, **272**
 Equivalent circuit with signal source, **272**
 Epitaxial layer, **630**
 Exclusive OR gate, **744**
 Extrinsic semiconductor, **62**
 Expression for collector :
 efficiency, **313**

F

Feedback, **335**
 Feedback amplifier, **337**
 JFET importance, **510**
 Field effect transistor, **507**
 Field emission, **34**
 Filter circuit, **103**
 Forward bias, **68**
 Forbidden gap, **51**
 Free electron, **6**
 Free-running multivibrator, **478**
 Frequency modulation, **426**
 Frequency response, **283**

G

Gain:
 power, **173**
 voltage, **173**
 gate, **507**
 ground, **24**

H

Hartley oscillator, **374**

Holding current, **558**
 Hole current, **61**
 Heat sink, **322**
 Hybrid, **643**

I

Inductor filter, **104**
 Insulated gate, **536**
 Integrated circuit, **628**
 Interstage coupling, **281**
 Intermediate frequency, **434**
 Intrinsic semiconductor, **62**
 Intrinsic stand off ratio, **592**
 Impedance matching, **296**
 Input impedance, **172**

J

Junction, pn, **66**
 Junction diode, **77**
 Junction transistor, **142**

K

Knee voltage, **72**

L

Large signal operation, **312**
 LC oscillators, **371-376**
 Leakage current, **71**
 Light-emitting diode (LED), **126**
 Load D.C. and A.C., **248, 249**
 Load line:
 a.c., **251**
 d.c., **249**
 Local oscillator, **433**
 Logic gates, **738**

M

Max. A.C. power output, **314**
 Max. collector efficiency, **314**
 Majority carriers, **65**
 Microelectronics, **627**
 Minority carriers, **65**
 Modulation:

 AM, **414**
 FM, **426**
 Monolithic IC, **629**
 MOSFET, **535**
 Multicolour LEDs, **128**
 Multivibrators :
 astable, **478**
 bistable, **482**
 monostable, **480**

N

NAND gate, **742**
 Negative feedback, **336**
 n-p-n transistor, **142**
 n-type semiconductor, **62**
 Noise, **311**
 NOR gate, **743**
 NOT gate, **742**

O

Operational Amplifiers, **662-728**
 Block diagram, **663**
 Input/output Polarity relation, **689**
 Voltage gain, **688**
 Values of supply voltage, **690**
 Optoisolator, **133**
 OR gate, **739**
 Oscillators:
 Collpits, **372**
 Crystal, **383**
 Hartley, **374**
 L.C., **371-376**
 Phase shift, **377**
 Tuned collector, **371**
 Wein bridge, **378**
 Oscilloscope, **616**
 Output resistance, **172**
 Over voltage detector, **595**
 Oxide coated emitter, **32**

P

p-type semiconductor, **64**
 Peak inverse voltage, **73**
 Pentavalent atoms, **63**

778 ■ Principles of Electronics

Phase-shift oscillator, **377**

Photo-diode, **130**

Photo-emission, **35**

Piezo-electric effect, **380**

π -filter, **104**

Pinch off voltage, **513**

p-n-junction, **66**

p-n-p transistor, **142**

Positive clipper, **487**

Power dissipation, **311**

Power gain, **173**

Push-pull amplifier, **326**

Q

Quartz crystal, **381**

Quiescent point, **167**

R

RC differentiator, **483**

RC integrator, **486**

RC oscillator, **377**

RC coupling, **289**

Rectifiers, **87**

Relaxation oscillator, **595**

Reverse bias, **68**

Ripple factor, **101**

S

Saturation collector current, **473**

Saturation region, **474**

Sawtooth wave, **619**

Secondary emission, **34**

SCR, **555**

Semiconductors, **56**

Shockley diode, **137**

Sideband frequencies, **418**

Stabilisation, **197**

Stand off voltage, **592**

Substrate, **629**

Superhetrodyne receiver, **433**

T

Thermal runaway, **197**

Thermionic emission, **30**

Thevenin's theorem, **15**

Thyristor, **555**

Transformer coupling, **294**

Transistor:

AM modulator, **419**

CB, **148**

CC, **162**

CE, **152**

Trivalent impurity, **64**

Tuned collector oscillator, **371**

Tunnel diode, **134**

U

Uni-junction transistor, **589**

Unipolar transistor, **510**

V

Varactor-diode, **136**

Voltage divider bias, **212**

Voltage regulator, **448**

Voltmeter, electronic, **609**

W

Wein bridge oscillator, **378**

Window, **631**

X

X-cut, **380**

Y

Y-cut, **380**

Z

Zener breakdown, **108**

Zener diode, **108**

Zener diode regulator, **110**

Zener symbol, **109**